

Electric Circuits for Physicists

2016

Shingo Katsumoto

2016年度
電子回路論 第1回

東京大学
理学部・理学系研究科
物理学専攻
物性研究所
勝本信吾

ノート・資料等の置き場



勝本信吾

Shingo Katsumoto



[自己紹介](#)

現在の研究テーマ

[論文リスト](#)

[「ポケットに電磁気を」が単行本になりました](#)

[出版された書籍](#)

[物理屋のための「電子回路論」講義ノート \(2016 Sept.-2017 Jan.\)](#)

[「半導体」講義ノート \(2016 May-2016 July\)](#)

[物理屋のための「電子回路論」講義ノート \(2015 Oct.-2016 Jan.\)](#)

- [研究紹介](#)
- [メンバー](#)
- [実験装置](#)
- [投稿](#)
- [出版リスト](#)
- [「半導体の基礎」](#)
- [アルバム](#)
- [物性研トップ](#)
- [共同利用](#)

2週に1回簡単な練習問題を出題 → 2週間以内に解答を提出
TAが採点してコメントをメール送付します
試験は期末レポート、練習問題と合わせて採点します

シラバス

1. 電磁場と電子回路
 - 1.1 この講義について
 - 1.2 電子回路とは
 - 1.3 2端子素子
 - 1.4 回路図
 - 1.5 抵抗器
 - 1.6 キャパシタ
 - 1.7 インダクタ
2. 線形回路序論
 - 2.1 線形システムと電子回路
 - 2.2 電源
 - 2.3 回路網
 - 2.4 4端子(2端子対)回路
 - 2.5 端子対回路の諸定理
 - 2.6 双対性
 - 2.7 受動素子と能動素子
3. 伝達関数と周波数応答・過渡応答
 - 3.1 受動素子2端子回路の伝達関数
 - 3.2 2端子受動素子回路
 - 3.3 受動素子回路の過渡応答
4. 増幅回路
 - 4.1 増幅回路と系の制御
 - 4.2 OPアンプ
 - 4.3 トランジスタ
 - 4.4 電場効果トランジスタ
5. 分布定数回路
 - 5.1 伝送路
 - 5.2 伝送路の伝播現象
 - 5.3 S行列(Sパラメタ)
 - 5.4 シュレディンガー方程式とLC伝送路

シラバス2

- 6. 信号, 雑音, 波形解析
 - 6.1 ゆらぎ
 - 6.2 増幅器の雑音
 - 6.3 変調とアナログ信号伝送
 - 6.4 離散化信号

- 7. デジタル信号とデジタル回路
 - 7.1 デジタル信号序論
 - 7.2 論理ゲート
 - 7.3 論理ゲートの実装
 - 7.4 論理演算の回路化と簡単化
 - 7.5 A-D/D-A コンバータ
 - 7.6 デジタルフィルター
 - 7.7 ハードウェア記述言語 : HDL

1. Electromagnetic field and electric circuits
 - 1.1 About this lecture
 - 1.2 What is electric circuit?
 - 1.3 Two-terminal devices
 - 1.4 Circuit diagrams
 - 1.5 Resistors
 - 1.6 Capacitors
 - 1.7 Inductors
2. Introduction to linear circuits
 - 2.1 Linear systems and electric circuits
 - 2.2 Power sources
 - 2.3 Networks
 - 2.4 4-terminal (2-terminal pair) circuits
 - 2.5 Theorems in terminal pair circuits
 - 2.6 Duality
 - 2.7 Passive devices, active devices

3. Transfer function and transient response
 - 3.1 Transfer function of passive two-terminal pair circuits
 - 3.2 Two-terminal passive circuits
 - 3.3 Transient response of passive circuits
4. Amplifiers
 - 4.1 System control and amplifiers
 - 4.2 Operational amplifiers
 - 4.3 Transistors
 - 4.4 Field effect transistors
5. Distributed constant circuits
 - 5.1 Transmission lines
 - 5.2 Propagation through transmission lines
 - 5.3 S matrix (S parameters)
 - 5.4 Schrodinger equation and LC transmission circuit

6. Signal, noise, waveform analysis
 - 6.1 Fluctuation
 - 6.2 Noise from amplifiers
 - 6.3 Modulation and analog signal transfer
 - 6.4 Discrete signal
7. Digital signal and digital circuits
 - 7.1 Introduction to digital signal
 - 7.2 Logic gates
 - 7.3 Logic circuits implementation
 - 7.4 Circuit implementation and simplification of logic operation
 - 7.5 AD/DA converters
 - 7.6 Digital filters
 - 7.7 Language to describe hardware: HDL

Outline Today

1. Electromagnetic field and electric circuits
 - 1.1 About this lecture
 - 1.2 What is electric circuit?
 - 1.3 Circuit diagrams
 - 1.4 Two-terminal devices
 - 1.5 Resistors
 - 1.6 Capacitors
 - 1.7 Inductors
2. Introduction to linear circuits
 - 2.1 Linear systems and electric circuits

Ch.1 Electromagnetic field and electric circuits



For what this lecture is?

Experimentalists:

Knowledges on electric circuit are indispensable.

Purposes:

Understand how circuits work.

Design circuits along research plans


General physicists:

Meta physics

Coupled pendulum and neutrino oscillation



Pendulum oscillation

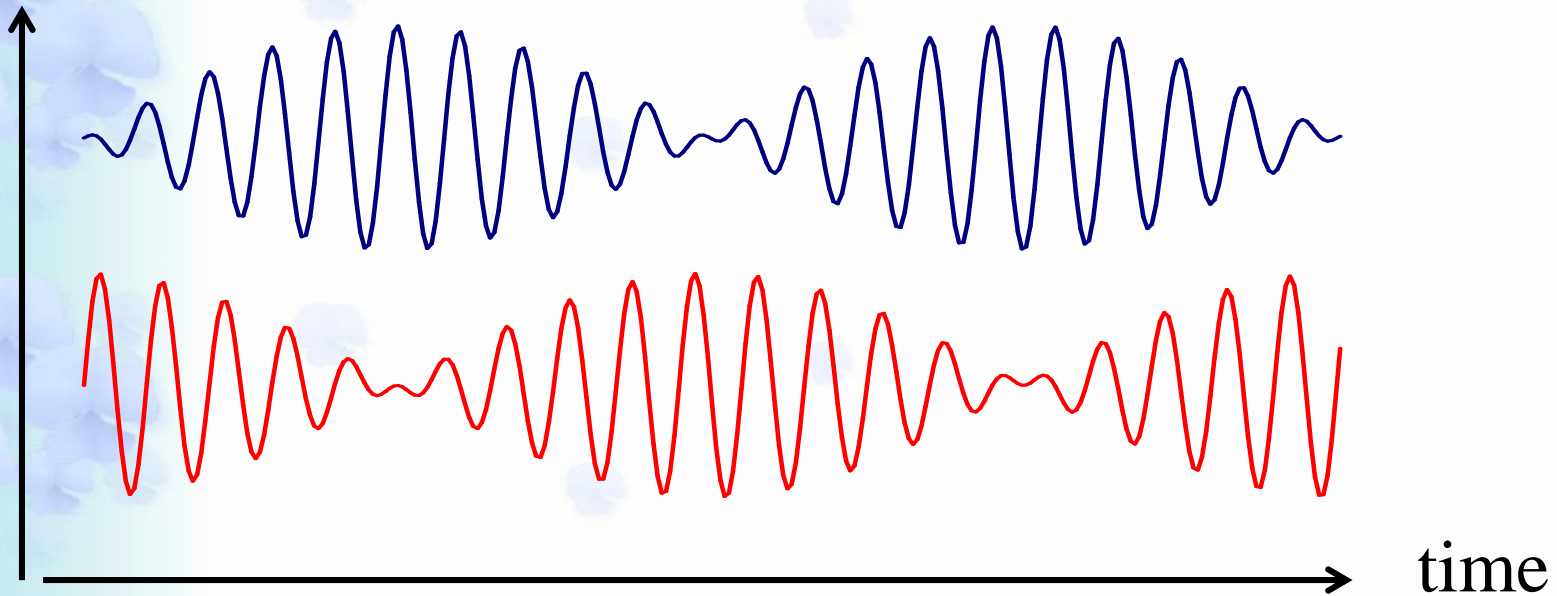

Electric Circuit: A treasure house of concept and language

Electric Circuit

Electromagnetic Field

- Lumped constant Circuit
- Distributed constant Circuit

Signal

- Noise
- Modulation
- Discrete signal

Material Science

- Metal
- Semi-conductor
- Ferromagnet

Linear response

- Transfer function
- Resonance
- Transient response

System stability

- Amplifier
- Feedback
- Nyquist diagram

Analog and digital

- Fourier tr.- z-tr.
- Analog filter - Digital filter

1.2 What is electric circuits?: Thunderbolt struck a plane!



Your answer?

1.



Fell down and crashed

2.



Damaged


3.



Nothing happened

Plasma frequency

$$m \frac{d^2 x}{dt^2} = -eE$$

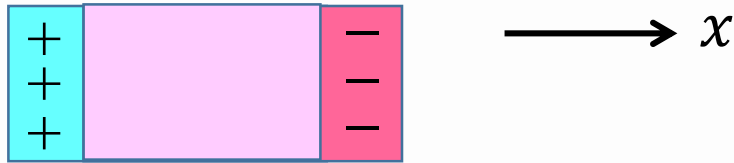

$$E = E_0 e^{-i\omega t}, \quad x = x_0 e^{-i\omega t} \rightarrow m\omega^2 x_0 = eE_0$$

$$\text{Electric polarization: } P = -n e x_0 = -\frac{n e^2 E_0}{m \omega^2}$$

$$\epsilon(\omega) = \frac{D(\omega)}{\epsilon_0 E(\omega)} = 1 + \frac{P(\omega)}{\epsilon_0 E(\omega)} = 1 - \frac{n e^2}{\epsilon_0 m \omega^2} = 1 - \frac{\omega_p^2}{\omega^2}$$

$$\omega_p^2 \equiv \frac{n e^2}{\epsilon_0 m} \quad : \text{ Plasma frequency}$$

$$\text{Cu: } n = 8.5 \times 10^{22} / \text{cc} \quad m^* = 1.3 m_0$$

$$f_p = \omega_p / (2\pi) = 2.3 \times 10^{15} \text{ Hz} \quad \lambda = 130 \text{ nm Near ultra-violet}$$

Metals are super-screening materials!



Equipotential lines

1.3 Various circuit diagrams




三田無線研究所
DELICA DX-CS-7

Picture diagram

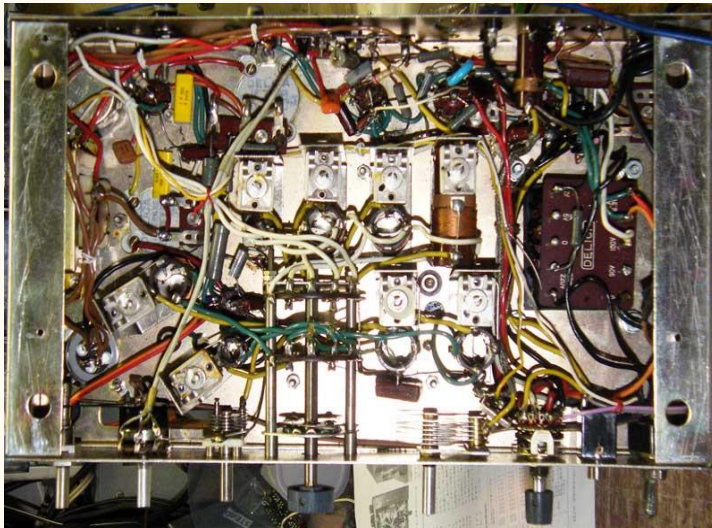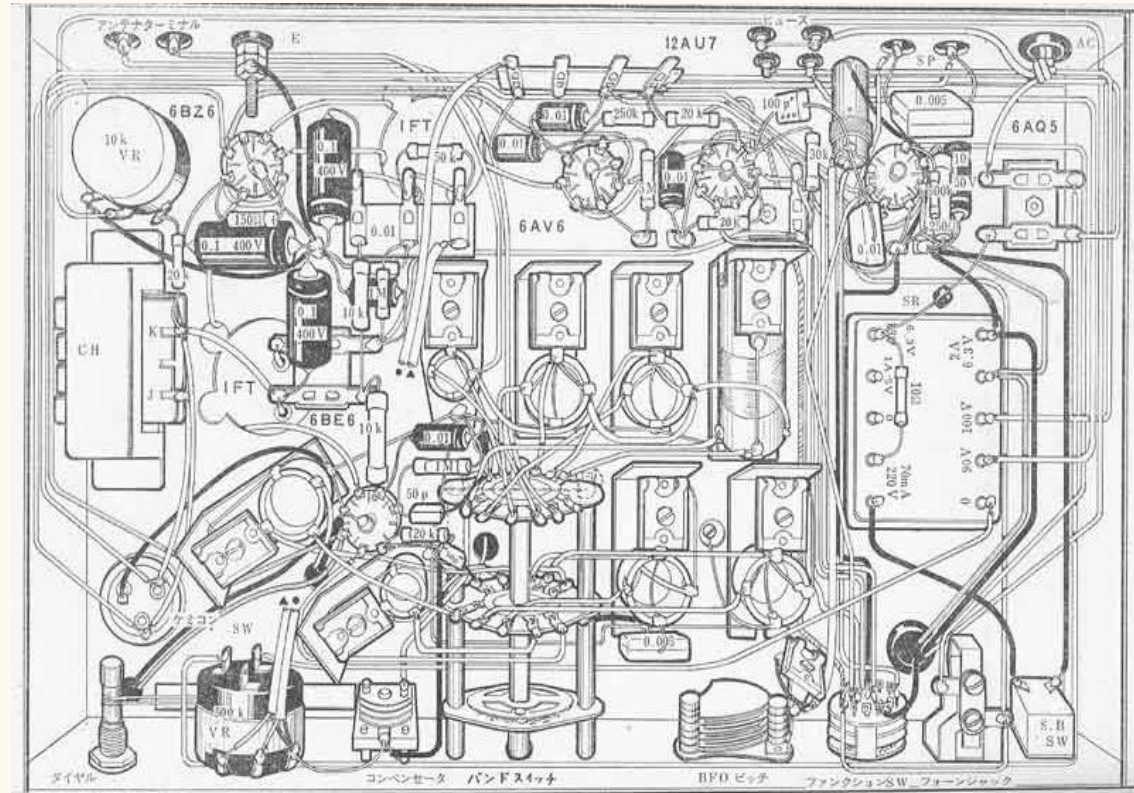


Various circuit diagrams

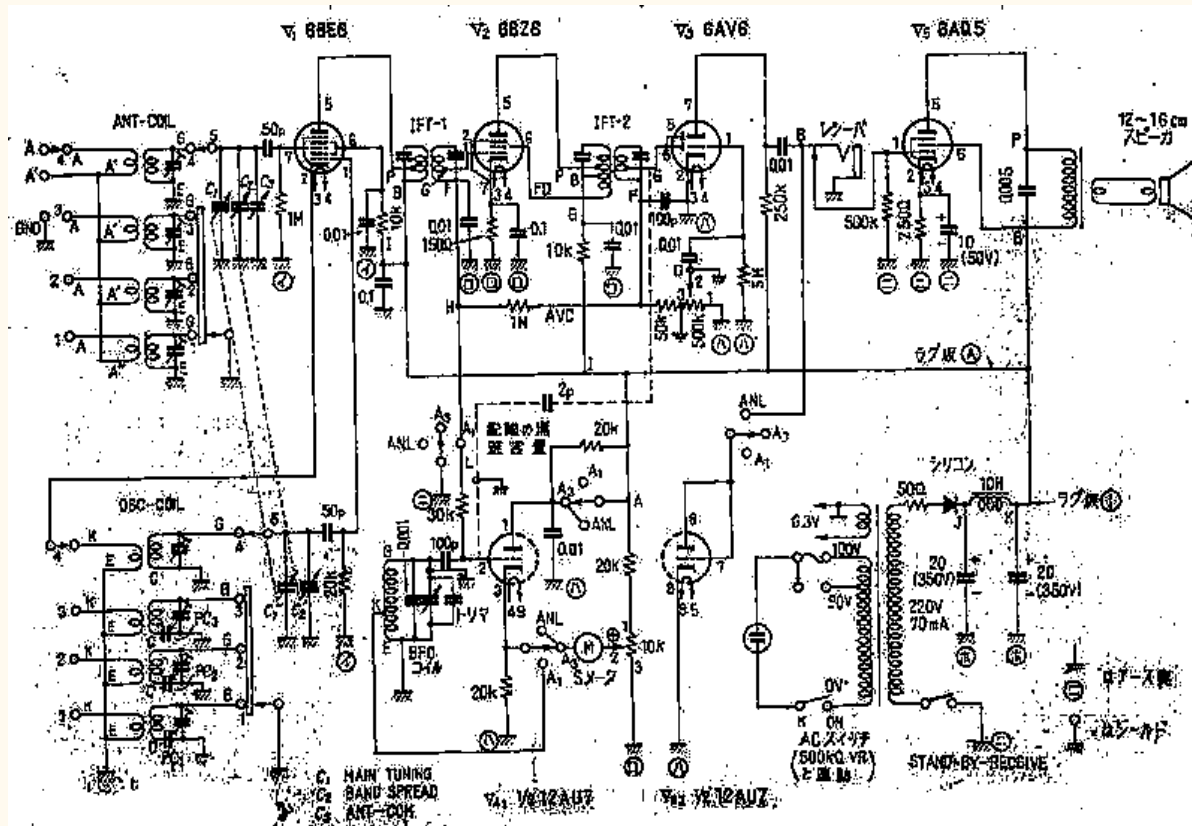


Parts + Wiring
= Wiring (Circuit) diagram

Block diagram

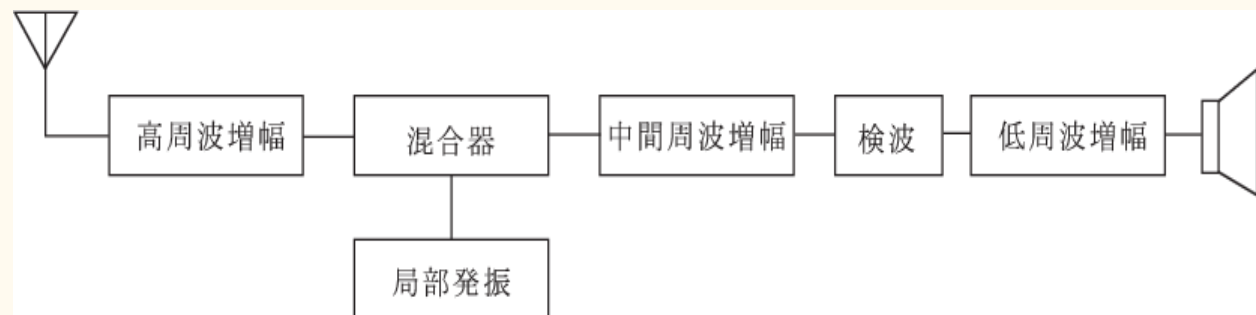

Wirings in electric circuits

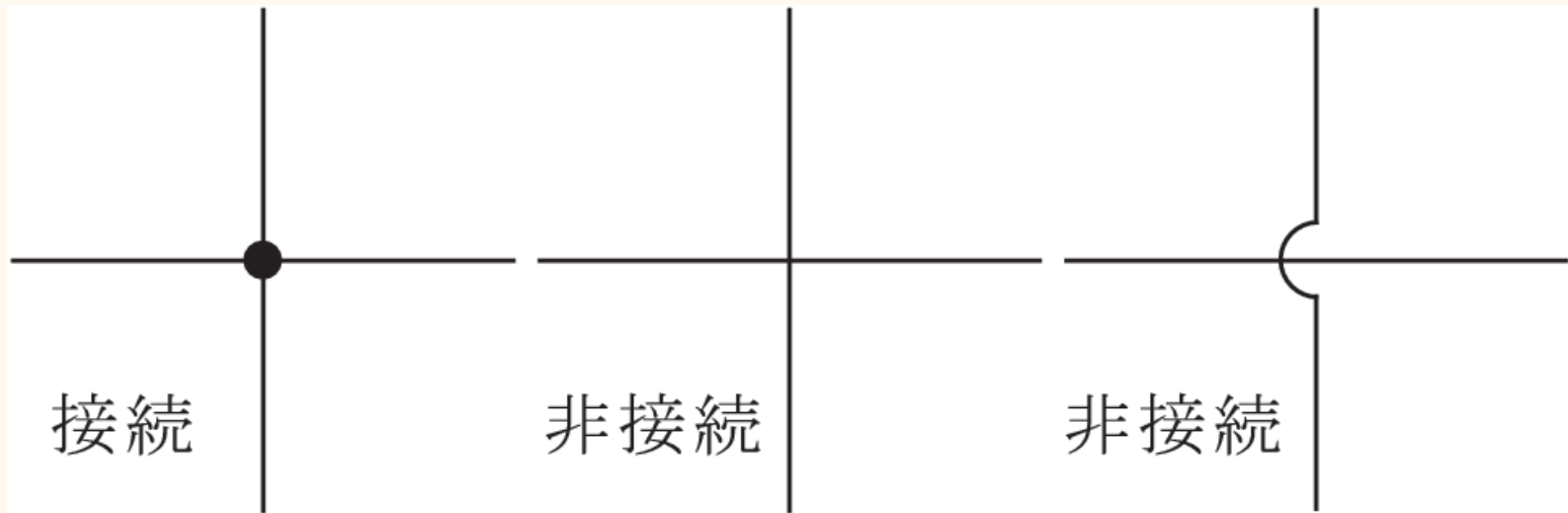

Connected

Not connected


Not connected

Violate electromagnetism theory


Concept of local electromagnetic field

= Lumped constant circuits (集中定数回路)

Circuit symbols for two-terminal devices

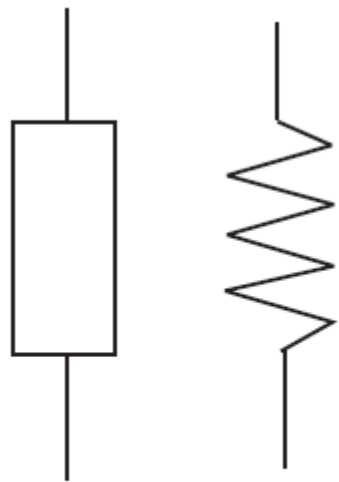

固定抵抗器

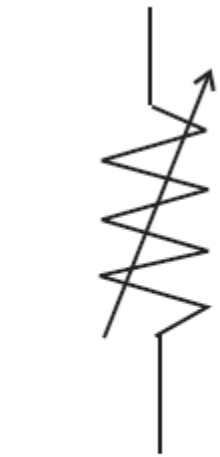


可変抵抗器



コンデンサ




可変
コンデンサ

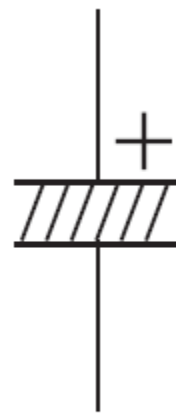

極性電解
コンデンサ




空芯コイル

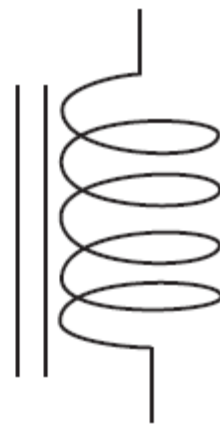


磁性体入り
コイル

Basic concepts in electric circuits

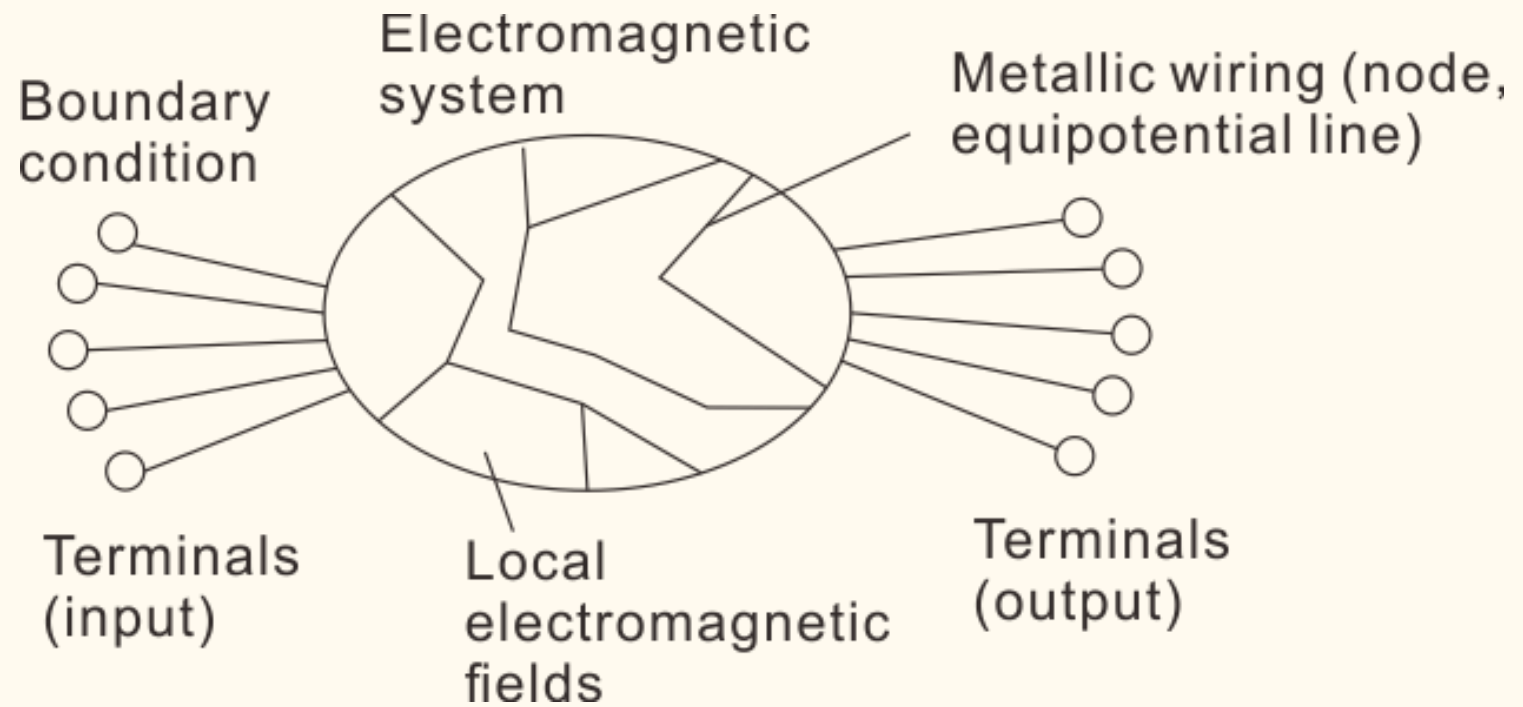


What is current-voltage characteristics?

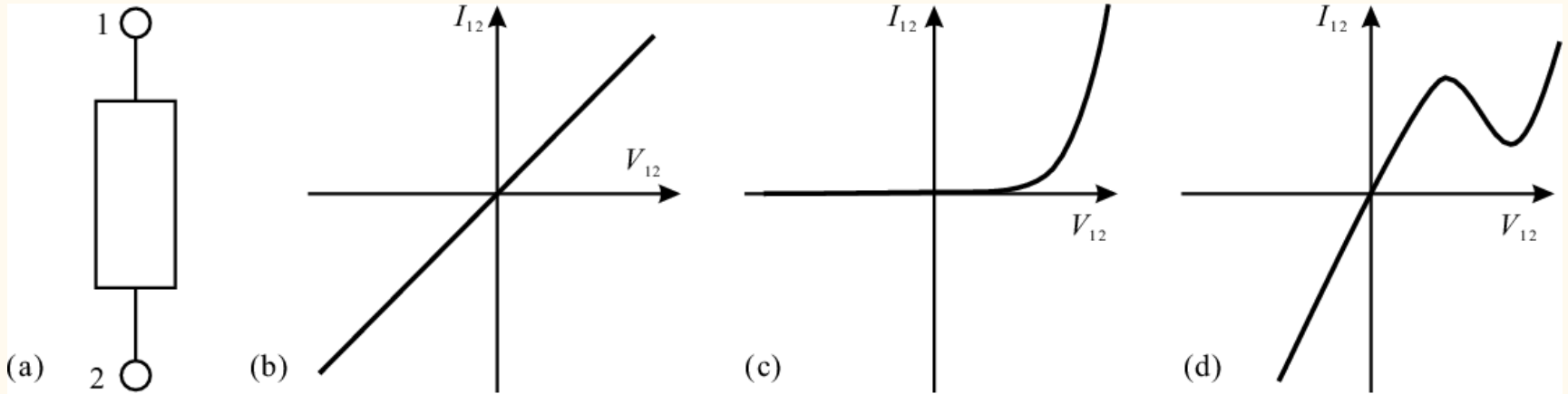

Resistor


What is current-voltage characteristics?

Curve tracer

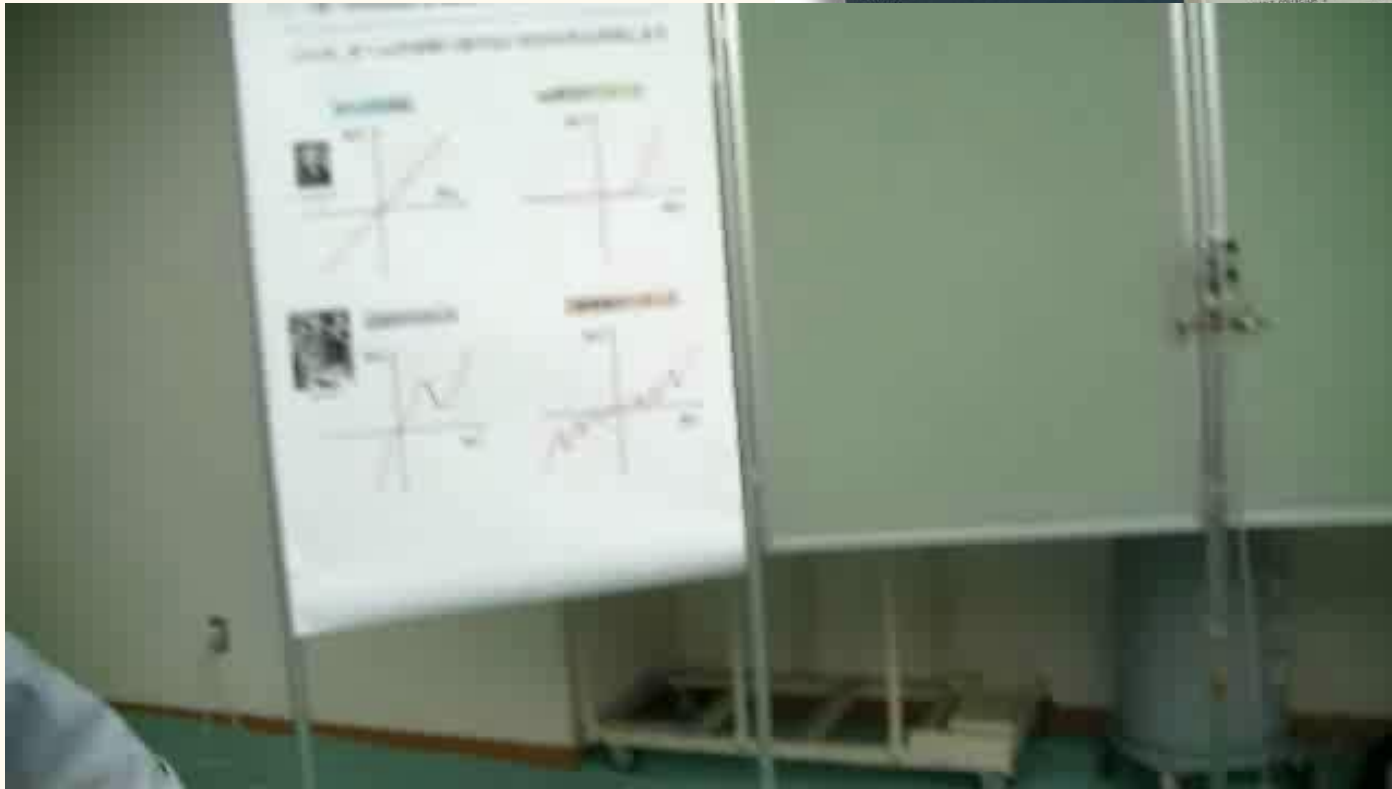

Variable resistors

Slide

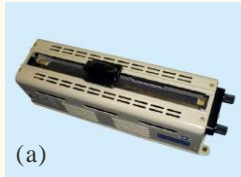

(a)



(b)



(c)




(d)


Carbon helical

Helical
potentiometer

Rotary switch
potentiometer

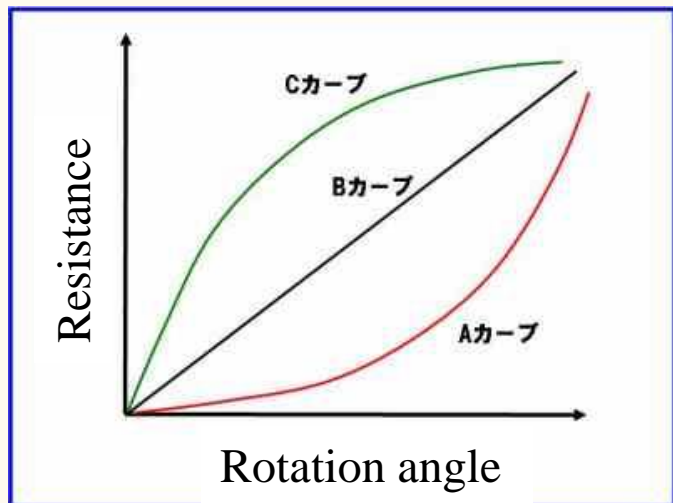


trimmer

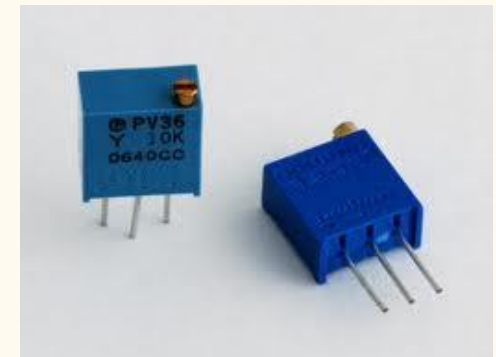

Cermet trimmer


Fixed resistors

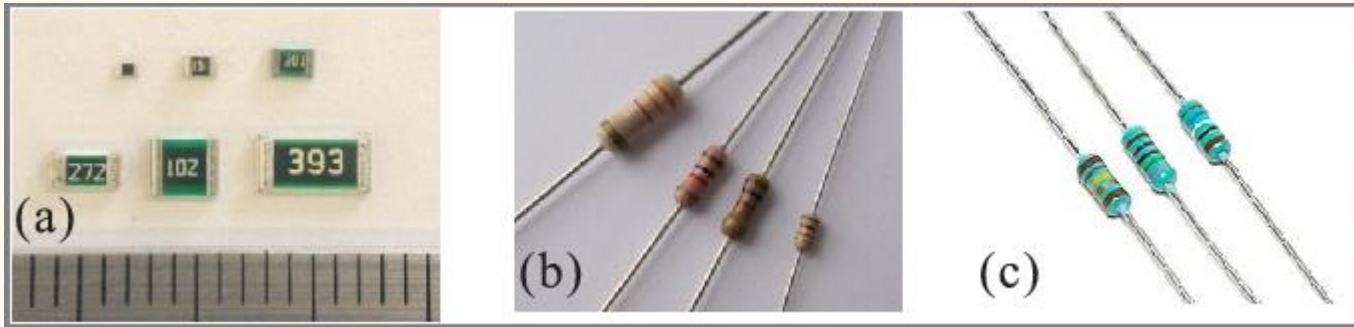


Chip resistors

Carbon film resistors

Metallic film resistors (spiral)


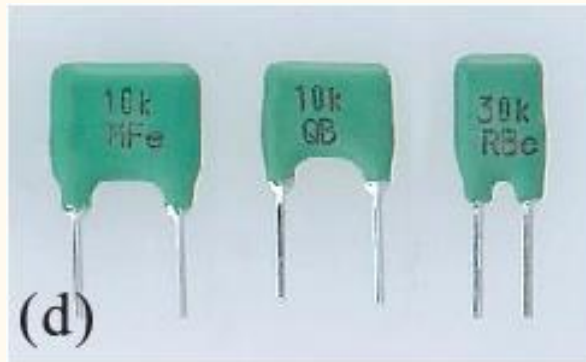


Metallic film resistors (meander)

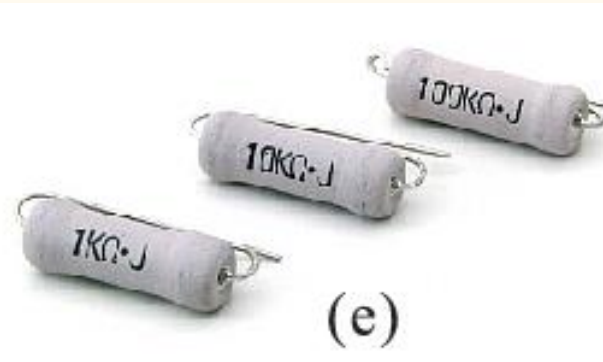


High power type

抵抗器のカラーコード

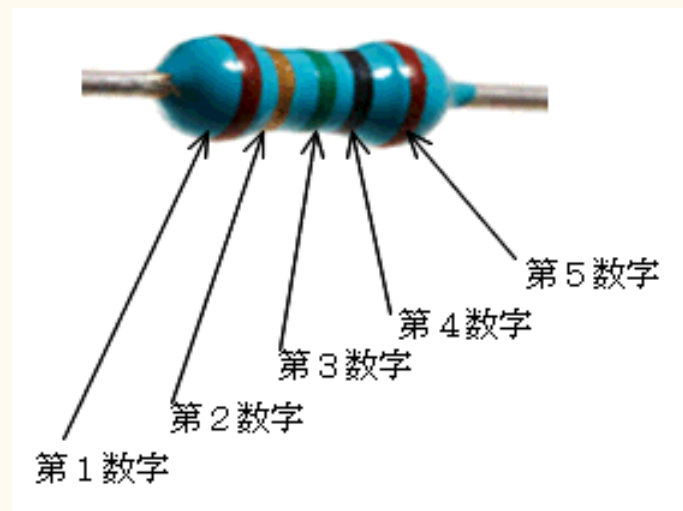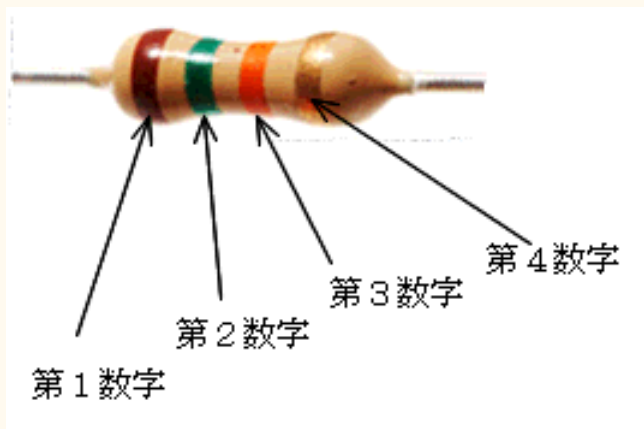

色	第1数字	第2数字	第3数字	第4数字	第5数字
黒	0	0	0	10^0	X
茶	1	1	1	10^1	±1%
赤	2	2	2	10^2	±2%
橙	3	3	3	10^3	X
黄	4	4	4	10^4	X
緑	5	5	5	10^5	X
青	6	6	6	10^6	X
紫	7	7	7	10^7	X
灰	8	8	8	10^8	X
白	9	9	9	10^9	X
金	X	X	X	10^{-1}	±5%
銀	X	X	X	10^{-2}	±10%
無色	X	X	X	X	±20%

Color code for resistors

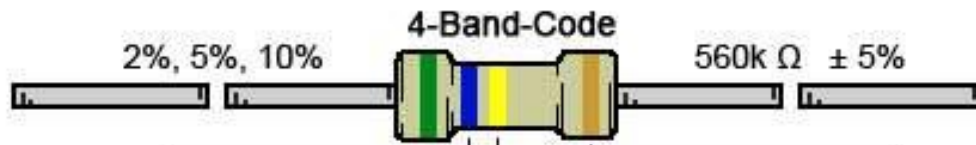

COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8		\pm 0.05%
White	9	9	9		
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)



Big
boys
race
our
young
girls
but
Violet
generally
wins.


Variable capacitors

$$C = \epsilon\epsilon_0 \frac{S}{d}$$



(a)

Steatite

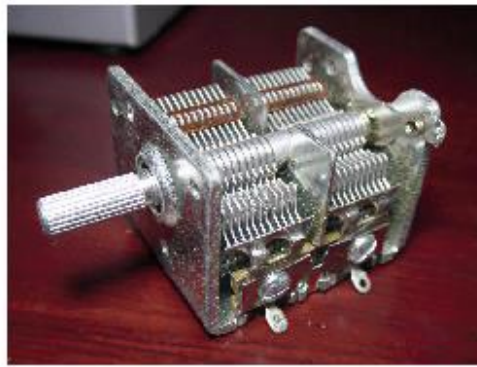

(b)

Tandem



(c)

Poly-Ethylene



(d)


Ceramic

Air capacitor


Fixed capacitors

Ceramic capacitors


Single disk pair type

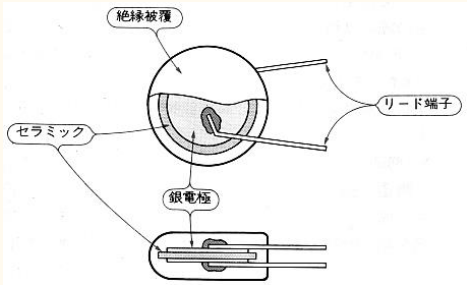

Stacked type

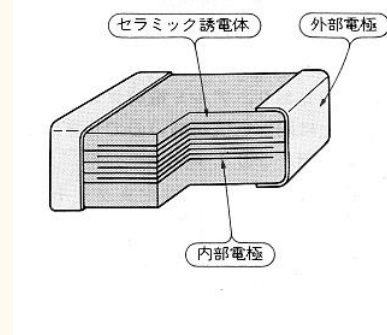


Film capacitors

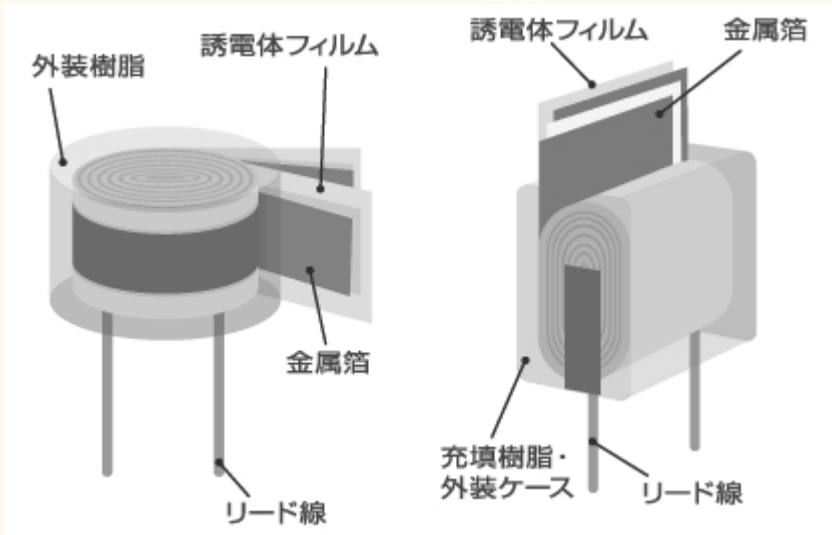

誘導





無誘導

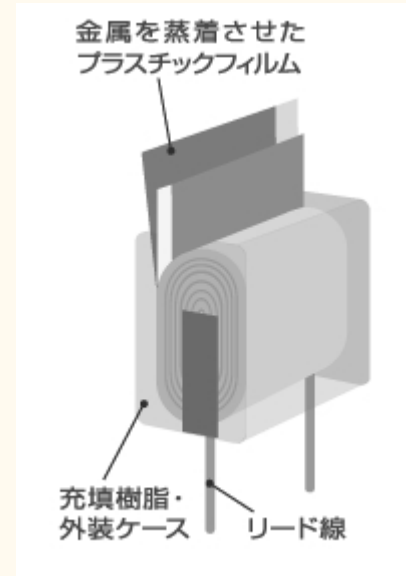


蒸着無誘導





Chemical capacitors

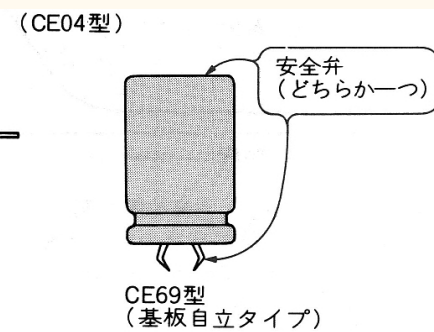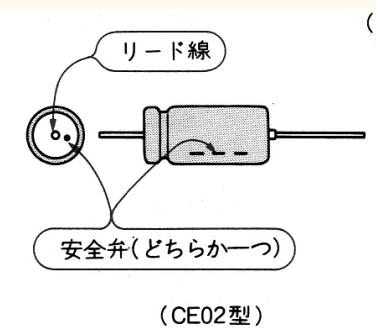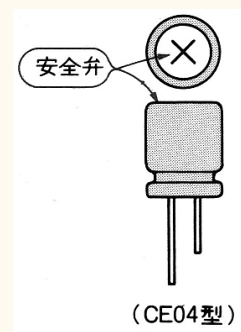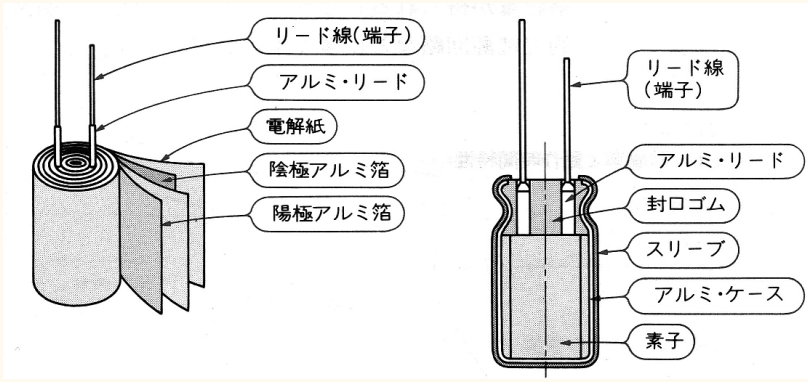

タンタル電解

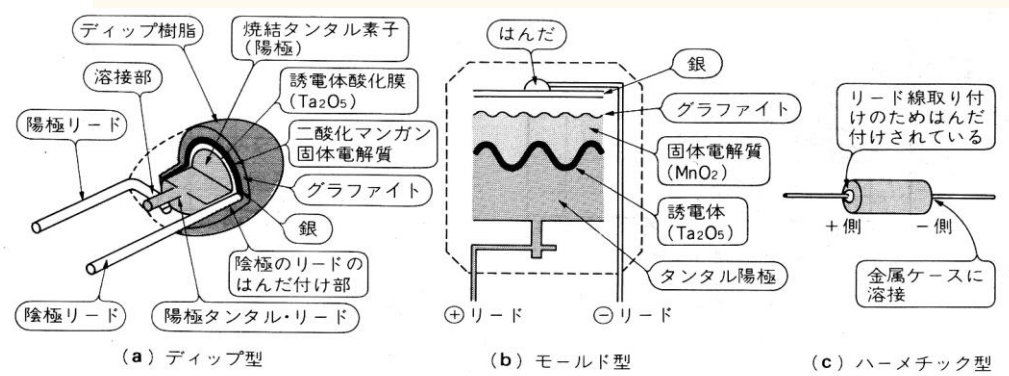

Surface mount chip capacitors

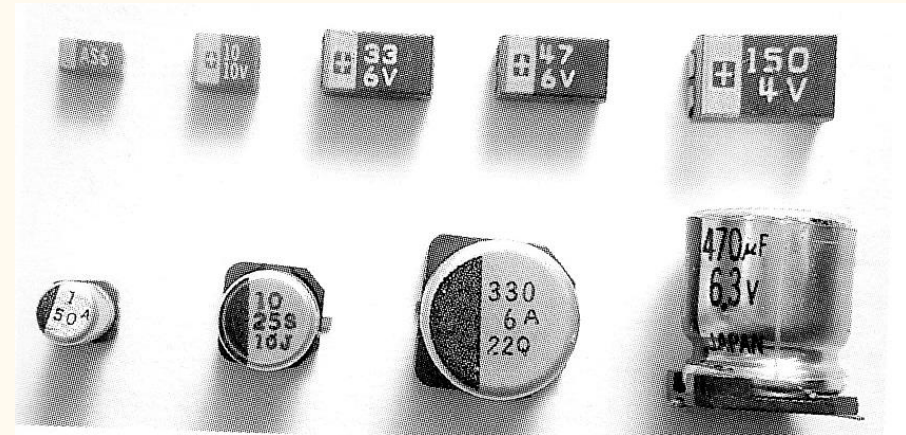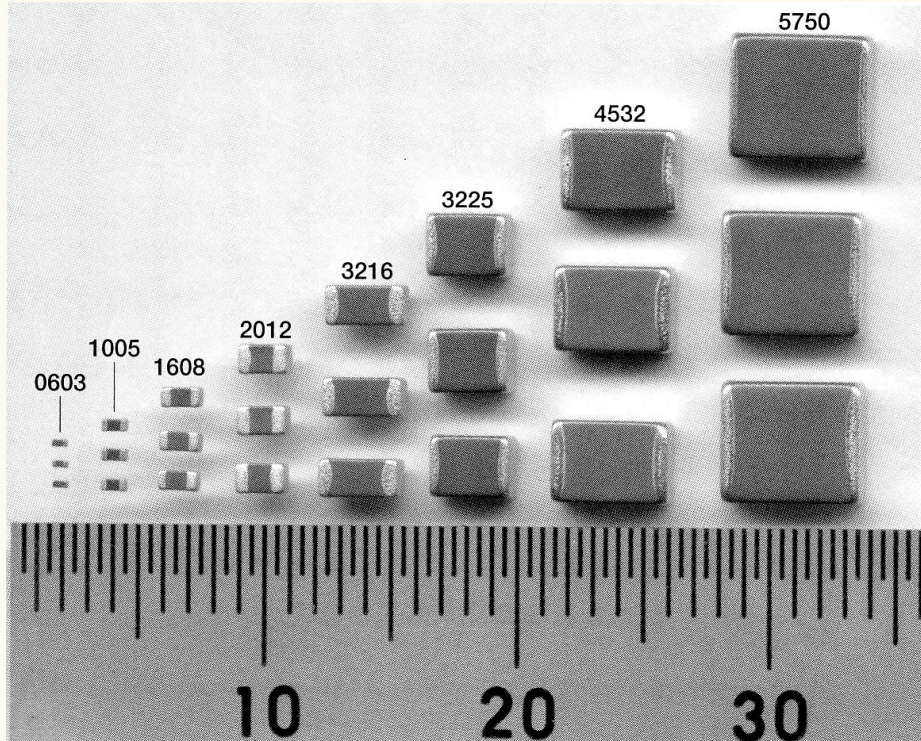


Variable inductors


$$L = K \times \mu \frac{N^2}{l} S = K \times \mu n N S$$

$$K(\text{Nagaoka coef.}) = \frac{4}{3\pi\sqrt{1-k^2}} \left[\frac{1-k^2}{k^2} K(k) - \frac{1-2k^2}{k^2} E(k) - k \right]$$
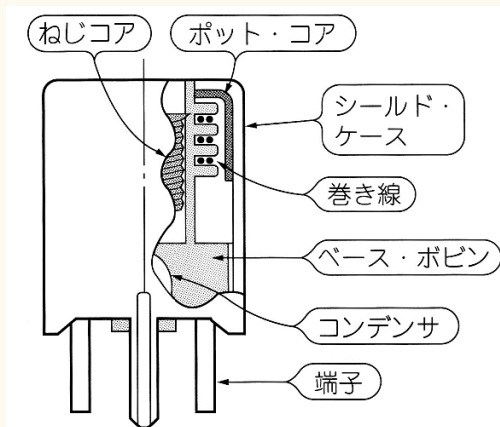
$$\frac{L}{2a} = \frac{\sqrt{1-k^2}}{k}$$




Fixed inductors

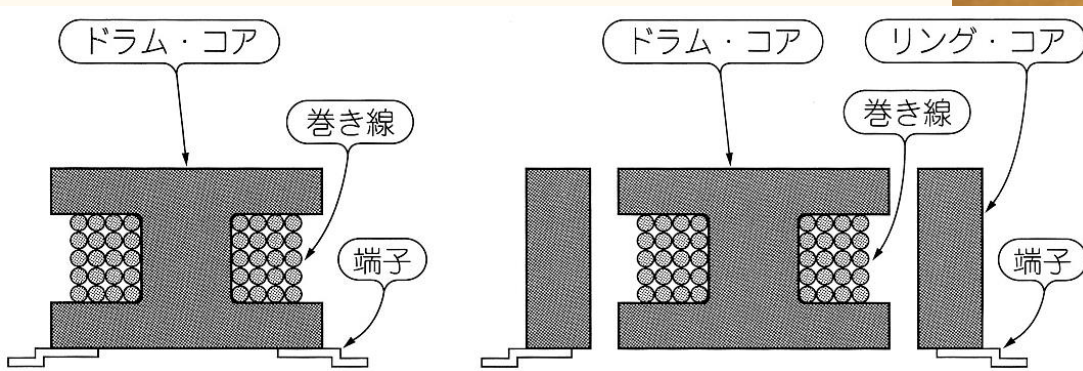


Open flux path

Closed flux path

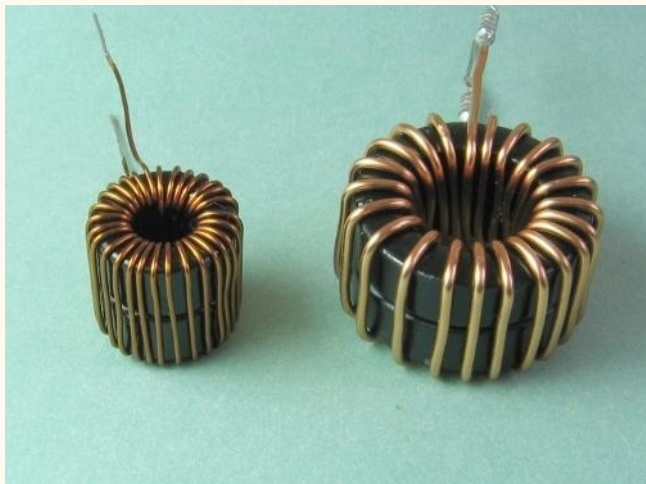

Toroidal coil

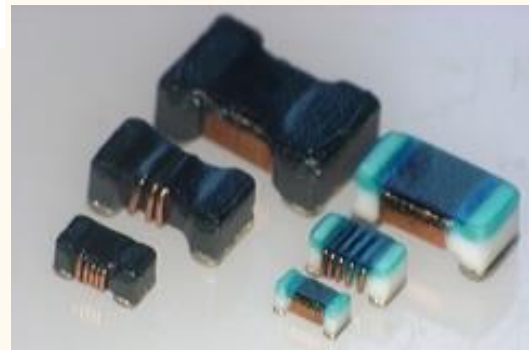

Chip inductor




Ch.2 Introduction to linear circuits

2.1 Linear system and electric circuit

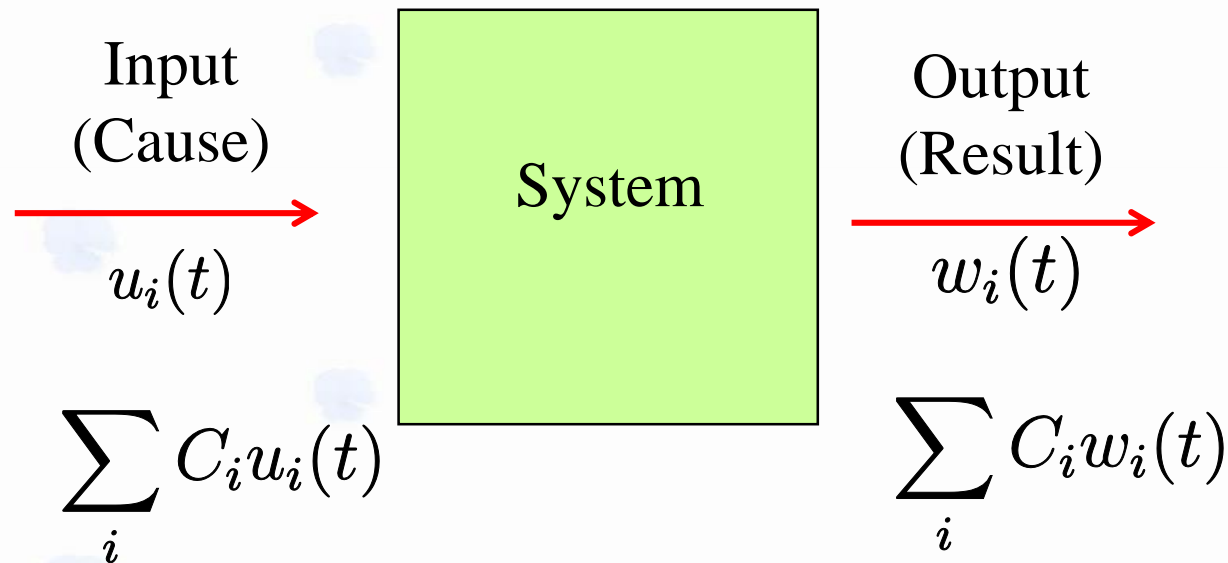2.1.1 What is linear system?

$$f(C_1x_1 + C_2x_2) = C_1f(x_1) + C_2f(x_2)$$



Linear system: definition

$$w(t) = \mathcal{R}\{u(t)\} \quad : \text{Response}$$

Requirements

$$\text{Invariance: } \forall t_1 \quad w(t - t_1) = \mathcal{R}\{u(t - t_1)\}$$

$$\text{Causality: } u(t) = 0 \ (t < t_1) \rightarrow w(t) = 0 \ (t < t_1)$$

Principle of superposition:

$$\forall C_1, C_2 \in C, \quad \mathcal{R}\{C_1 u_1(t) + C_2 u_2(t)\} = C_1 w_1(t) + C_2 w_2(t)$$


$$\mathcal{R}\left\{\sum_i C_i u_i(t)\right\} = \sum_i C_i w_i(t)$$

$$\mathcal{R}\left\{\int_{-\infty}^{\infty} c(q) u(q, t) dq\right\} = \int_{-\infty}^{\infty} c(q) \mathcal{R}\{u(q, t)\} dq$$

Transfer function

Variable $q \rightarrow$ time t

$$c(t) = \begin{cases} 1 & |t| \leq \delta t/2, \\ 0 & \text{others} \end{cases}$$

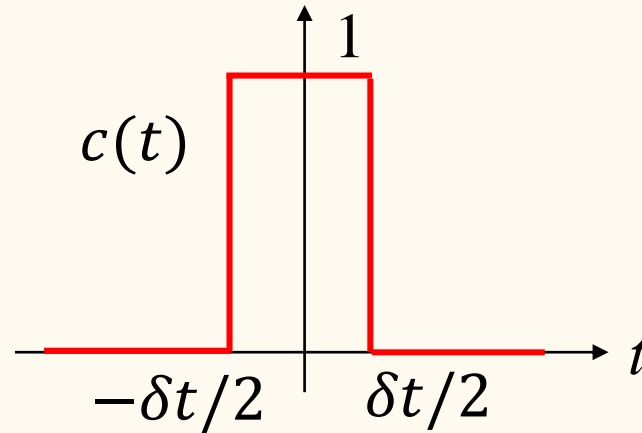

$$u(t) = \sum_i u(t_i) c(t - t_i) \quad \rightarrow \quad u(t) = \int_{-\infty}^{\infty} dt' u(t') c'(t - t')$$
$$c'(t - t') = \delta(t - t')$$

$$w(t) = \mathcal{R}\{u(t)\} = \mathcal{R}\left\{ \int_{-\infty}^{\infty} u(t') \delta(t - t') dt' \right\}$$
$$= \int_{-\infty}^{\infty} u(t') \mathcal{R}\{\delta(t - t')\} dt' = \int_{-\infty}^{\infty} u(t') \xi(t, t') dt'$$

Transfer function (Impulse response)

$\xi(t, t') \equiv \mathcal{R}\{\delta(t - t')\}$: Impulse response, weight function

Invariance $\rightarrow \xi(t, t_1) = \xi(t - t_1)$

$$w(t) = \int_{-\infty}^{\infty} u(t')\xi(t - t')dt' = \int_{-\infty}^{\infty} u(t - t')\xi(t')dt'$$

Convolution

Fourier transform:

$$X(\omega) = \int_{-\infty}^{\infty} x(t)e^{-i\omega t}dt, \quad x(t) = \int_{-\infty}^{\infty} X(\omega)e^{i\omega t}\frac{d\omega}{2\pi}$$

$$W(\omega) = U(\omega)\underline{\Xi(\omega)}$$

Transfer function



Summary

1. Electromagnetic field and electric circuits

Metals: super screening material

Circuit diagrams

Local electromagnetic field

2. Introduction to linear circuits

Transfer function