

# 電子回路論 第2回

理学系研究科・物理専攻 (物性研究所) 勝本信吾

2016.10.5

## Electric Circuits No.2

Shingo Katumoto

# ノート・資料等の置き場

<http://kats.issp.u-tokyo.ac.jp/kats/>



勝本信吾

Shingo Katsumoto



[自己紹介](#)

現在の研究テーマ

[論文リスト](#)

[「ポケットに電磁気を」が単行本になりました](#)

[出版された書籍](#)

[物理屋のための「電子回路論」講義ノート \(2015 Oct.-2016 Jun.\)](#)

[研究紹介](#)  
[メンバー](#)  
[実験装置](#)  
[投稿](#)  
[出版リスト](#)

2週に1回簡単な練習問題を出題 → 2週間以内に解答を提出

試験は期末レポート。練習問題と合わせて採点します

## Ch.1 Electromagnetic field and electric circuits

### Metals: super-screening material

(but not superconducting. The difference is important in designing superconducting circuits.)

### Local electromagnetic field



→ **Lumped constant circuits** (集中定数回路)

local magnetic fields (parts) are connected by metallic wires → **Circuit diagrams**

### Resistors, Capacitors and Inductors

## Ch.2 Introduction to linear response systems

# Outline Today

1. Transfer function (伝達関数) (continued)
2. Representative passive devices in the linear treatment
3. Impedance, admittance and other parameters in the linear treatment
4. Power sources
5. Circuit networks
6. Four terminal (two terminal-pair) circuits
7. Circuit theorems

# Linear response: Transfer function

response      input

$$\begin{aligned} \underline{w(t)} &= \mathcal{R}\{\underline{u(t)}\} = \mathcal{R}\left\{\int_{-\infty}^{\infty} u(t')\delta(t-t')dt'\right\} = \int_{-\infty}^{\infty} u(t')\underline{\mathcal{R}\{\delta(t-t')\}}dt' \\ &= \int_{-\infty}^{\infty} u(t')\xi(t-t')dt' = \int_{-\infty}^{\infty} u(t-t')\xi(t')dt' \end{aligned}$$

impulse response

$$X(\omega) = \int_{-\infty}^{\infty} x(t)e^{-i\omega t}dt \quad W(\omega) = U(\omega)\Xi(\omega)$$

Transfer function

Laplace:

$$X(s) = \int_0^{\infty} e^{-st}x(t)dt \quad W(s) = U(s)\Xi(s)$$

Expansion to the complex plane:  $s \rightarrow \sigma + i\omega$

On the imaginary axis (the frequency space)

$$W(i\omega) = U(i\omega)\Xi(i\omega)$$

# Impedance

Current to voltage

$$V_{12} = \hat{A}I_{12} \quad \left\{ \begin{array}{ll} V_{12} = RI_{12} & \text{resistor} \\ V_{12} = \frac{q(t)}{C} = \frac{1}{C} \int^t I_{12}(t') dt' & \text{capacitor} \\ V_{12} = L \frac{dI_{12}}{dt} & \text{inductor} \end{array} \right.$$

$$\Xi(i\omega) = \left\{ \begin{array}{ll} \int_{-\infty}^{\infty} e^{-st} [R\delta(t)] dt = R & \text{resistor} \\ \int_{-\infty}^{\infty} e^{-i\omega t} \left[ \frac{1}{C} \int^t \delta(t') dt' \right] dt = \frac{1}{i\omega C} & \text{capacitor} \\ \int_{-\infty}^{\infty} e^{-st} \left[ L \frac{d}{dt} \delta(t) \right] dt = i\omega L & \text{inductor} \end{array} \right.$$

↓

Impedance  $Z(i\omega)$

Voltage to current


$$\mathcal{J}(i\omega) = Y(i\omega)\mathcal{V}(i\omega)$$

Admittance  $Y(i\omega)$

$$Y(i\omega) = \frac{1}{Z(i\omega)}$$


# Example of equivalent circuit 「等価回路」の例

Spring pendulum (ばね振り子)

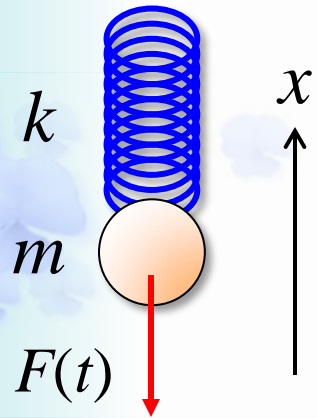

$$m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + kx = F(t)$$

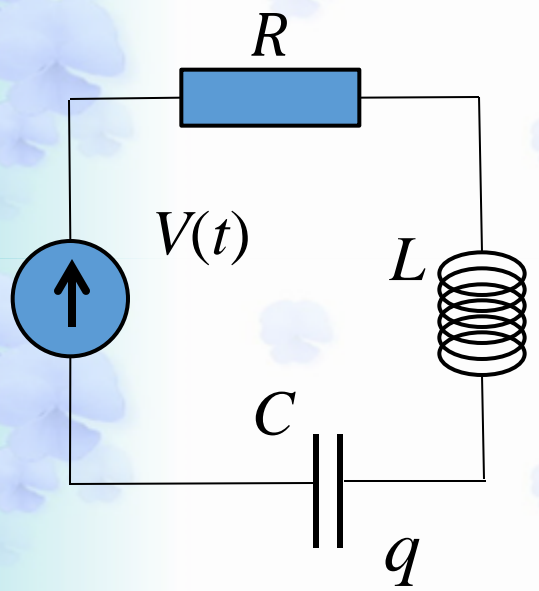RLC circuit with electromotive force (電源を接続したRLC回路)



$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = V(t)$$

Parallelism

並行論





## 2.2 Power sources


An active device: electric power source, electromotive force

Realistic power source: ideal power source + non-ideal factors

Ideal voltage source

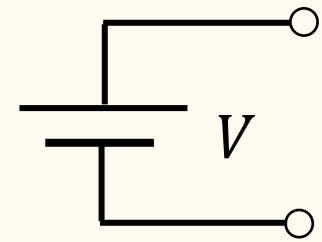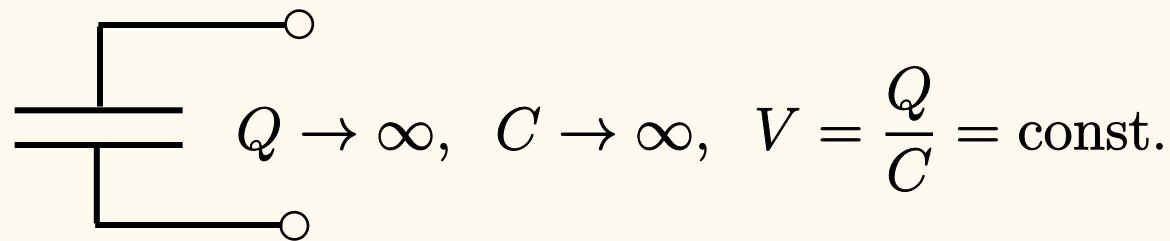

Voltage source  
+resistor


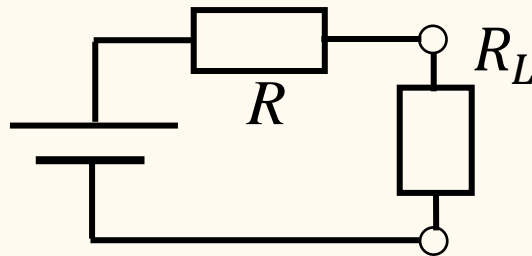


$$J = \frac{V}{R + R_L}$$


$$V_{out} = \frac{R_L}{R_L + R} V$$

Ideal current source
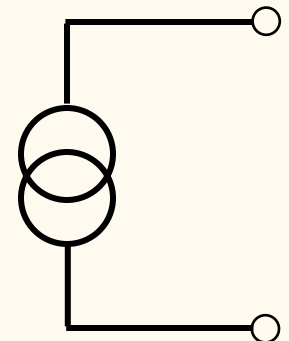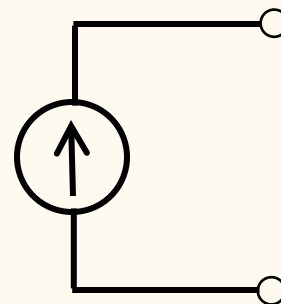
$$R \rightarrow \infty, V \rightarrow \infty, J = \frac{V}{R} = \text{const.}$$



# Power consumption

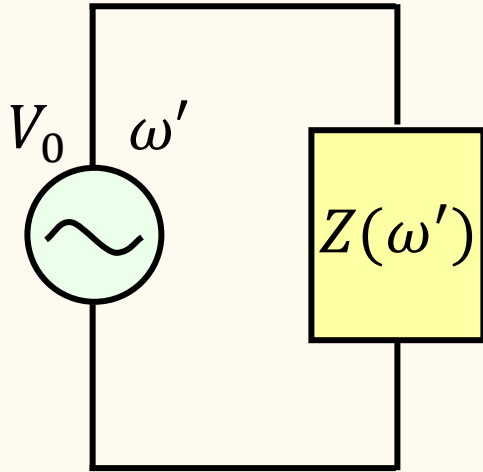

Energy dissipation per unit time:  $P = VJ$

Electric power consumption

$$V(\omega', t) = V_0 e^{i\omega' t}$$

$$\mathcal{V}(i\omega) = \mathcal{F}\{V\} = 2\pi V_0 \delta(\omega - \omega')$$

$$J(\omega', t) = 2\pi \int_{-\infty}^{\infty} \frac{V_0}{Z(i\omega)} \delta(\omega - \omega') e^{i\omega t} \frac{d\omega}{2\pi} = \frac{V_0}{Z(i\omega')} e^{i\omega' t} = \frac{V(\omega', t)}{Z(i\omega')}$$

$$V = V_0 \cos \omega' t \quad W(\omega', t) = V(\omega', t) J(\omega', t) = V_0^2 \cos^2 \omega' t / Z(\omega')$$

Complex instantaneous power

$$\overline{W}(\omega') = \frac{V_0^2}{2Z(\omega')}$$

$$P(\omega') \equiv \text{Re}[\overline{W}(\omega')]$$

$$Q(\omega') \equiv \text{Im}[\overline{W}(\omega')]$$

Effective power  
(有効電力)

Reactive power  
(無効電力)

# Power consumption (2)

$|\overline{W}(\omega')|$  Apparent power (皮相電力)

$$I_M \equiv \frac{\operatorname{Re}[\overline{W}(\omega')]}{|\overline{W}(\omega')|} = \cos [\arg(\overline{W}(\omega'))] \equiv \cos \phi$$

Moment (力率)

$\phi$ : Phase shift between voltage and current


$$\overline{W}(\omega') = |\overline{W}(\omega')|e^{i\phi} \quad : \text{generally holds}$$

$$\overline{W}(\omega') = V^*(\omega')J(\omega')$$

$$W = P = \frac{V_0^2}{2R} \quad \frac{V_0}{\sqrt{2}} \quad : \text{effective value}$$

## 2.3 Circuit network

### 2.3.1 Kirchhoff's law

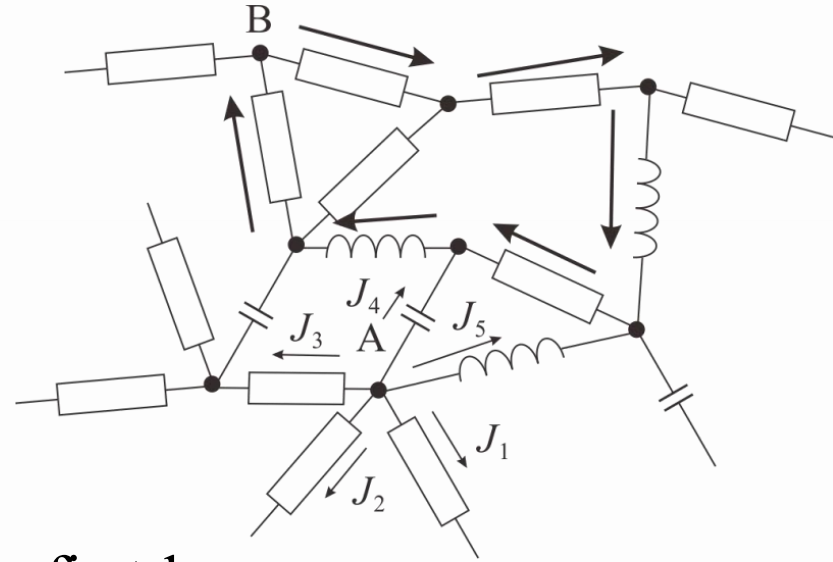

At all nodes  $\sum_i J_i = 0$  Kirchhoff's first law

↑ Charge conservation  $\frac{\partial \rho}{\partial t} + \text{div} \mathbf{J} = 0$   
 $\frac{\partial \rho}{\partial t}$   
 $= 0$

For all looping paths  $\sum_j V_j = 0$  Kirchhoff's second law

↑ Single-valuedness of electric potential


## 2.3 Circuit network (2)

From Kirchhoff's law, synthetic admittance and impedance are

for parallel connection: 
$$Y_{\text{tot}} = \sum_{i=1}^n Y_i, \quad Z_{\text{tot}} = \left( \sum_{i=1}^n Z_i^{-1} \right)^{-1}$$

for series connection: 
$$Y_{\text{tot}} = \left( \sum_{i=1}^n Y_i^{-1} \right)^{-1}, \quad Z_{\text{tot}} = \sum_{i=1}^n Z_i$$

Ex.)

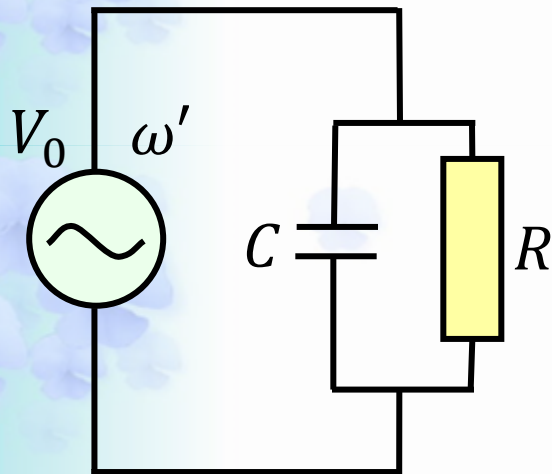

$$Z(i\omega) = \left( \frac{1}{R} + i\omega C \right)^{-1}, \quad Y(i\omega) = \frac{1}{R} + i\omega C$$

$$P(\omega) = \frac{V_0^2}{R} \cos^2 \omega t, \quad Q(\omega) = \omega C V_0^2 \cos^2 \omega t$$

$$\frac{P(\omega)}{Q(\omega)} = \frac{1}{\omega C R} = \tan \delta \quad : \text{Dissipation factor}$$

## 2.3.3 Superposition theorem

Network: node, (directional) branch : directional graph (digraph)

All the branches: electromotive force  $E_i$ , resistance  $R_i$

$$A\{(R)\} \begin{pmatrix} J_1 \\ \vdots \\ J_m \end{pmatrix} = \begin{pmatrix} E_1 \\ \vdots \\ E_m \end{pmatrix} \quad \mathbf{R} = \begin{pmatrix} R_1 \\ \vdots \\ R_m \end{pmatrix}$$


Superposition theorem:

The total current distribution is the superposition of those for single electromotive forces.

## 2.3.4 Ho (鳳) – Thevenin's theorem

Pick up two nodes in the network under consideration. The voltage between these two nodes is  $V_0$ . Set all the electromotive forces to zero and measure the resistance between the two nodes. The result is  $R_0$ . Now connect the two nodes with resistance  $R$  and reset the electromotive forces to the original values. Then the current through resistance  $R$  is

$$J = V_0 / (R + R_0)$$

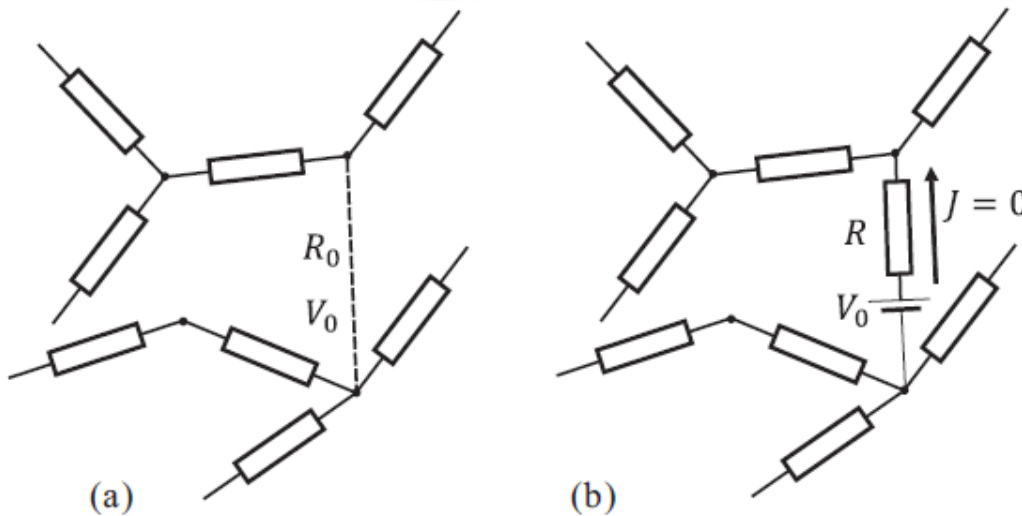

## 2.3.5 Tellegen's theorem

$i = 1, \dots, n$ : index of nodes,  $j = 1, \dots, m$ : index of branches

$$a_{ij} = \begin{cases} 1 & : i \text{ is the start of } j, \\ -1 & : i \text{ is the end of } j, \\ 0 & : \text{others} \end{cases} \quad \text{incidence matrix}$$

$$\forall j : \sum_{i=1}^n a_{ij} = 0 \quad : \text{redundancy in } \{a_{ij}\}$$

$\rightarrow (n - 1) \times m$  matrix  $D$  : irreducible incidence matrix

Kirchhoff's first law:  $D\mathbf{J} = 0$   $J_j$ : current along branch  $j$

$\mathbf{W}$ :  $W_i$  electrostatic potential of node  $i$ ,  $\mathbf{V}$ :  $V_j$  voltage across branch  $j$

$$i \bullet \xrightarrow{j} \bullet k \quad V_j = W_i - W_k = a_{ij}W_i - a_{kj}W_k$$

$$\mathbf{V} = {}^t\mathcal{D}\mathbf{W} \quad ({}^t\mathcal{D}: \text{transpose}) \quad (\text{Kirchhoff's second law})$$


$$\sum_{i=1}^m V_i J_i = ({}^t\mathcal{D}\mathbf{W}) \cdot \mathbf{J} = {}^t\mathbf{W}\mathcal{D}\mathbf{J} = 0 \quad \mathbf{V} \perp \mathbf{J}$$




# 4-terminal (2-terminal pair) circuits 4端子回路

Terminal pair (端子对)

Current: circulation, no net current

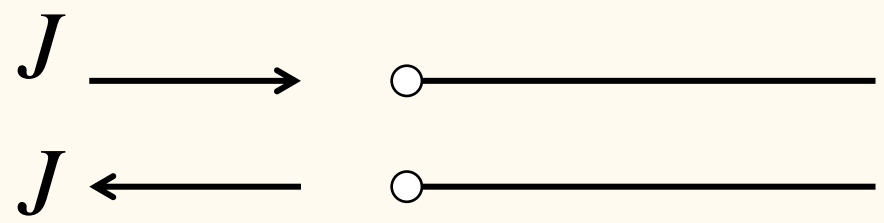


2-terminal pair (4-terminal) circuit

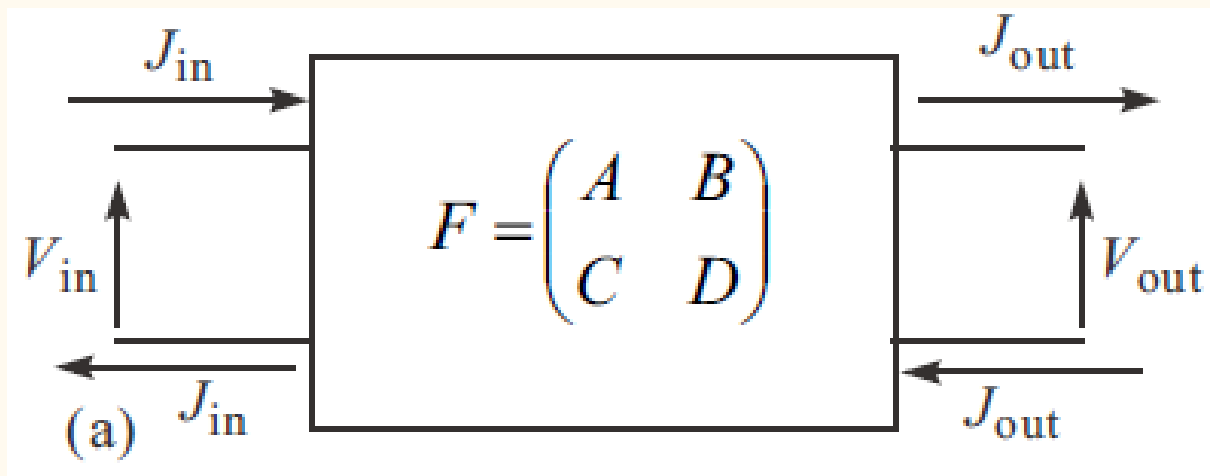

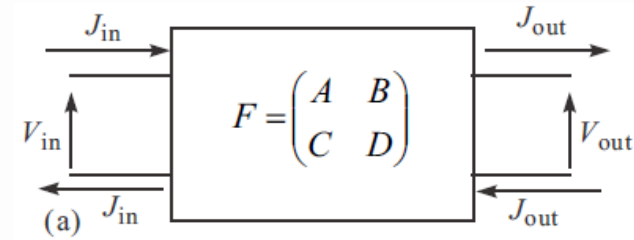
# F-matrix of 4-terminal circuit

$$\begin{pmatrix} V_{\text{in}} \\ J_{\text{in}} \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_{\text{out}} \\ J_{\text{out}} \end{pmatrix} \equiv F \begin{pmatrix} V_{\text{out}} \\ J_{\text{out}} \end{pmatrix}$$




$$A = \left( \frac{V_{\text{in}}}{V_{\text{out}}} \right)_{J_{\text{out}}=0}, \quad B = \left( \frac{V_{\text{in}}}{J_{\text{out}}} \right)_{V_{\text{out}}=0}, \quad C = \left( \frac{J_{\text{in}}}{V_{\text{out}}} \right)_{J_{\text{out}}=0}, \quad D = \left( \frac{J_{\text{in}}}{J_{\text{out}}} \right)_{V_{\text{out}}=0}.$$
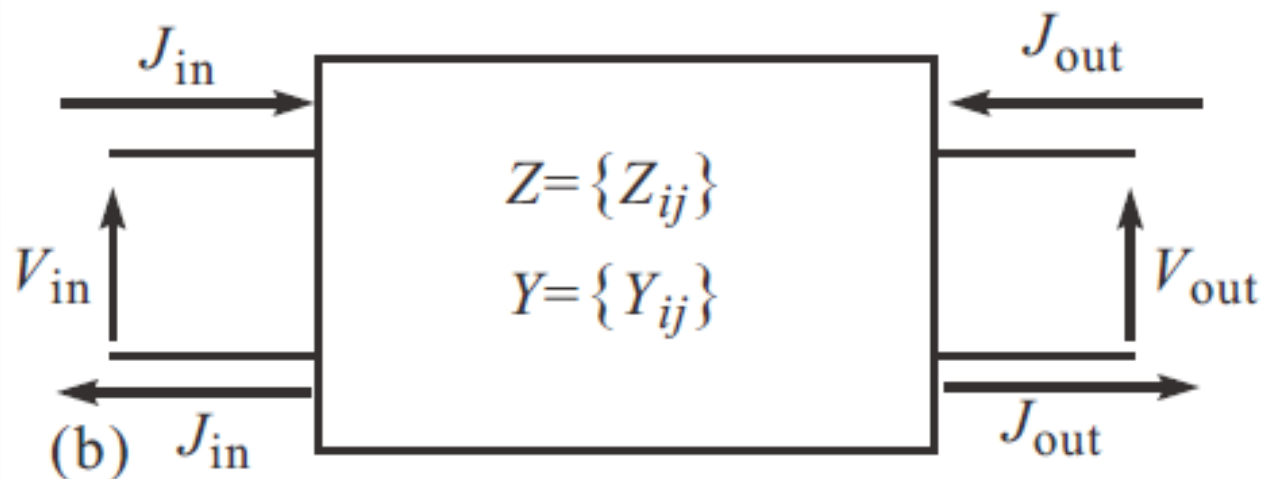
$$\begin{pmatrix} V_{\text{out}} \\ J_{\text{out}} \end{pmatrix} = \begin{pmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{pmatrix} \begin{pmatrix} V_{\text{in}} \\ J_{\text{in}} \end{pmatrix} \equiv K \begin{pmatrix} V_{\text{in}} \\ J_{\text{in}} \end{pmatrix}$$







# Impedance matrix, Admittance matrix

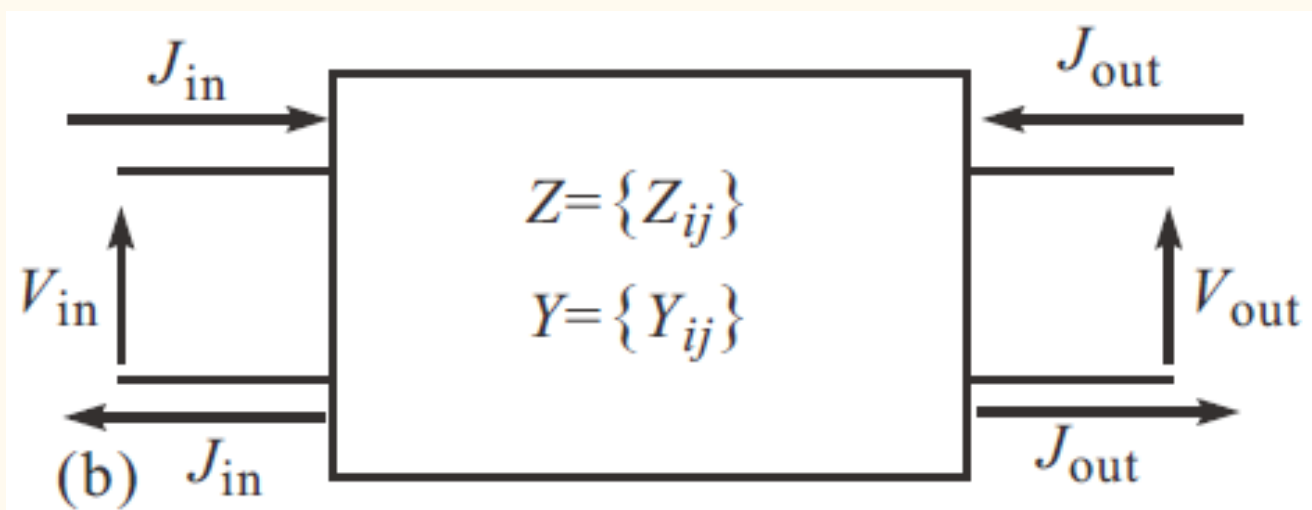

$$\begin{pmatrix} V_{in} \\ V_{out} \end{pmatrix} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} \begin{pmatrix} J_{in} \\ J_{out} \end{pmatrix} \equiv Z \begin{pmatrix} J_{in} \\ J_{out} \end{pmatrix}$$


$$\begin{pmatrix} J_{in} \\ J_{out} \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} V_{in} \\ V_{out} \end{pmatrix} \equiv Y \begin{pmatrix} V_{in} \\ V_{out} \end{pmatrix}$$

# Examples with impedances

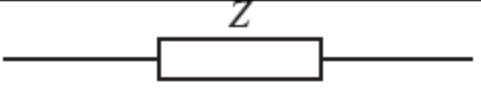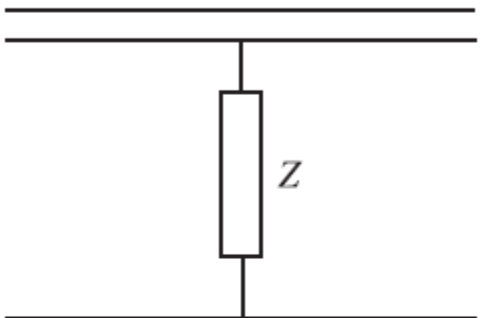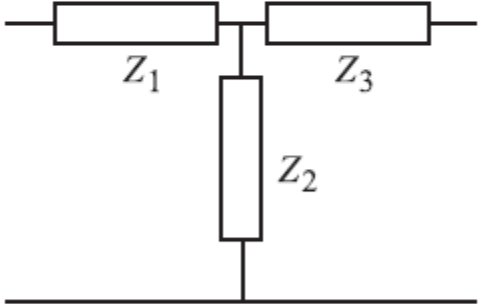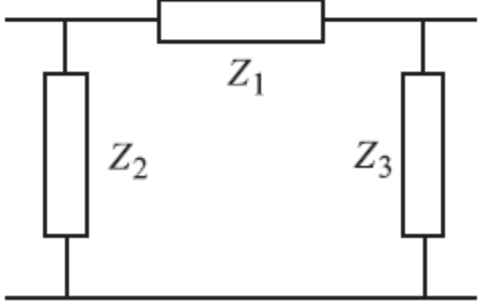	A	B	C	D
	1	$Z$	0	1
	1	0	$\frac{1}{Z}$	1
	$1 + \frac{Z_1}{Z_2}$	$\frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$	$\frac{1}{Z_2}$	$1 + \frac{Z_3}{Z_2}$
	$1 + \frac{Z_1}{Z_3}$	$Z_1$	$\frac{Z_1 + Z_2 + Z_3}{Z_2 Z_3}$	$1 + \frac{Z_1}{Z_2}$


# Connections of 4-terminal circuits

Cascade

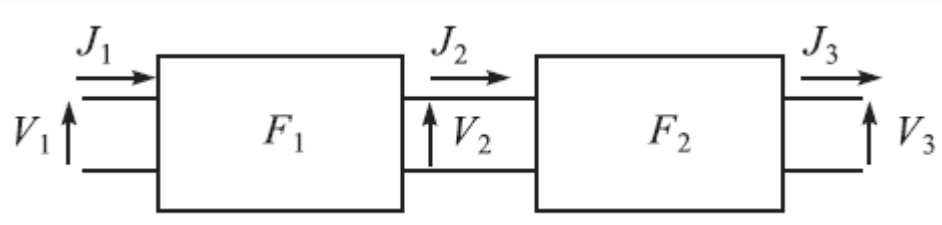


$$F_{\text{tot}} = \prod_{i=1}^N F_i$$

Series

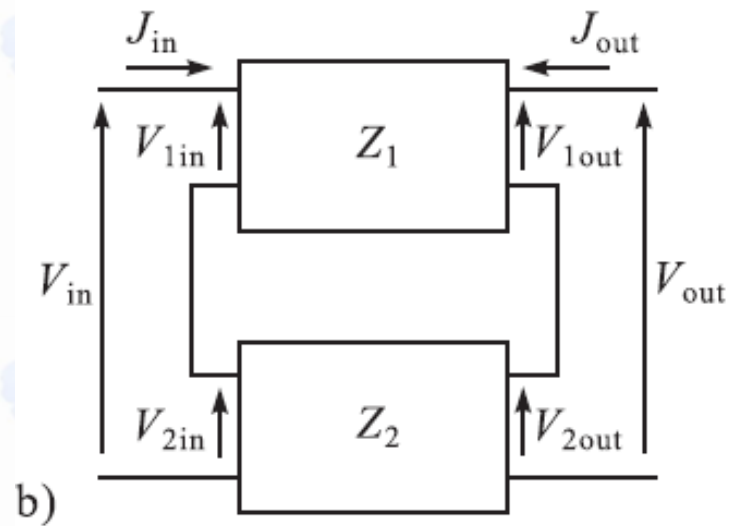

$$Z_{\text{tot}} = \sum_{i=1}^N Z_i$$


Parallel

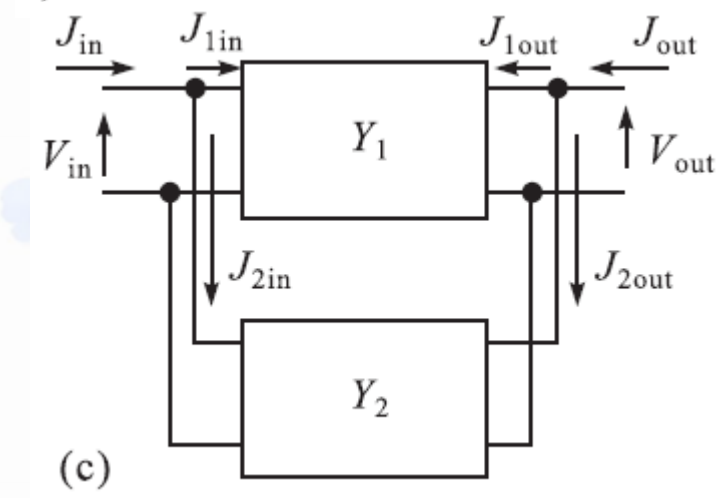


$$Y_{\text{tot}} = \sum_{i=1}^N Y_i$$

# Theorems for terminal-pair circuits


## Superposition theorem

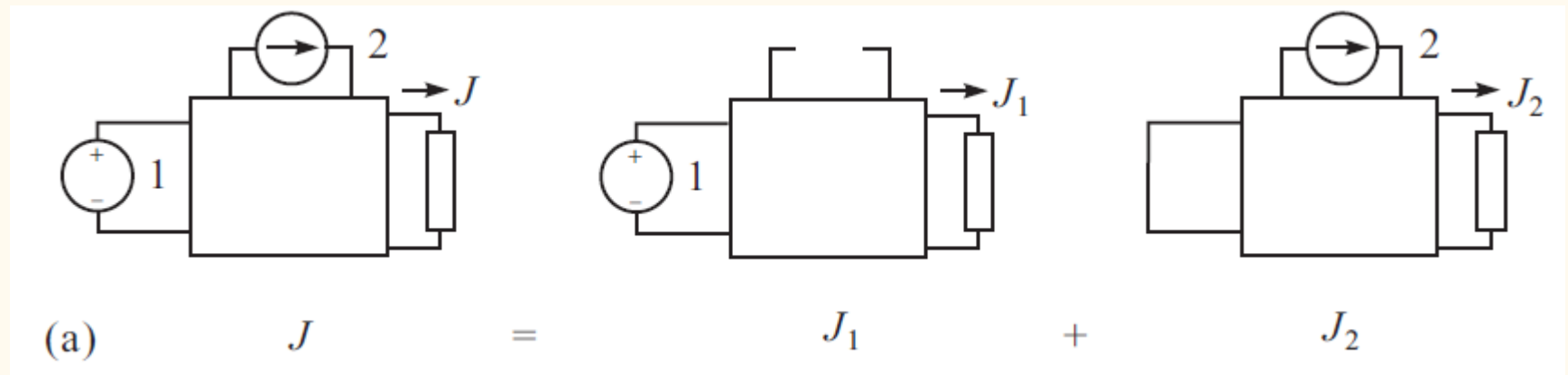

## Ho-Thevenin's theorem

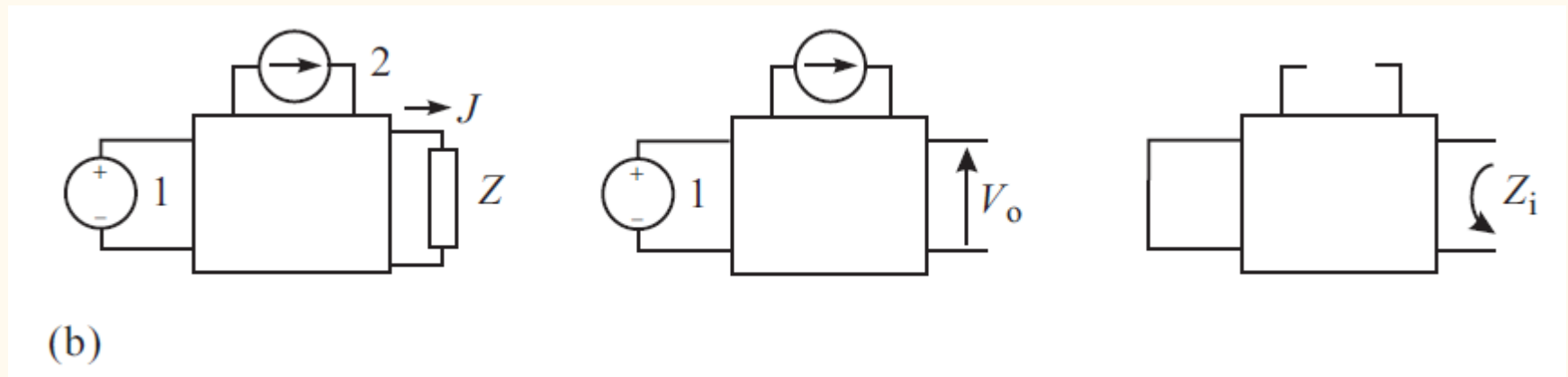

# Norton's theorem

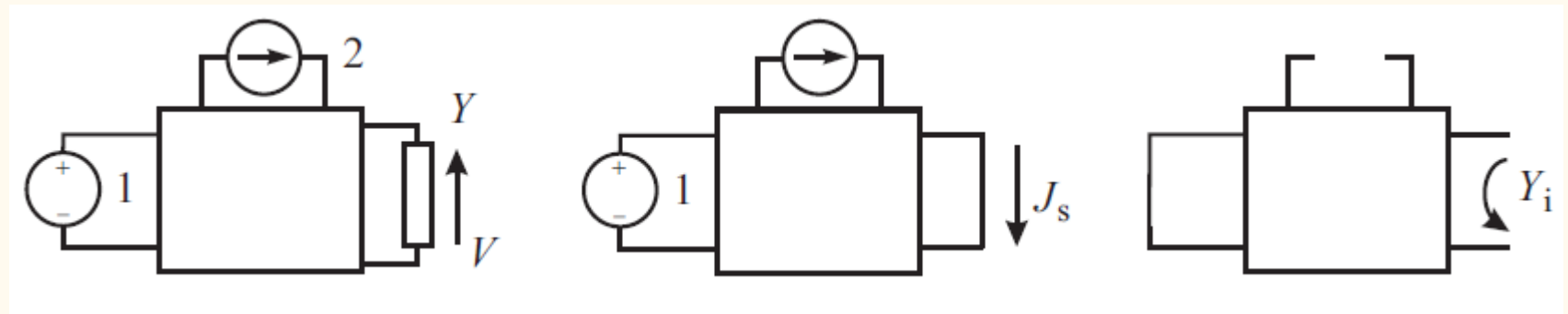

$$V = \frac{J_s}{Y + Y_i}$$

# Duality 双対性

直列接続	並列接続
開放	短絡
電場	磁場
キルヒホッフの第2法則	キルヒホッフの第1法則
電圧	電流
インピーダンス	アドミッタンス
抵抗	コンダクタンス
静電容量	インダクタンス
鳳-テブナンの定理	ノートンの定理




# Duality

Series	Parallel
Open	Short
Voltage	Current
Impedance	Admittance
Capacitance	Inductance
Electric field	Magnetic field
Resistance	Conductance
Ho-Thevenin	Norton
Kirchhoff's 2 <sup>nd</sup> law	Kirchhoff's 1 <sup>st</sup> law

# Power Sources in Lab. 電源の雑知識

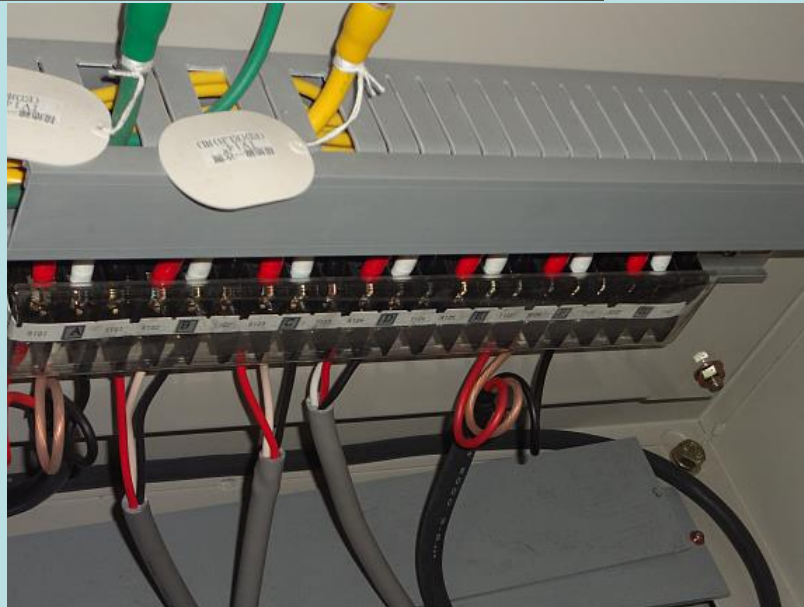
## AC Power from distribution board 配電盤からの電力供給


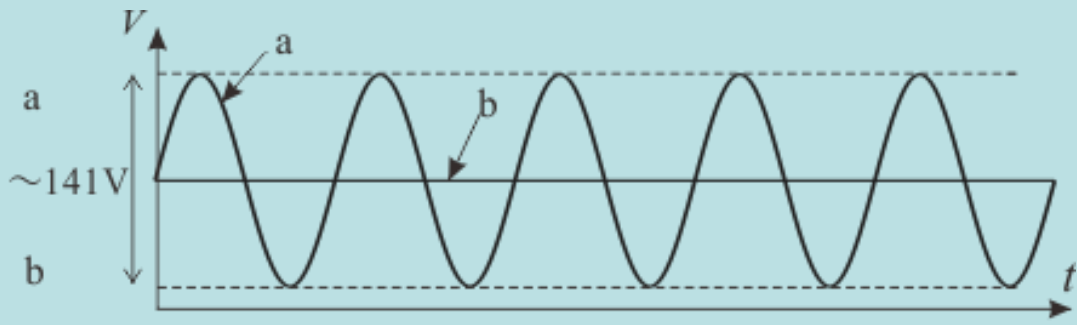
# AC Power from distribution board 配電盤からの電力供給


单相 2 線式  
(100 V)

電圧線 ————— a  
Single-phase 2-wire  
中性線 ————— b  
(GND)



单相 3 線式  
(100 V, 200 V)

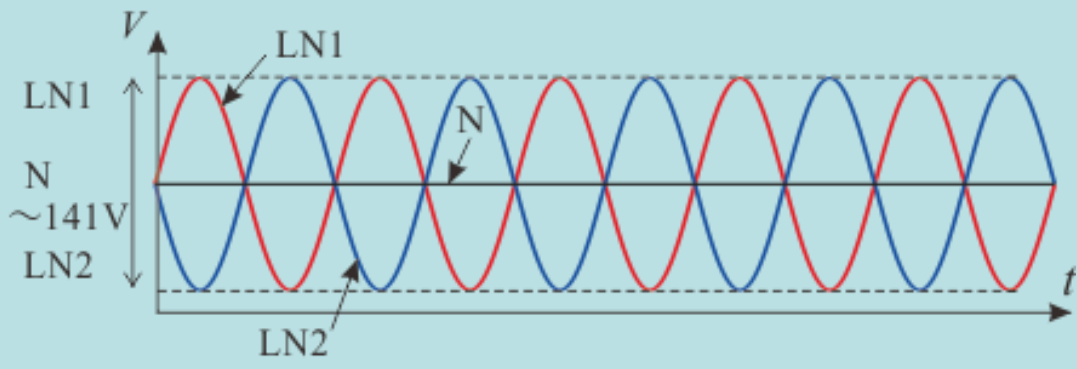
電圧線 ————— LN1  
中性線 ————— N  
(GND)  
電圧線 ————— LN2



Single-phase 3-wire


3 相 3 線式

第一相 ————— R  
第二相 ————— S  
第三相 ————— T

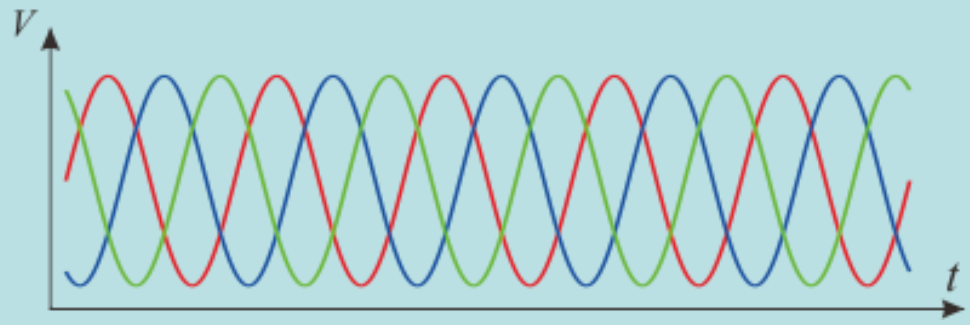

Three-phase 3-wire
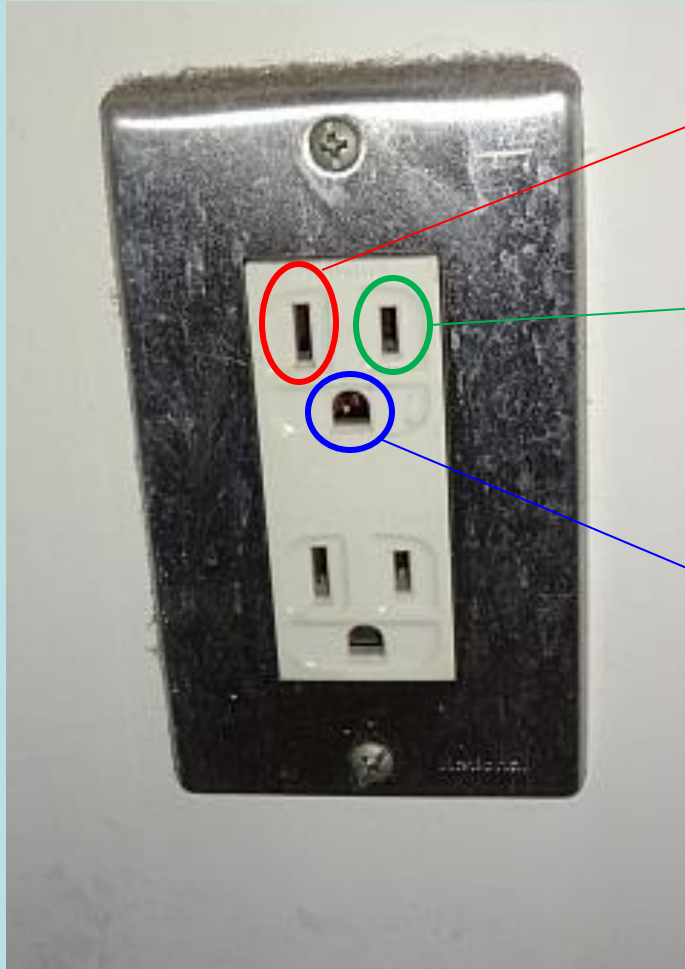
# Japanese outlet tap definition 日本式コンセント



Cold line 中性線

Hot line 電圧線





Ground 接地線

検電ドライバー  
Electroscopic  
Screwdriver



# DC Stabilized Power Supply 直流安定化電源

## Series (Dropper) regulation

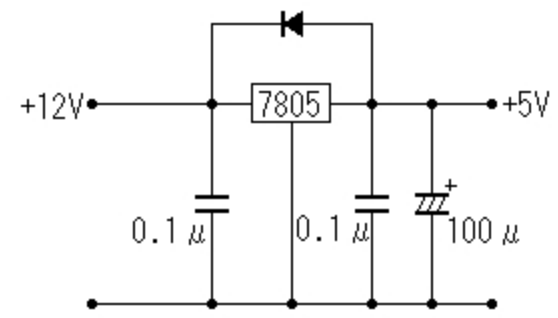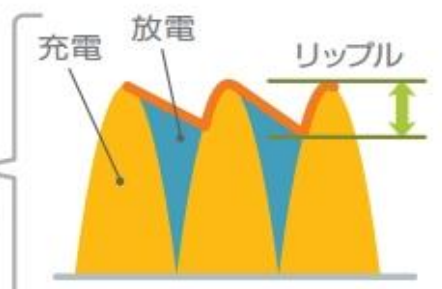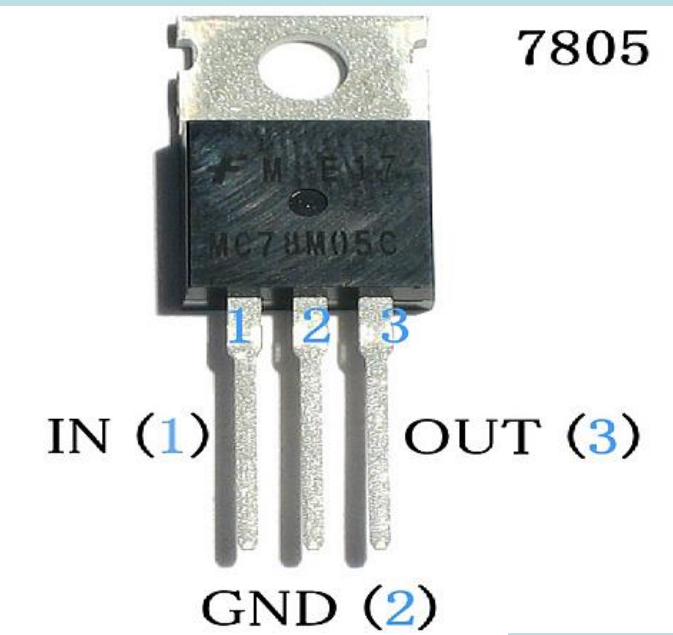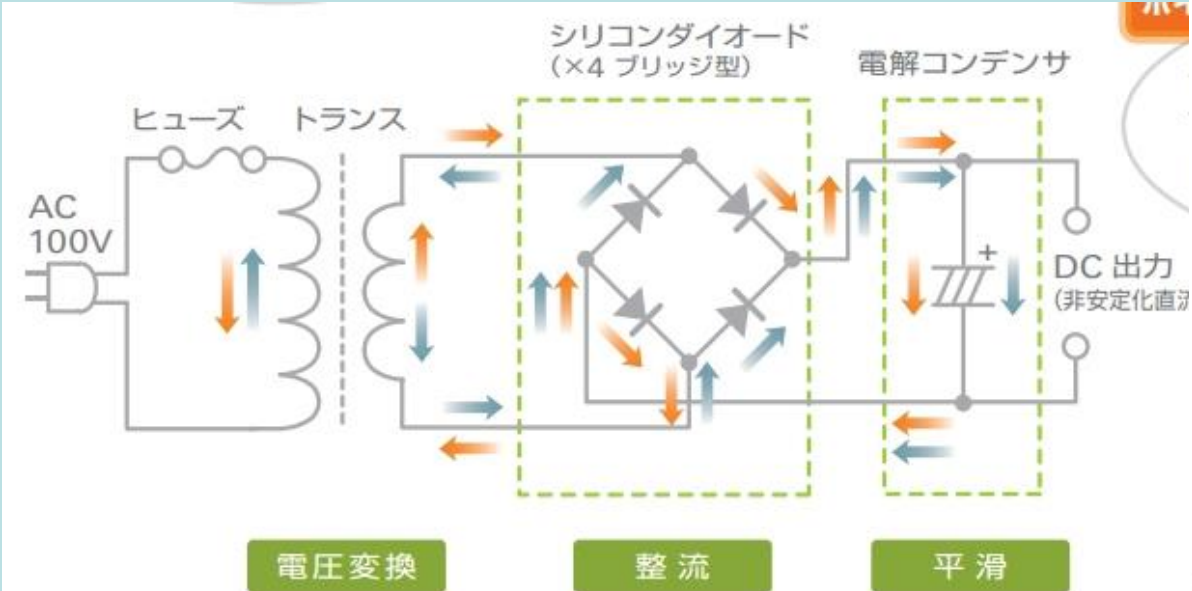

From TDK web page

# Series regulator power supply



Uni-polar



Dual tracking




High precision



Bi-polar current source

# Switching regulation

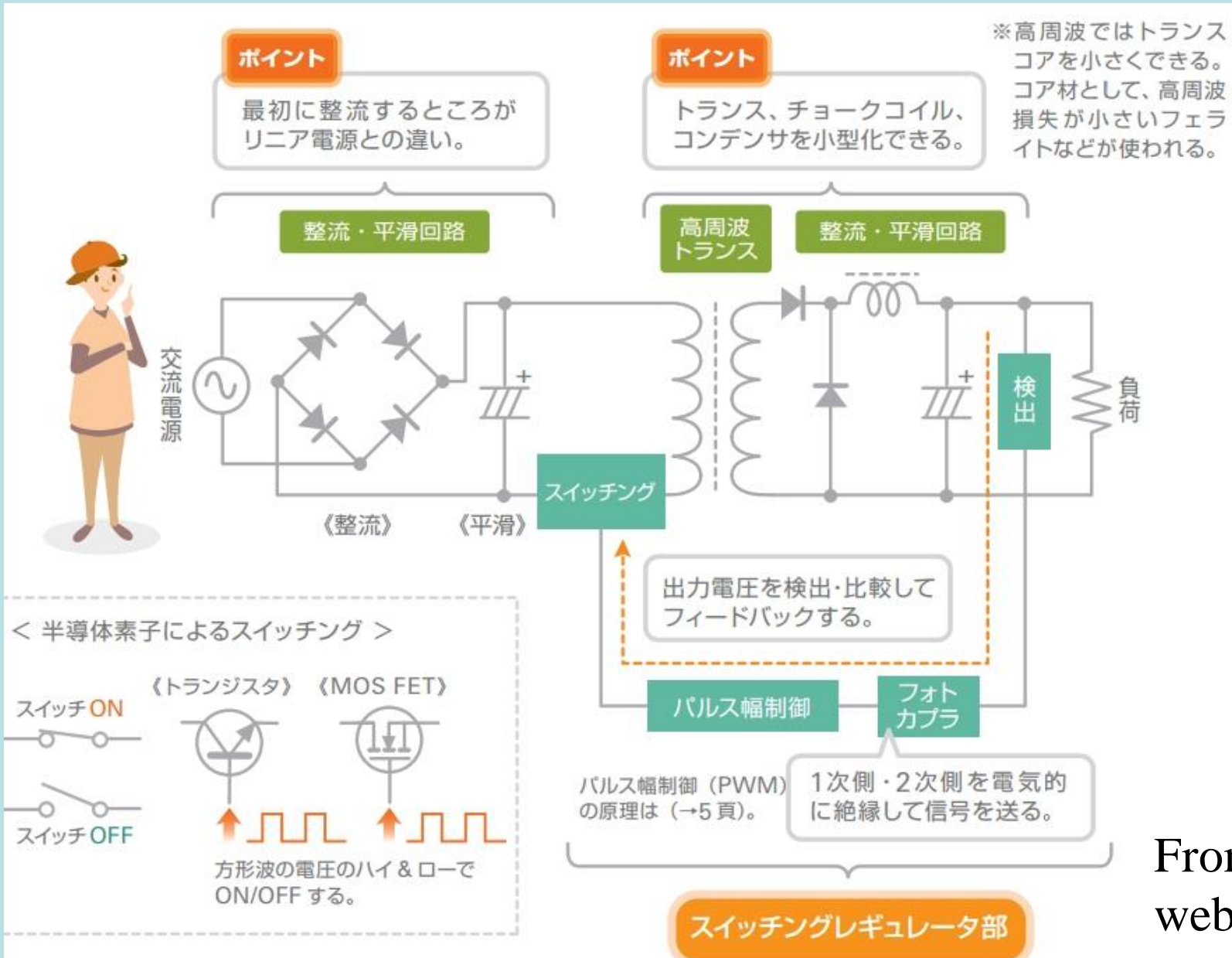

From TDK web page

# Switching regulator power supply





Molecular beam epitaxy  
Control panel





# Bin 電源ビン

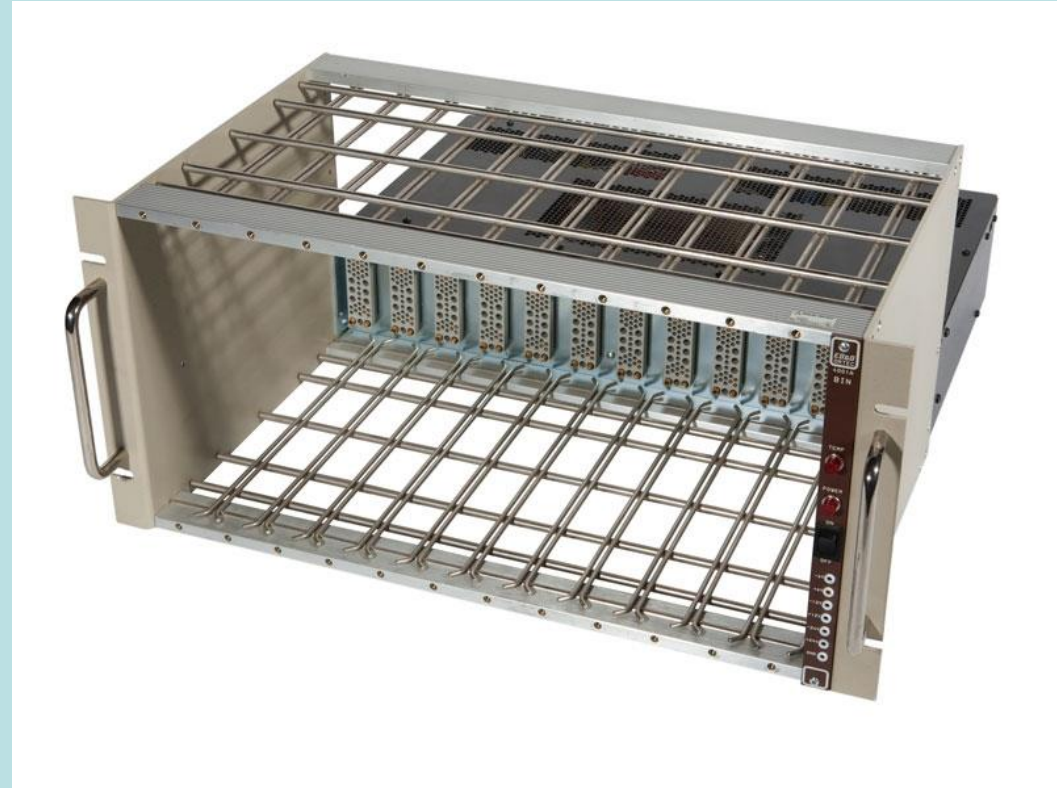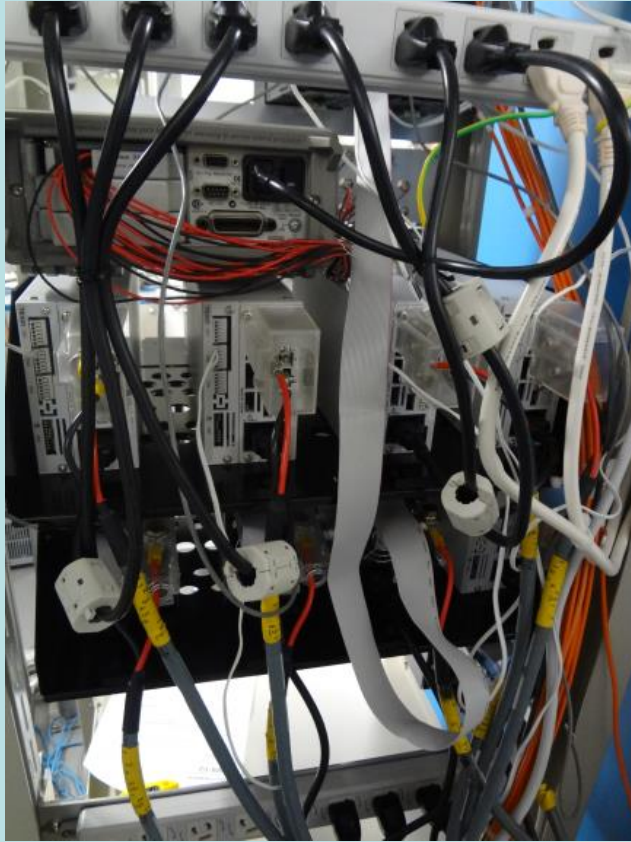


Complicated power lines



Bin

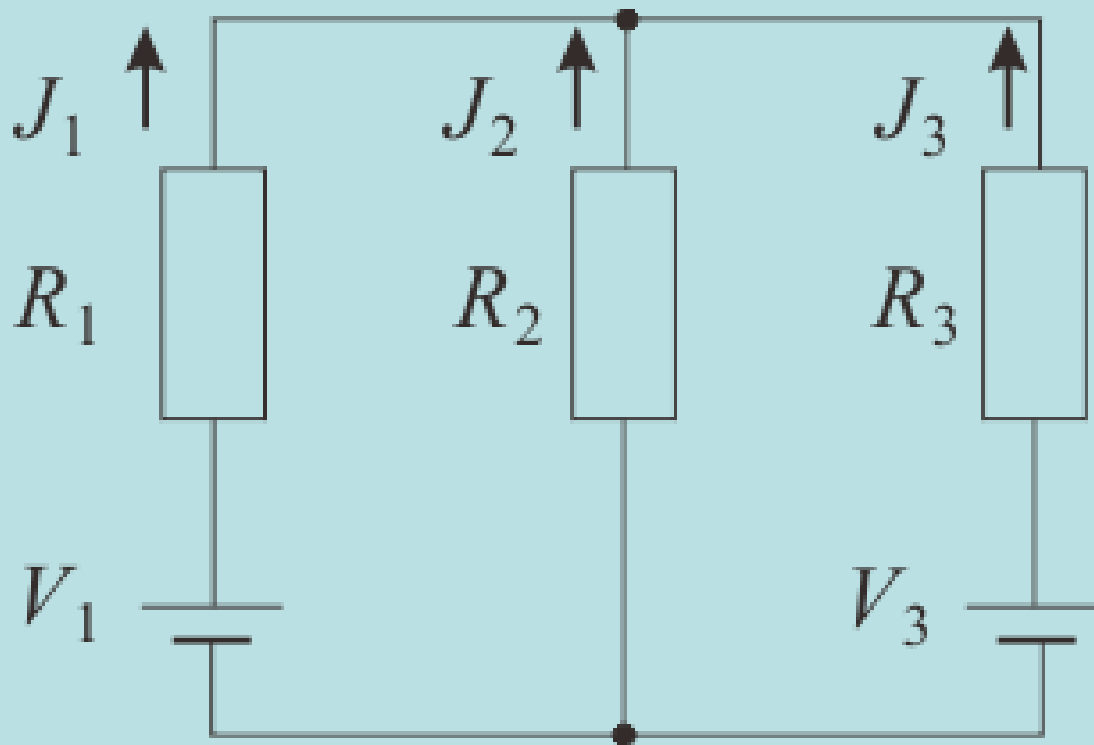
# Exercise A-1

Express  $J_1$ ,  $J_2$ ,  $J_3$  with other parameters.


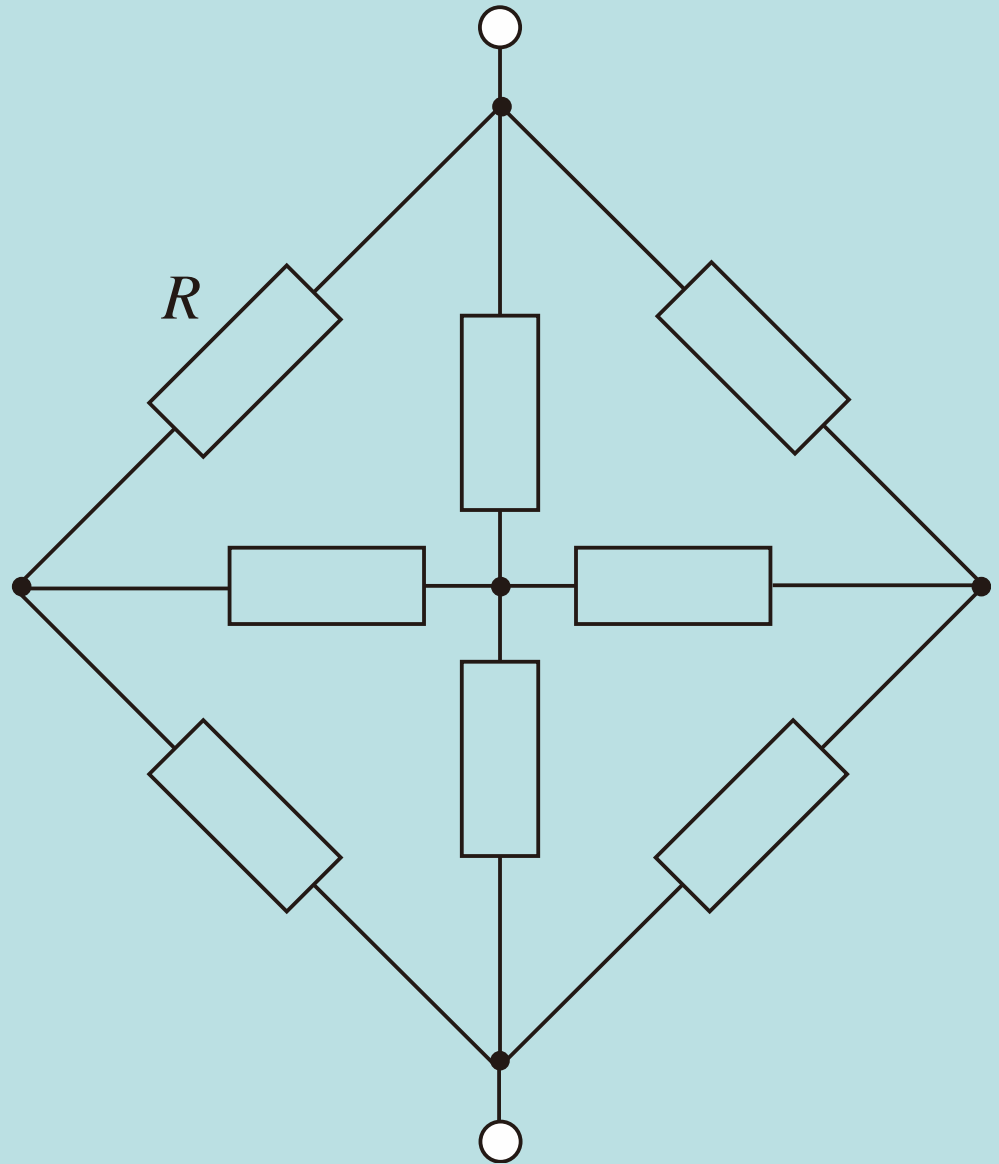
# Exercise A-2

All the resistors have the same resistance  $R$ . Obtain the combined resistance.



# Exercise A-3

Obtain the effective value of voltage for the saw tooth wave.

