

# 電子回路論第3回

## Electric Circuits for Physicists

東京大学理学部・理学系研究科

物性研究所

勝本信吾

Shingo Katsumoto




# 電源の雑知識 (続き)

Miscellaneous knowledge  
on power supplies (continued)






# DC Stabilized Power Supply 直流安定化電源

## Series (Dropper) regulation

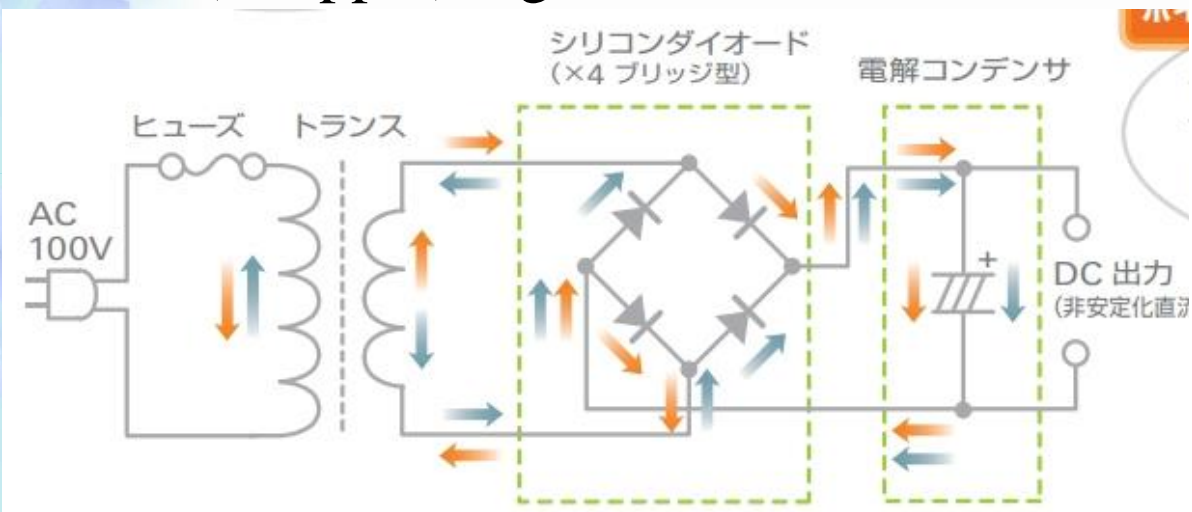

電圧変換      整流      平滑

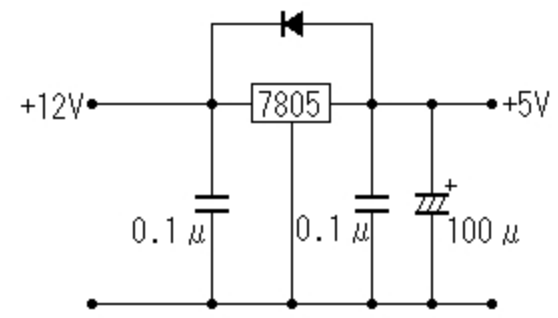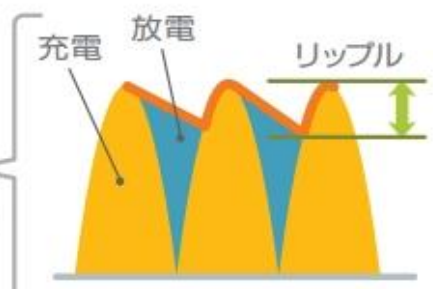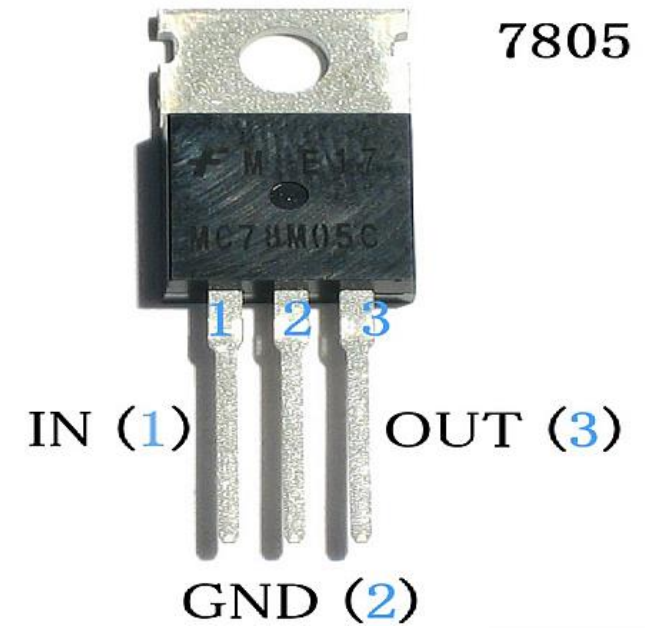

From TDK web page

# Series regulator power supply



Uni-polar



Dual tracking





High precision



Bi-polar current source

# Switching regulation

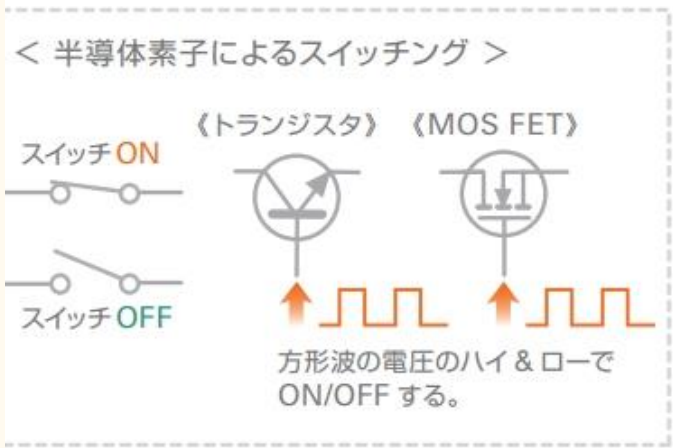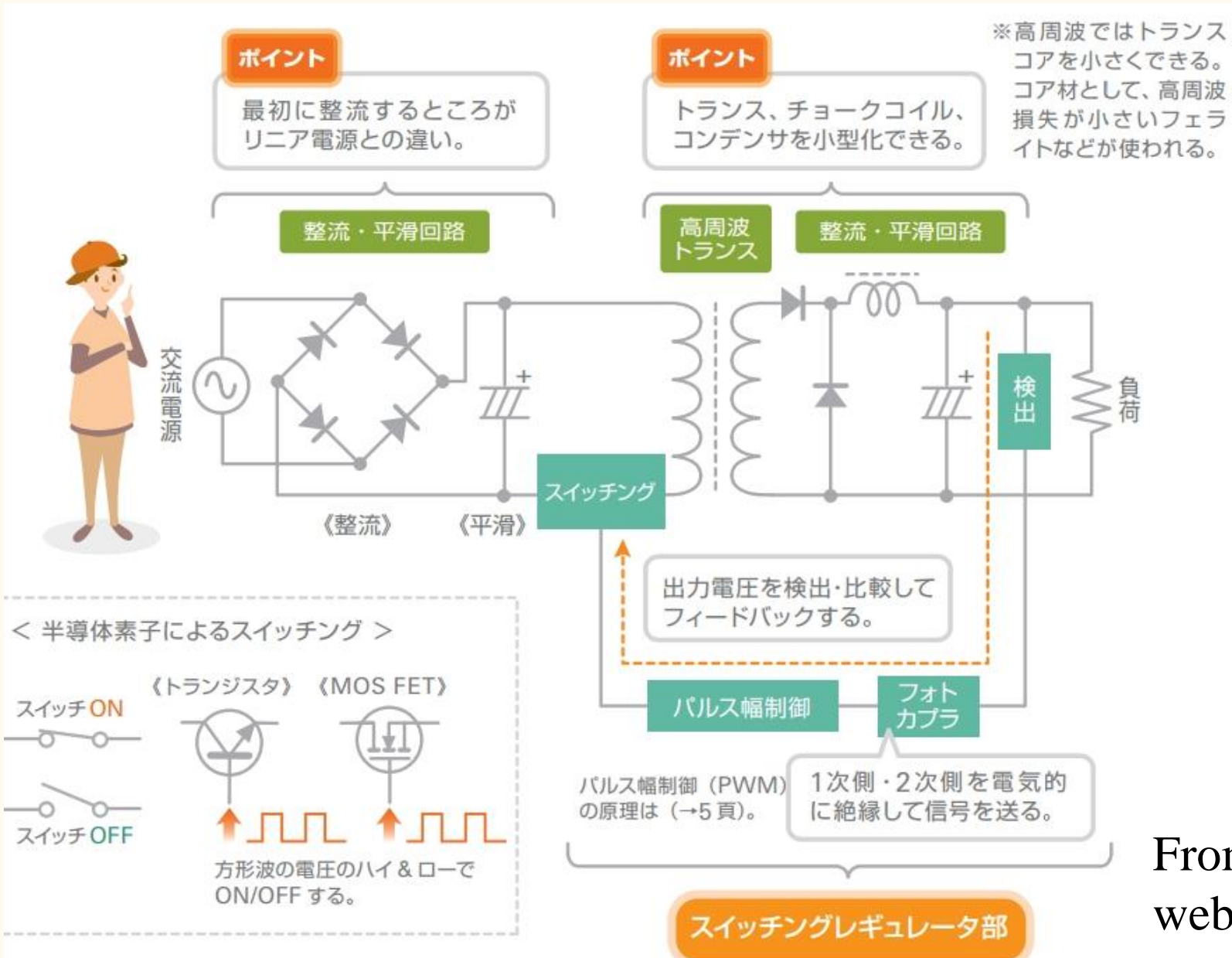

From TDK web page



# Switching regulator power supply




Molecular beam epitaxy  
Control panel




# Bin 電源ビン



Complicated power lines

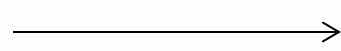

Bin

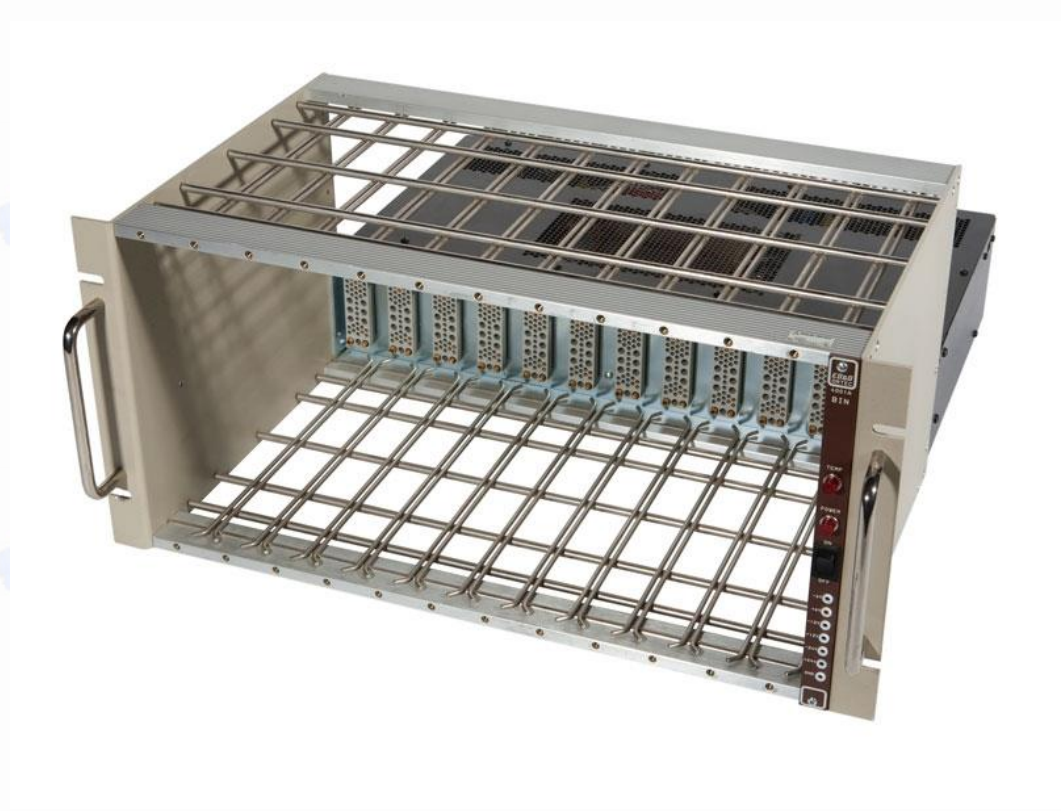



# Outline Today

2.5 Theorems for paired terminal circuits

Superposition, Ho-Tevenin, Reciprocity

2.6 Duality

2.7 Passive devices (elements) and active devices

## **Ch.3 Transfer function and transient response**

3.1 Transfer function of single-pair terminal circuits

Resonance circuit

Bode plot

General properties


Appendix B Bridges and balance circuits

Appendix C General properties of resonance circuits



# Theorems for terminal-pair circuits


## Superposition theorem

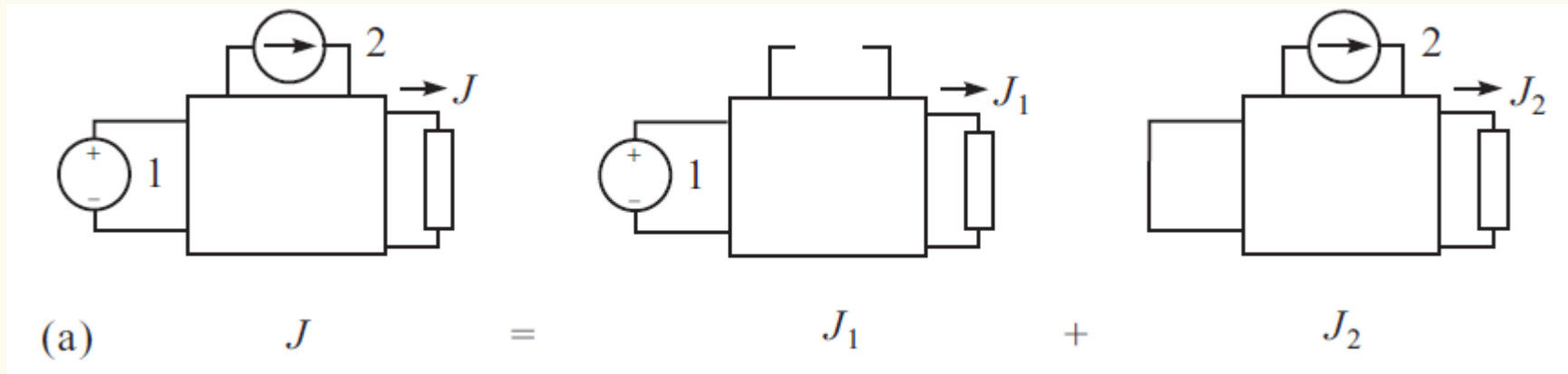

$$J = \sum_i J_i$$

$J_i$ : The current caused by  $i$ -th power source.

# Ho-Thevenin's theorem

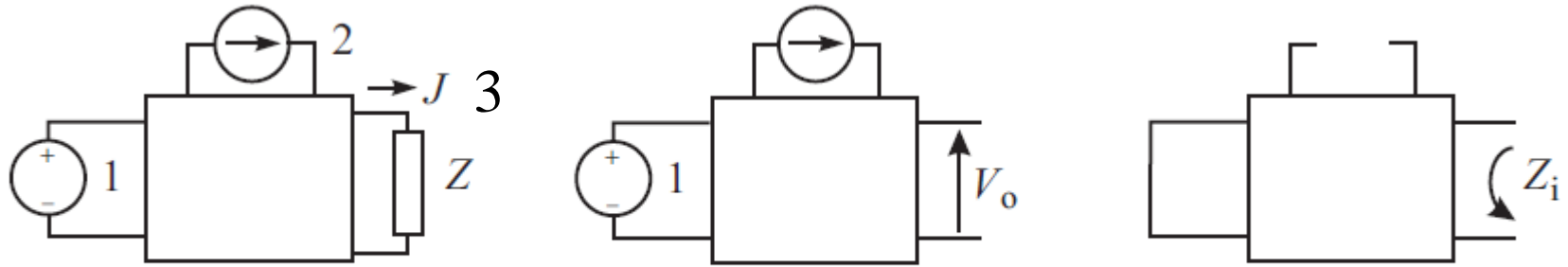

(b)


Consider a circuit with an open terminal pair (No.3). Obtain current  $J$  when the open pair is connected with impedance  $Z$ .

1. Measure the open terminal voltage  $V_0$ .
2. Turn off all the power sources (voltage sources: short, current sources: open). Measure the open circuit impedance  $Z_i$ .

Then

$$J = \frac{V_0}{Z + Z_i}$$


Because:

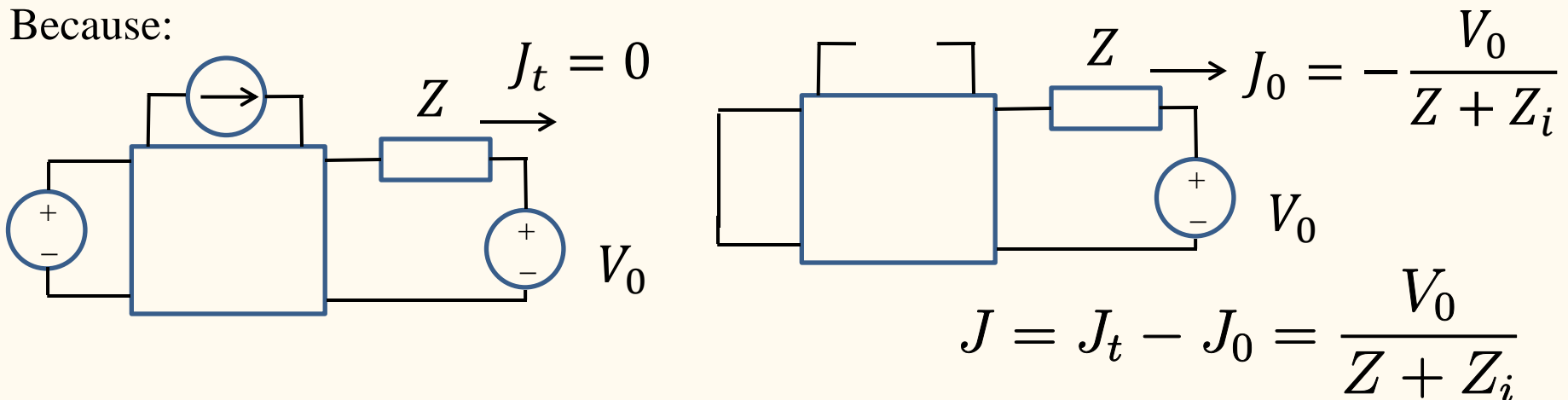

$$J = J_t - J_0 = \frac{V_0}{Z + Z_i}$$



# Norton's theorem

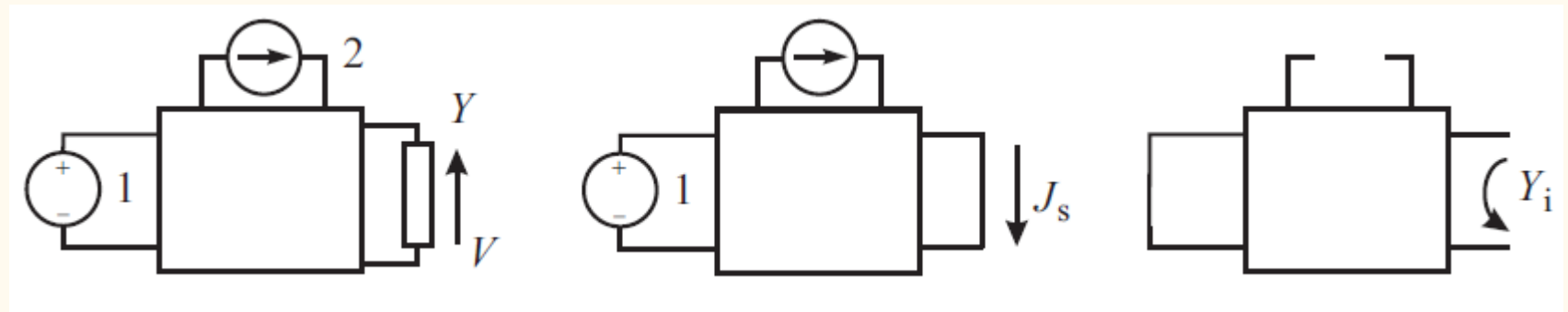

$$V = \frac{J_s}{Y + Y_i}$$

Dual theorem for Ho-Tevenin.

# Comments on Tellegen's theorem

$i = 1, \dots, n$ : index of nodes,  $j = 1, \dots, m$ : index of branches

$$a_{ij} = \begin{cases} 1 & : i \text{ is the start of } j, \\ -1 & : i \text{ is the end of } j, \\ 0 & : \text{others} \end{cases} \quad \text{incidence matrix}$$

redundancy  $\rightarrow (n - 1) \times m$  matrix  $D$  : irreducible incidence matrix

$J_j, V_j$  : current and voltage along branch  $j$ ,  $W_i$  : potential of node  $i$ .

Kirchhoff's first law:  $DJ = 0$       Second law:  $V = {}^tDW$

$$\sum_{i=1}^m \underbrace{V_i J_i}_{\text{Power of } i\text{-th branch}} = ({}^tDW) \cdot J = {}^tW D J = 0 \quad V \perp J$$

## Comments

1. Power conservation law
2. Holds for any kind of circuit (irrespective of linear, or non-linear)
3. Holds for two independent circuit conditions (as long as  $D$  is the same)



# Reciprocity theorem


An  $n$ -terminal pair linear circuit

At one state  $(V_1, J_1), (V_2, J_2), \dots, (V_n, J_n),$

at another state  $(V'_1, J'_1), (V'_2, J'_2), \dots, (V'_n, J'_n)$

$$\sum_{i=1}^n V_i J'_i = \sum_{i=1}^n V'_i J_i$$

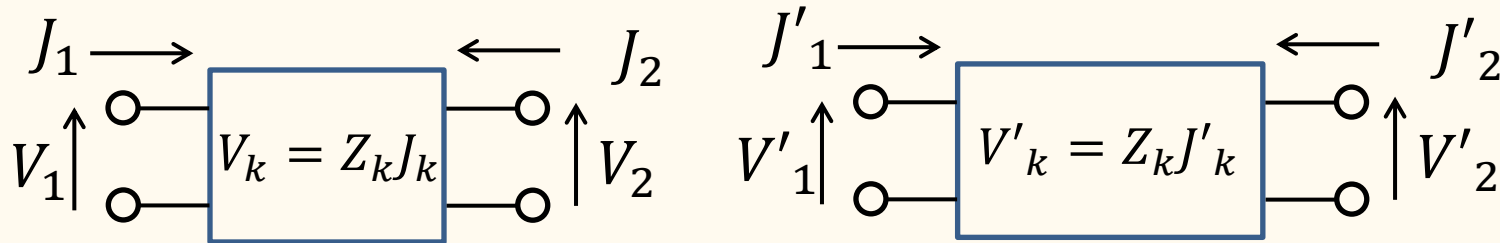Proof: Consider a two terminal-pair circuit with  $m$  branches.



Tellegen's theorem  
(and comment no.3)

$$-V_1 J'_1 - V_2 J'_2 + \sum_k V_k J'_k = 0$$

$$-V'_1 J_1 - V'_2 J_2 + \sum_k V'_k J_k = 0$$

$$V_k J'_k = V'_k J_k = Z_k J_k J'_k$$

$$\therefore V_1 J'_1 + V_2 J'_2 = V'_1 J_1 + V'_2 J_2 \quad //$$

(This also holds for circuits with mutual inductances.)

## 2.6 Duality 双対性

直列接続	並列接続
開放	短絡
電場	磁場
キルヒホッフの第2法則	キルヒホッフの第1法則
電圧	電流
インピーダンス	アドミッタンス
抵抗	コンダクタンス
静電容量	インダクタンス
鳳-テブナンの定理	ノートンの定理




## 2.6 Duality

Series	Parallel
Open	Short
Voltage	Current
Impedance	Admittance
Capacitance	Inductance
Electric field	Magnetic field
Resistance	Conductance
Ho-Thevenin	Norton
Kirchhoff's 2 <sup>nd</sup> law	Kirchhoff's 1 <sup>st</sup> law

## 2.7 Definition: Passive elements and active elements

Two terminal: current  $J$ , voltage  $V$        $JV \geq 0$ : passive element

$JV < 0$ : active element

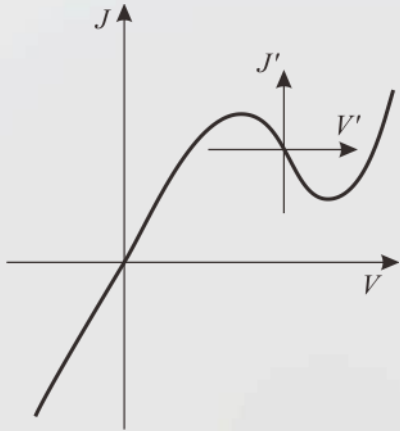

Locally active two-terminal element

More than three-terminal: treat as a terminal pair circuit



$$P = J_{in}V_{in} + J_{out}V_{out}$$

$P \geq 0$ : passive element

$P < 0$ : active element



# Ch.3 Transfer function and transient response

# 3.1 General Properties of Resonance and Resonance Circuits

## 3.1.1 Resonance Phenomena

Harmonic oscillator:  $\frac{d^2q}{dt^2} = -\omega_0^2q$

Kirchhoff's law


$$L \frac{dJ_L}{dt} = -L \frac{d^2q_L}{dt^2} = \frac{q}{C} = RJ_R = R \frac{dq_R}{dt}$$

$$dq_L + dq_R + dq = 0$$

$$\frac{d^2q}{dt^2} + \frac{1}{CR} \frac{dq}{dt} + \frac{1}{LC}q = \frac{d^2q}{dt^2} + \frac{1}{\tau} \frac{dq}{dt} + \omega_0^2q = 0$$

$$q = \exp(\lambda t) \quad \lambda = \frac{1}{2\tau} \left[ -1 \pm \sqrt{1 - 4(\omega_0\tau)^2} \right] \approx -\frac{1}{2\tau} \pm i\omega_0 \quad (\omega_0\tau \gg 1)$$

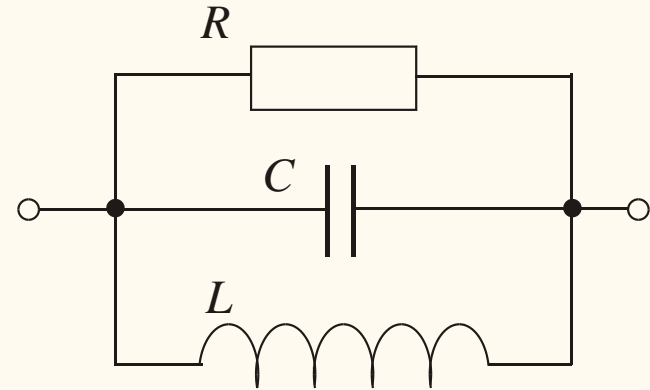Resonant (angular) frequency  $\omega_0 \equiv \frac{1}{\sqrt{LC}}$








# Transfer function, resonance and phase shift

$$Z_{\text{tot}}(i\omega) = \left[ \frac{1}{R} + i \left( \omega C - \frac{1}{\omega L} \right) \right]^{-1}$$


$$\omega_0 \equiv \frac{1}{\sqrt{LC}}$$

Resonance: Reactance = 0

Total Phase Shift Change:  $\pi$

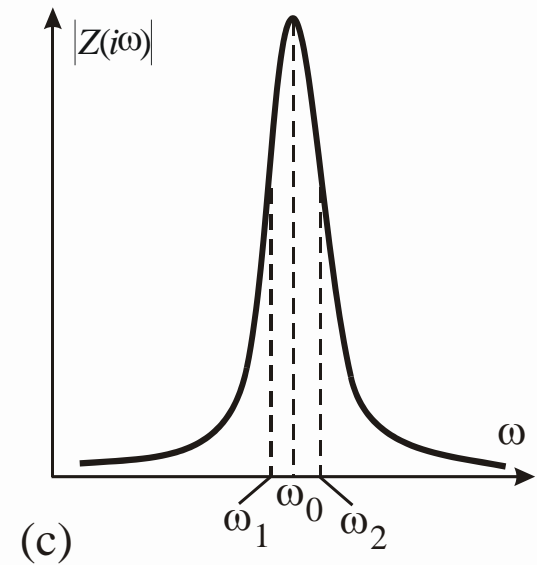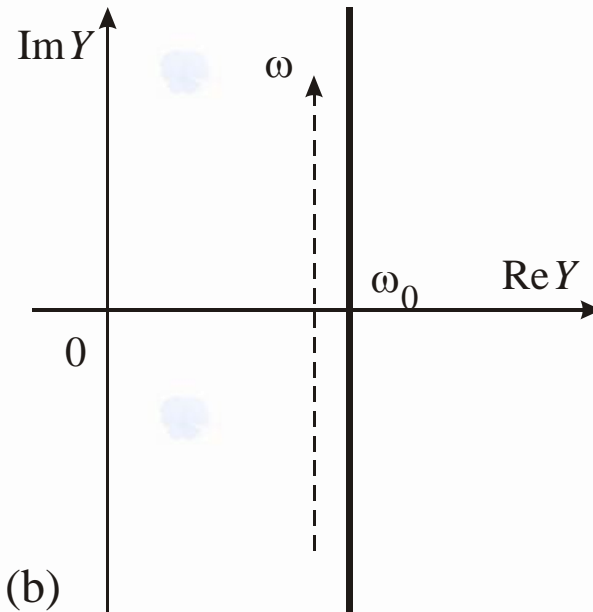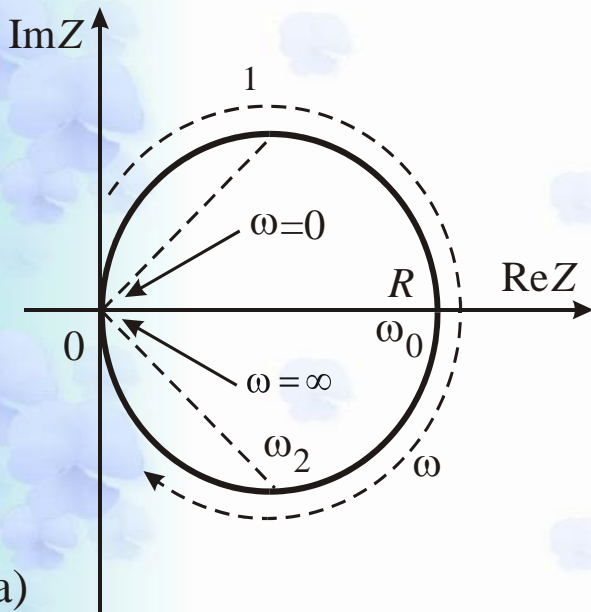


# Bode diagram


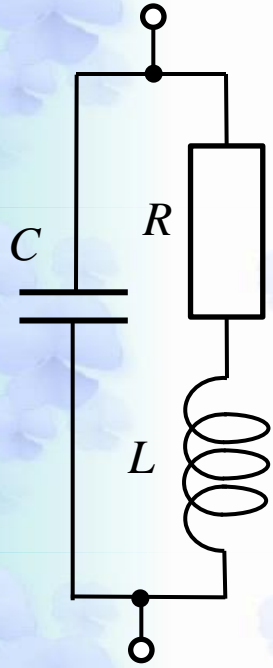


$$Q \approx \omega_0 \frac{L}{R}$$
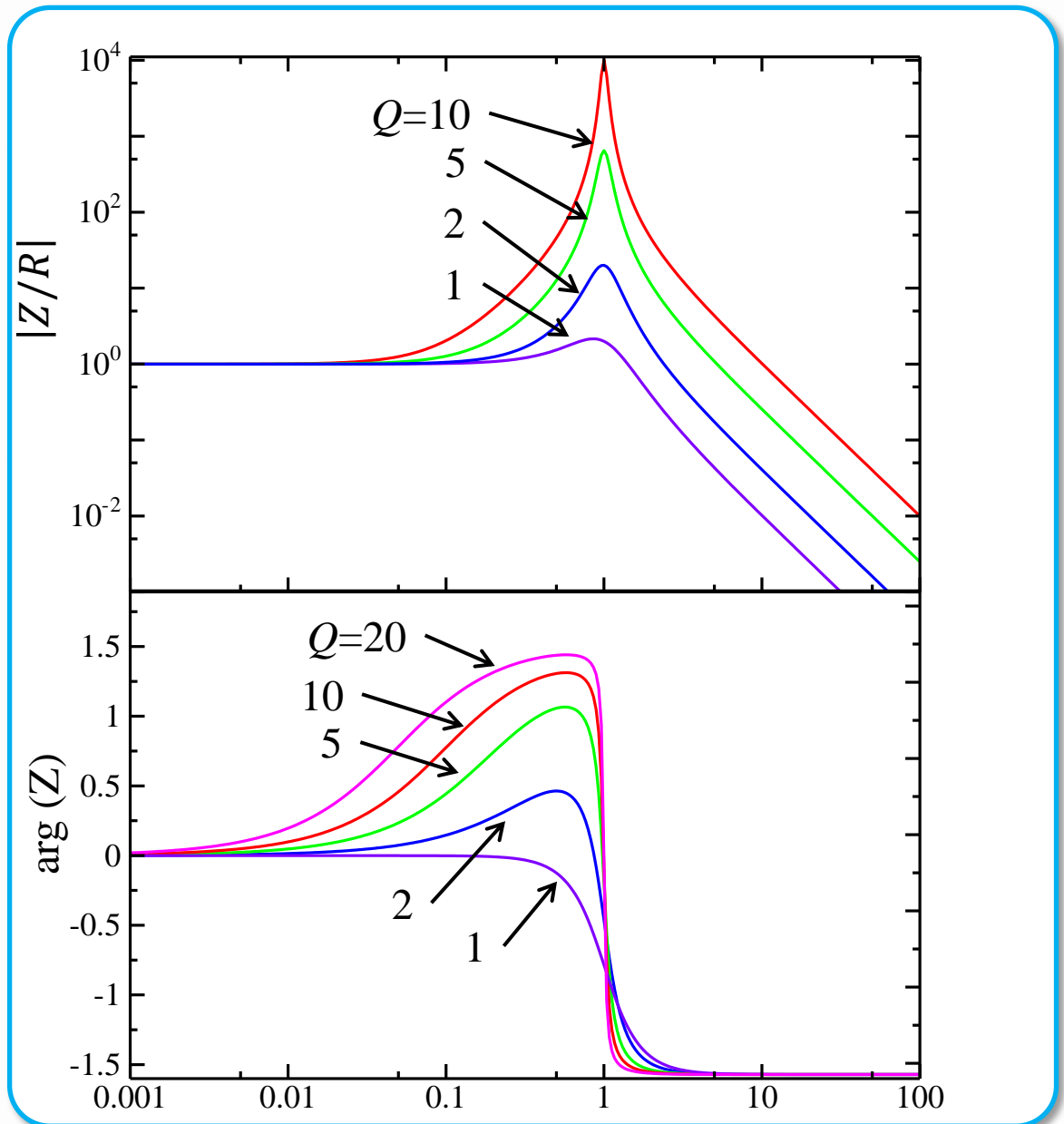
$$Z(i\omega) = \frac{R + i\omega L}{1 - \omega^2 LC + i\omega CR} = \frac{R + i\omega L}{1 - \frac{\omega^2}{\omega_0^2} + i\omega CR}$$



# Transient response of resonant circuit

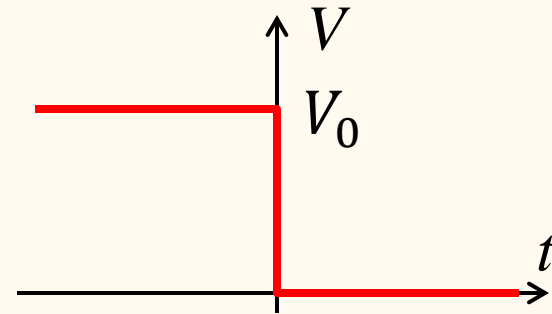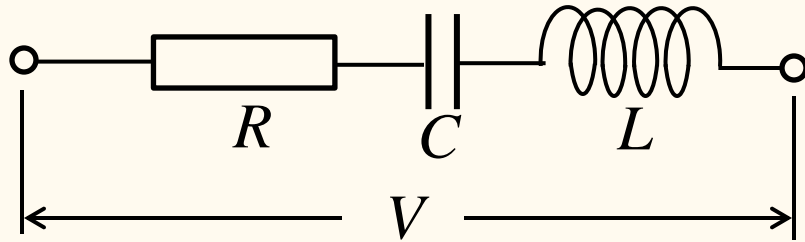

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0 \quad (t > 0), \quad q(0) = CV_0$$

$$q(t) = CV_0 e^{st} \rightarrow Ls^2 + Rs + C^{-1} = 0$$

$$s = (-\omega_0 \pm \sqrt{\omega_0^2 - 4\alpha^2}) / (2\alpha) \quad \alpha \equiv (CR)^{-1}$$

$(\omega_0/2) < \alpha \rightarrow$  imaginary part

$$q(t) = CV_0 \exp[(-\gamma \pm i\omega_s)t], \quad \gamma \equiv \frac{\omega_0^2}{2\alpha}, \quad \omega_s \equiv \omega_0 \left(1 - \frac{\omega_0^2}{4\alpha^2}\right)^{1/2}$$

Damped oscillation with time constant  $\gamma^{-1}$ , frequency  $\omega_s$

# Transient response of resonance circuit (transfer function)

Synthesized impedance, admittance

$$Z_{\text{tot}}(s) = sL + R + \frac{1}{sC}, \quad Y_{\text{tot}}(s) = Z_{\text{tot}}(s)^{-1}$$

Zero (pole) of  $Z_{\text{tot}}(s)$  ( $Y_{\text{tot}}(s)$ )  $s = (-\omega_0 \pm \sqrt{\omega_0^2 - 4\alpha^2}) / (2\alpha)$

$Z_{\text{tot}}(s_0) = 0$       Time constant:  $\text{Re}(s_0)$     Frequency:  $\text{Im}(s_0)$

Laplace transformation of voltage:  $V(s)$


$$\underline{J(t)} = \frac{1}{2\pi i} \int_{c-i\infty}^{c+i\infty} Y(s)V(s)e^{st} ds = \sum_i R(s_i)V(s_i)e^{s_i t} \quad (c > 0)$$

Natural current


$s_i$ : poles of  $Y(s)$      $R(s_i) = Y(s)(s - s_i)|_{s=s_i}$



# Driving point impedance

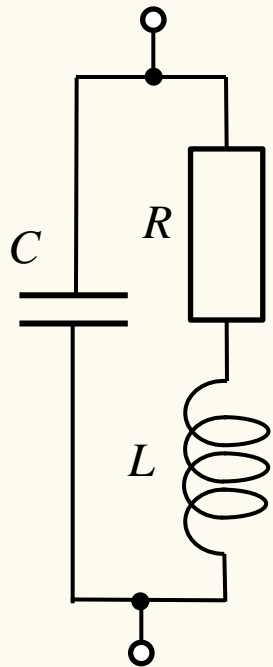

Open

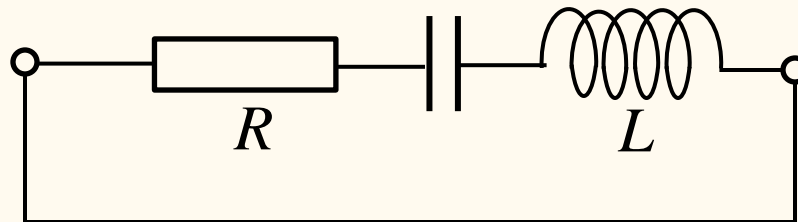

Short

=


$$Z_{\text{tot}}(s) = sL + R + \frac{1}{sC}$$

$$Z_{\text{tot}}^{(2)}(s) = \left( \frac{1}{R + sL} + sC \right)^{-1} = \frac{sL + R}{s^2LC + sRC + 1}$$

$Z_{\text{tot}}(s)$  zero is pole for  $Z_{\text{tot}}^{(2)}(s)$

# Resistance bridge 抵抗ブリッジ

## Wheatstone bridge

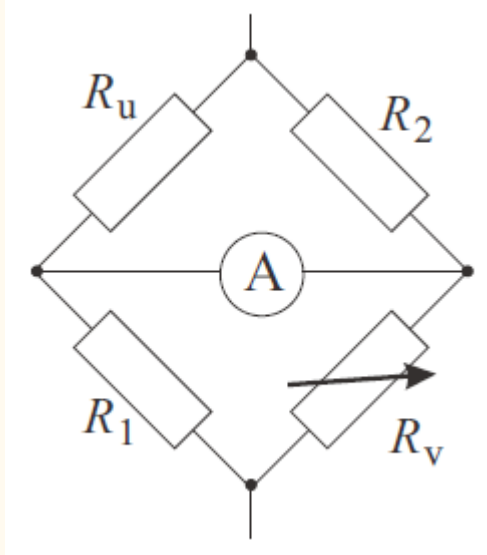


AVS-47 Resistance bridge

Not a “bridge” circuit!



# Schering Bridge

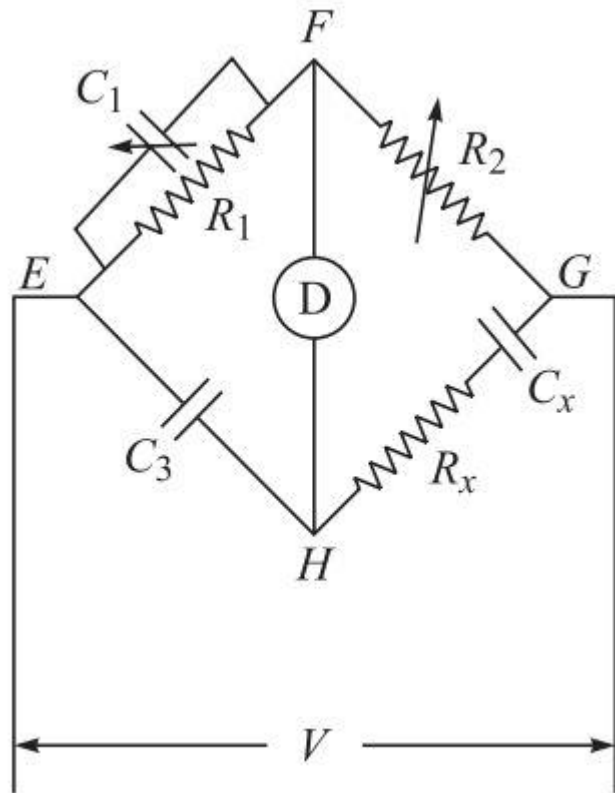

$$Z_1 Z_x = Z_2 Z_3, \quad Z_x = Z_2 Z_3 Y_1$$


$$Z_x = R_x + \frac{1}{i\omega C_x}, \quad Z_2 = R_2, \quad Z_3 = \frac{1}{i\omega C_3}, \quad Y_1 = \frac{1}{R_1} + i\omega C_1$$

$$R_x + \frac{1}{i\omega C_x} = R_2 \frac{1}{i\omega C_3} \left( \frac{1}{R_1} + i\omega C_1 \right)$$


$$R_x = \frac{R_2 C_1}{C_3}, \quad C_x = \frac{R_1}{R_2} C_3$$

# Hartshorn bridge

## Magnetic moment measurement

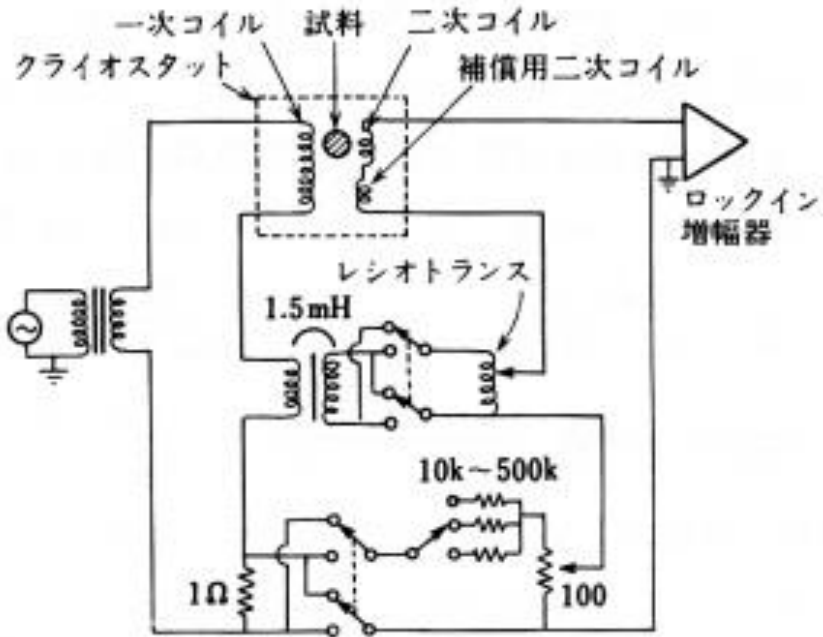

## Resistance measurement

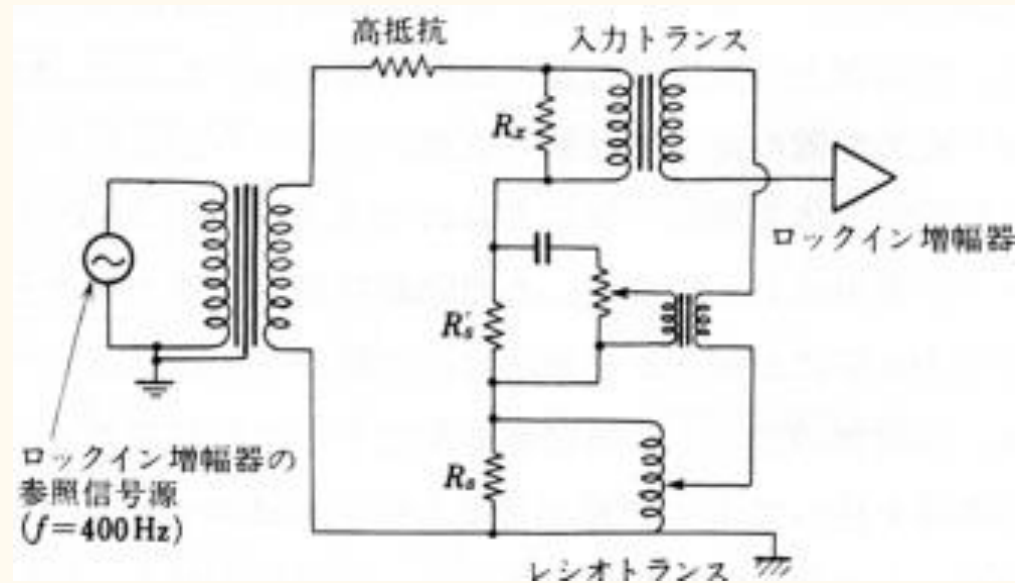



# Capacitance bridge キャパシタンスブリッジ



General Radio  
3-terminal  
Capacitance bridge


Agilent E4981A



# Kondo Resonance and Phase shift




Jun Kondo

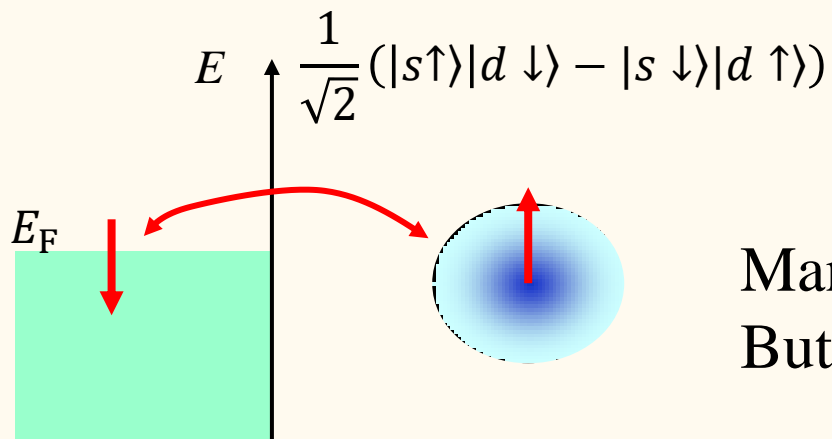


Many body resonance.  
But still has the phase shift of  $\pi/2$  !


Co atoms on Ag (111) surface

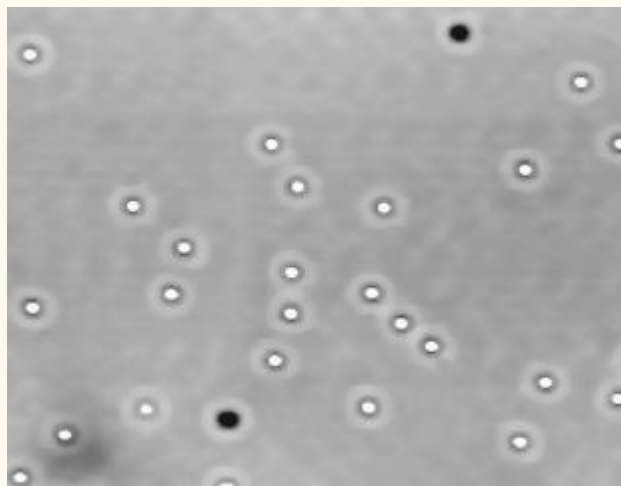

Co (magnetic)

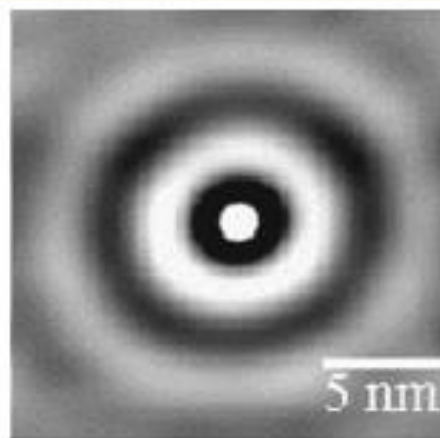

Defect (non-magnetic)

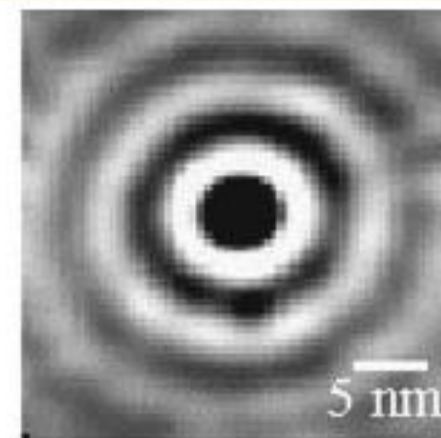


Schneider et al., Phys. Rev. B65, 121406 (2002).


# Quartz crystal filter



(a)

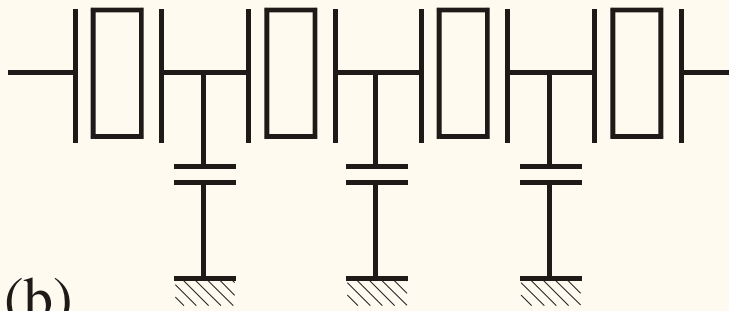

(b)

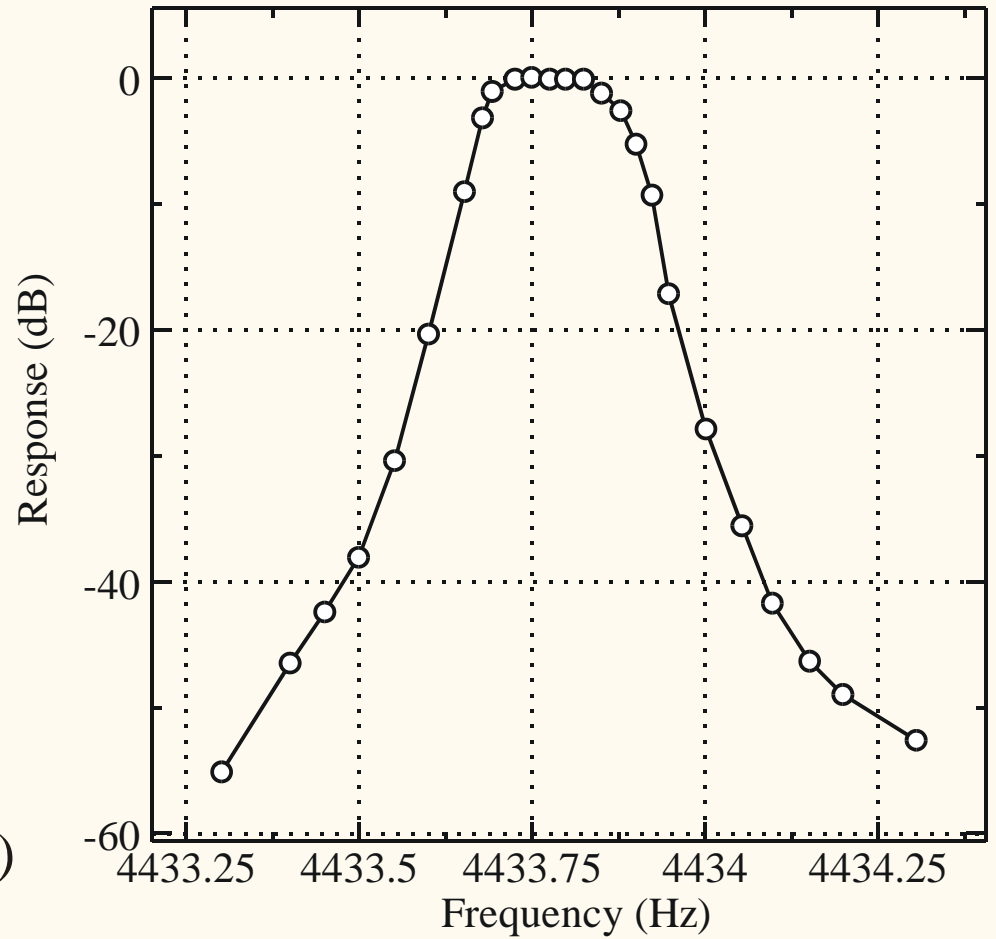

(c)

Download LTSpice from the web site of Linear Technology



# What is Spice?

## SPICE: Simulation Program with Integrated Circuit Emphasis

A language which describes electronic circuits (corresponding to circuit diagrams).

ex) a CR circuit and a dc power source

```
* 0---R1---1---C1---2---V1---0
```

```
R1 0 1 10
```

```
C1 1 2 20
```

```
V1 2 0 5
```

```
.END
```

Graphical user interface: Circuit diagram

Linear Technology  
web site



The screenshot shows the Linear Technology website interface. At the top, there is a search bar and navigation links for "国内ニュースサイト", "ENGLISH", "中文网站", "品質", "採用", "問い合わせ", and "MyLinear". Below this is a main navigation bar with "製品", "ソリューション", "デザインサポート", "購入", and "会社概要". The main content area features a product highlight for the LTC6430, which includes a circuit diagram of an op-amp and a list of key features: "利得ブロック : 15dB", "OIP3 : +50dBm", and "3.3dB NF". To the right of the product highlight is a sidebar with "LTSPICE IV" resources, including "ダウンロード LTspice IV", "LTspiceデモ回路", and "LTspice資料". Below the product highlight is a "製品リリース" (Product Releases) section listing various LT products and their descriptions. At the bottom right, there is a "ビデオ" (Video) section with a video thumbnail and the text "LT4321 PoE理想ダイオードブリッジコントローラ - 製品概要ビデオ" and "全てのビデオを見る".



Home > デザインサポート > ソフトウェア

## Design Simulation and Device Models

リニアテクノロジーは高性能なスイッチング・レギュレータやアンプ、データ・コンバータ、フィルタなどを使用した回路を、初めての設計者でも短時間に容易に評価できるよう、**LTspice**・**LTpowerCAD**・**LTpowerPlay**のソフトウェアと、**LTspice**・**LTpowerCAD**・**LTpowerPlay**の**モデル**を提供しています。


- LTspice IV
- LTpowerCAD
- LTpowerPlay
- Amplifier Simulation & Design
- Filter Simulation & Design
- Timing Simulation & Design
- Data Converter Evaluation Software
- Dust Networks Starter Kits

### LTSPICE IV

#### LTspice IV

LTspice IVは高性能なSpice IIIシミュレータと回路図入力、波形ビューワに改善を加え、スイッチング・レギュレータのシミュレーションを容易にするためのモデルを搭載しています。Spiceの改善により、スイッチング・レギュレータのシミュレーションは、通常のSpiceシミュレータ使用時に比べて著しく高速化され、ほとんどのスイッチング・レギュレータにおいて波形表示をほんの数分で行なうことができます。Spiceとリニアテクノロジーのスイッチング・レギュレータの80%に対応するMacro Model、200を超えるオペアンプ用モデルならびに抵抗、トランジスタ、MOSFETモデルをここからダウンロードできます。

- [LTspice IV \(Windows用\)をダウンロード \(2014年5月5日更新\)](#)
- [LTspice IV \(Mac OS X 10.7+用\)をダウンロード](#)
- [関連情報 & ショートカット](#)
- [Mac OS X用ショートカット](#)
- [スタート・ガイド](#)
- [ユーザ・ガイド\(ヘルプ・ファイル参照\)](#)
- [トランスの使用](#)
- [デモ回路集](#)
- [セミナーの開催予定を見る](#)

LTspiceのツイッターをフォロー 

LTspiceに関するビデオを見る 

### LTPOWERCAD

MYLINEAR ログイン



# Summary



Theorems for paired terminal circuits

Superposition, Ho-Tevenin, Reciprocity

Duality

Passive devices (elements) and active devices

**Transfer function and transient response**

Transfer function of single-pair terminal circuits

Resonance circuit

Bode plot

General properties