



電子回路論第6回

Electric Circuits for Physicists

東京大学理学部・理学系研究科
物性研究所
勝本信吾

Shingo Katsumoto

Outline



4.3 Feedback control

4.3.1 Disturbance and noise

4.3.2 PID control


4.4 PN junction transistors

4.4.1 Diodes

4.4.2 Bipolar junction transistors


 
4.5 Field effect transistors

Comment: Use of OP-amp at saturation voltages





Compare V_{in} with 0

Comparator

  

Hurwitz criterion

Adolf Hurwitz
1859 - 1919

  

$$\Xi(s) = \frac{G(s)}{1 + h(s)G(s)}$$

Pole equation: (denominator) $= a_n s^n + a_{n-1} s^{n-1} + \dots + a_0$
 $= a_n (s - p_1) \dots (s - p_n) = 0$

$\forall j = 0, 1, \dots, n : a_j > 0$ (or < 0) (Otherwise the system is unstable.)

Hurwitz matrix
 $n \times n$

$$H = \begin{pmatrix} a_{n-1} & a_{n-3} & a_{n-5} & \cdots & 0 \\ a_n & a_{n-2} & a_{n-4} & \cdots & 0 \\ \hline 0 & a_{n-1} & a_{n-3} & \cdots & 0 \\ 0 & a_n & a_{n-2} & \cdots & 0 \\ \hline \vdots & \vdots & \vdots & \vdots & \vdots \\ 0 & 0 & 0 & \cdots & a_0 \end{pmatrix}$$

Hurwitz criterion

Hurwitz determinants $H_j \equiv |H[1, \dots, j; 1, \dots, j]|$

$$H_1 = a_{n-1}, \quad H_2 = \begin{vmatrix} a_{n-1} & a_{n-3} \\ a_n & a_{n-2} \end{vmatrix}, \quad H_3 = \begin{vmatrix} a_{n-1} & a_{n-3} & a_{n-5} \\ a_n & a_{n-2} & a_{n-4} \\ 0 & a_{n-1} & a_{n-3} \end{vmatrix}, \dots$$

Hurwitz criterion

$$H_j > 0 \quad (j = 2, \dots, n = 1)$$


$H_1, H_n > 0$ is trivial from the assumption.

Another expression:

Divide the denominator to odd and even parts $O(s)$ and $E(s)$.
If the zeros of $O(s)$ and $E(s)$ are aligned on the imaginary axis alternatively, the system is stable.

Disturbance and noise on feedback control

 - Circuit treatment of fluctuations:
- Prepare external power sources
 - Express them as transfer functions




$$Y(s) = \frac{G(s)}{F(s)} [G_C(s)R(s) + D(s) + G_C(s)H(s)N(s)]$$

$$F(s) \equiv 1 + G_C(s)G(s)H(s)$$

PID control

Compensator
(controller)

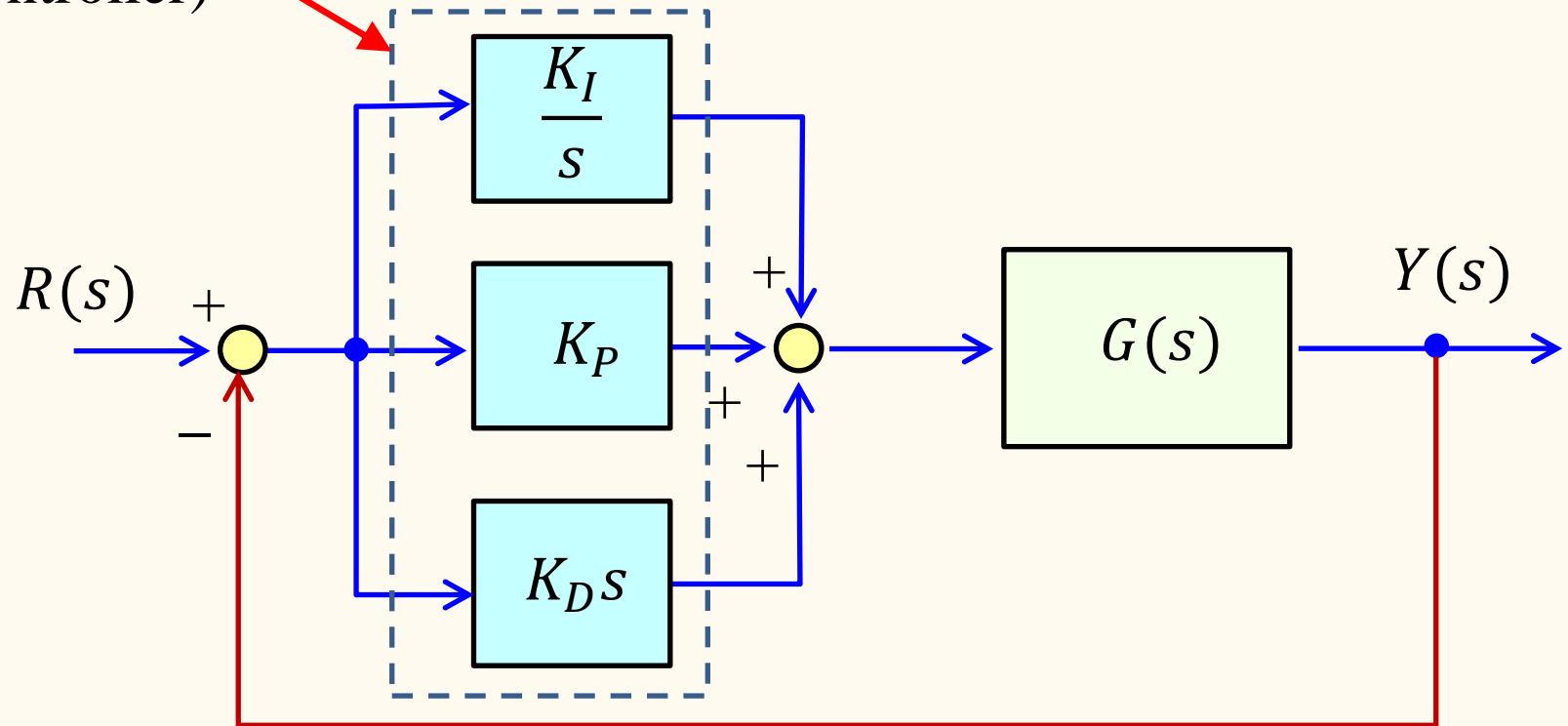P: proportional, I: integral, D: derivative




$$G_c(s) = K_P + \frac{K_I}{s} + K_D s$$

PID controllers

OMRON




invensys
EUROTHERM

 


4.4 Example of active element: Transistors

Three types of semiconductors

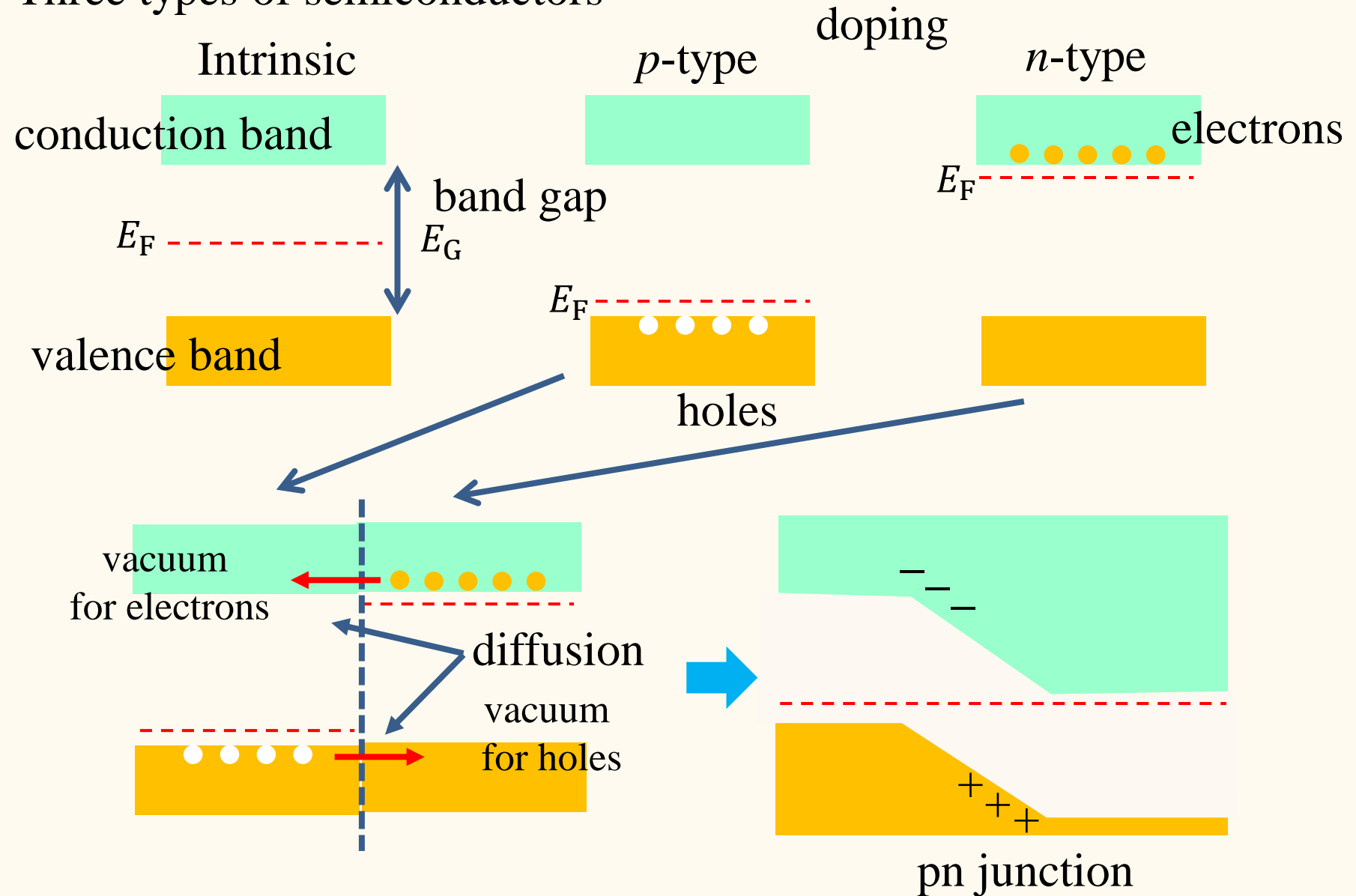

pn junction thermodynamics

 


$$F = U - TS$$

Voltage (internal energy cost)


Diffusion (entropy)

Minimization of F → Built-in (diffusion) voltage V_{bi}

 4.4.1 I-V characteristics of pn junctions




Reverse bias
enhances V_{bi} : no go

 

Forward bias
overcomes V_{bi} : go

Minority
carrier injection


Rectification

 

$$J = J_0 \left[\exp\left(\frac{eV}{k_B T}\right) - 1 \right]$$

Shockley theory


Injection of minority carriers

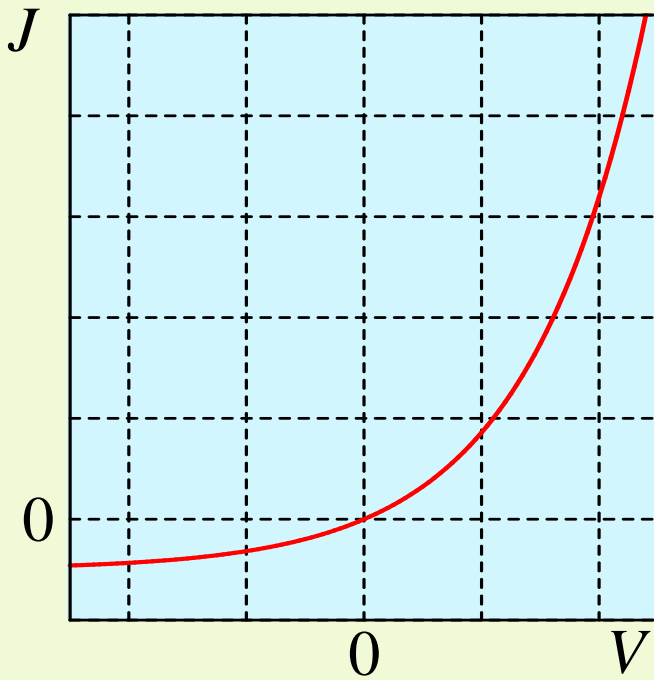

$$J = e(v_n n_p + v_p p_n) \left[\exp \frac{eV}{k_B T} - 1 \right]$$

minority carrier
current

Barrier overflow

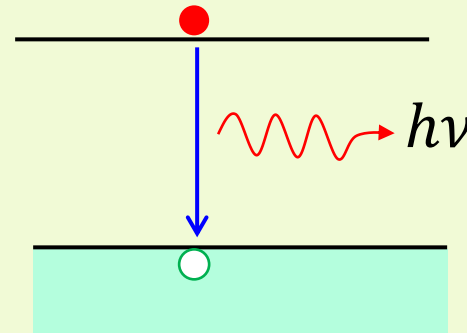

light emitting
diode

Fate of injected minority carriers:
Radiative recombination

Nick Holonyak Jr.




Photo: A. Mahmoud
Isamu Akasaki




Photo: A. Mahmoud
Hiroshi Amano



Photo: A. Mahmoud
Shuji Nakamura

 

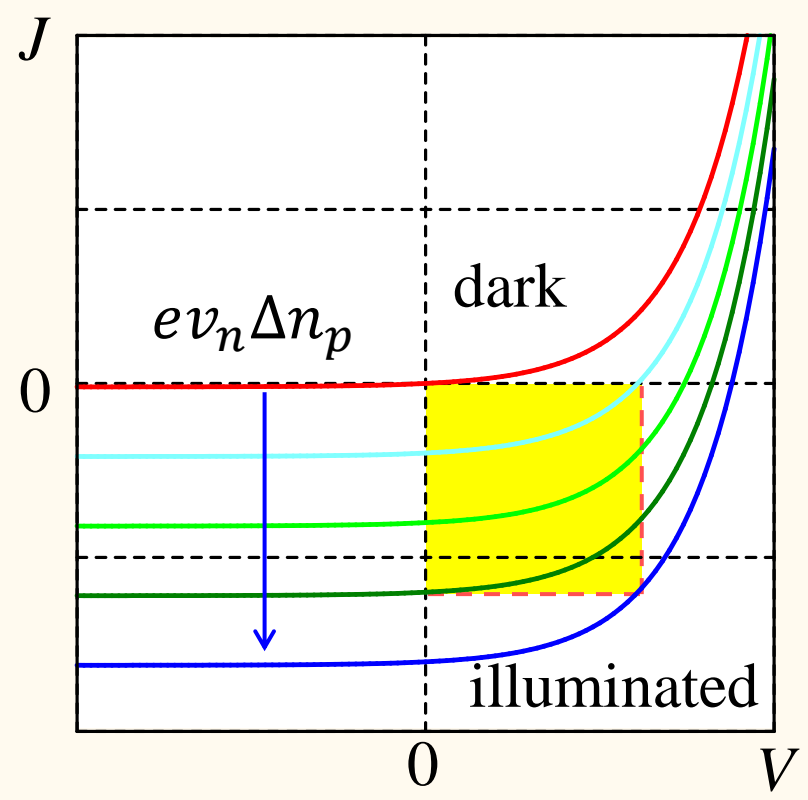Solar cell (injection of minority carriers with illumination)



$$J_{e0} = ev_n n_p \left[\exp \frac{eV}{k_B T} - 1 \right]$$

$$J_e = ev_n n_p \exp \frac{eV}{k_B T} - ev_n (n_p + \Delta n_p)$$


$$= J_{n0} - \underline{ev_n \Delta n_p} \text{ External injection}$$



Gerald Pearson,
Daryl Chapin
and Calvin Fuller
at Bell labs. 1954



 4.3.2 Discovery and invention of bi-polar transistors




The first point contact transistor
(Dec. 1947

The paper published in June 1948.)




John Bardeen, William Shockley,
Walter Brattain 1948 Bell Labs.




Bipolar junction transistor

 

Field effect transistor

   


 Bipolar transistor structures and symbols



PNP type

$$L_B < L_h$$



 


NPN type


$$L_B < L_e$$

Similar characteristics PNP and NPN: complementary


Base-Collector characteristics

   


How a bipolar transistor amplifies?

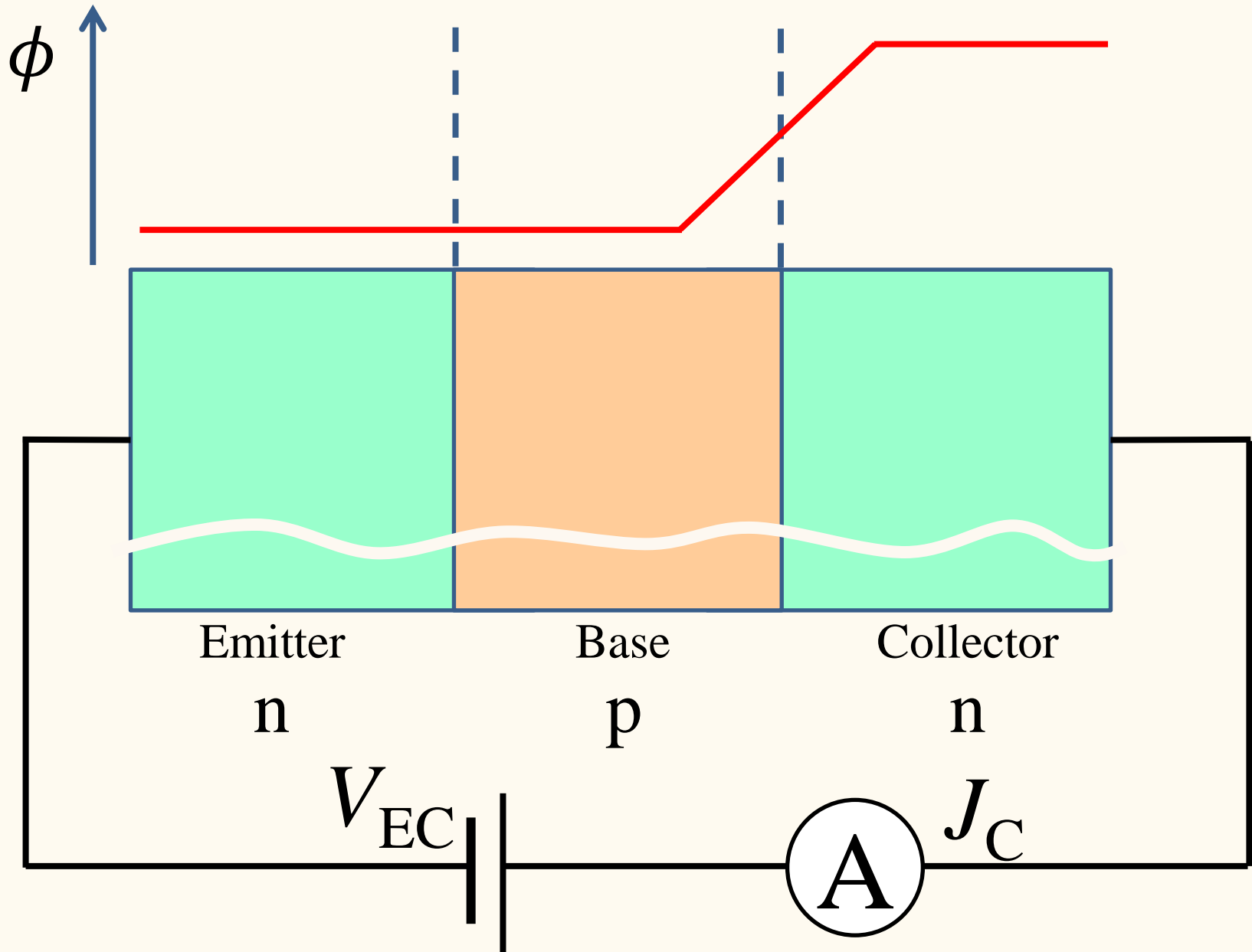




How a bipolar transistor amplifies?

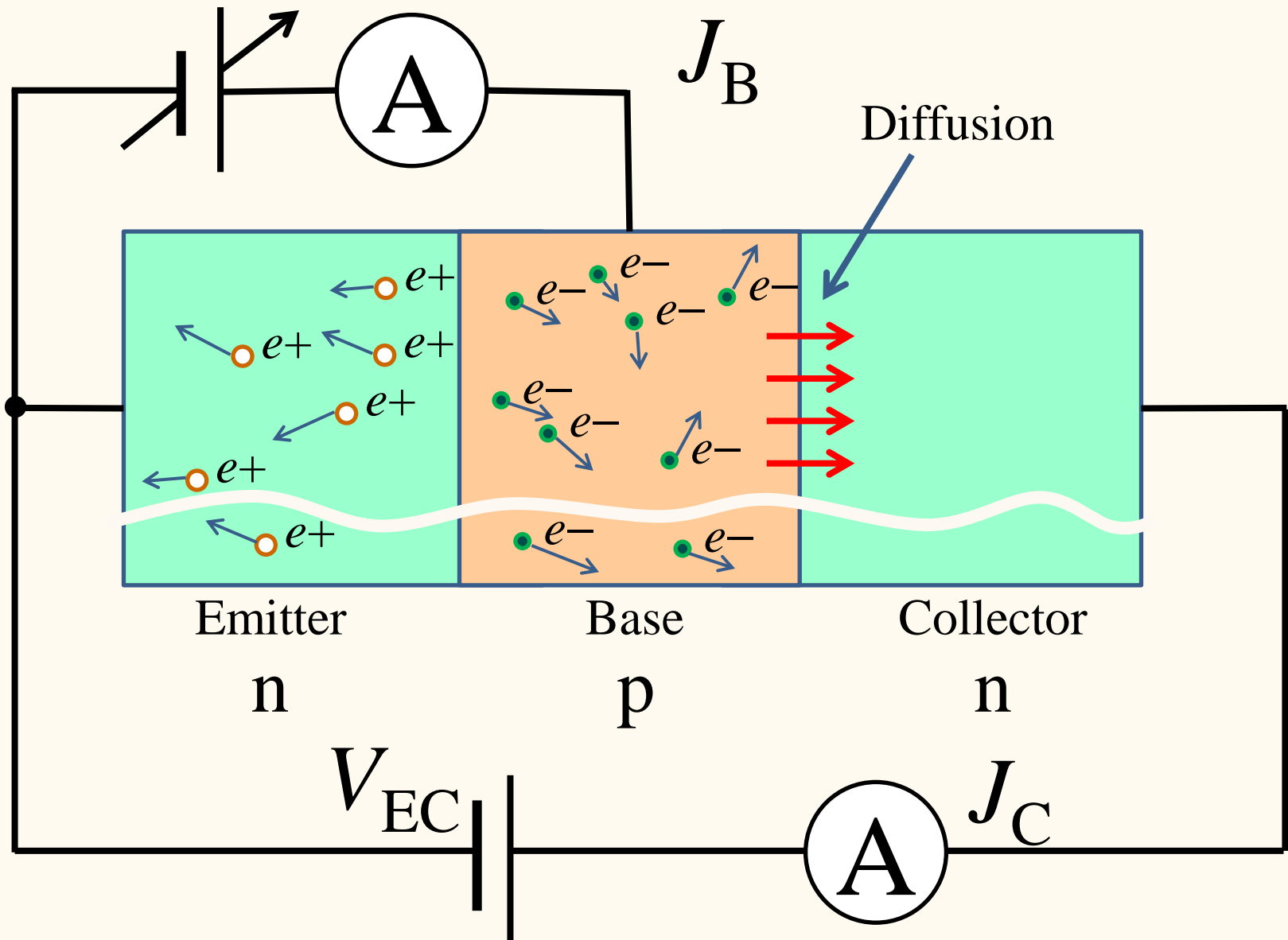


Base-Collector characteristics

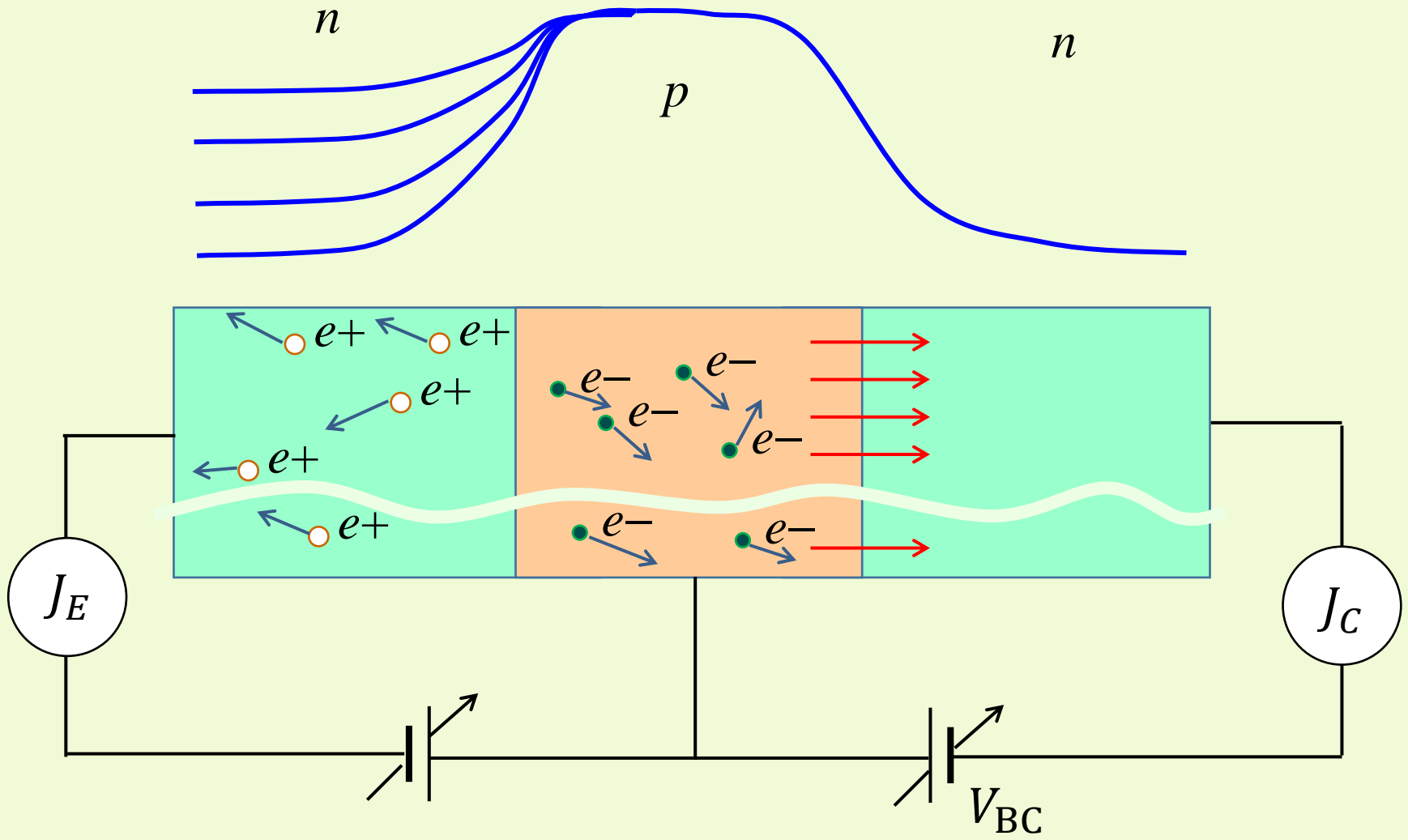

Collector-Emitter characteristics

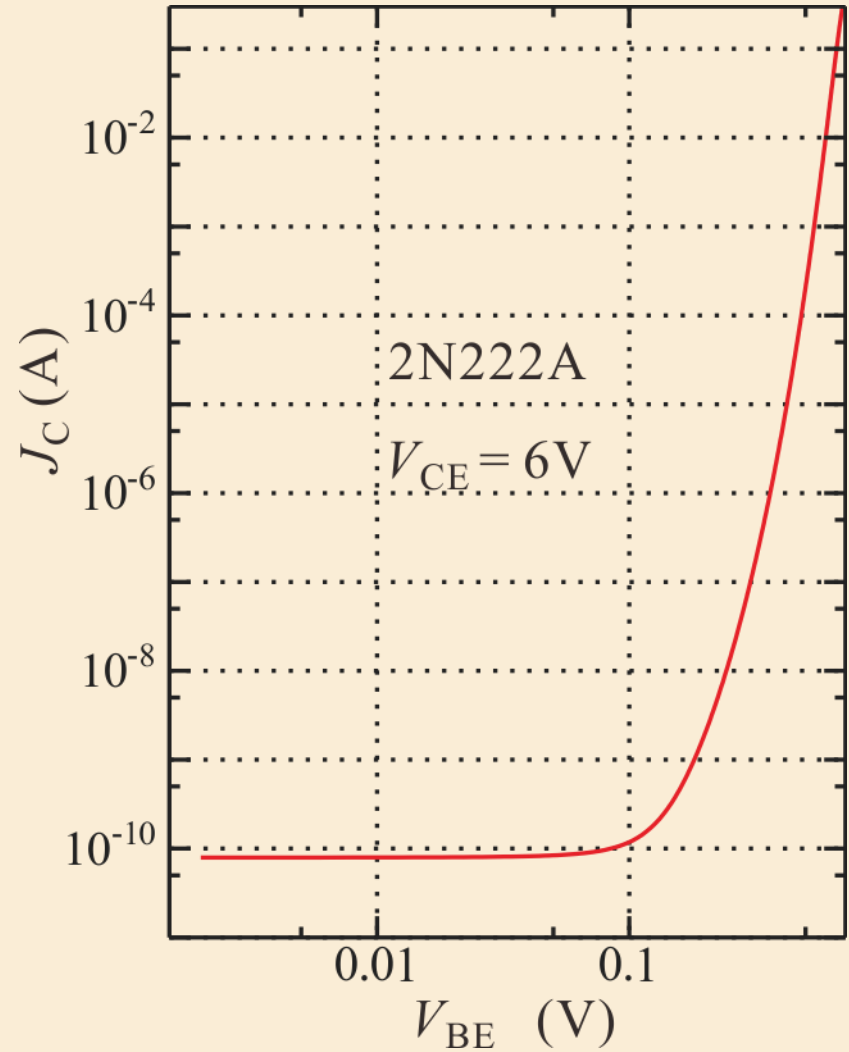  


 Current amplification : Linearize with quantity selection




$$J_C = \underline{h_{FE}} J_B$$

Emitter-common current gain

 


Linear approximation of bipolar transistor

Hybrid matrix

 

 
$$\begin{pmatrix} V_1 \\ J_2 \end{pmatrix} = \begin{pmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{pmatrix} \begin{pmatrix} J_1 \\ V_2 \end{pmatrix}.$$



$$j_2 \begin{pmatrix} v_1 \\ j_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} j_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} h_i & h_r \\ h_f & h_o \end{pmatrix} \begin{pmatrix} j_1 \\ v_2 \end{pmatrix}$$


h-parameters

(lower case:
local linear approximation)

 

Concept of bias circuits for non-linear devices

Common emitter amplifier

 


For small amplitude (high-frequency) circuits




All the capacitors can be viewed as short circuits.

For bias (dc) circuits



 
All the capacitors can be viewed as break line.



Concept of equivalent circuit

   


   Concept of equivalent circuit: Where is feedback?



$$\begin{aligned}
 A &= \frac{v_o}{v_i} \\
 &= \frac{h_{fe} R_C}{h_{ie} + R_E (1 + h_{fe})} \\
 &\approx \frac{R_C}{R_E} \quad h_{fe} \gg 1
 \end{aligned}$$


Current amplification: Emitter follower

 




$$\frac{v_o}{v_i} = \frac{j_b(1 + h_{fe})(R_E \parallel R_o)}{j_b[h_{ie} + (1 + h_{fe})(R_E \parallel R_o)]}$$
$$\approx 1 \quad (h_{fe} \gg 1)$$

v_o does not depend on load resistance

\Rightarrow Very low output resistance

 

Complementary transistors

   

Symmetric characteristics: Complementary

Symmetric: Small collector current (idling current) for zero input.


Example of transistor datasheet

TOSHIBA



2SC1815(L)

TOSHIBA Transistor Silicon NPN Epitaxial Type (PCT process)

2SC1815(L)

 

Unit: mm

  

1. EMITTER
2. COLLECTOR
3. BASE

Audio Frequency Voltage Amplifier Applications
Low Noise Amplifier Applications

- High breakdown voltage, high current capability
: $V_{CEO} = 50 \text{ V (min)}$, $I_C = 150 \text{ mA (max)}$
- Excellent linearity of h_{FE}
: $h_{FE} (2) = 100 \text{ (typ.)}$ at $V_{CE} = 6 \text{ V}$, $I_C = 150 \text{ mA}$
: $h_{FE} (I_C = 0.1 \text{ mA})/h_{FE} (I_C = 2 \text{ mA}) = 0.95 \text{ (typ.)}$
- Low noise: $NF = 0.2\text{dB (typ.)}$ ($f = 1 \text{ kHz}$).
- Complementary to 2SA1015 (L). (O, Y, GR class).

JEDEC	TO-92
JEITA	SC-43
TOSHIBA	2-5F1B

Example of transistor datasheet

TOSHIBA

2SC1815(L)

TOSHIBA Transistor Silicon NPN Epitaxial Type (PCT process)


2SC1815(L)

Electrical Characteristics (Ta = 25°C)

Characteristics		Symbol	Test Condition	Min	Typ.	Max	Unit
Collector cut-off current		I_{CBO}	$V_{CB} = 60\text{ V}, I_E = 0$	—	—	0.1	μA
Emitter cut-off current		I_{EBO}	$V_{EB} = 5\text{ V}, I_C = 0$	—	—	0.1	μA
DC current gain		$h_{FE} (1)$ (Note)	$V_{CE} = 6\text{ V}, I_C = 2\text{ mA}$	70	—	700	
		$h_{FE} (2)$	$V_{CE} = 6\text{ V}, I_C = 150\text{ mA}$	25	100	—	
Saturation voltage	Collector-emitter	$V_{CE}(\text{sat})$	$I_C = 100\text{ mA}, I_B = 10\text{ mA}$	—	0.1	0.25	V
	Base-emitter	$V_{BE}(\text{sat})$	$I_C = 100\text{ mA}, I_B = 10\text{ mA}$	—	—	1.0	
Transition frequency		f_T	$V_{CE} = 10\text{ V}, I_C = 1\text{ mA}$	80	—	—	MHz
Collector output capacitance		C_{ob}	$V_{CB} = 10\text{ V}, I_E = 0, f = 1\text{ MHz}$	—	2.0	3.5	pF
Base intrinsic resistance		$r_{bb'}$	$V_{CE} = 10\text{ V}, I_E = -1\text{ mA}, f = 30\text{ MHz}$	—	50	—	Ω
Noise figure		NF (1)	$V_{CE} = 6\text{ V}, I_C = 0.1\text{ mA}$ $R_G = 10\text{ k}\Omega, f = 100\text{ Hz}$	—	0.5	6	dB
		NF (2)	$V_{CE} = 6\text{ V}, I_C = 0.1\text{ mA}$ $R_G = 10\text{ k}\Omega, f = 1\text{ kHz}$	—	0.2	3	


Note: $h_{FE} (1)$ classification O: 70~140, Y: 120~240, GR: 200~400, BL: 350~700

Example of transistor datasheet

 


Cut-off frequency as a function of I_C


 
h_{fe} linear model availability
in the range of I_C .



 Common emitter (grounded emitter) amplifier circuit




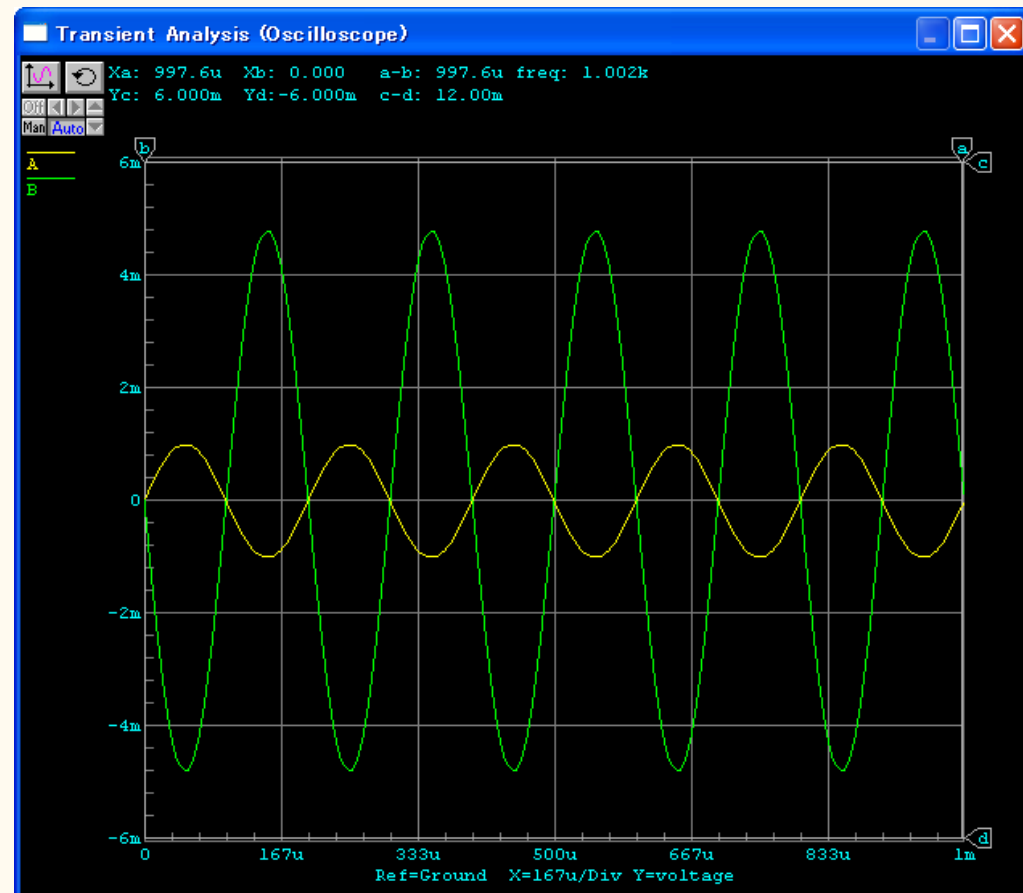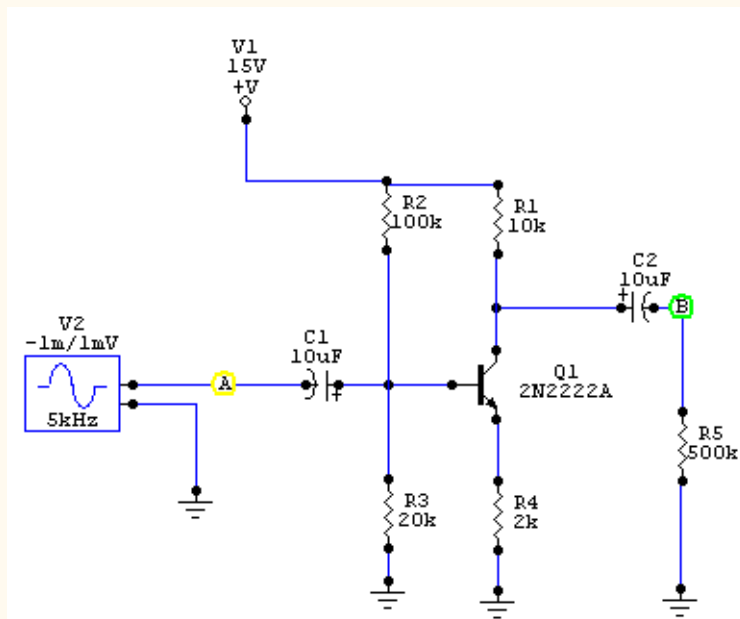
$$\Delta V_C = R_2 \Delta J_C \approx R_2 \Delta J_E = R_2 \frac{\Delta V_E}{R_4} = \frac{R_2}{R_4} \Delta V$$




4.4 Field effect transistor (FET)


Junction FET (JFET)

  


Circuit symbols

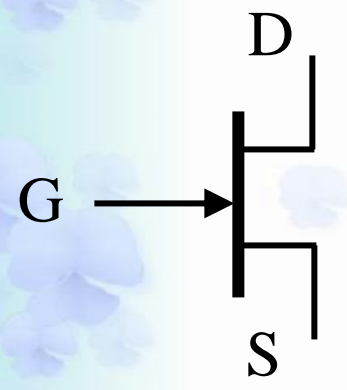

n-channel


 


p-channel





 


Pinch-off

MES-FET

  

MOS-FET

    
 


Simplified
CMOS inverter
circuit

Low leakage
current

Single gate input
both on/off switch

Static characteristics of FET

  

$$J_G \simeq 0, \quad g_m \equiv \left(\frac{\partial J_D}{\partial V_{GS}} \right)_{V_D = \text{const.}}, \quad \text{transconductance}$$

$$J_D = f(V_G, V_D)$$

$$r_d \equiv \left(\frac{\partial V_D}{\partial J_D} \right)_{V_{GS} = \text{const.}} \quad \text{Drain resistance}$$

Locally linear approximation
$$\dot{j}_d = g_m v_{gs} + \frac{v_d}{r_d}$$

References

Feedback

- 土谷武士, 江上正 「現代制御工学」 (産業図書, 2000)
- J. J. Distefano, et al. “Schaum’s outline of theory and problems of feedback and control systems” 2nd ed. (McGraw-Hill, 1990)


OP amp. circuit design

- 岡村迪夫 「OPアンプ回路の設計」 CQ出版社
- J. K. Roberge, K. H. Lundberg, “Operational Amplifiers: Theory and Practice” (MIT, 2007).
<http://web.mit.edu/klund/www/books/opamps181.pdf>

BJT, FET circuits


- 松澤昭 「基礎電子回路工学」 (電気学会, 2009).
- S. M. Sze, K. K. Ng, “Physics of Semiconductor Devices” (Wiley, 2007).

Exercise C-1

 


In the circuit shown in the left, at point P, a waveform in the lower panel was observed. Here V_+ and V_- are power source voltages for + and - respectively.

 Draw a rough sketch of the waveform for V_{out} .



“Rough sketch” should contain the levels and the timing of folding points. Write a short comment why V_{out} should be in such a form.

Exercise C-2

 

Consider a differential amplifier with the open loop gain

$$A(s) = \frac{A_0 \omega_1 \omega_2}{s(s + \omega_1)(s + \omega_2)}.$$

So the gain diverges with $s \rightarrow 0$ but here we ignore this instability. The input impedance is ∞ , and the output impedance is 0.


It is now placed in a circuit with a feedback shown in the left.

Obtain the stability condition for γ .

(hint) Apply the Hurwitz criterion for zeros of even and odd parts of the denominator.

Or just calculate H_2 .

Exercise C-3

 

Let us view a bipolar transistor plus an emitter resistance as a four terminal circuit as shown in the left figure.

Obtain the Y (admittance) matrix defined below for this circuit.

Calculate each element in the Y matrix for $r_e = 25\Omega$, $h_{ie} = 500\Omega$, $h_{fe} = 200$

$$\begin{pmatrix} j_1 \\ j_2 \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix}$$