

電子回路論第7回

Electric Circuits for Physicists



東京大学理学部・理学系研究科
物性研究所
勝本信吾

Shingo Katsumoto

Outline

4.5 Field Effect Transistors (FETs)

Ch.5 Distributed constant circuits

5.1 Transmission lines

5.1.1 Coaxial cables


5.1.2 Lecher lines

5.1.3 Micro-strip lines




5.2 Wave propagation through transmission lines

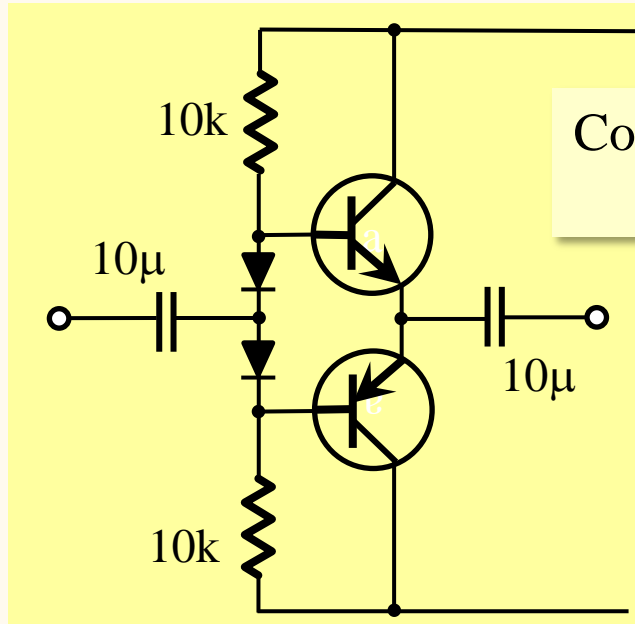5.2.2 Connection and termination of transmission lines

Combination of an OP-amp and discrete transistors




Complementary push-pull

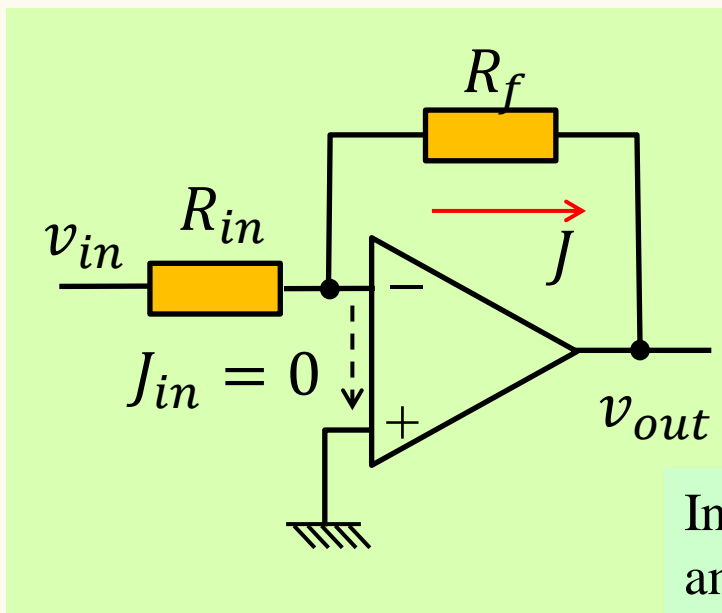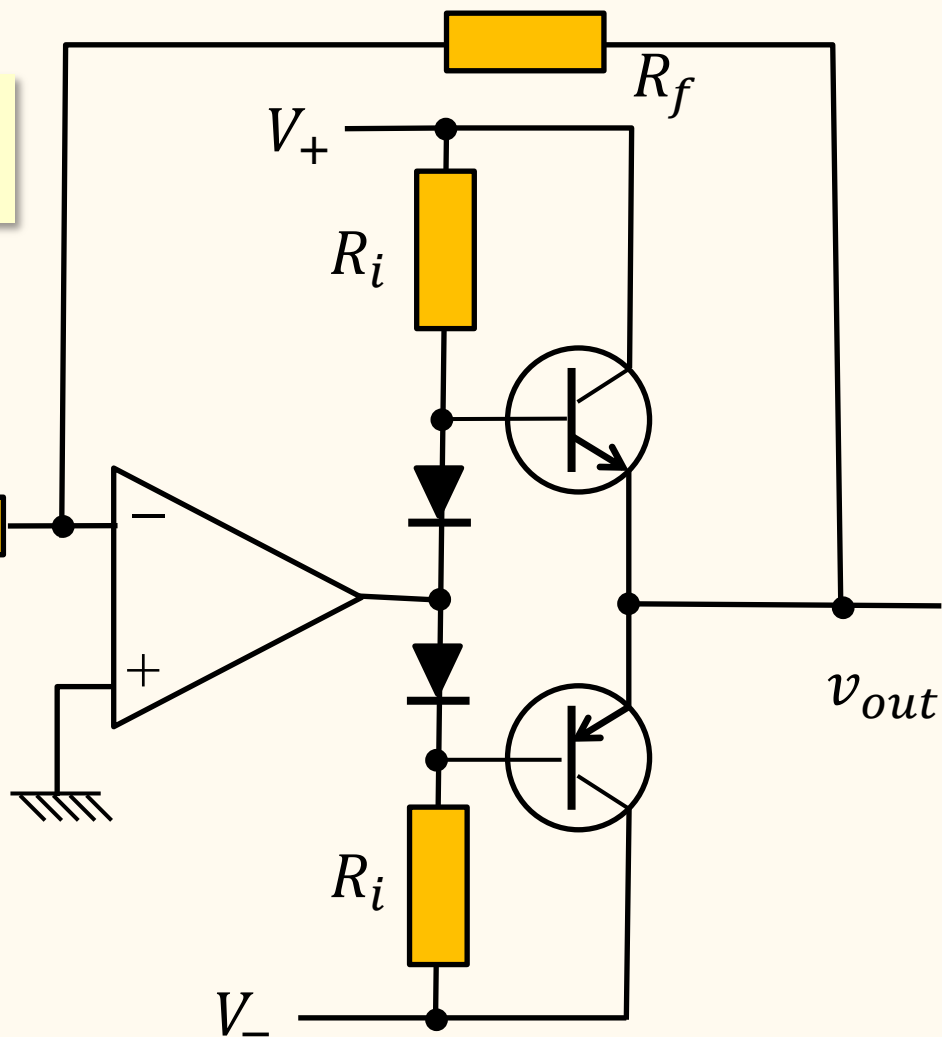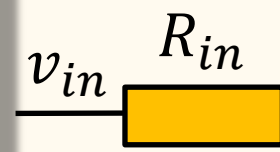

Inversion amplifier

Voltage, current booster

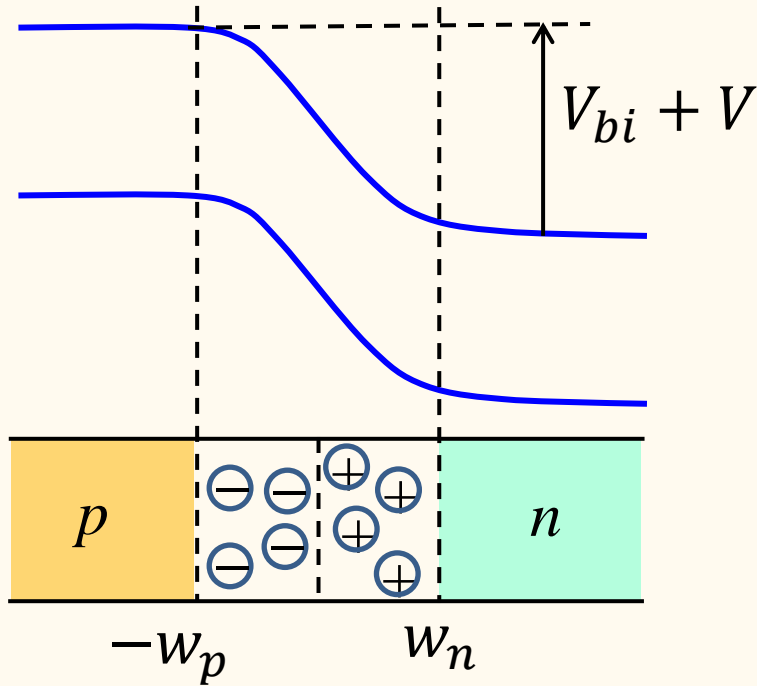Depletion layer width with reverse bias voltage



Poisson equation

$$\frac{d^2\phi}{dx^2} = -aq(x) \quad (a \equiv (\epsilon\epsilon_0)^{-1})$$

$$\begin{cases} q = -eN_A & (-w_p \leq x \leq 0), \\ q = eN_D & (0 \leq x \leq w_n) \end{cases}$$


$$\phi(-\infty) = 0$$

$$\phi(-w_p) = 0, \quad \left. \frac{d\phi}{dx} \right|_{-w_p} = 0,$$

$$\phi(w_n) = V + V_{bi}, \quad \left. \frac{d\phi}{dx} \right|_{w_n} = 0$$

$$\phi(x) = \begin{cases} (aeN_A/2)(x + w_p)^2 & (-w_p \leq x \leq 0), \\ V + V_{bi} - (aeN_D/2)(x - w_n)^2 & (0 \leq x \leq w_n) \end{cases}$$

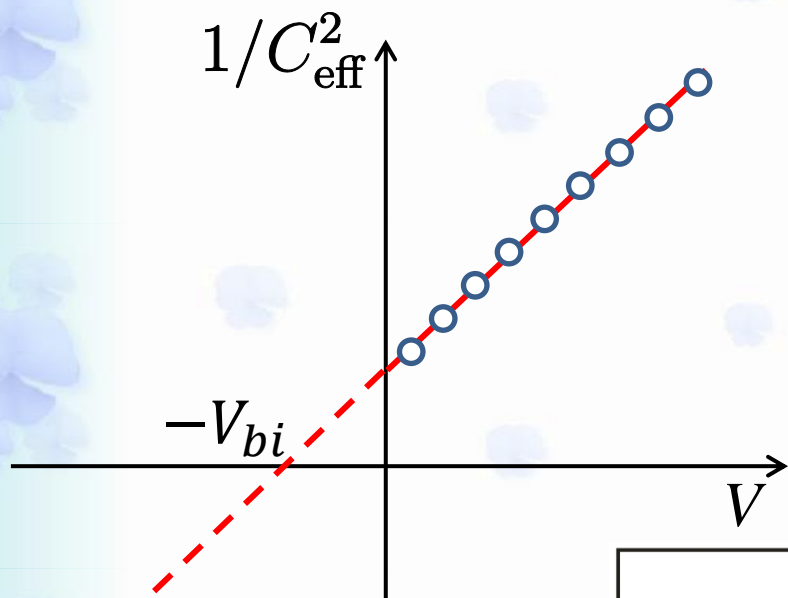Effective capacitance and reverse bias voltage




$$\frac{1}{C_{\text{eff}}^2} = \frac{2}{\epsilon\epsilon_0 e N_D} (V + V_{bi})$$

Doping profiler

Varicap diode





KB505

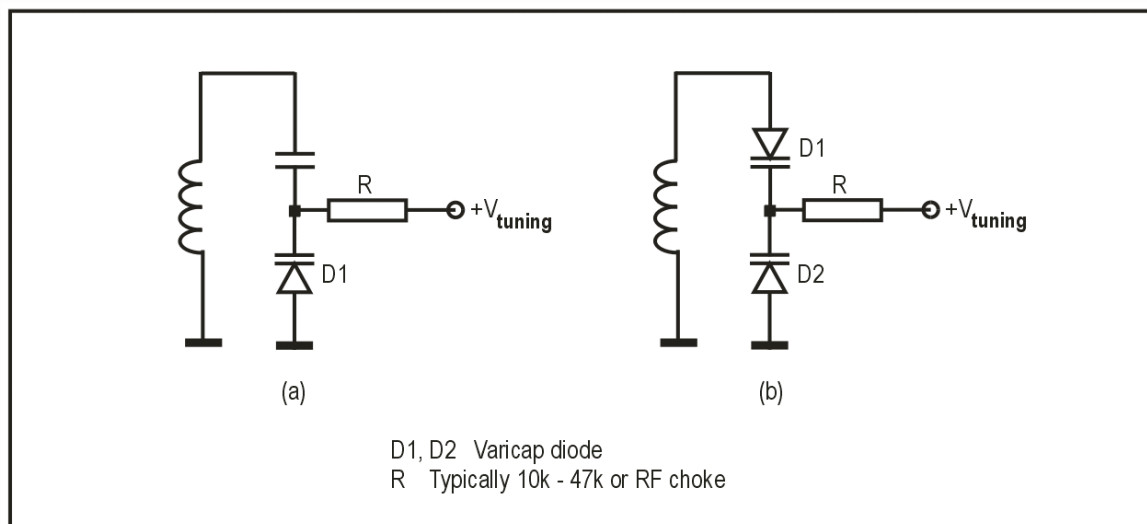


Frequency modulation
Phase lock loop

4.4 Field effect transistor (FET)


Junction FET (JFET)

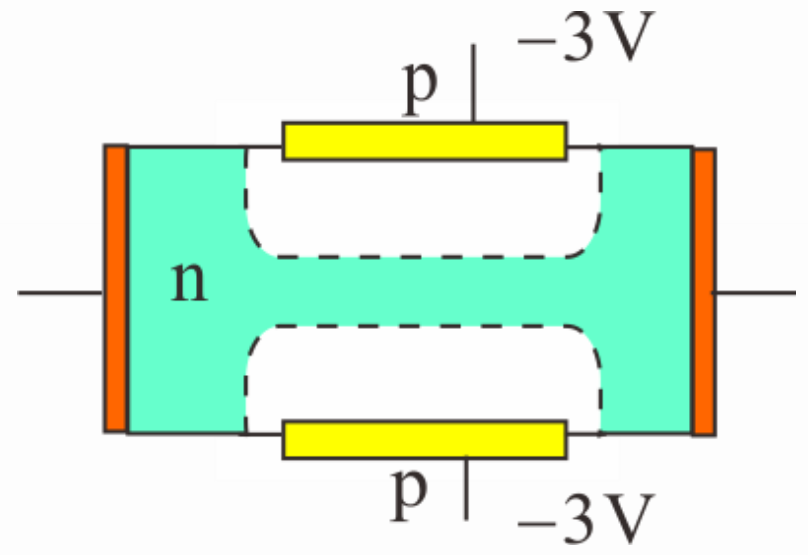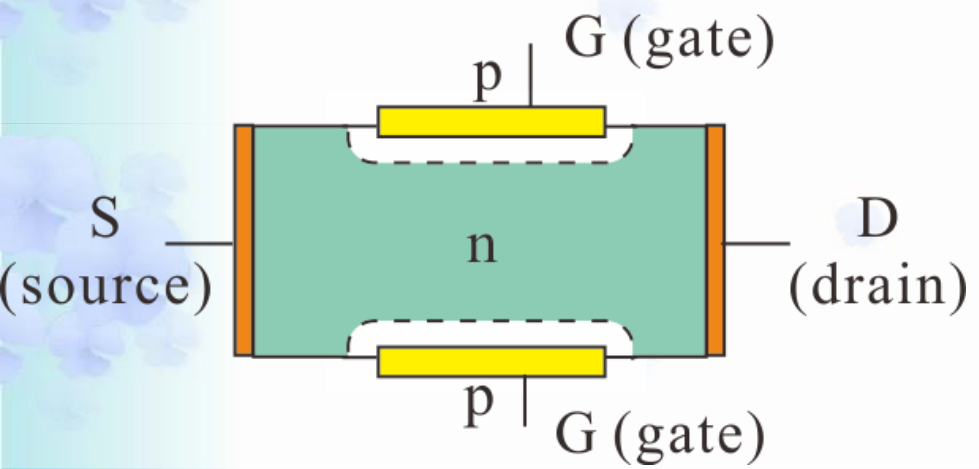


Circuit symbols

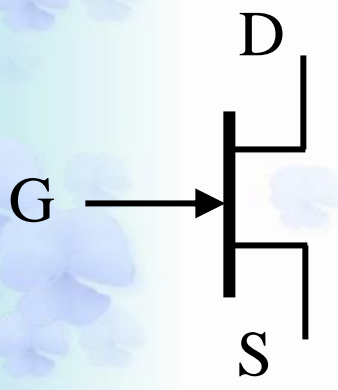

n-channel

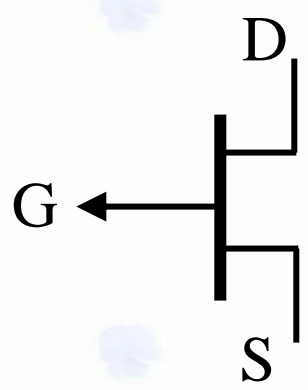


p-channel

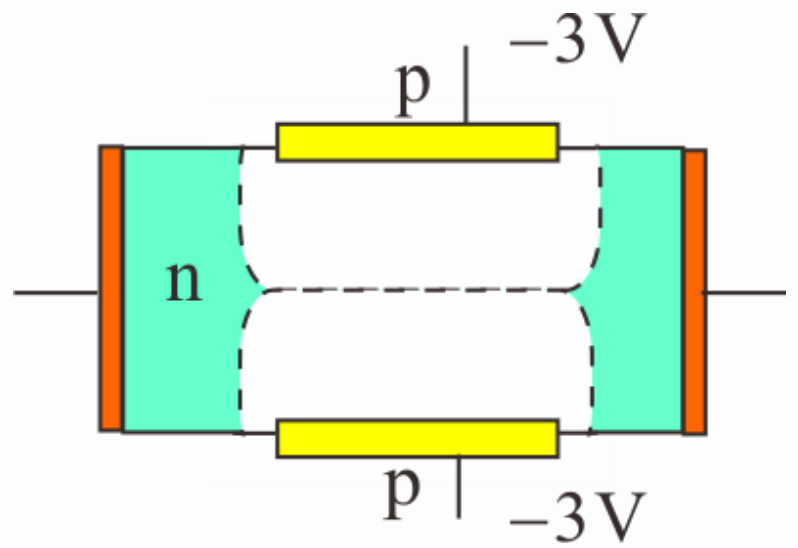


Pinch-off

Static characteristics of FET

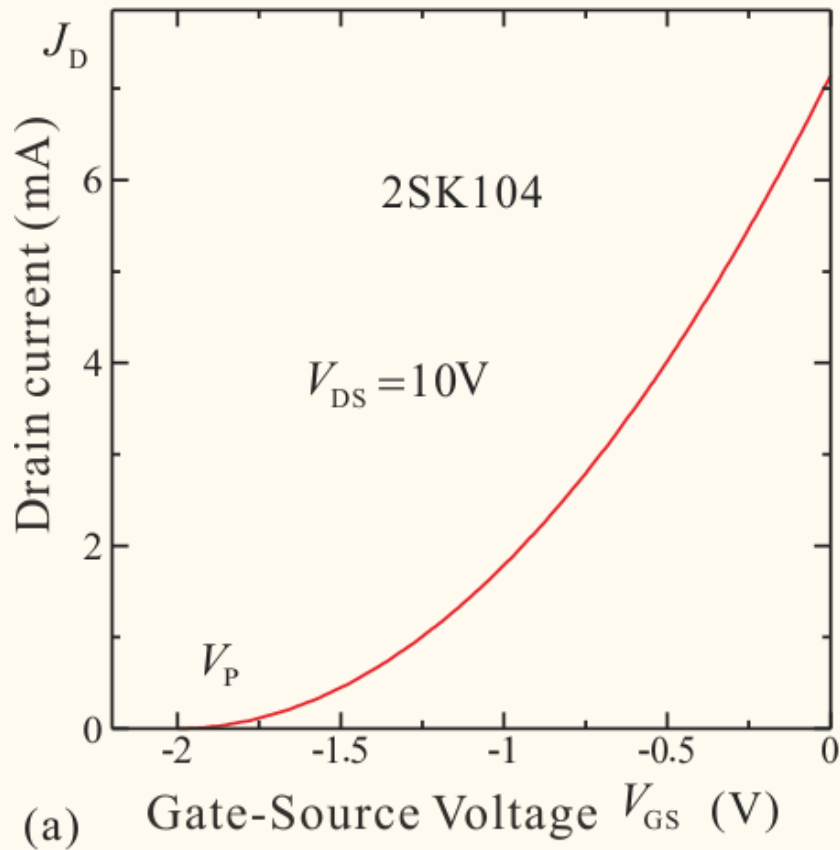

(a)

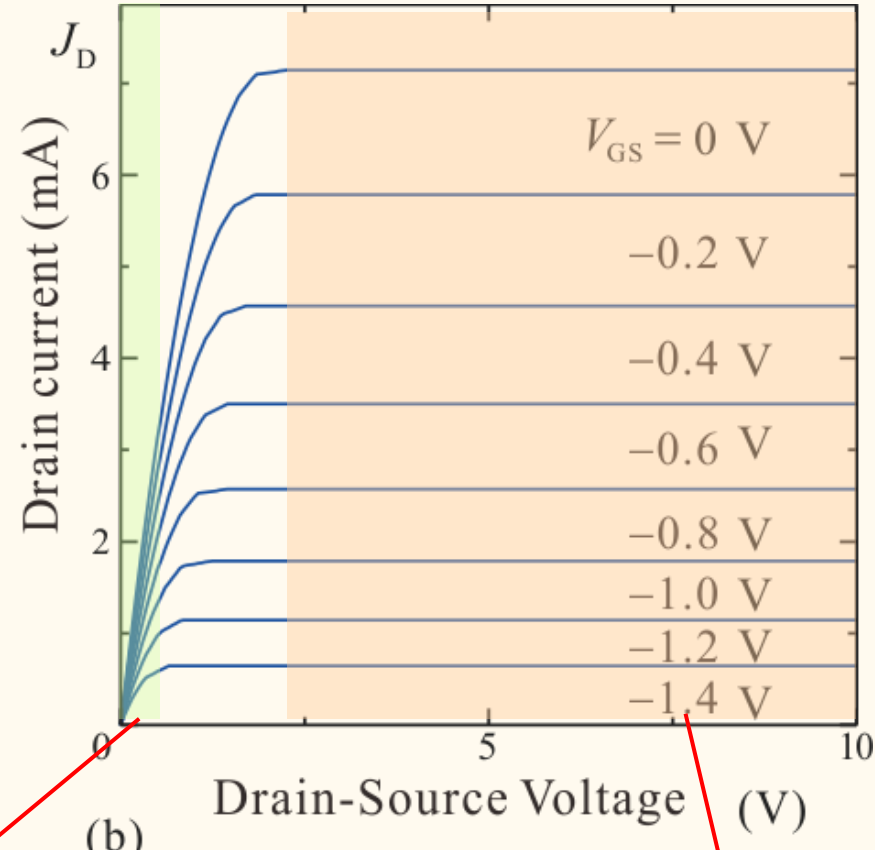


(b)

Ohmic area

Space charge limited area

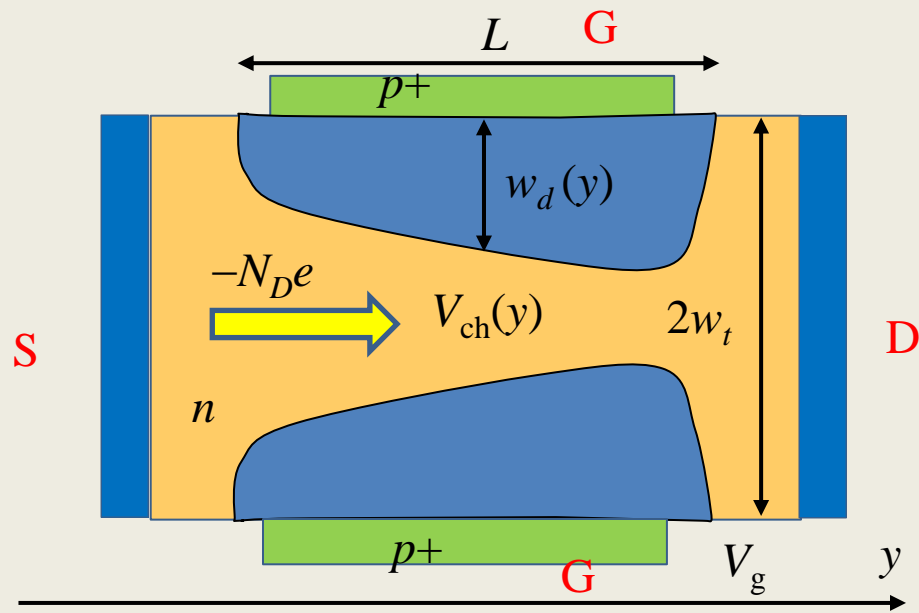Space-charge limitation of source-drain current



$$V(y) = V_g + V_{vi} - V_{ch}(y)$$

$$w_d(y) = \sqrt{\frac{2\epsilon\epsilon_0 V(y)}{eN_D}}$$

$$J_{ch} = \underbrace{eN_D\mu_n}_{\text{conductivity}} \underbrace{\frac{dV_{ch}}{dy}}_{\text{electric field}} \cdot \underbrace{2[w_t - w_d(y)]W}_{\text{channel width}}$$



$$J_{ch}L = \int_0^L J_{ch} dy = 2eN_D\mu_n W \int_0^L (w_t - w_d) \frac{dV}{dy} dy = 2w_t eN_D\mu_n W \int_{V_0}^{V_L} \left(1 - \frac{w_d}{w_t}\right) dV$$

pinch off (internal) voltage: $w_d(V_c) = w_t$ $V_c = \frac{eN_D w_t^2}{2\epsilon\epsilon_0}$

$$J_{ch} = \frac{2N_D e \mu_n W w_t}{L} \left[V_L - V_0 + \frac{2}{3\sqrt{V_c}} (V(V_0)^{3/2} - V(V_L)^{3/2}) \right]$$

Only valid for $w_d < w_t/2$.

Static characteristics of FET

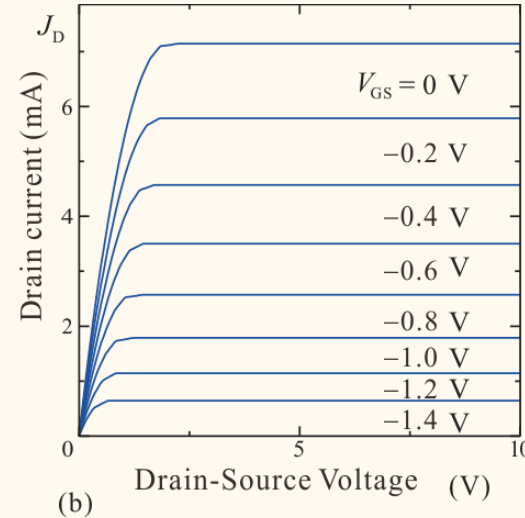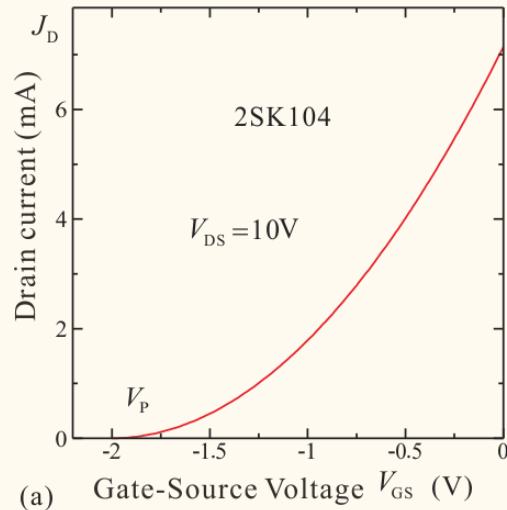

$$J_G \simeq 0, \quad J_D = f(V_G, V_D) \quad g_m \equiv \left(\frac{\partial J_D}{\partial V_{GS}} \right)_{V_D = \text{const.}} \quad \text{transconductance}$$

Low bias current:
small power consumption

$$r_d \equiv \left(\frac{\partial V_D}{\partial J_D} \right)_{V_{GS} = \text{const.}} \quad \text{Drain resistance}$$

Locally linear approximation


$$\dot{j}_d = g_m v_{gs} + \frac{v_d}{r_d}$$

$$v_d = -\underbrace{r_d g_m}_{\text{Amplification factor (voltage gain)}} v_{gs} + r_d \dot{j}_d$$


Amplification factor (voltage gain) $\equiv \mu$

Biasing circuits for FETs

Fixed bias circuit

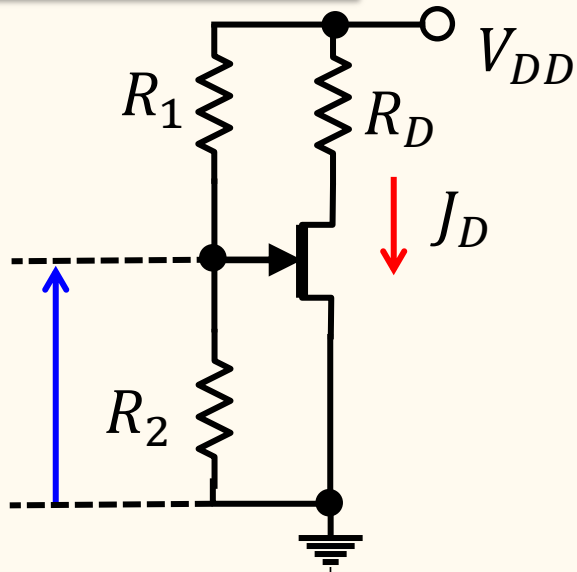

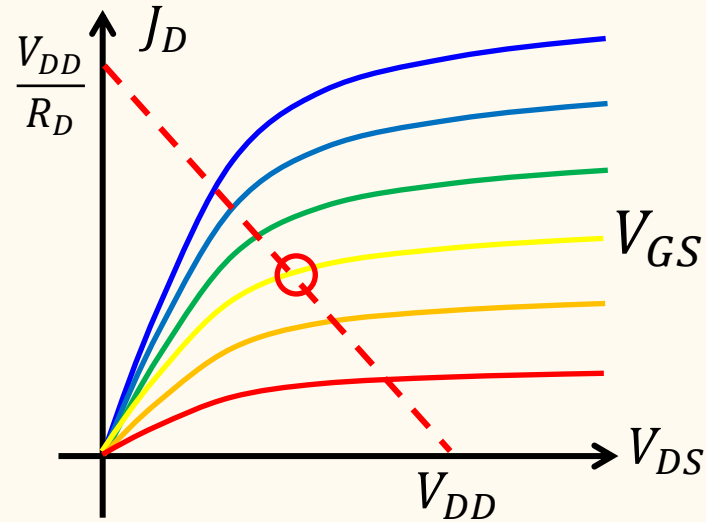
$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD}, \quad V_{DS} = V_{DD} - R_D J_D$$




Self-biasing circuit


Generally more stable

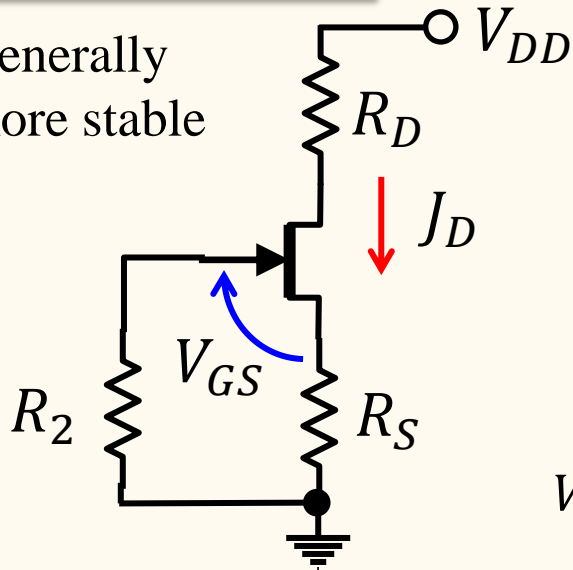






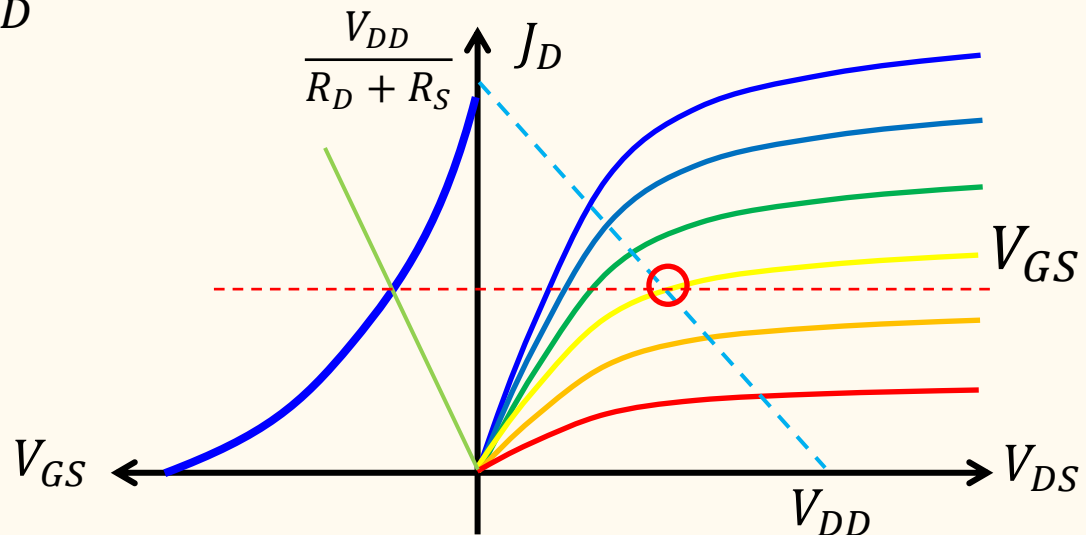
$$V_{GS} = -R_S J_D, \quad V_{DS} = V_{DD} - (R_D + R_S) J_D$$





Equivalent signal circuits for FET

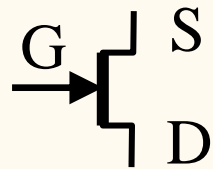






$$\mu = r_d g_m$$

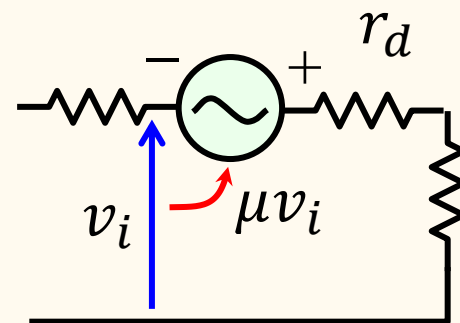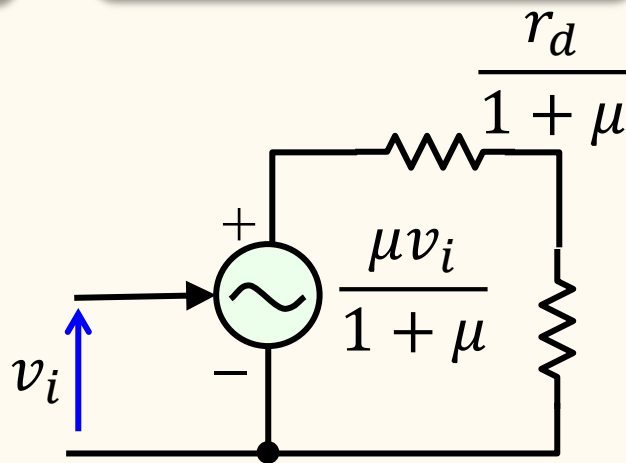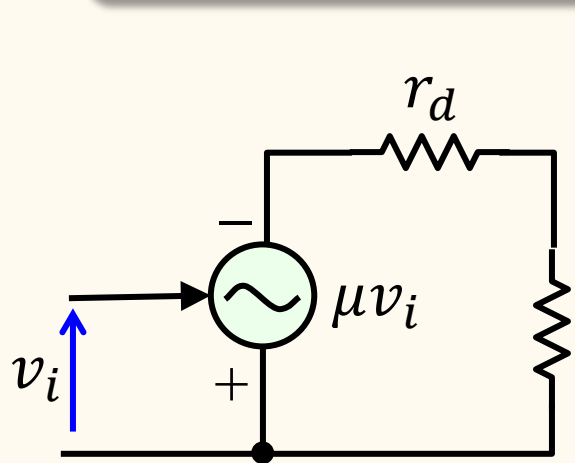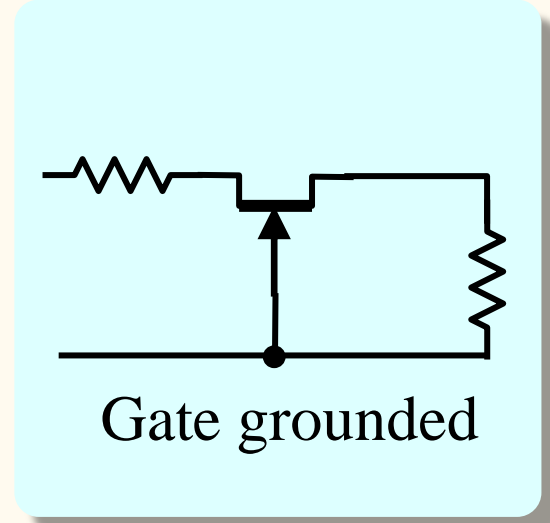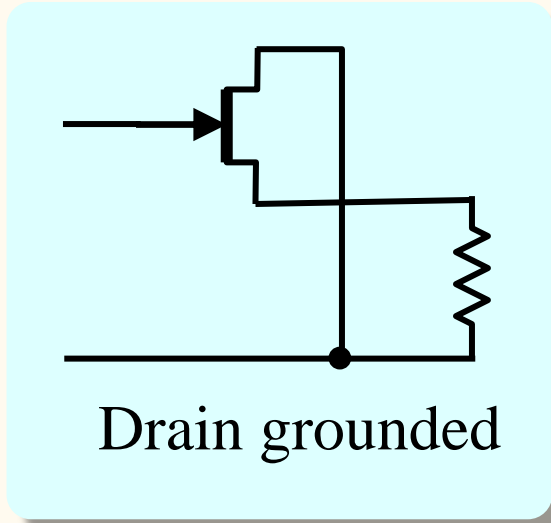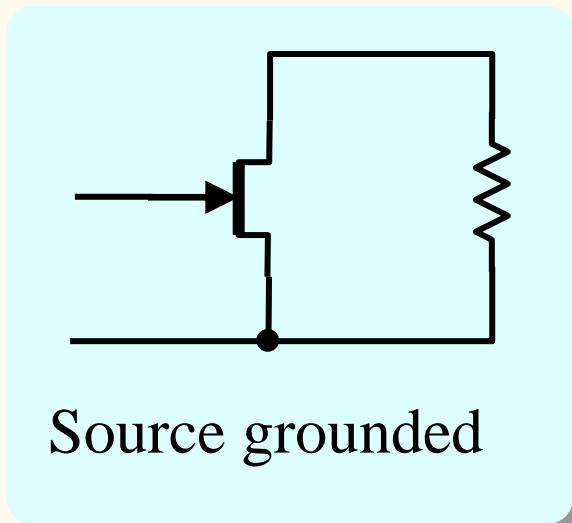

MES-FET

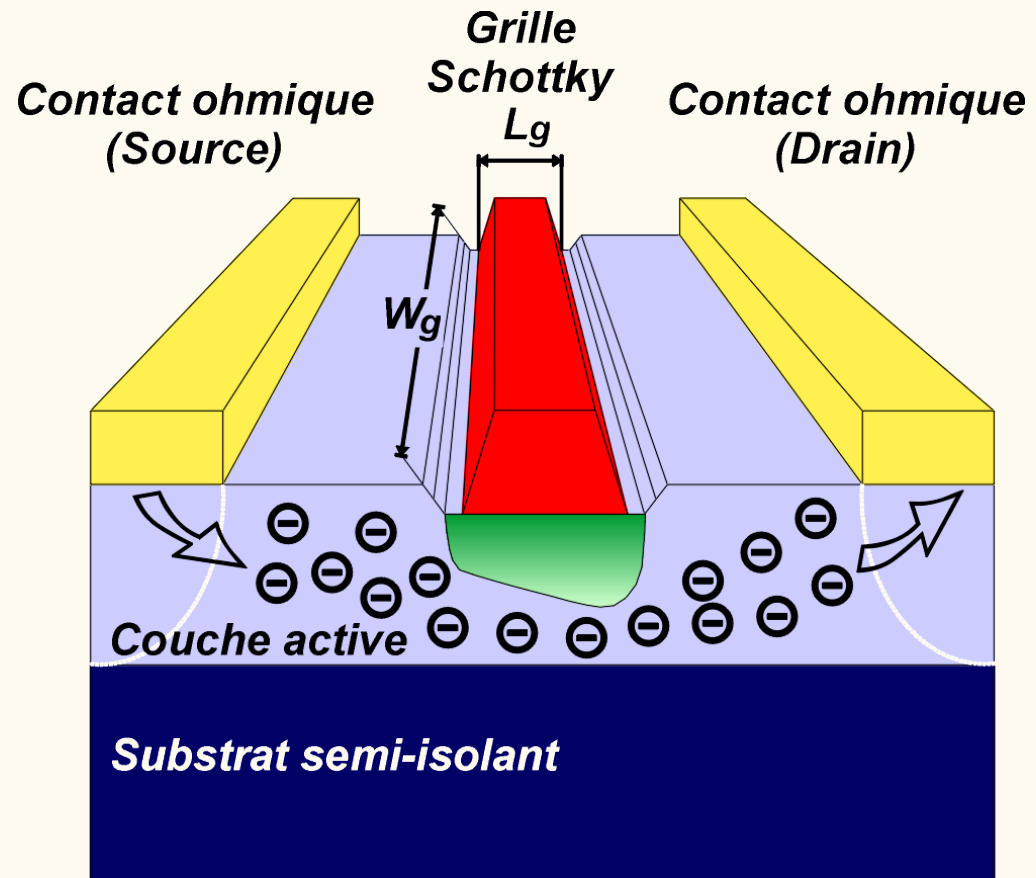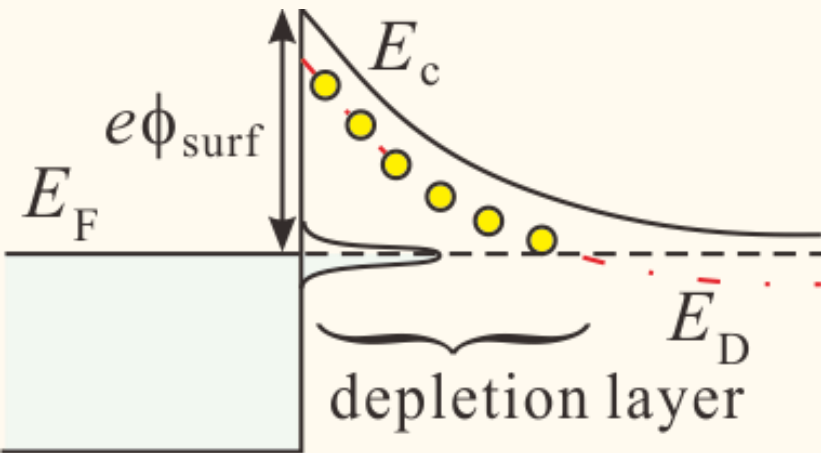

MOS-FET

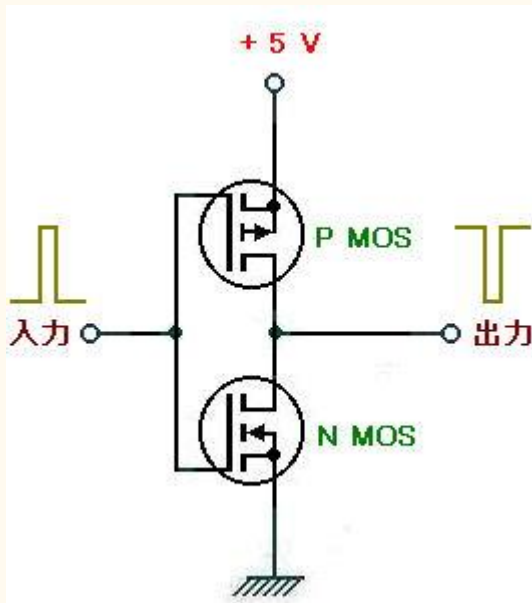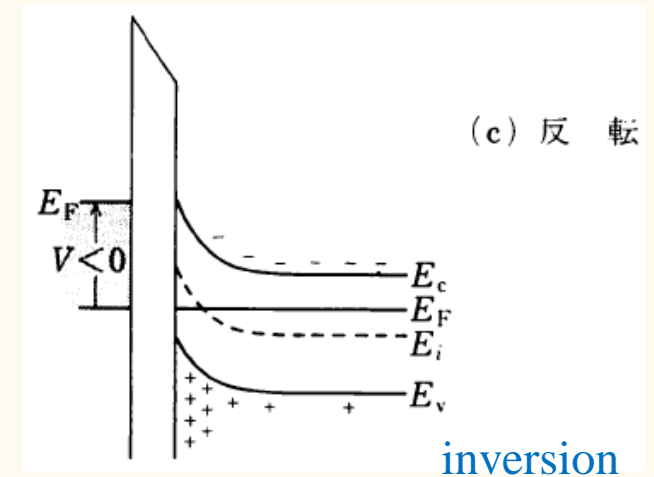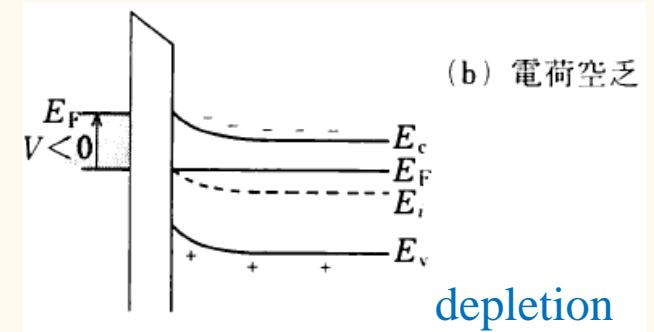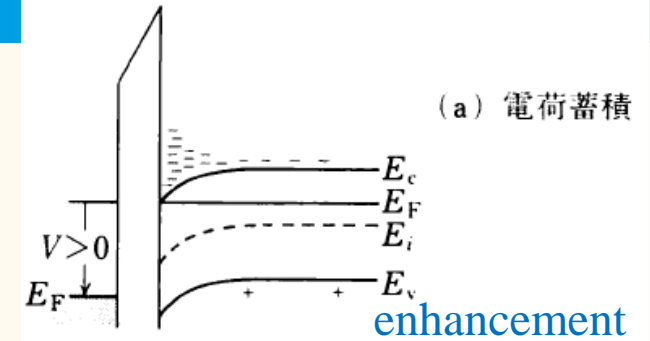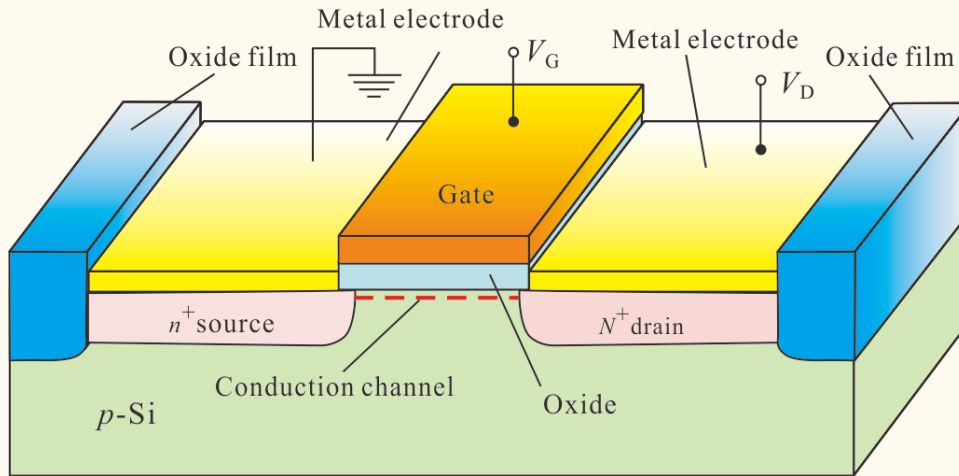


Simplified
CMOS inverter
circuit

Low leakage
current

Single gate input
both on/off switch


MOSFET switching characteristics

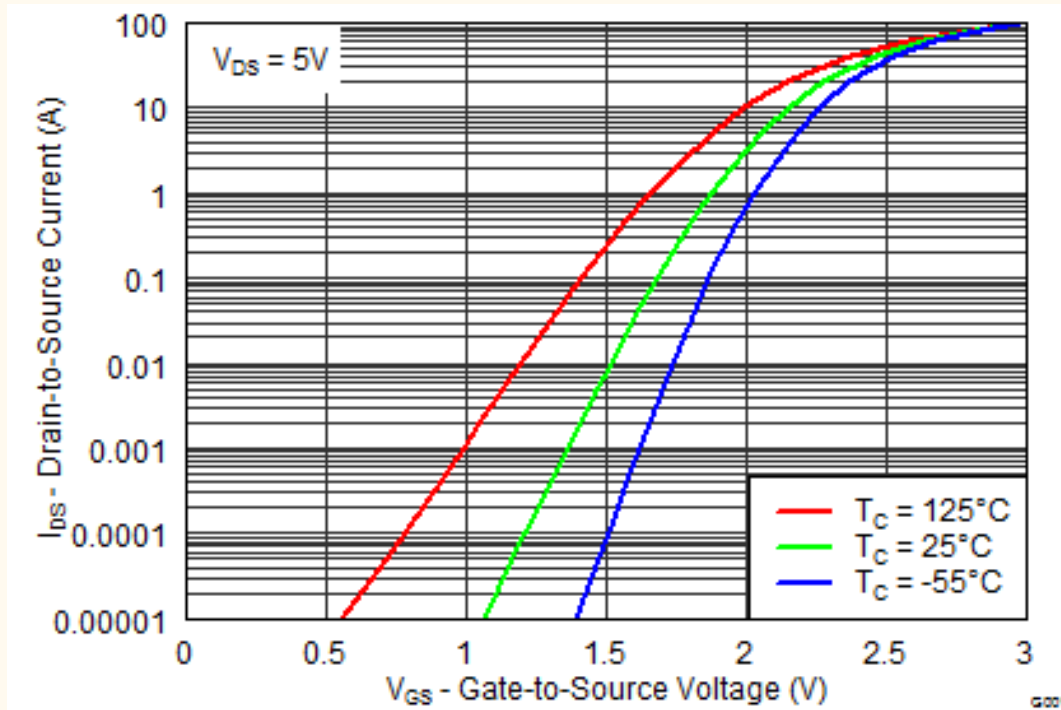From datasheet CSD87381P power MOSFET (Texas instr.).



More than 7 orders change in I_D within 3 V change of V_{GS} .

Ch.5 Distributed constant circuits

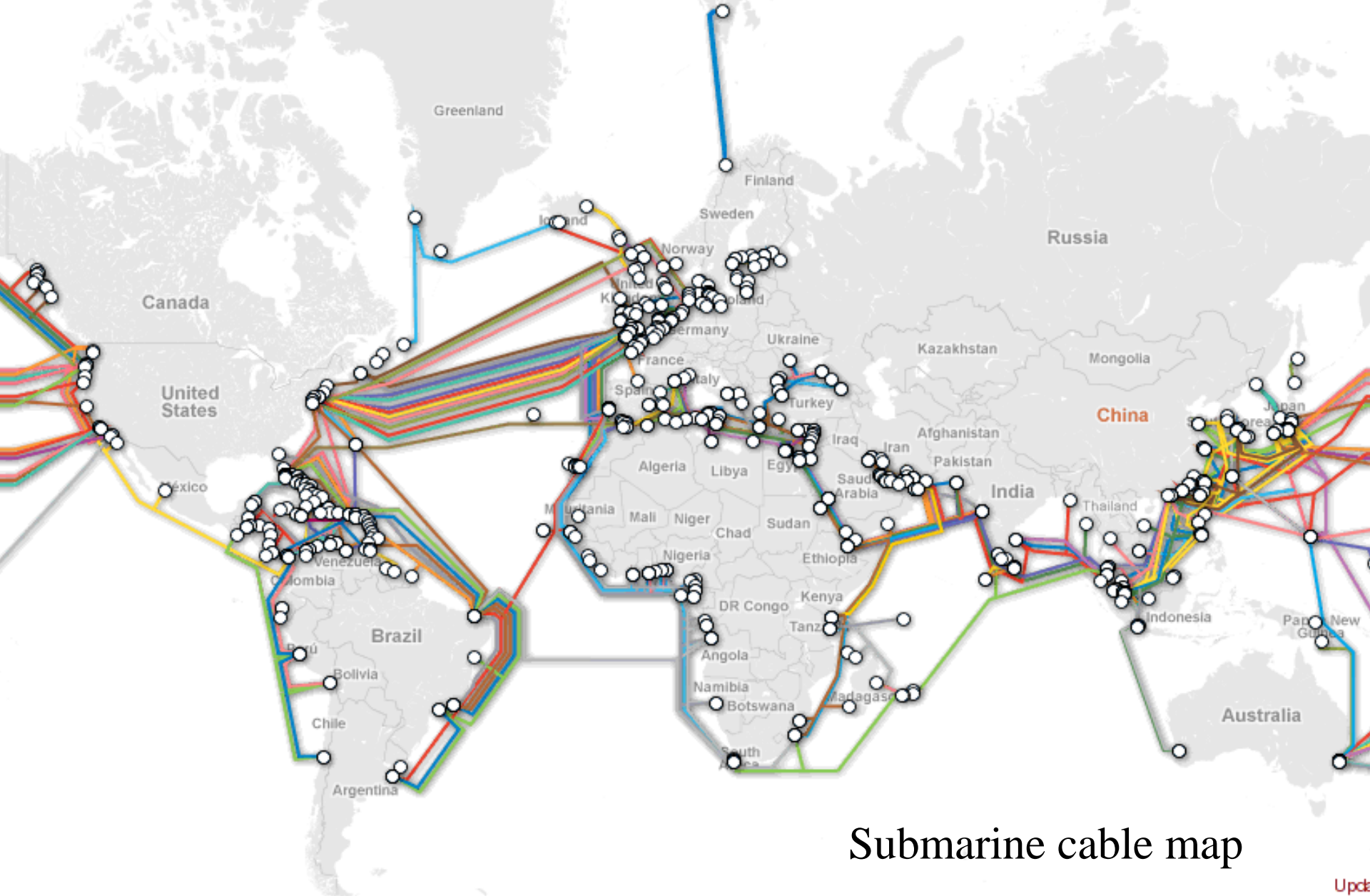


Distributed constant circuit concept

1. In what case we need to consider distributed constant circuits?

Characteristic sizes of devices \gtrsim wavelength of electromagnetic signal


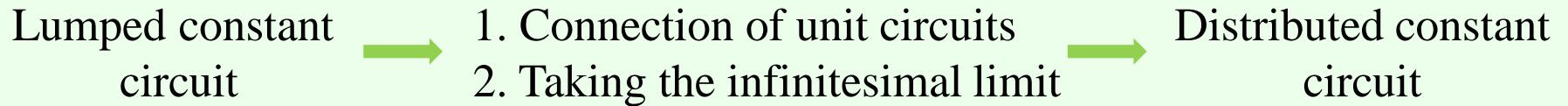
2. A typical scheme to make the shift for distributed circuit




3. Distributed constant circuits : transmission lines

Coaxial cables, Lecher lines, micro-strip lines, waveguides, optical fibers

5.1.1 Coaxial cable

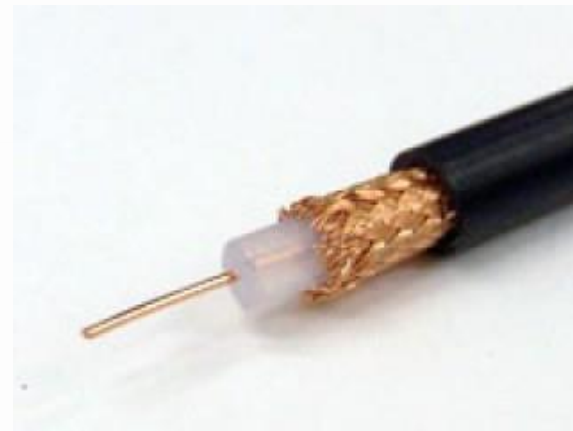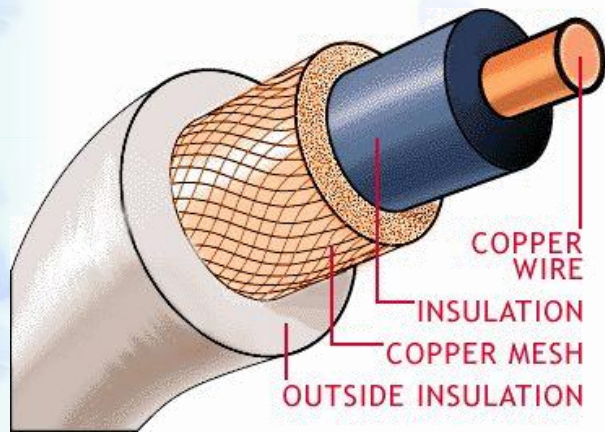


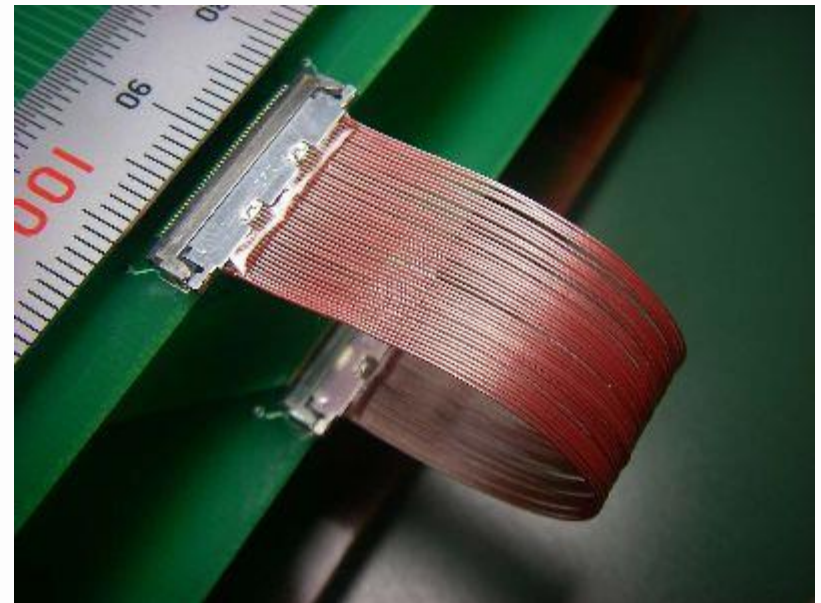Thin coaxial cable AWG50 ($\phi 25\mu\text{m}$)




Transmission line as a series of infinitesimal terminal-pairs

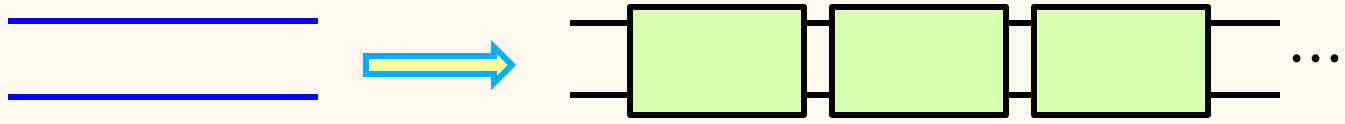Transmission line → divide into four terminal circuits




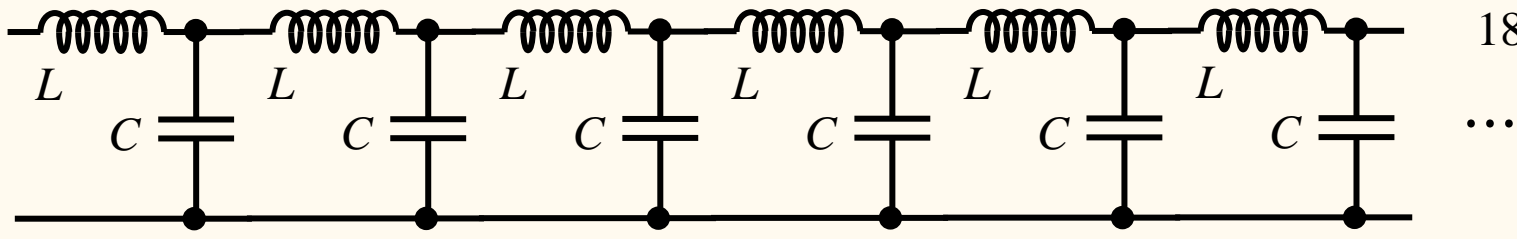Each unit should have delay. Ignore energy dissipation.



Oliver Heaviside
1850- 1925

Then take the infinitesimal limit

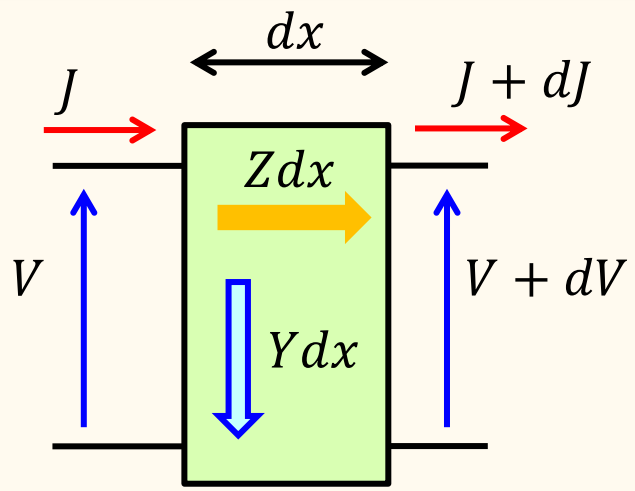

Width → 0, Number → ∞

$$dV = -JZdx, \quad dJ = -VYdx$$

$$\begin{cases} \frac{d^2 J}{dx^2} = YZJ, \\ \frac{d^2 V}{dx^2} = YZV \end{cases}$$

Telegraphic equation

Characteristic impedance

$$\kappa \equiv \sqrt{YZ} \quad (\text{dimension: } L^{-1})$$

$$J(x, t) = J(0, t) \exp(\pm \kappa x), \quad V(x, t) = V(0, t) \exp(\pm \kappa x)$$

–: Progressive, +: Retrograde

$$\frac{V}{J} = \mp \frac{Z}{\kappa} = \mp \sqrt{\frac{Z}{Y}}$$


Characteristic impedance

Pure reactance $Y = i\omega C$, $Z = i\omega L$ For L and C model


$$\kappa = \sqrt{-\omega^2 LC} = i \frac{\omega}{\omega_0}, \quad \omega_0 \equiv \frac{1}{\sqrt{LC}} \quad (\text{dimension: velocity})$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

Coaxial cable setup

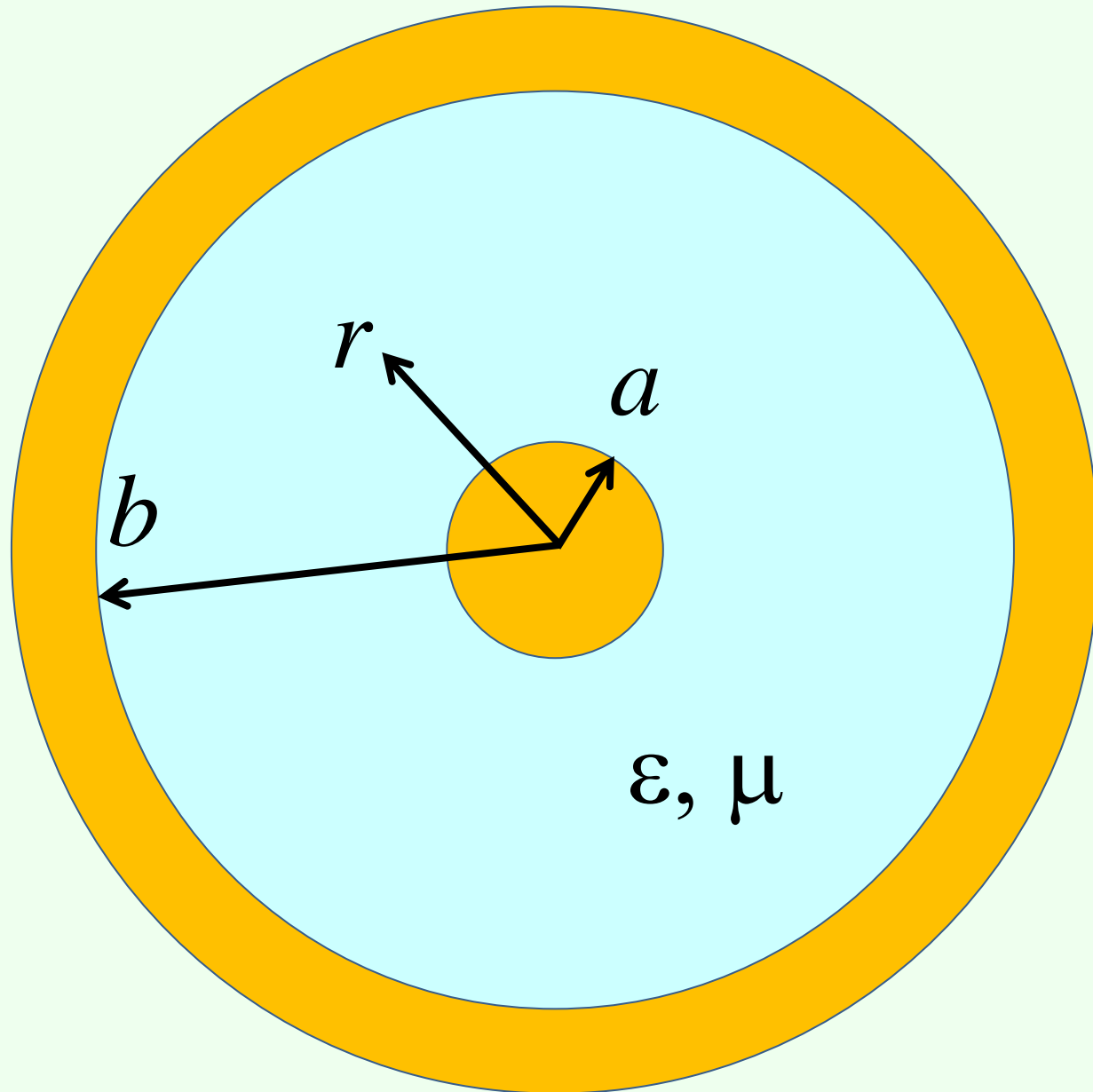

Maxwell theory

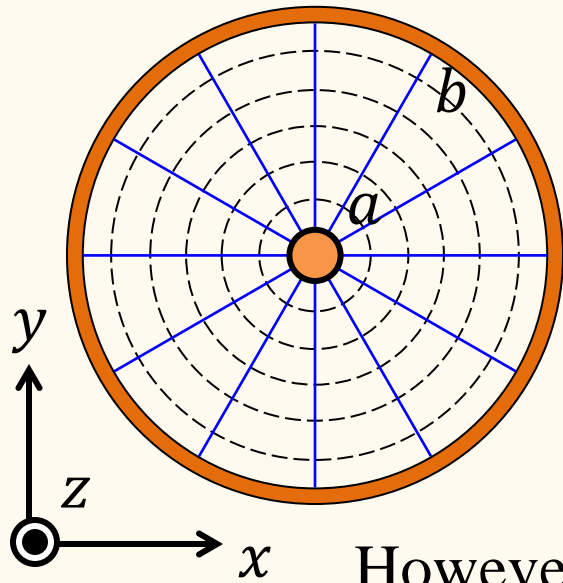

$$E = E_0(x, y)e^{i\omega t - \gamma z}, \quad H = H_0(x, y)e^{i\omega t - \gamma z}$$

From Maxwell equations

$$(\omega^2 \epsilon \mu + \gamma^2) \begin{pmatrix} E_x \\ E_y \end{pmatrix} = \begin{pmatrix} -\gamma \partial_x & -i\omega \mu \partial_y \\ -\gamma \partial_y & i\omega \mu \partial_x \end{pmatrix} \begin{pmatrix} E_z \\ H_z \end{pmatrix},$$

$$(\omega^2 \epsilon \mu + \gamma^2) \begin{pmatrix} H_x \\ H_y \end{pmatrix} = \begin{pmatrix} i\omega \mu \partial_y & -\gamma \partial_x \\ -i\omega \mu \partial_x & -\gamma \partial_y \end{pmatrix} \begin{pmatrix} E_z \\ H_z \end{pmatrix}.$$

However in TEM (transverse electric and magnetic) mode:

$$E_z = H_z = 0 \quad \text{i.e., the RHSs are zero.}$$

For the fields along x and y to survive, $\omega^2 \epsilon \mu + \gamma^2 = 0 \quad \therefore \gamma = \pm i\omega \sqrt{\epsilon \mu}$

Propagation velocity
$$v = \frac{\omega}{\omega \sqrt{\epsilon \mu}} = \frac{1}{\sqrt{\epsilon \mu}}$$

In such a case, from Maxwell equations: $\text{rot}_{xy} \mathbf{H} = 0, \quad \text{rot}_{xy} \mathbf{E} = 0$

→ Potentials are conceivable for \mathbf{H} and \mathbf{E} .

Maxwell theory

$$\mathbf{E} = \nabla_{xy} \mathcal{U} / \sqrt{\epsilon}, \quad \mathbf{H} = \nabla_{xy} \mathcal{V} / \sqrt{\mu}$$

$$\frac{\partial \mathcal{U}}{\partial x} = \frac{\partial \mathcal{V}}{\partial y}, \quad \frac{\partial \mathcal{U}}{\partial y} = -\frac{\partial \mathcal{V}}{\partial x} \quad \text{Cauchy-Riemann theorem}$$

$$\text{Characteristic impedance: } Z_0 = \frac{\mathcal{U}_a - \mathcal{U}_b}{J \sqrt{\epsilon}}$$

If we can express V and J in the form of distributed constant circuit model (L and C model), the equivalence is certified.

Capacitance part

$$V = \frac{q}{\epsilon} \int_a^b \frac{dr}{2\pi r} = \frac{q}{2\pi\epsilon} \log \frac{b}{a} = \frac{q}{C}$$
$$\therefore C = \frac{2\pi\epsilon}{\log(b/a)}$$

Maxwell theory

Inductance part

Core current J , shield current $-J$

$$H(r) = \frac{J}{2\pi r}, \quad B(r) = \frac{\mu J}{2\pi r}$$

Flux per length: $\Phi = \int_a^b dr B(r) = \frac{\mu J}{2\pi} \log \frac{b}{a}$

Self inductance per length: $L = \frac{\mu}{2\pi} \log(b/a)$

$$Z_0 = \sqrt{\frac{L}{C}} = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \log \left(\frac{b}{a} \right)$$

cf. Characteristic impedance of vacuum $Z_0 = \sqrt{\frac{\mu_0}{\epsilon_0}} \approx 376\Omega$

Coaxial cable 2

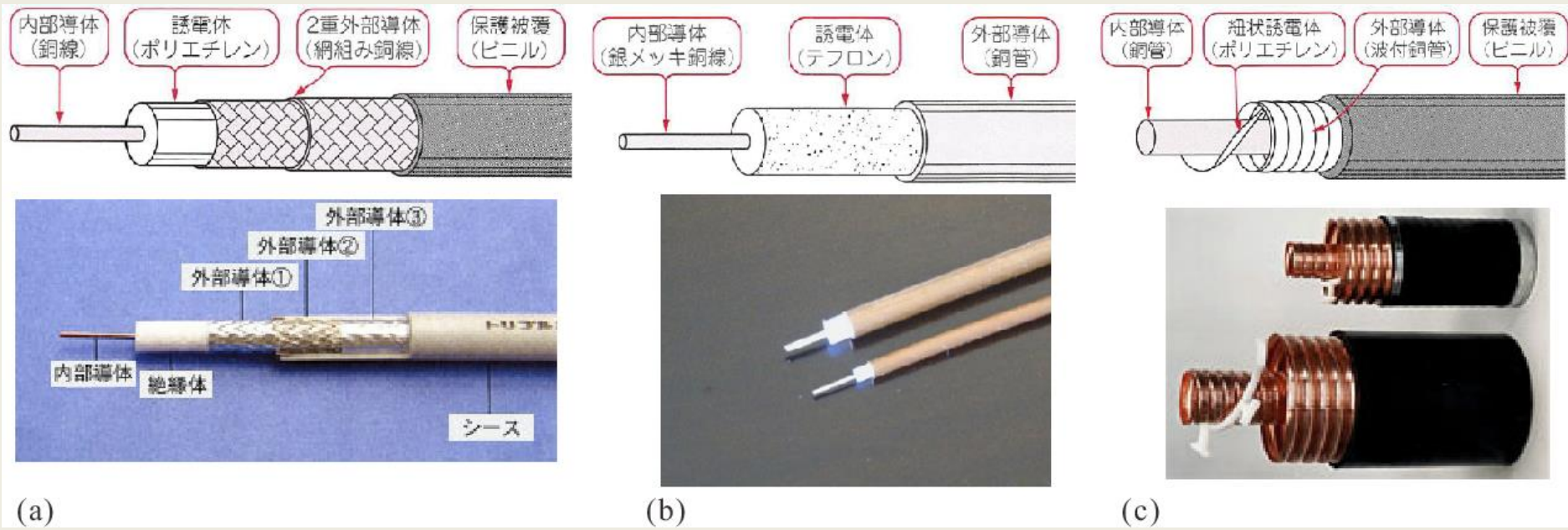


図12 同軸ケーブルの型名 (JIS C3501)



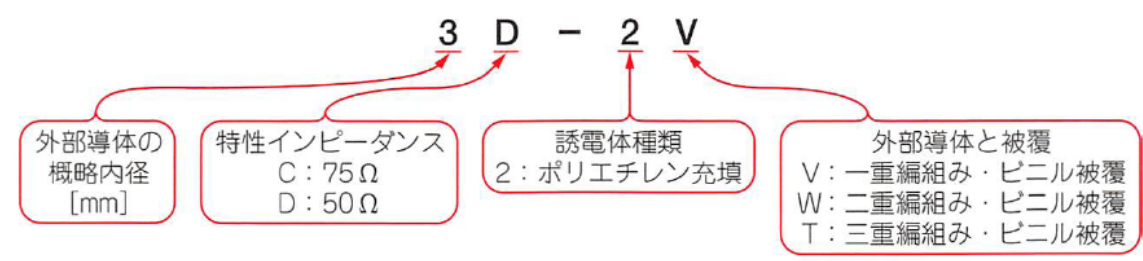


図13 MIL規格での同軸ケーブル型名の例

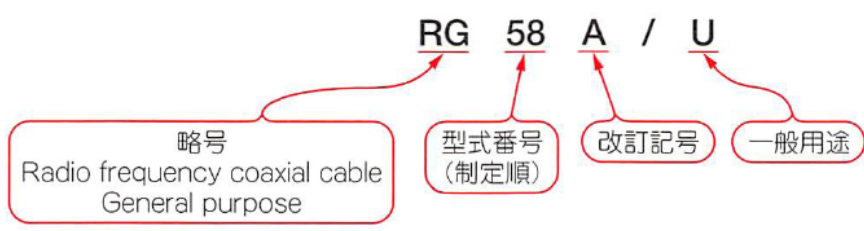

Coaxial connectors

図22 同軸コネクタの構造(概念図)

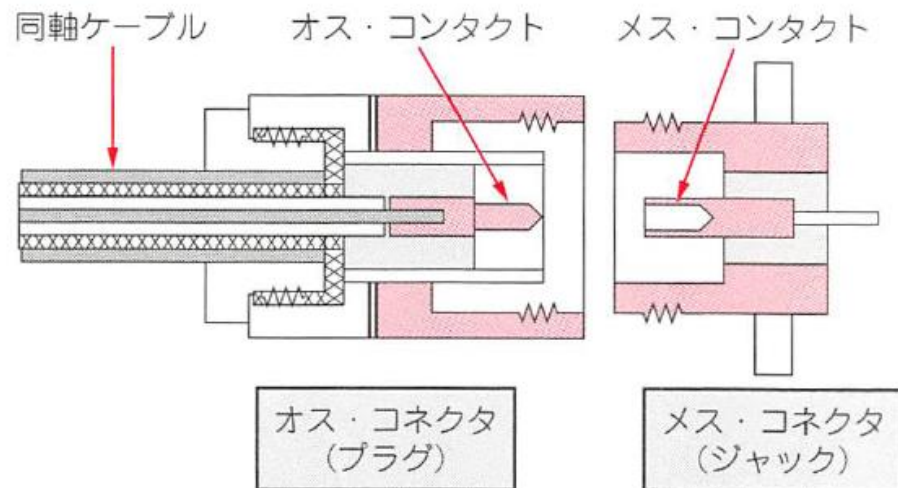


代表的な同軸コネクタの最高使用周波数例

形式	外部導体内径	最高使用周波数
BNC	約 7 mm	2 ~ 4 GHz
N	約 7 mm	10 ~ 18 GHz
7 mm	7 mm	~ 18 GHz
SMA	4.15 mm	18 GHz
3.5 mm	3.5 mm	26.5 GHz
K	2.92 mm	40 GHz
2.4 mm	2.4 mm	50 GHz
V	1.85 mm	65 GHz
W	1.1 mm	110 GHz
1.0 mm	1.0 mm	110 GHz

Coaxial connectors

写真2 N型コネクタ

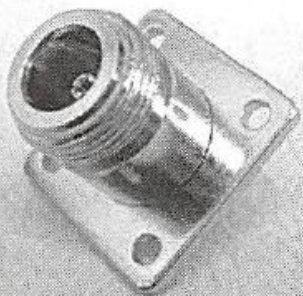

(a) フランジ付きジャック




(b) プラグ




(c) プラグ [(b)を分解]


写真3 BNC型コネクタ

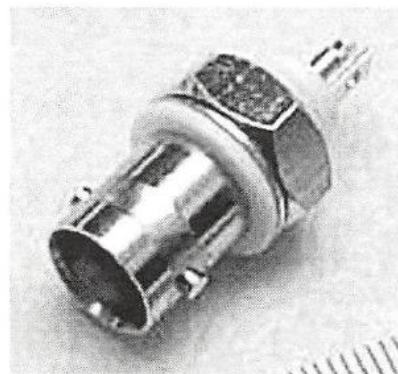

(a) 絶縁型ジャック
(高周波に向かない)

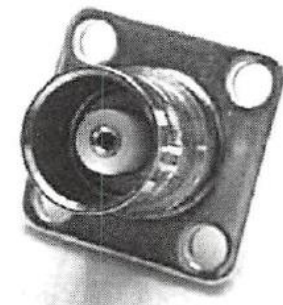


(b) フランジ付きジャック

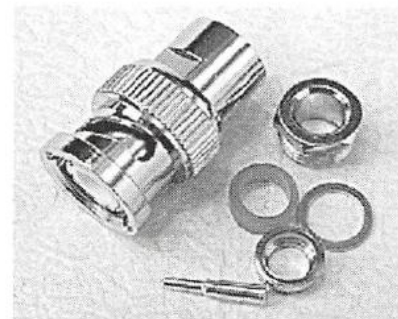

(c) プラグ

Coaxial connectors 2

SMA-type

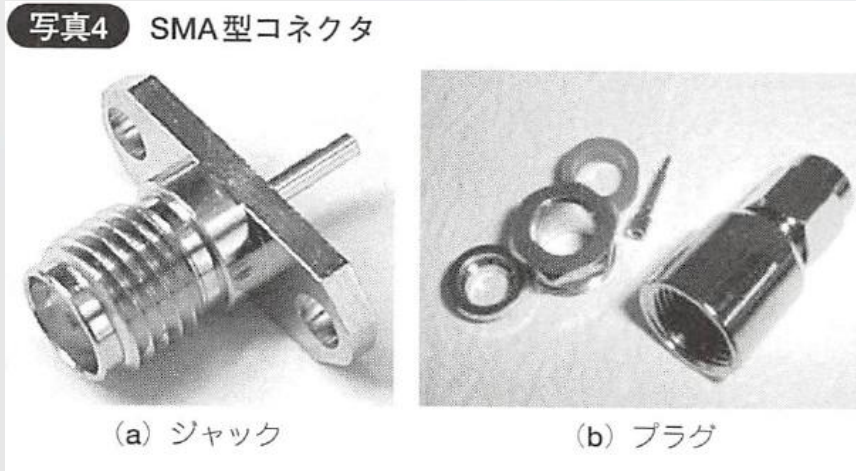


jack

plug

K-type

写真6 K型コネクタ

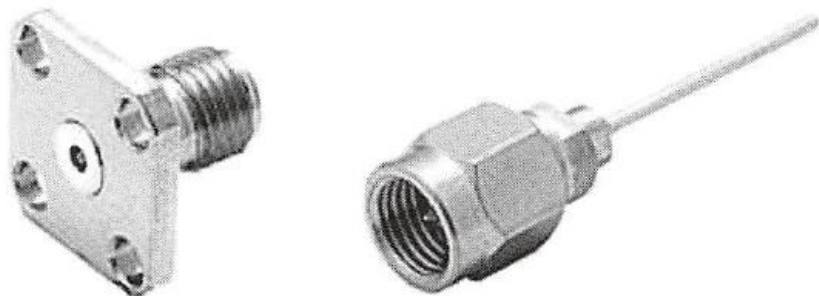


(a) ジャック

(b) プラグ

V-type

写真7 V型コネクタ

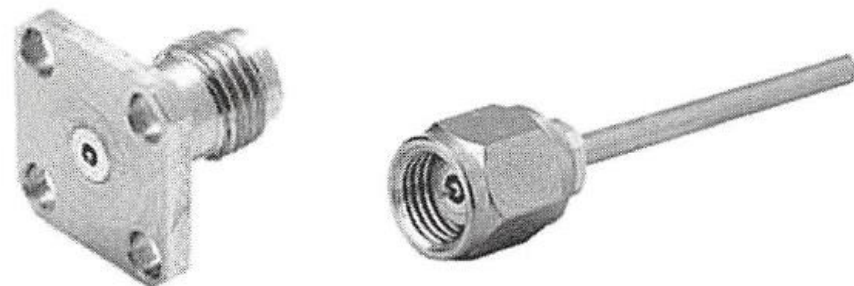

(a) ジャック

(b) プラグ

LEMO cables and connectors

MFBモデル



MSBモデル




<http://www.lemo.com/>


High-energy physics experiment,
etc.



Lecher line

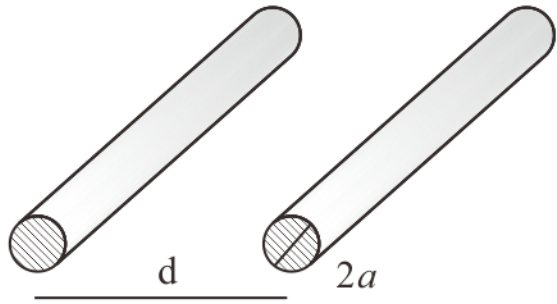

(a)

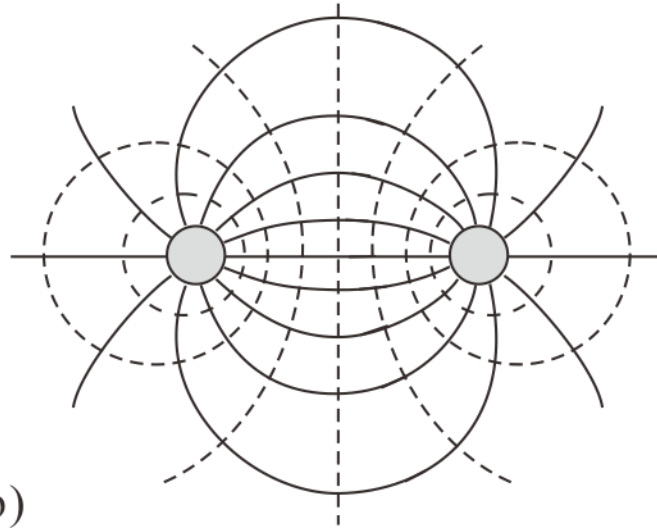


(b)




(c)

$$\phi_1 = -\phi_2 = \frac{J\sqrt{\mu}}{2\pi} \log \frac{d}{a} \quad Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{1}{\pi} \log \frac{d}{a}$$


Micro strip line

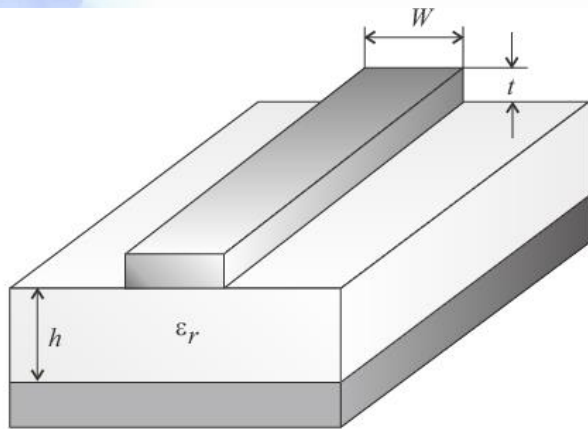

(a)

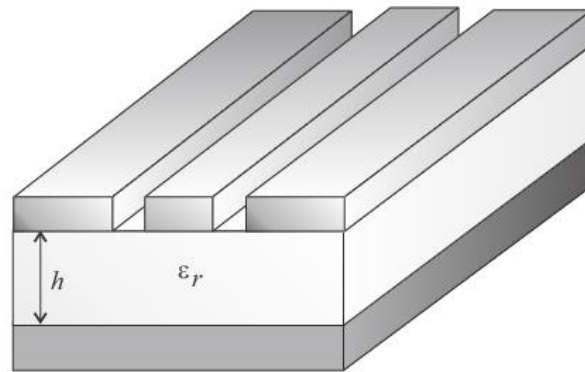

(b)

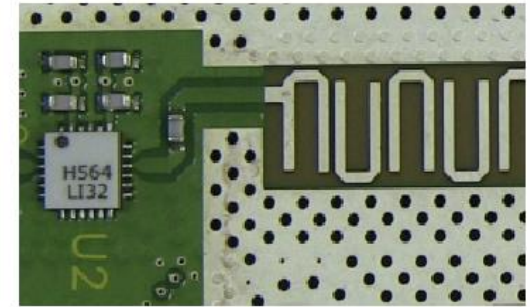

(c)


Wide ($W/h > 3.3$) strip

$$Z(W, h, \epsilon_r) = \frac{Z_{F0}}{2\sqrt{\epsilon_r}} \left\{ \frac{W}{2h} + \frac{1}{\pi} \log 4 + \frac{\epsilon_r + 1}{2\pi\epsilon_r} \log \left[\frac{\pi e}{2} \left(\frac{W}{2h} + 0.94 \right) \right] \frac{\epsilon_r - 1}{2\pi\epsilon_r^2} \log \frac{e\pi^2}{16} \right\}^{-1}$$

Narrow ($W/h < 3.3$) strip

$$Z(W, h, \epsilon_r) = \frac{Z_{F0}}{\pi\sqrt{2(\epsilon_r + 1)}} \left\{ \log \left[\frac{4h}{W} + \sqrt{\left(\frac{4h}{W} \right)^2 + 2} \right] - \frac{1}{2} \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(\log \frac{\pi}{2} + \frac{1}{\epsilon_r} \log \frac{4}{\pi} \right) \right\}$$

Connection and termination

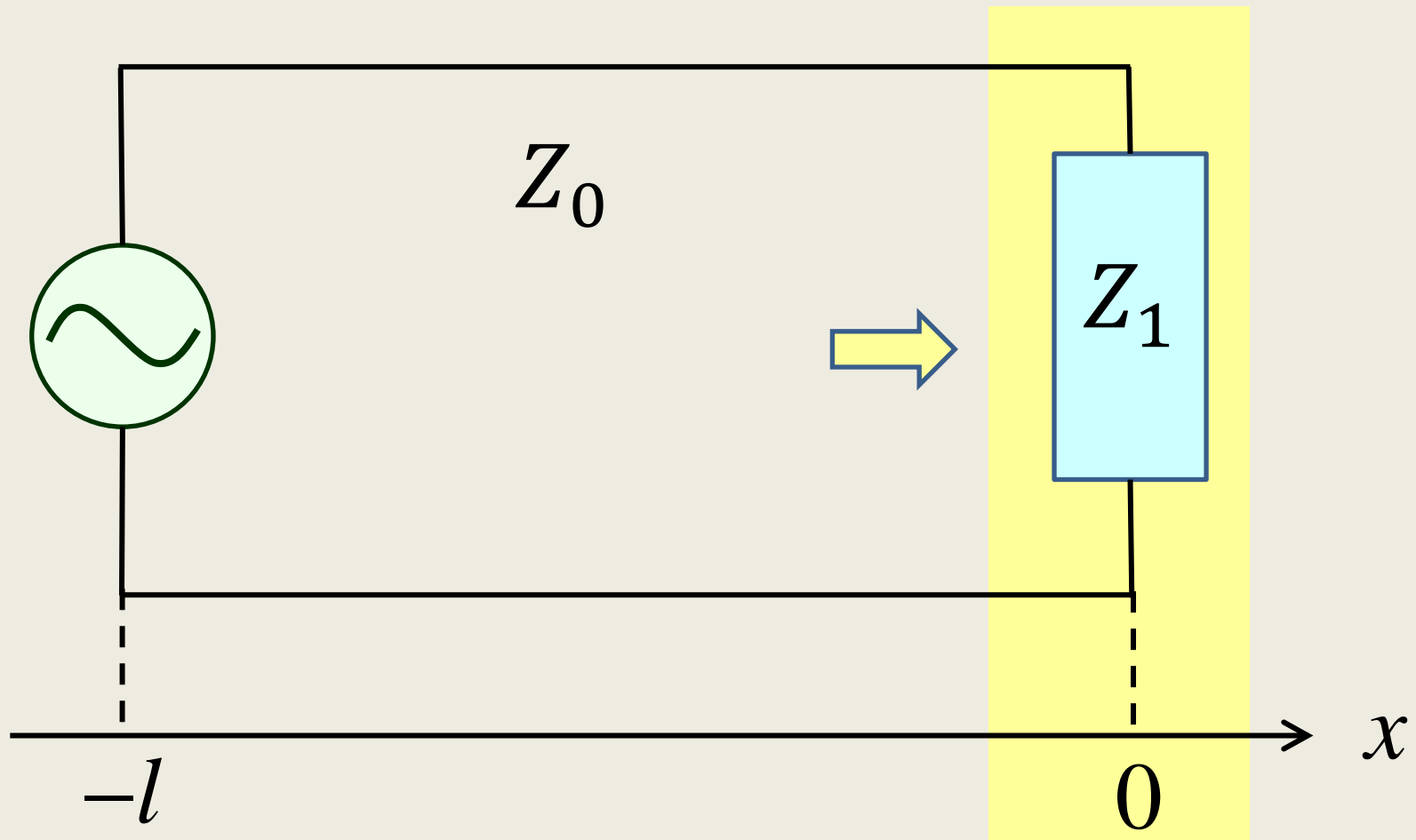

Connection and termination

$$\text{At } x = 0: \begin{cases} J = J_+ + J_- & \text{(definition right positive)} \\ \text{progressive} & \text{retrograde} \\ V = V_+ + V_- = Z_0(J_+ - J_-) \end{cases}$$

$$Z_1 = \frac{V}{J} = \frac{J_+ - J_-}{J_+ + J_-} Z_0$$

$$\text{Reflection coefficient: } r = \frac{V_-}{V_+} = -\frac{J_-}{J_+} = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$Z_1 = Z_0$: no reflection, i.e., **impedance matching**

$Z_1 = +\infty$ (open circuit end) : $r = 1$, i.e., **free end**

$Z_1 = 0$ (short circuit end) : $r = -1$, i.e., **fixed end**

Connection and termination

Finite reflection \rightarrow Standing wave

$$\text{Voltage-Standing Wave Ratio (VSWR):} = \frac{1 + |r|}{1 - |r|}$$

At $x = -l$

$$\left. \begin{aligned} V &= V_{+0} \exp(\kappa l) + V_{-0} \exp(-\kappa l) = [J_{+0} \exp(\kappa l) - J_{-0} \exp(-\kappa l)] Z_0 \\ J &= J_{+0} \exp(\kappa l) + J_{-0} \exp(-\kappa l) \end{aligned} \right\}$$

$$Z_l = \frac{V}{J} = \frac{J_{+0} e^{\kappa l} - J_{-0} e^{-\kappa l}}{J_{+0} e^{\kappa l} + J_{-0} e^{-\kappa l}} Z_0$$

Reflection coefficient:

$$r_l = \frac{V_-}{V_+} = \frac{V_{-0} e^{-\kappa l}}{V_{+0} e^{\kappa l}} = r \exp(-2\kappa l)$$


SWR measurement

SWR Meters:

Desktop types




Cross-meter

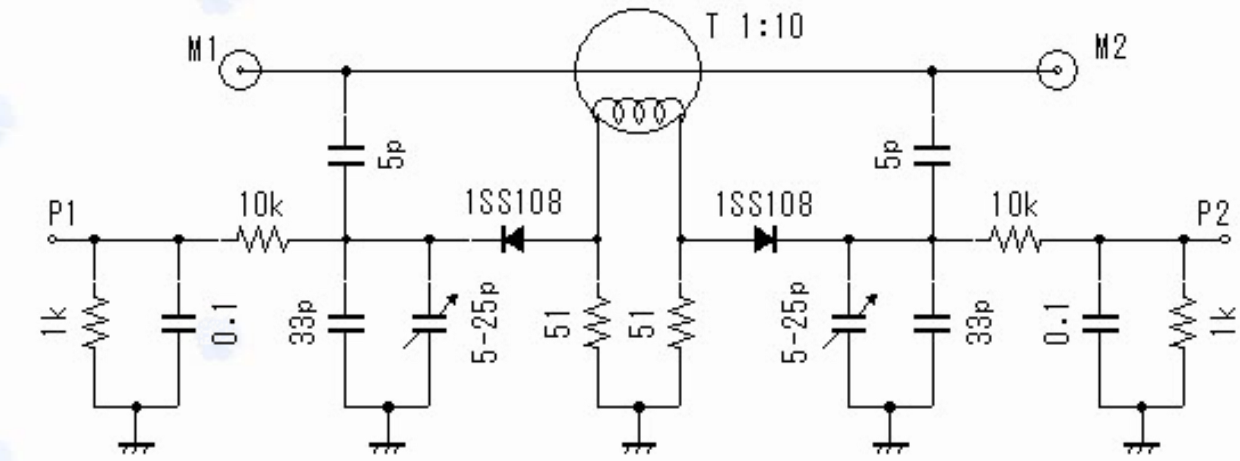

Handy type

Connection and termination

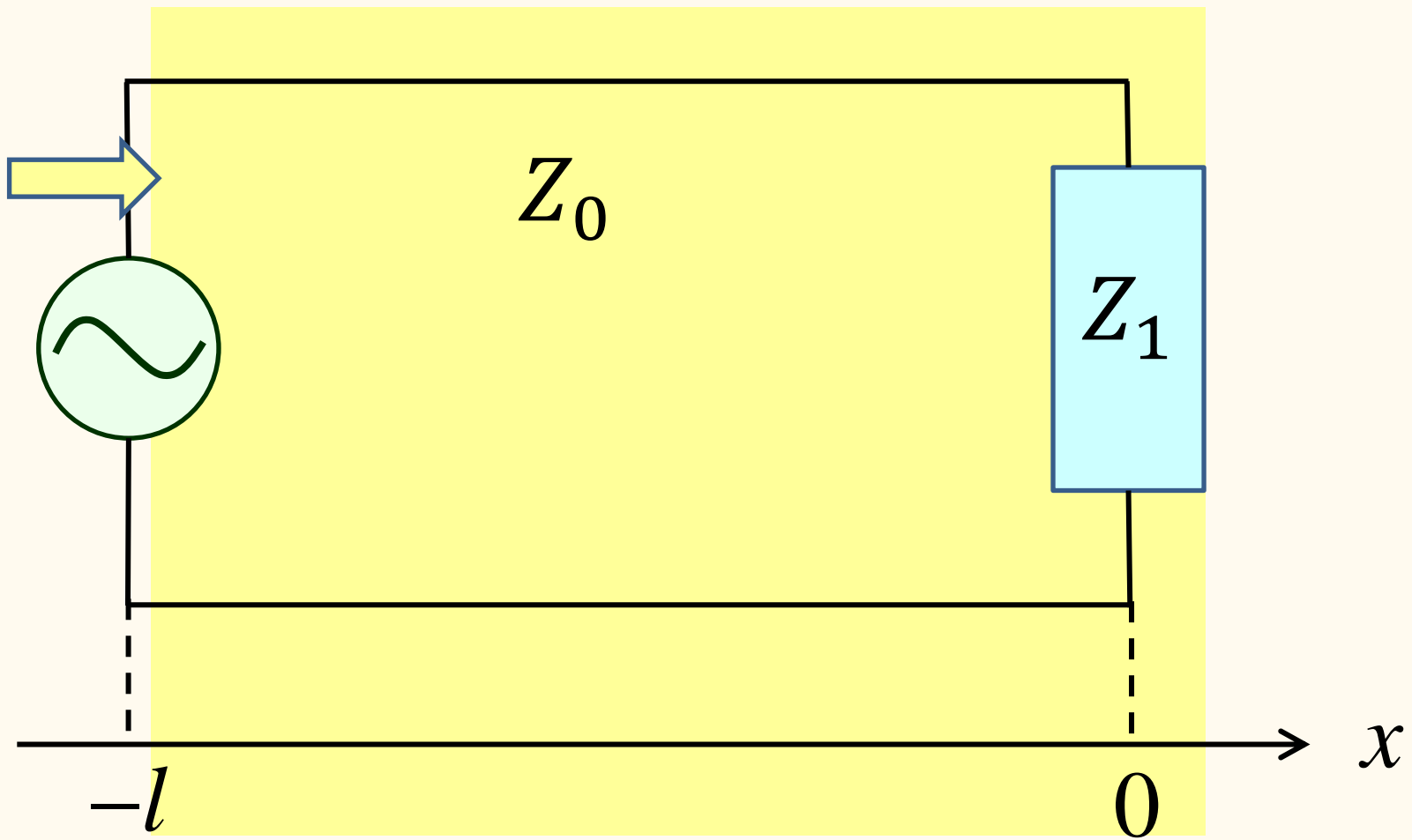

Connection and termination

Transmission line connection.

Characteristic impedance Z_0, Z_0'

At the connection point, only the local relation between V and J affects the reflection coefficient.

The local impedance from the left hand side is Z_0' .

$$r = \frac{Z_0' - Z_0}{Z_0' + Z_0}$$