
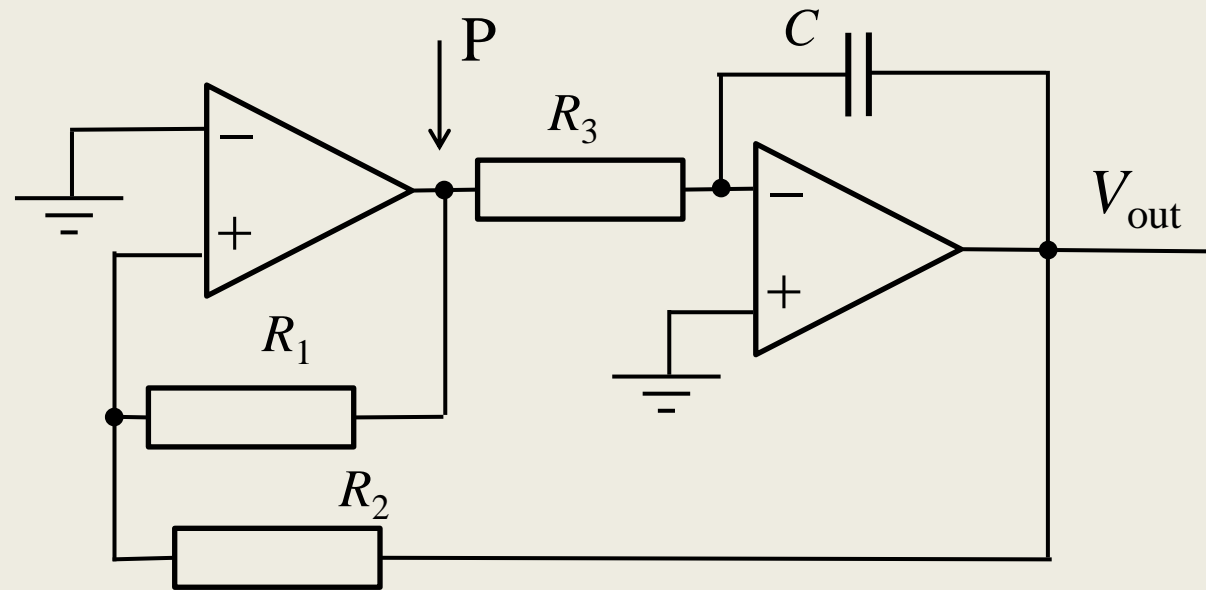


# Exercise C-1

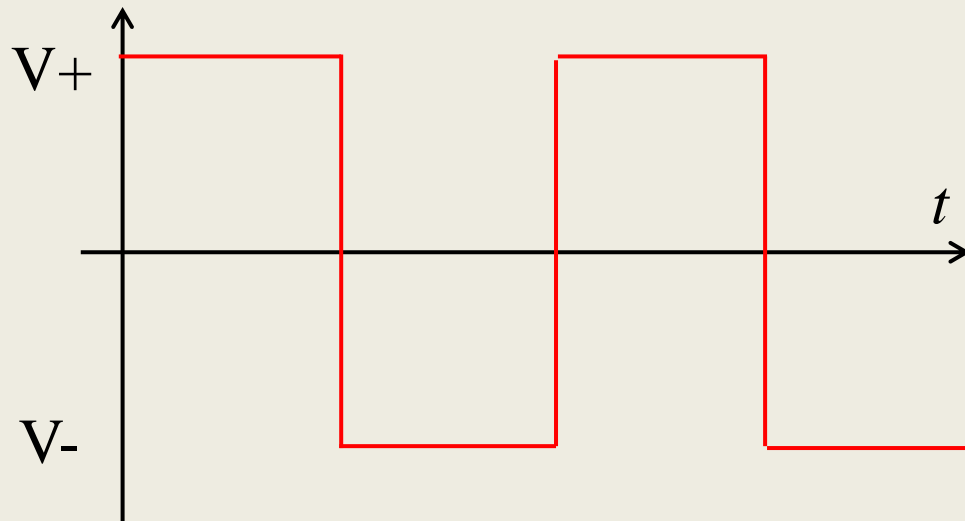


In the circuit shown in the left, at point P, a waveform in the lower panel was observed. Here  $V_+$  and  $V_-$  are power source voltages for + and - respectively.

Draw a rough sketch of the waveform for  $V_{out}$ .



“Rough sketch” should contain the levels and the timing of folding points. Write a short comment why  $V_{out}$  should be in such a form.

## Exercise C-2

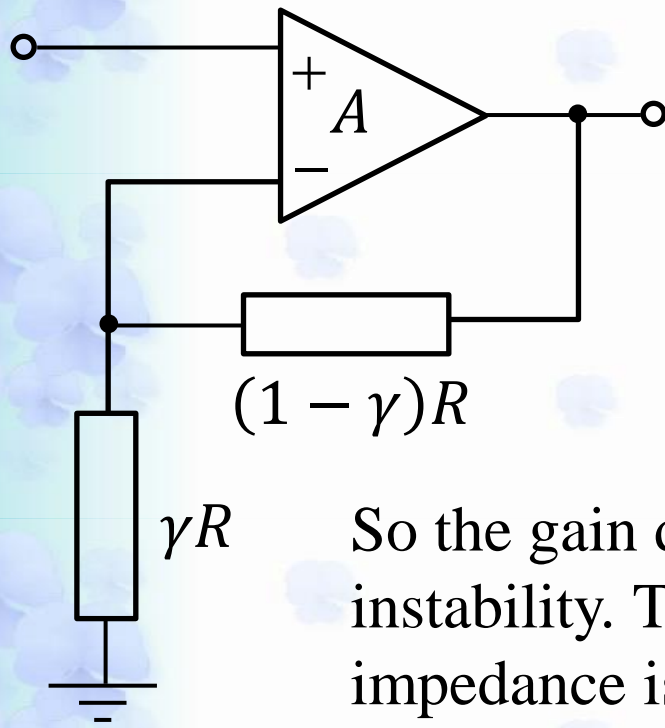

Consider a differential amplifier with the open loop gain

$$A(s) = \frac{A_0\omega_1\omega_2}{s(s + \omega_1)(s + \omega_2)}.$$

So the gain diverges with  $s \rightarrow 0$  but here we ignore this instability. The input impedance is  $\infty$ , and the output impedance is 0.


It is now placed in a circuit with a feedback shown in the left.

Obtain the stability condition for  $\gamma$ .

(hint) Apply the Hurwitz criterion for zeros of even and odd parts of the denominator.

Or just calculate  $H_2$ .

# Exercise C-3

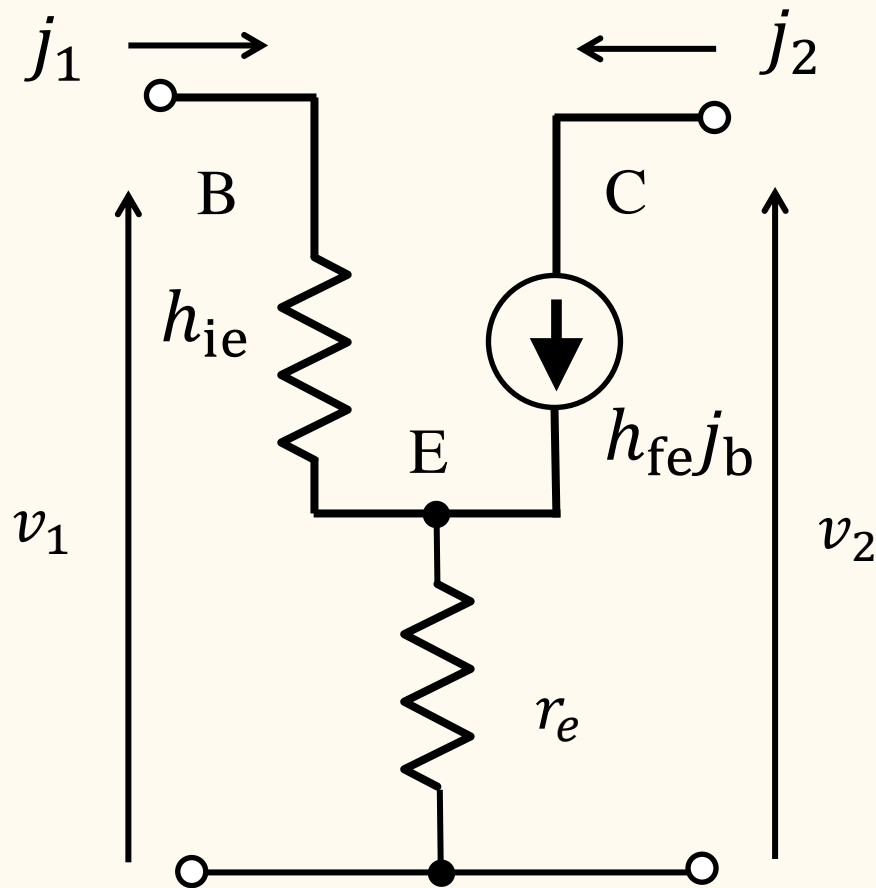

Let us view a bipolar transistor plus an emitter resistance as a four terminal circuit as shown in the left figure.

Obtain the Y (admittance) matrix defined below for this circuit.

Calculate each element in the Y matrix for  $r_e = 25\Omega$ ,  $h_{ie} = 500\Omega$ ,  $h_{fe} = 200$

$$\begin{pmatrix} j_1 \\ j_2 \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix}$$