

Electric Circuit for Physicists

電子回路論 第9回

東京大学理学部・理学系研究科
物性研究所
勝本信吾


Shingo Katsumoto

Review: Distributed constant circuit concept

1. In what case we need to consider distributed constant circuits?

Characteristic sizes of devices \gtrsim wavelength of electromagnetic signal

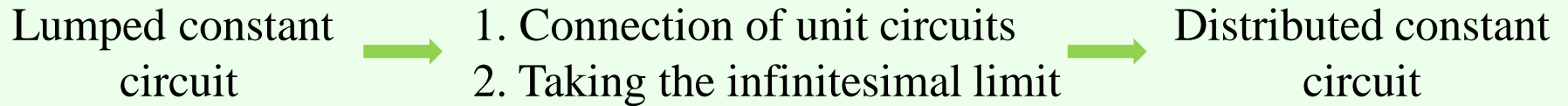2. A typical scheme to make the shift for distributed circuit



3. Distributed constant circuits : transmission lines

Coaxial cables, Lecher lines, micro-strip lines

Characteristic impedance

Transmission line: Series of two-terminal pair circuits

Width $\rightarrow 0$, Number $\rightarrow \infty$

$$dV = -JZ dx, \quad dJ = -VY dx$$

Z : Impedance per unit length, Y : Admittance per unit length

$$\frac{d^2 J}{dx^2} = YZJ, \quad \frac{d^2 V}{dx^2} = YZV \quad \text{Telegraphic equation}$$

$$\kappa \equiv \sqrt{YZ} \quad \begin{cases} J(x, t)_{\mp} = J_{\mp}(0, t) \exp(\pm \kappa x) \\ V_{\mp}(x, t) = V_{\mp}(0, t) \exp(\pm \kappa x) \end{cases}$$

-: Progressive, +: Retrograde

$$\frac{V_{\pm}}{J_{\pm}} = \mp \frac{Z}{\kappa} = \mp \sqrt{\frac{Z}{Y}} \equiv \mp Z_0 \quad \text{Characteristic impedance}$$

Pure reactance transmission line

Pure reactance $Y = i\omega C$, $Z = i\omega L$

$$\kappa = \sqrt{-\omega^2 LC} = i \frac{\omega}{\omega_0}, \quad \omega_0 \equiv \frac{1}{\sqrt{LC}}$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad \text{Characteristic impedance}$$

For coaxial cable:

From Maxwell equation $Z_0 = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \log \frac{b}{a}$

cf. Characteristic impedance of vacuum

$$Z_0 = \sqrt{\frac{\mu_0}{\epsilon_0}} \approx 376\Omega$$

Connection and termination

$$\text{At } x = 0: \begin{cases} J = J_+ + J_- & \text{(definition right positive)} \\ \text{progressive} & \text{retrograde} \\ V = V_+ + V_- = Z_0(J_+ - J_-) \end{cases}$$

$$Z_1 = \frac{V}{J} = \frac{J_+ - J_-}{J_+ + J_-} Z_0$$

$$\text{Reflection coefficient: } r = \frac{V_-}{V_+} = -\frac{J_-}{J_+} = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$Z_1 = Z_0$: no reflection, i.e., **impedance matching**

$Z_1 = +\infty$ (open circuit end) : $r = 1$, i.e., **free end**

$Z_1 = 0$ (short circuit end) : $r = -1$, i.e., **fixed end**

Connection and termination

Finite reflection \rightarrow Standing wave

$$\text{Voltage-Standing Wave Ratio (VSWR):} = \frac{1 + |r|}{1 - |r|}$$

At $x = -l$

$$\left. \begin{aligned} V &= V_{+0} \exp(\kappa l) + V_{-0} \exp(-\kappa l) = [J_{+0} \exp(\kappa l) - J_{-0} \exp(-\kappa l)] Z_0 \\ J &= J_{+0} \exp(\kappa l) + J_{-0} \exp(-\kappa l) \end{aligned} \right\}$$

$$Z_l = \frac{V}{J} = \frac{J_{+0} e^{\kappa l} - J_{-0} e^{-\kappa l}}{J_{+0} e^{\kappa l} + J_{-0} e^{-\kappa l}} Z_0$$

Reflection coefficient:

$$r_l = \frac{V_-}{V_+} = \frac{V_{-0} e^{-\kappa l}}{V_{+0} e^{\kappa l}} = r \exp(-2\kappa l)$$

Exercise 4-3

$l=1\text{km}$ の伝送線路がある。終端側を短絡したところ、電源側から測定したインピダンスは $0.6i \Omega$ であった。一方、終端側を開放して電源側からアドミタンスを測定すると $4 \times 10^{-6}i \text{ S}$ であった。
この伝送線路の特性インピダンスを求めよ。

Consider a transmission line with the length $l = 1\text{km}$. First we short-circuited the end and measured the impedance from the signal source and obtained $0.6i \Omega$. Next we opened the end and measured the admittance from the signal source and obtained $4 \times 10^{-6}i \text{ S}$.

What is the characteristic impedance of the transmission line?

Connection and termination

Transmission line connection.

Characteristic impedance Z_0, Z_0'

At the connection point, only the local relation between V and J affects the reflection coefficient.

The local impedance from the left hand side is Z_0' .

$$r = \frac{Z_0' - Z_0}{Z_0' + Z_0}$$

5.2.3 Smith chart, Immittance chart

End impedance Z_1 : Normalized end impedance $Z_n \equiv Z_1/Z_0$

$$Z_n = x + iy, \quad r = u + iw \quad (x, y, u, w \in \mathbb{R})$$

$$u + iw = r = \frac{Z_n - 1}{Z_n + 1} = \frac{(x - 1) + iy}{(x + 1) + iy}$$

$$\left. \begin{aligned} x - 1 &= (x + 1)u - yw \\ y &= yu + w(x + 1) \end{aligned} \right\}$$

$$x: \text{ constant} \rightarrow \left(u - \frac{x}{x + 1}\right)^2 + w^2 = \frac{1}{(x + 1)^2} \quad \text{constant resistance circle}$$


$$y: \text{ constant} \rightarrow (u - 1)^2 + \left(w - \frac{1}{y}\right)^2 = \frac{1}{y^2} \quad \text{constant reactance circle}$$

5.3 S matrix (S parameters)

How to treat multipoint (crossing point) systematically?

Transmission lines: wave propagating modes \rightarrow Channels

$$\mathbf{b} = \begin{pmatrix} b_1 \\ \vdots \\ b_i \\ \vdots \\ b_n \end{pmatrix} = \begin{pmatrix} S_{11} & \cdots & S_{1i} & \cdots & S_{1n} \\ \vdots & \ddots & & & \vdots \\ S_{i1} & & S_{ii} & & S_{in} \\ \vdots & & & \ddots & \vdots \\ S_{n1} & \cdots & S_{ni} & \cdots & S_{nn} \end{pmatrix} \begin{pmatrix} a_1 \\ \vdots \\ a_i \\ \vdots \\ a_n \end{pmatrix} = \boxed{\mathbf{S}} \mathbf{a}$$

 S matrix

Reciprocity $S_{ij} = S_{ji}$

Unitarity $\sum_j S_{ji} S_{jk}^* = \delta_{ik}$ In case, no dissipation,
no amplification.

Two-terminal pair S matrix $\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix}$

5.3 S-matrix (S-parameters)

Application to electric transmission lines

What is conserved in the propagation with no dissipation? Energy

$$\begin{cases} a_n = \frac{V_{n+}}{\sqrt{Z_{0n}}} = J_{n+} \sqrt{Z_{0n}}, & \text{Incident power wave} \\ b_n = \frac{V_{n-}}{\sqrt{Z_{0n}}} = J_{n-} \sqrt{Z_{0n}} & \text{Reflected (transmitted) power wave} \end{cases}$$

(assumption: common wave velocity
→ Z_0 common for channels)

Simplest case: series impedance Z_S

Terminate 2 with $Z_0 \rightarrow a_2 = 0$

$$S_{11} = \frac{V_{1-}}{V_{1+}} = \frac{V_1 - Z_0 J_1}{V_1 + Z_0 J_1} = \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{(Z_S + Z_0) - Z_0}{(Z_S + Z_0) + Z_0} = \frac{Z_S}{Z_S + 2Z_0}$$

$$S_{21} = \frac{V_{2-}}{V_{1+}} = \frac{V_2}{E_1/2} = \frac{2V_2}{V_1 + Z_0 J_1} = \frac{2Z_0 J_1}{(Z_S + Z_0) J_1 + Z_0 J_1} = \frac{2Z_0}{Z_S + 2Z_0}$$

5.3 S-matrix (S-parameters)

Terminate 1 with $Z_0 \rightarrow a_1 = 0$ (should be symmetric)

$$S_{12} = \frac{2V_1}{V_2 + Z_0 J_2} = \frac{2Z_0 J_2}{(Z_S + Z_0)J_2 + Z_0 J_2} = \frac{2Z_0}{Z_S + 2Z_0}$$

$$S_{22} = \frac{Z_S}{Z_S + 2Z_0}$$

Generally

$$S = \frac{1}{\det Z} \times \begin{pmatrix} (Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21} & 2Z_0Z_{12} \\ 2Z_0Z_{21} & (Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21} \end{pmatrix}$$

Cascade connection of S-matrices

$$\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \mathbf{S} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix} = \begin{pmatrix} r_L & t_R \\ t_L & r_R \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix}$$

$r_{L,R}, t_{L,R}$: complex reflection, transmission coefficients satisfying

$$T_{L,R} = |t_{L,R}|^2 = 1 - R_{L,R} = 1 - |r_{L,R}|^2$$

$$\begin{aligned} \mathbf{S}_{AB} &= \begin{pmatrix} r_L^{AB} & t_R^{AB} \\ t_L^{AB} & r_R^{AB} \end{pmatrix} \\ &= \begin{pmatrix} r_L^A + t_R^A r_L^B (I - r_R^A r_L^B)^{-1} t_L^A & t_R^A (I - r_L^B r_R^A)^{-1} t_R^B \\ t_L^B (I - r_R^A r_L^B)^{-1} t_L^A & r_R^B + t_L^B (I - r_R^A r_L^B)^{-1} r_R^A t_R^B \end{pmatrix} \end{aligned}$$

$$(I - r_R^A r_L^B)^{-1} = I + r_R^A r_L^B + (r_R^A r_L^B)^2 + \dots$$

Conduction channels in quantum transport



Rolf Landauer




Electron (quantum mechanical) waves also have propagating modes in solids.

→ Conduction channel

Landauer eq.:

the conductance of a single perfect quantum channel is $\frac{e^2}{h}$

AB ring S-matrix model

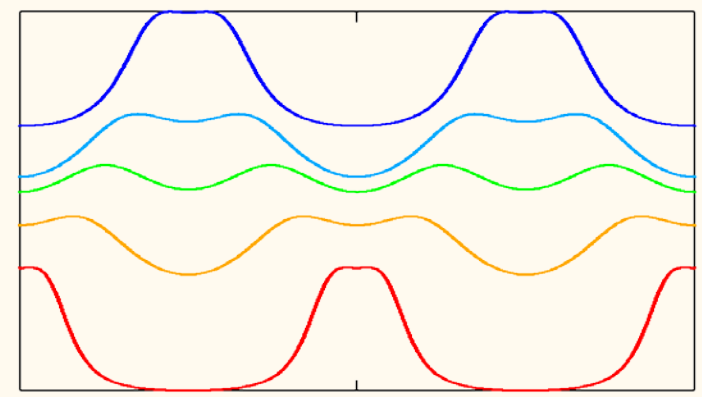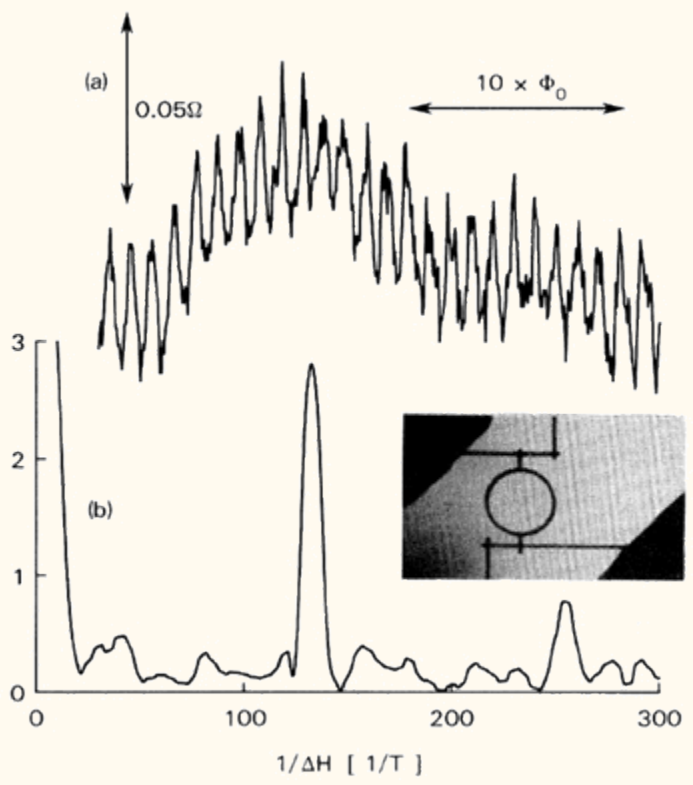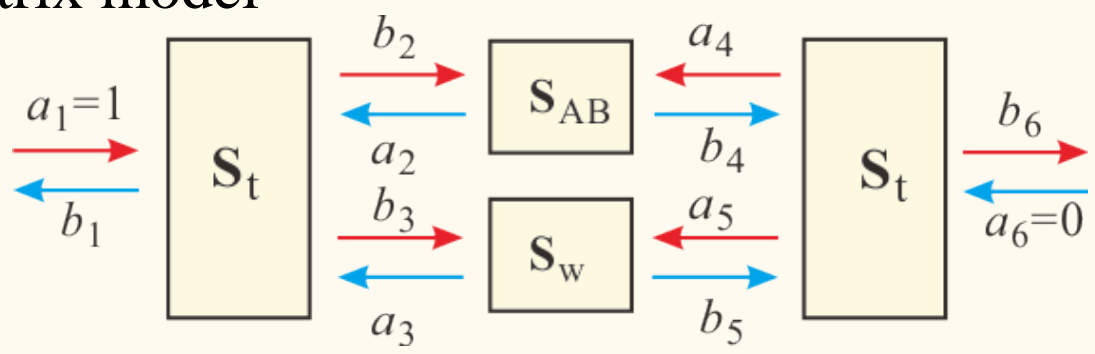


S-parameter representation of high-frequency devices

Ex) NE76084 MES FET 0.5~18GHz



S_{11}

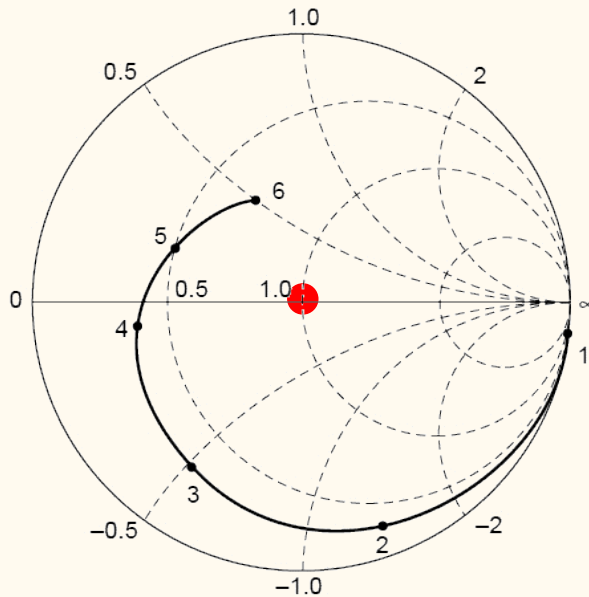

Needs impedance matching circuits

If we know Z-parameters:

From Ho-Thevenin theorem

$$Z_S = Z_{22}^i - \frac{Z_{12}^i Z_{21}^i}{50 + Z_{11}^i}, \quad Z_L = Z_{11}^o - \frac{Z_{12}^o Z_{21}^o}{50 + Z_{22}^o}$$

$\{Z_{ij}\}$: BJT (FET) Z-parameters, again Ho-Thevenin says

$$Z_l = Z_{11} - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}}, \quad Z_r = Z_{22} - \frac{Z_{12} Z_{21}}{Z_S + Z_{11}}$$

Impedance matching with S-parameters

Generally the unitarity does not hold for amplification.

$$R_{\text{in}} = S_{11} + \frac{S_{12}S_{21}R_L}{1 - S_{22}R_L} \quad R_{\text{out}} = S_{22} + \frac{S_{12}S_{21}R_S}{1 - S_{11}R_S}$$

Matching condition: $R_L = R_{\text{out}}^*$, $R_S = R_{\text{in}}^*$

Solution $R_S = \frac{B_1 \pm \sqrt{B_1^2 - 4|M|^2}}{2M}$, $R_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|N|^2}}{2N}$ with

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\det S|^2, \quad B_2 = 1 - |S_{11}|^2 + |S_{22}|^2 - |\det S|^2,$$

$$N = S_{22} - S_{11}^* \det S, \quad M = S_{11} - S_{22}^* \det S$$

maximum available power gain $G_{\text{max}} = \left| \frac{S_{21}}{S_{12}} \right| (K - \sqrt{K^2 - 1})$

$$K = \frac{1 + |\det S|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{12}S_{21}|} \quad \text{stability factor}$$

Impedance matching designer

<http://home.sandiego.edu/~ekim/e194rfs01/jwmatcher/matcher2.html>

http://leleivre.com/rf_lcmatch.html

5.4 Giving mass to LC transmission line

Constant finite mass: $E = \hbar\omega \propto k^2$

(Schrodinger eq.: Parabolic partial differential equation)

Coupling between linear dispersions: mass mechanism *cf.* Higgs

C : capacitance per unit length

L : inductance per inverse unit length

K : inductance per unit length

$$\frac{1}{\sqrt{LC}} = \omega_0 \text{ unchanged with } dx \rightarrow 0$$

$$Z = i\omega K, \quad Y = \frac{1 - (\omega/\omega_0)^2}{i\omega L}$$

$$ik = \kappa = \sqrt{YZ} = i\sqrt{\frac{K}{L} \left[\left(\frac{\omega}{\omega_0}\right)^2 - 1 \right]}$$

$$\eta^2 \equiv \frac{K}{L}$$

5.4 Giving mass to LC transmission line

$$\omega \gg \omega_0 \rightarrow k \sim \eta \frac{\omega}{\omega_0} \quad \text{No dispersion}$$

$$\text{Velocity: } c^* = \frac{\omega}{k} = \frac{\omega_0}{\eta} = \frac{1}{\sqrt{KC}}$$

$$\omega \sim \omega_0 \quad \omega = \omega_0 + \delta\omega$$

$$k^2 \approx 2\eta^2 \frac{\delta\omega}{\omega_0} \quad \therefore \epsilon \equiv \hbar\delta\omega = \frac{\hbar k^2}{2(\eta^2/\omega_0)} = \frac{\hbar^2 k^2}{2m^*}$$


$$m^* \equiv \frac{\hbar\eta^2}{\omega_0}$$

$$E_0 = \hbar\omega_0 = \frac{\hbar\eta^2}{\omega_0} \cdot \left(\frac{\omega_0}{\eta}\right)^2 = m^* c^{*2}$$


References

1. 市川古都美, 市川裕一
「高周波回路設計のためのSパラメータ詳解」(CQ出版社, 2007).
2. 北野正雄「量子力学の基礎」(共立出版, 2010)
3. 勝本信吾「メゾスコピック系」(朝倉書店, 2002),
「半導体量子輸送物性」(培風館, 2014).
4. 勝本信吾「量子の匠」(丸善, 2014).
5. R. Collier, “Transmission Lines” (Cambridge, 2013).


Toda lattice

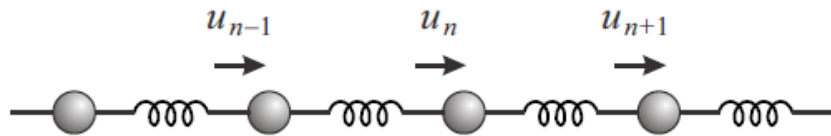

(a)

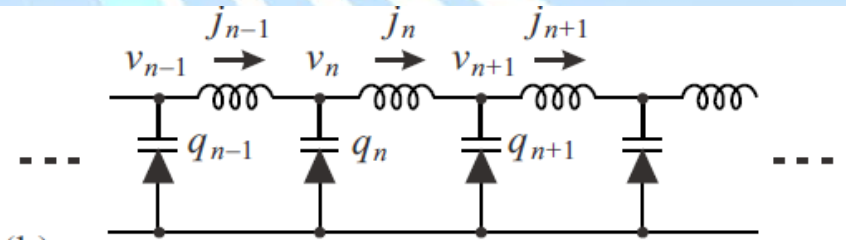

(b)

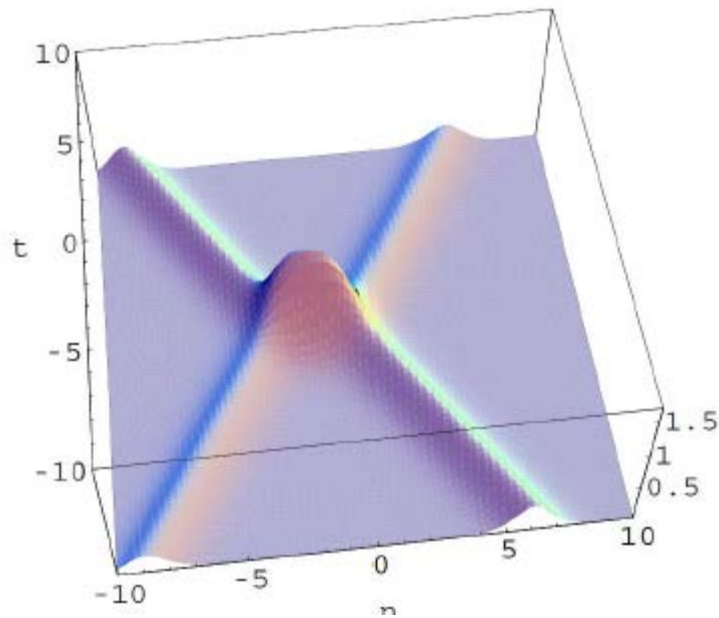

$$u_n = \frac{\tau_{n+1}\tau_{n-1}}{\tau_n^2} - 1,$$

$$\tau_n = 1 + e^{2\eta_1} + e^{2\eta_2} + A_{12}e^{2(\eta_1+\eta_2)},$$


$$\eta_i = \kappa_i n + \sigma_i \omega_i t + \delta_i, \quad \sigma_i = \pm 1, \quad \omega_i = \sinh \kappa_i,$$

$$A_{12} = \frac{ab \sinh^2(\kappa_1 - \kappa_2) - m(\sigma_1 \omega_1 - \sigma_2 \omega_2)^2}{m(\sigma_1 \omega_1 + \sigma_2 \omega_2)^2 - ab \sinh^2(\kappa_1 + \kappa_2)}$$

Vari-cap



Varicap BB505

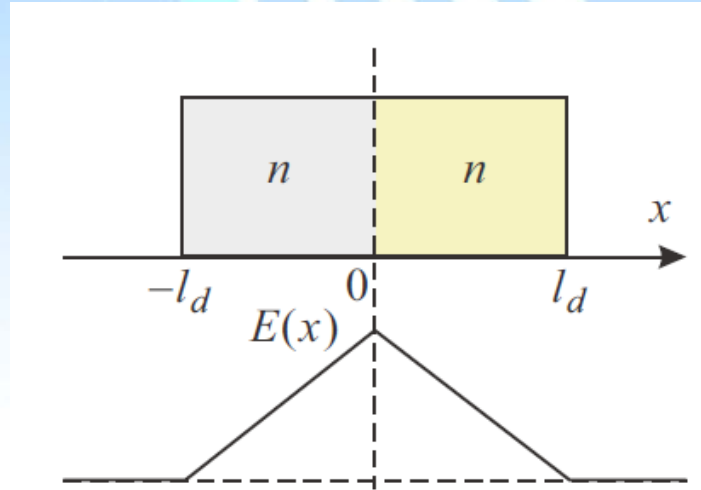


$$V_b = \frac{en}{\epsilon} \int_{-l_d}^0 2(x + l_d) dx + \frac{en}{\epsilon} \int_0^{l_d} 2(l_d - x) dx = \frac{2enl_d^2}{\epsilon}$$

$$V + V_b = \frac{2en}{\epsilon} \left(l_d + \frac{Q}{nS} \right)^2 \quad \therefore C = \frac{dQ}{dV} = \sqrt{\frac{\epsilon}{2en}} \frac{nS}{\sqrt{V + V_b}}$$

$$V + V_b = V_0 + \delta V \quad \delta V \rightarrow V$$

L-Varicap transmission line

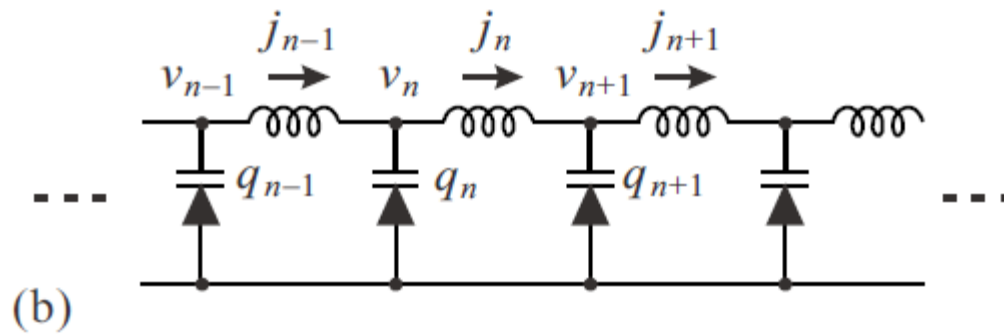

$$L \frac{dJ_n}{dt} = v_n - v_{n-1},$$

$$\frac{dq_n}{dt} = J_{n-1} - J_n,$$

$$q_n = \int_0^{v_n} C(V) dV, \quad C(V) = \frac{Q(V_0)}{F(V_0) + V - V_0}$$

$$q_n = Q(V_0) \log \left[1 + \frac{V_n}{F(V_0)} \right] + \text{const.}$$

$$\frac{d^2}{dt^2} \log \left[1 + \frac{V_n}{F(V_0)} \right] = \frac{1}{LQ(V_0)} (V_{n-1} + V_{n+1} - 2V_n)$$

Solitons in non-linear circuit




International Journal of Bifurcation and Chaos, Vol. 9, No. 4 (1999) 571-590
© World Scientific Publishing Company

CIRCUIT IMPLEMENTATIONS OF SOLITON SYSTEMS*

ANDREW C. SINGER
*Department of Electrical and Computer Engineering,
University of Illinois, Urbana, IL 61801, USA*

ALAN V. OPPENHEIM
Department of Electrical Engineering, MIT, Cambridge, MA 02139, USA

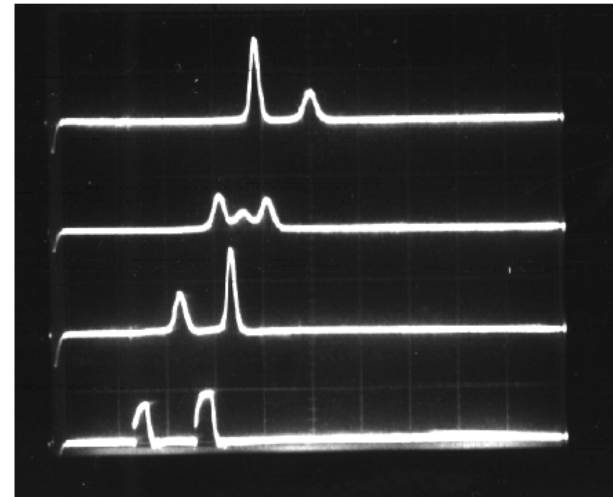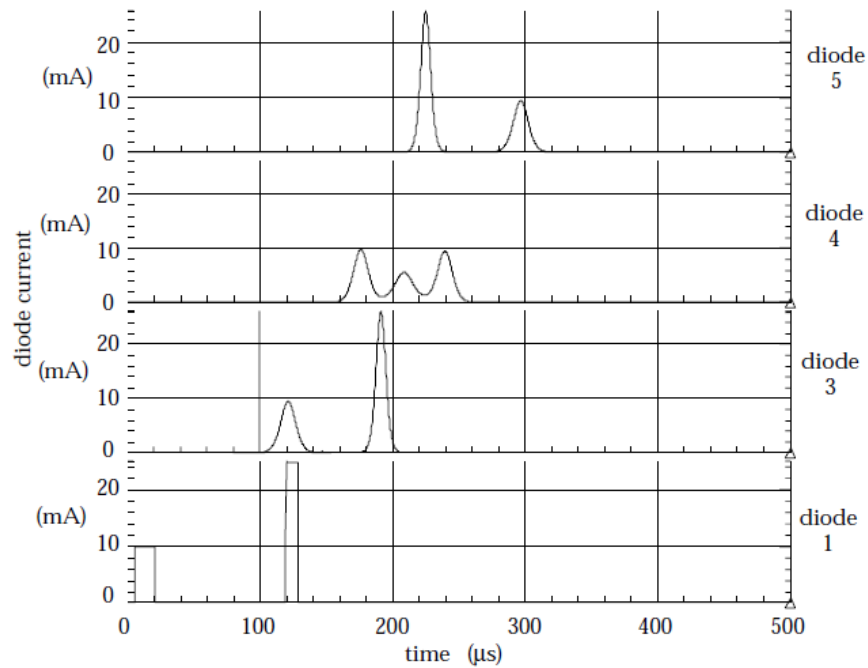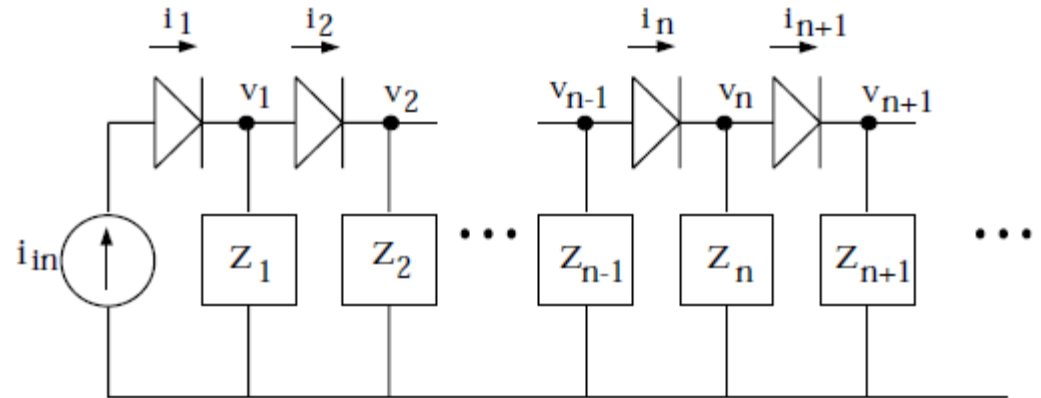Received May 27, 1998; Revised October 6, 1998



Toda lattice circuit, Soliton circuit


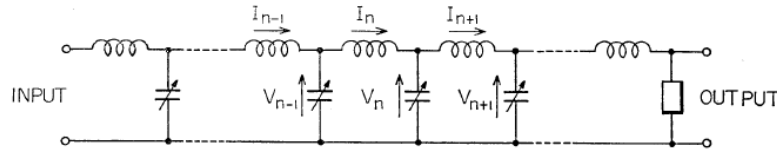


Fig. 1. A nonlinear network equivalent to a one-dimensional anharmonic lattice. The circuit element have an inductance $L=22 \mu\text{H}$ or capacitance $C(V)=27 V^{-0.48} \text{ pF}$.

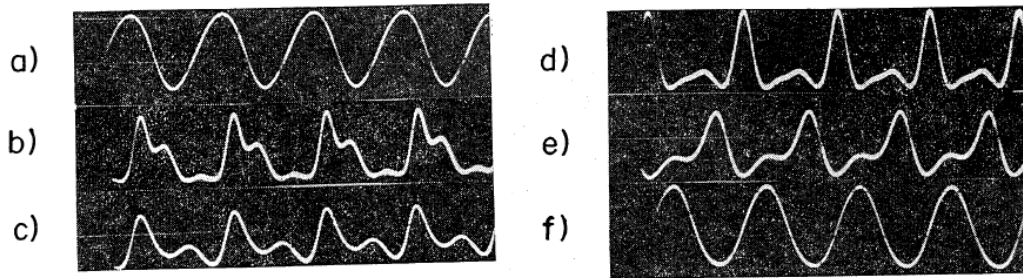

J. PHYS. SOC. JAPAN 28 (1970) 1366~1367

Studies on Lattice Solitons by Using Electrical Networks

Ryogo HIROTA and Kimio SUZUKI

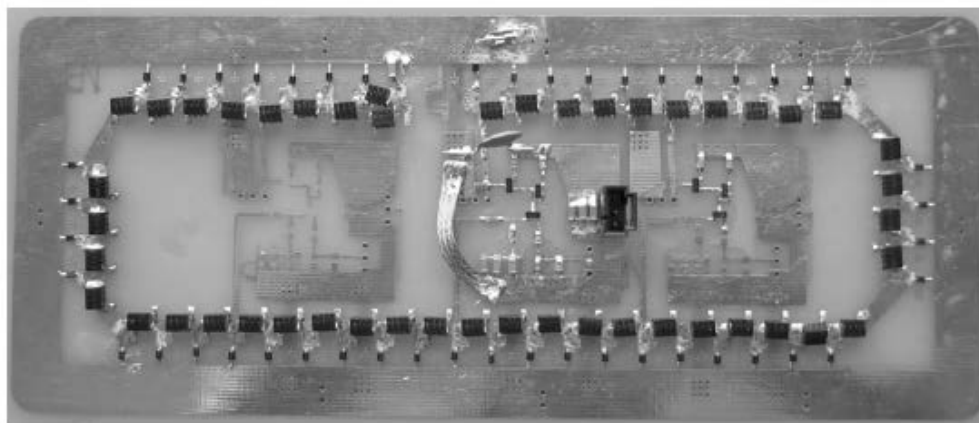


Fig. 16. Microwave soliton oscillator prototype.

