

# 電子回路論第14回

## Electric Circuits for Physicists #14

東京大学理学部・理学系研究科  
物性研究所  
勝本信吾  
Shingo Katsumoto




# Outline

- PLD, FPGA Hardware technique
- Hardware description language (HDL)
- Neural network and FPGA

# 7.8 Circuit realization with Hardware Description Language (HDL)


## PLD/FPGA with HDL

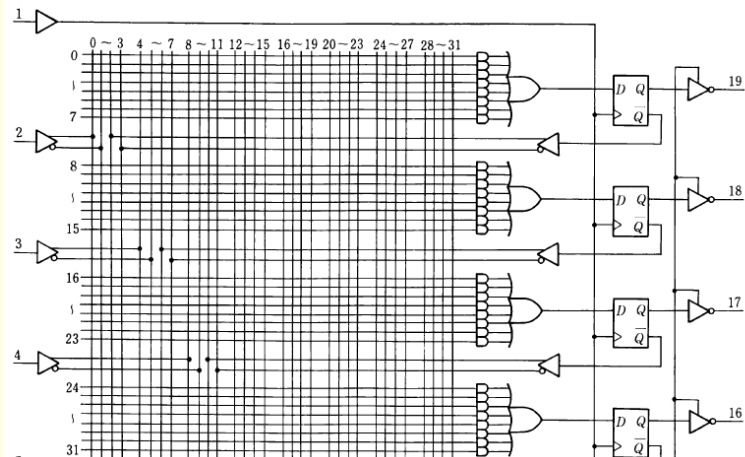Example of programmable logic device (PLD) circuit




Example of field-programmable gate array (FPGA) circuit

FPGA  $\in$  PLD

 



# Configuration of FPGA

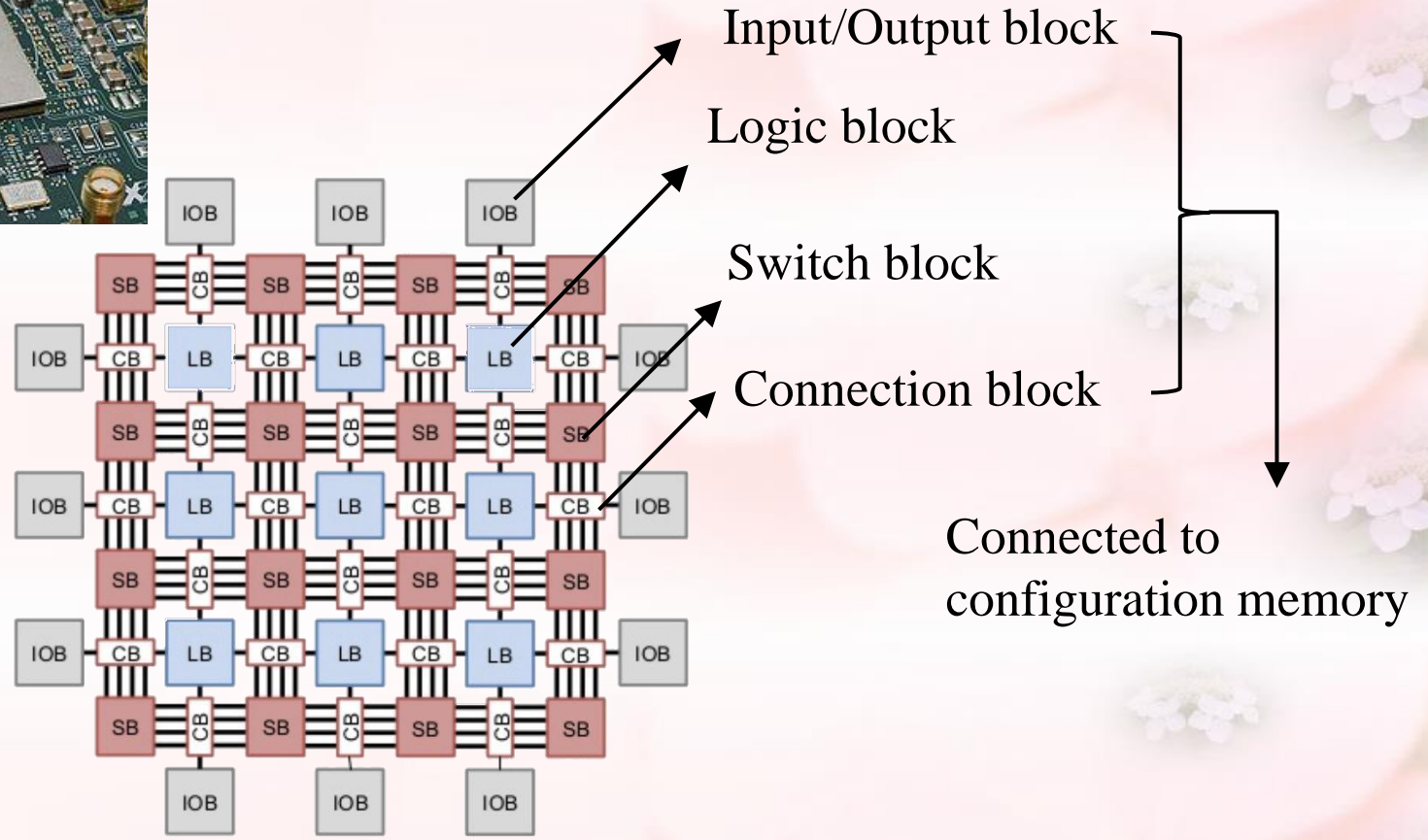
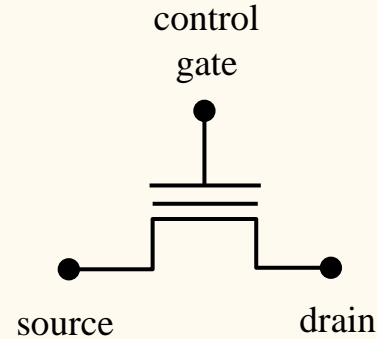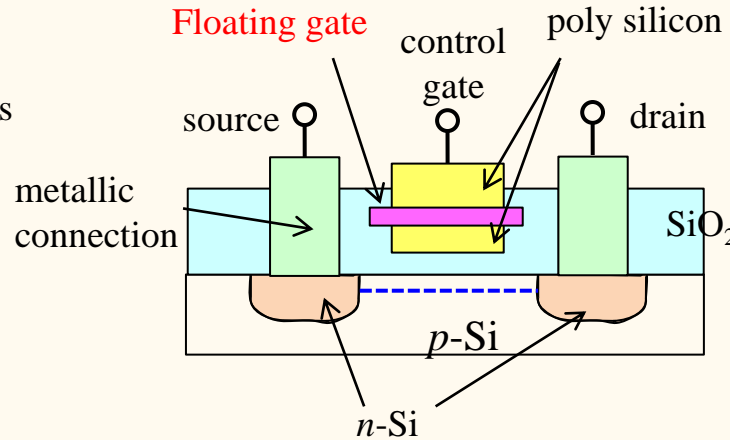
## Flush memory

One of electrically erasable programmable read-only memories (EEPROMs)

Quantum tunneling process charge up/discharge the floating gate




Fujio Masuoka
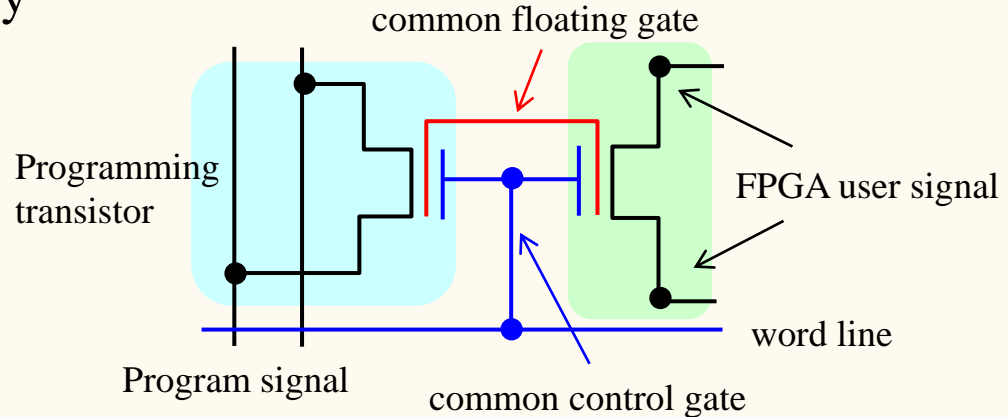
## Programmable switch with flush memory


Programming transistor SD 5 V, control gate -11 V → ON, SD 0 V, CG 16 V → OFF

- Rewritable, non-volatile, small number of device, live at power-up
- Device size is large, on-resistance is high, load capacitance is large, memory lifetime?




# Programming technology (2)

## Anitifuse

 

## Actel (c), QuickLogic (c)

 

Recently metal-metal type is dominant.

The inverse process of fusing. That is, short circuit with high voltage and current.


Fusing was also used.

- Long, stable memory life. Small device size. Small on resistance.
- Not rewritable. Program needs extra transistors. Available percentage (fidelity) is low.

 
## Static memory (SRAM type, mainstream method now)

SRAM does not need refreshing but volatile.


- Large device size, resources, large on resistance, stray capacitance
- State-of-art CMOS technology can be used



Positive feedback loop and latch.

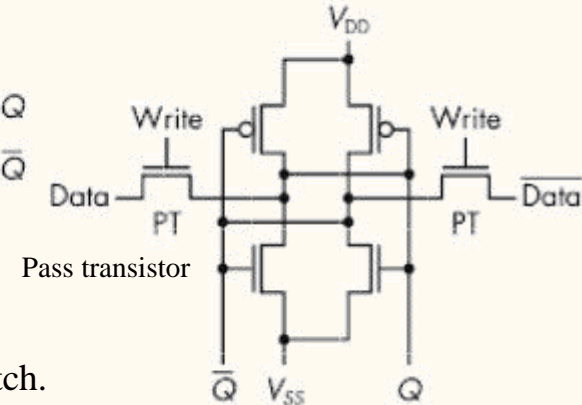
 
# Simple example of logic block configuration



## Circuit level understanding of FPGA

Let us consider a majority rule circuit. The truth table is given.

Truth table of majority rule


A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

C \ AB	00	01	11	10
0			1	
1		1	1	1

Karnaugh mapping

$$M = AB + AC + BC$$

(is not required for LUT)


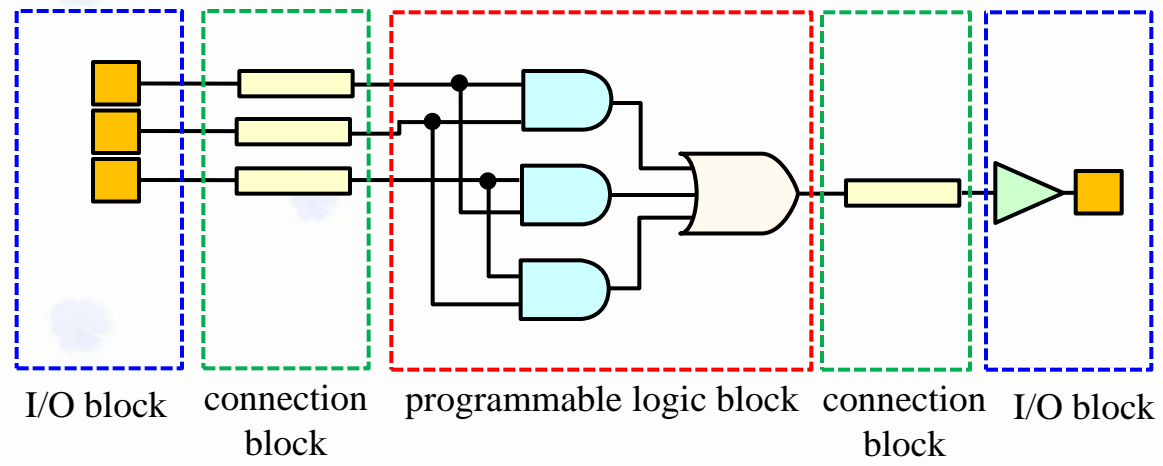


# Various ways to realize logic block


## Resource

## Majority rule implementation


Product term

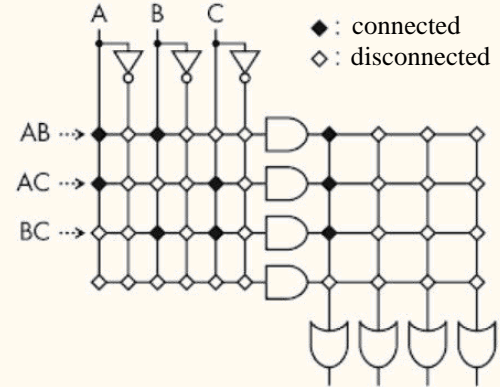 

Look up table

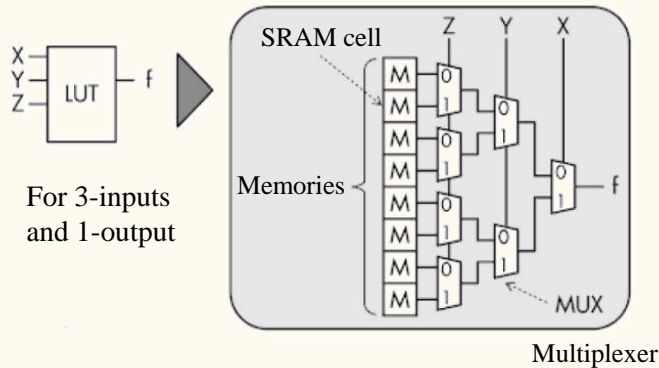

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

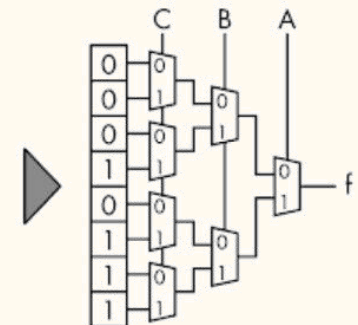





# Advance type FPGA

## Integration of DSP, FPU, etc.

(from Xilinx Zynq product brief)

### BROADCAST CAMERA APPLICATION EXAMPLE

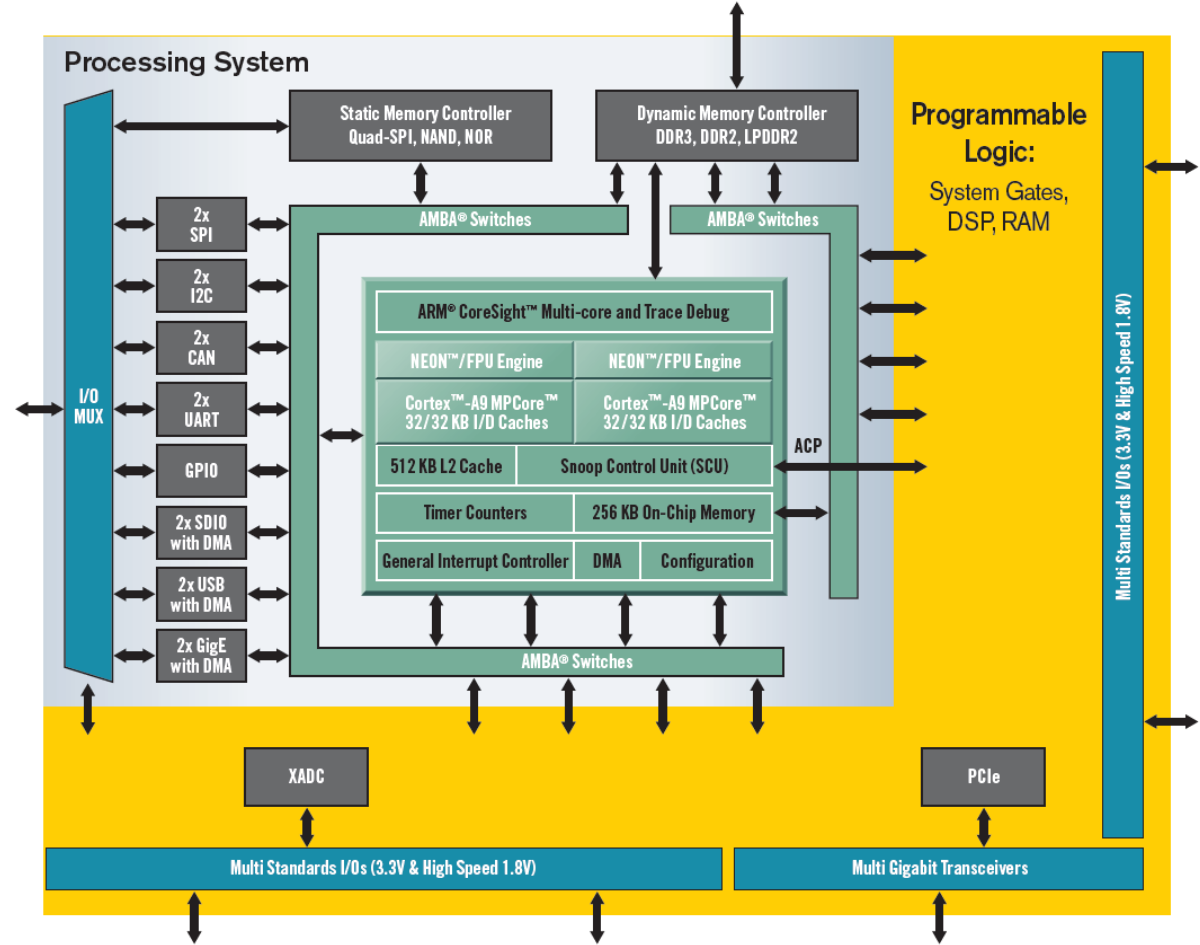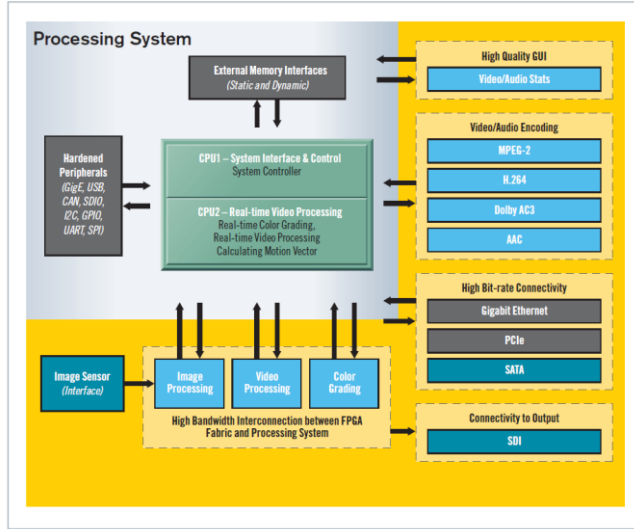


# Hardware description language (HDL)

HDL { VHDL  
Verilog HDL

```
-- Library declaration -----  
library IEEE;  
use IEEE, STD_LOGIC_1164.ALL;  
-- Entity declaration -----  
entity NAND_CIRCUIT is  
port(  
A : in std_logic;  
B : in std_logic;  
C : out std_logc  
);  
end NAND_CIRCUIT;  
-- Architecture declaration -----  
architecture RTL of NAND_CIRCUIT is  
signal ab : std_logic;  
begin  
ab <= A and B;  
C <= not ab;  
end RTL;
```

VHDL example for

 

RTL: register transfer level



Translation or High level synthesis (高位合成) or Behavioral synthesis:

System name	Cyber Work Bench	Vivado-HLS	Catapult C	Impulse C	Symphony C Compiler	C-to-Silicon Compiler
Company	<a href="#">NEC</a>	<a href="#">Xilinx</a>	Mentor Graphics	Impulse Accelerated Technologies	Synopsis	Cadence
Language	System-C/ <a href="#">ANSI-C</a>	<a href="#">C/C++</a>	<a href="#">ANSIC++</a> /System C	<a href="#">ANSI C</a>	<a href="#">C/C++</a>	System C

Behavior description with high-level languages → Synthesis of HDL codes


Not almighty. Because high-level languages generally use large memories but there are not such size of memories being close to hand in the case of FPGA.

# Neural Network (NN)

  

# Feedforward neural network or multi-layer perceptron

unit or perceptron 4-input example

 


$$u = w_1x_1 + w_2x_2 + w_3x_3 + w_4x_4 + b$$

vector:  $w$  weight  
 $b$  bias


$$z = f(u) \quad : \text{activation function (generally non-linear)}$$

double layer

 

$$u_j = \sum_{i=1}^I w_{ji}x_i + b_i, \quad z_j = f(u_j) \quad \text{or}$$
$$u = \mathbf{W}x + b, \quad z = \mathbf{f}(u)$$

 Now it is (conceptually) easy to extend to multi-layer



Many layers  
→ Deep neural network



# Learning

input  $x \rightarrow$  desired output  $d$       training data  $\{(x_1, d_1), (x_2, d_2), \dots, (x_N, d_N)\}$   
training samples

Learning: tune  $w$  to minimize distance between  $\{d_j\}$  and the network output  $\{y(x_j, w)\}$

$$E(w) = \frac{1}{2} \sum_{n=1}^N \|d_n - y(x_n, w)\|^2 \quad : \text{typical error function} \rightarrow \text{minimize}$$

Overfitting (overlearning) problem:

 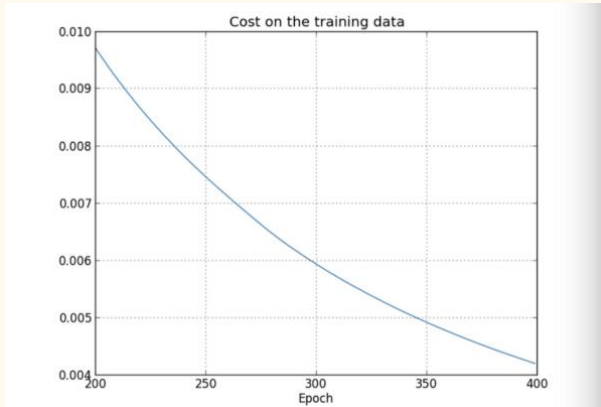

Trapping to local minima


<https://towardsdatascience.com/>

- Back propagation → However this leads to the vanishing gradient problem
- Pretraining
  - Deep belief network (DBN)
    - decompose into restricted Boltzmann machine (RBM)
    - learning for each RBM
    - Transfer to feedforward NN

Autoencoder

# Exceptionally “learnable” NN without pretraining

Convolutional neural network (CNN)

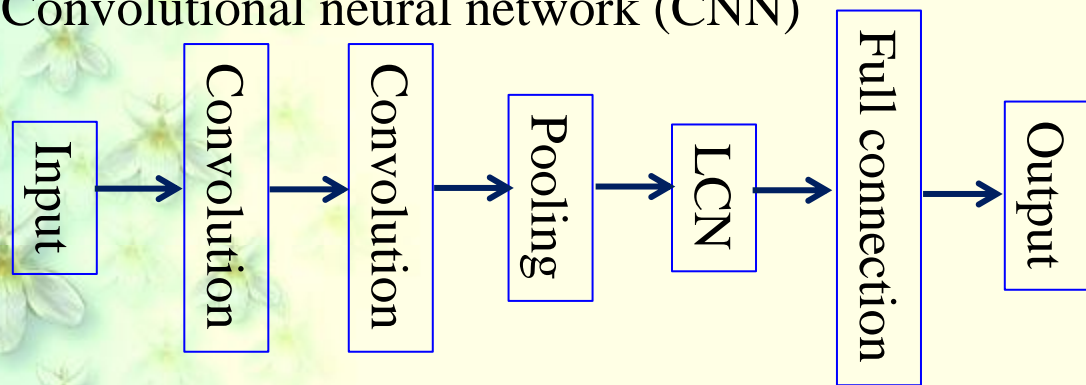

$\otimes$



=




filter1

$\otimes$



=

 

filter2

convolution

Input:  $W \times W$  image  
elements:  $x_{ij}$


Filter:  $H \times H$  image  
elements:  $h_{ij}$

$$u_{ij} = \sum_{p=0}^{H-1} \sum_{q=0}^{H-1} x_{i+p, j+q} h_{pq}$$

Pooling

 - Average
- Max
- Lp (some point between above)






## Deep learning from scratch

- Explains from introduction of Python to your PC
- Concise and to the points
- Python examples

# Perceptron expression for logic gates

Perceptron

 

$$y = \begin{cases} 0 & (w_1x_1 + w_2x_2 \leq \theta), \\ 1 & (w_1x_1 + w_2x_2 > \theta). \end{cases}$$

AND




$$(w_1, w_2, \theta) = (0.5, 0.5, 0.7) \quad : \text{ just an example}$$

NAND



$$(w_1, w_2, \theta) = (-0.5, -0.5, -0.7)$$

OR

 


$$(w_1, w_2, \theta) = (0.6, 0.6, 0.5)$$

# Why FPGA fits for DNNs?


Layer by layer learning calculation → can be done in parallel naturally.  
Calculation along transition lines → also can be done in parallel.

FPGA card specialized for DNNs (Xilinx)

 


# Overview
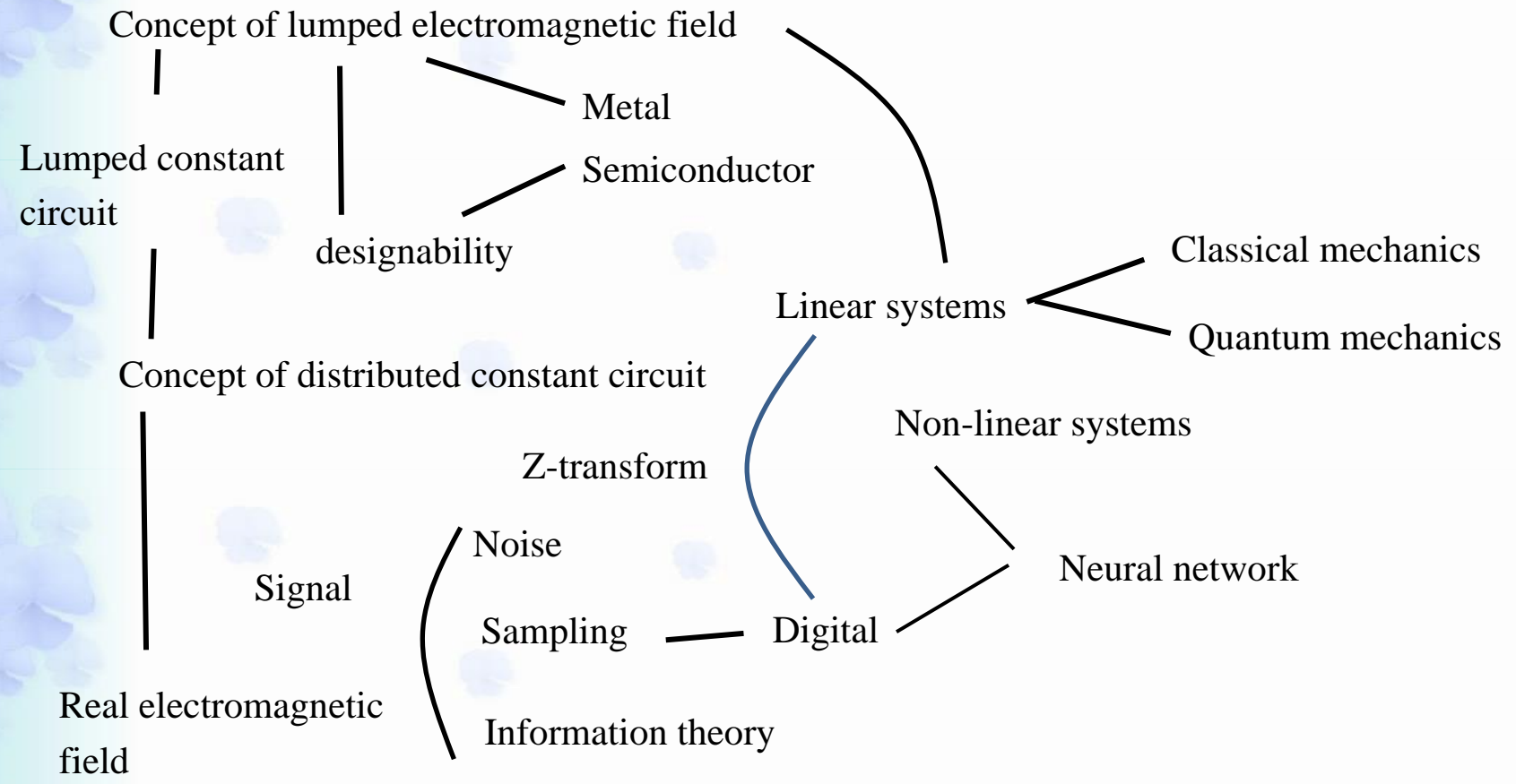
## Electric Circuits: Treasury of Languages and Concepts



# Supplement for amplifier and noise

## Equivalent noise band width (ENBW)

 


Attenuation gradient	k
-6 db/oct	1.57
-12 db/oct	1.11
-18 db/oct	1.05
-24 db/oct	1.03

$$\text{gain band width GBW} = A \times f_c$$

OP amp. spec. sheet: (open loop gain)  $\times$  (cut off freq.)

# Supplement amplifier and noise

 

1.  $R_S$  thermal noise =  $\sqrt{4kTR_S}$
2.  $R_{f1} \parallel R_{f2}$  thermal noise =  $\sqrt{4kT(R_{f1} \parallel R_{f2})}$
3. Input voltage noise  $e_n$ , current noise  $i_n$
4. Current noise times source resistance =  $i_n \times R_S$
5. Current noise times feedback resistance =  $i_n \times (R_{f1} \parallel R_{f2})$

$$(\text{output noise}) = \sqrt{e_1^2 + e_2^2 + e_3^2 + e_4^2 + e_5^2} \times G \times \sqrt{\text{ENBW}}$$