

# 電子回路論第4回

## Electric Circuits for Physicists #4

東京大学理学部・理学系研究科  
物性研究所  
勝本信吾

Shingo Katsumoto

# Review


Last week we introduced

Resonance: Represented as a zero-point in impedance. A pole in admittance.

$$Z(s_{\text{res}}) \sim Z_0(s - s_{\text{res}}), \quad Y(s) \sim \frac{A}{s - s_{\text{res}}} \quad (s \sim s_{\text{res}})$$

Bode diagram: Plots of the absolute value and the argument of a transfer function as a function of frequency.

# A Pole on the Real Axis


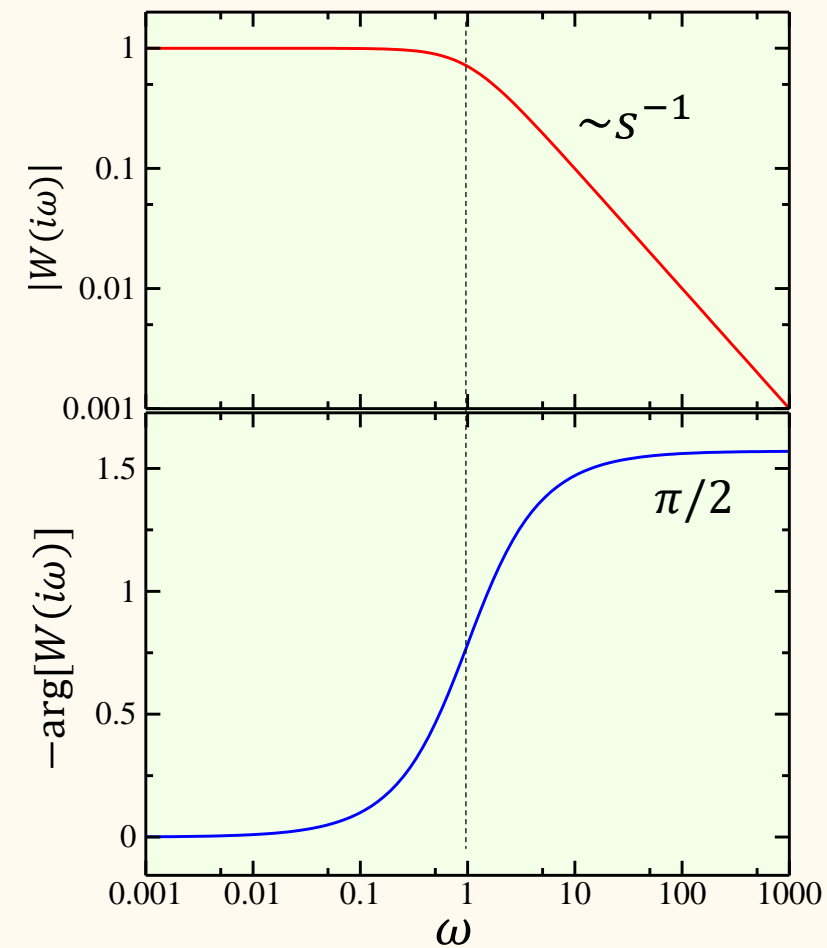


Linear system with transfer function


$$W(s) = \frac{1}{s + 1}$$

$$s = \sigma + i\omega \quad (\text{dimensionless})$$

Circuit example: Z of

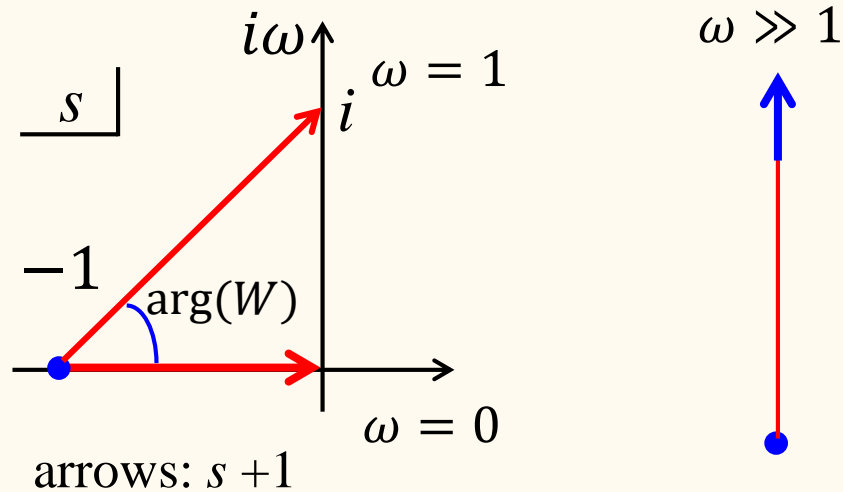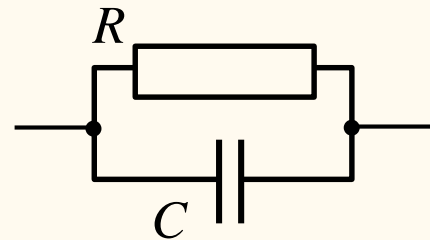


# A Pole with Finite Imaginary Part

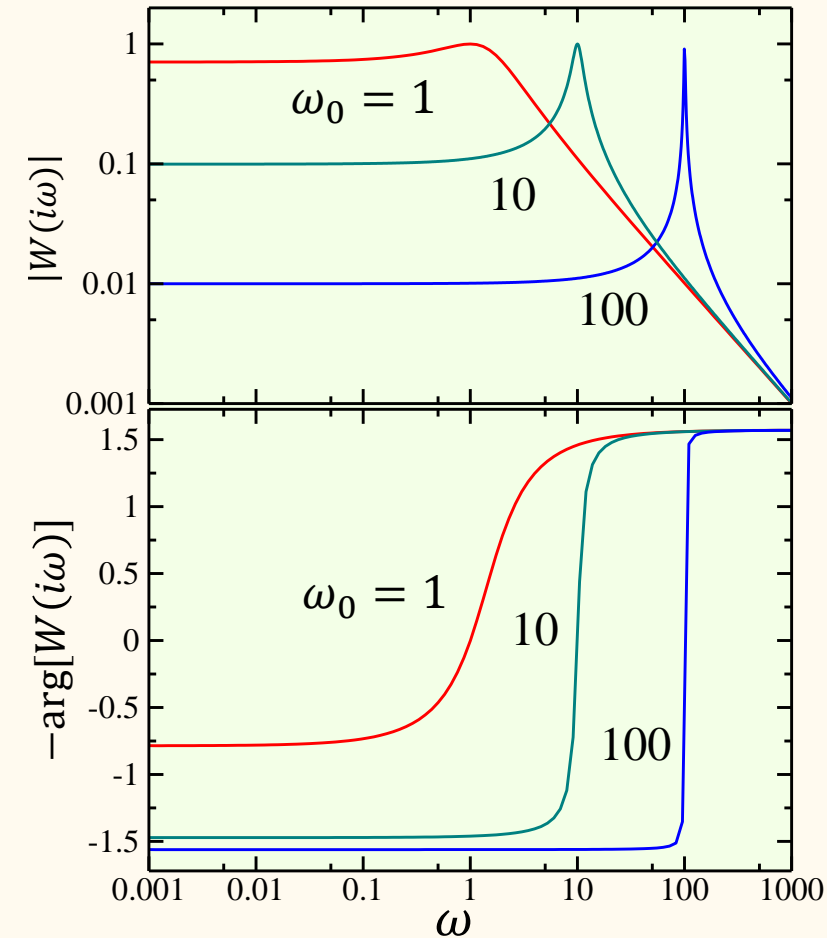

$$W(s) = \frac{1}{s + 1 - i\omega_0} \quad (*1)$$

Corresponds to resonance.

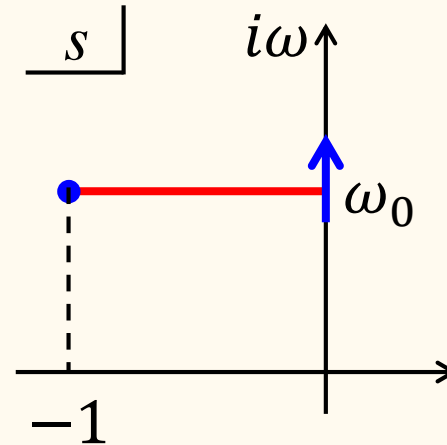(This approximately holds for  $\omega \sim \omega_0$ )



(\*1 Complex poles in transfer function always appear as conjugate pairs.)

# Zeros and Poles of Transfer Function

$$W(s) = B \frac{(s - \beta_1) \cdots (s - \beta_m)}{(s - \alpha_1) \cdots (s - \alpha_n)} \quad \{\alpha_j\} : \text{Poles}, \quad \{\beta_j\} : \text{Zeros}$$

(generally represented in rational formula)


$$\ln |W(i\omega)| = \ln B + \sum_{j=1}^m \ln |i\omega - \beta_j| - \sum_{j=1}^n \ln |i\omega - \alpha_j|,$$

Bode plot


$$\arg[W(i\omega)] = \arg(B) + \sum_{j=1}^m \arg(i\omega - \beta_j) - \sum_{j=1}^n \arg(i\omega - \alpha_j)$$

Bode plots are sum of those for single poles and zeros.
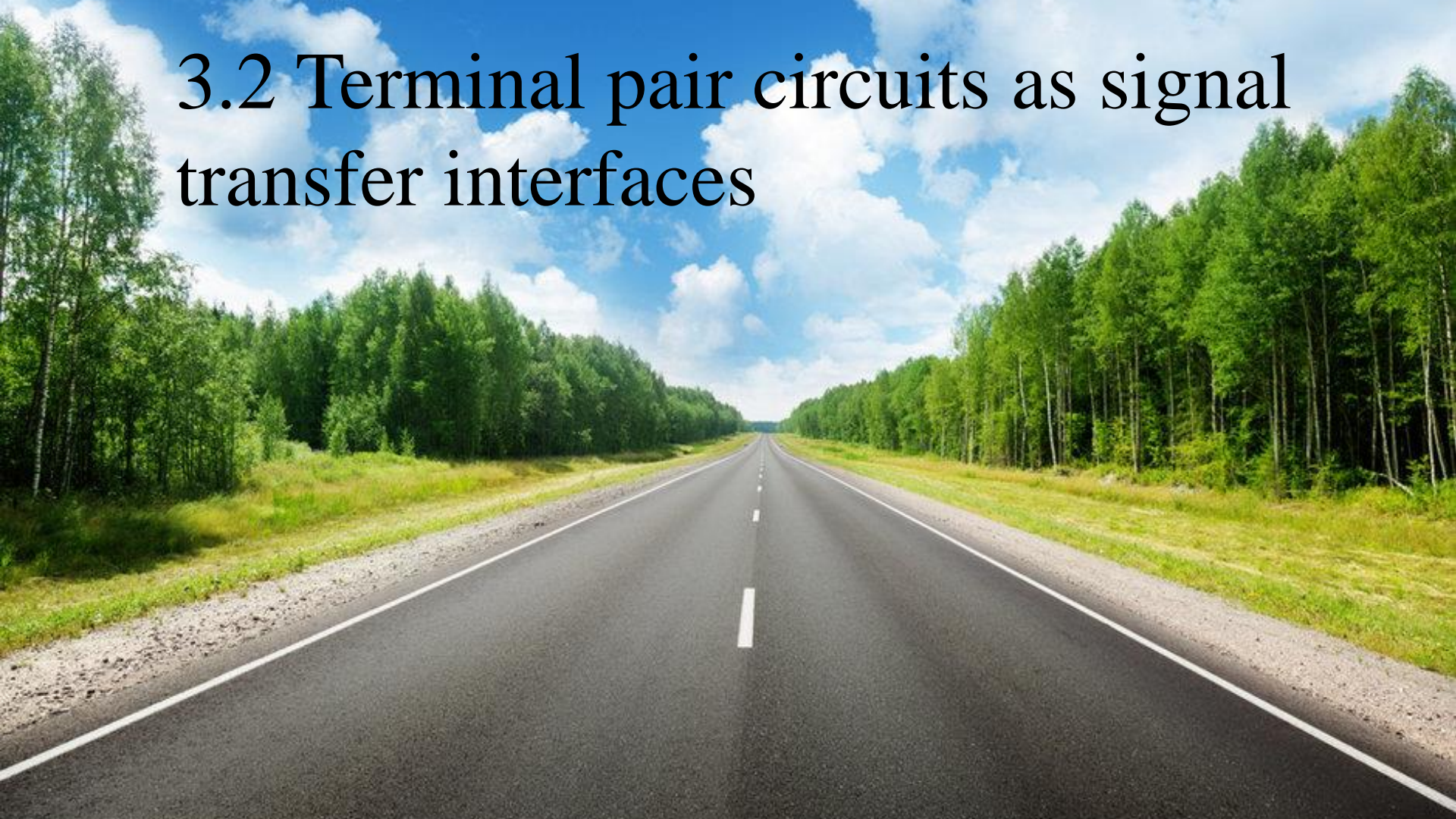
## 3.2 Terminal pair circuits as signal transfer interfaces



## 3.2.1 Impedance matching

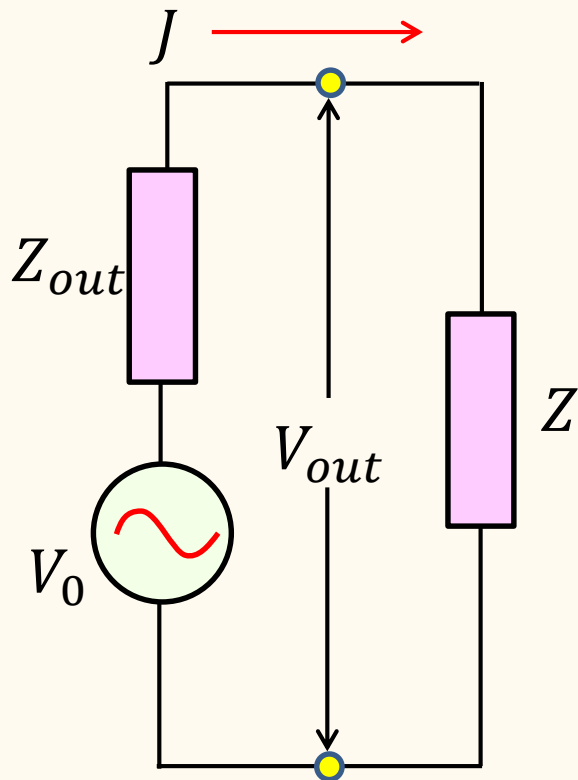

Efficient transfer of energy from electro-motiveforce

$$V_{out}(i\omega) = V_0(i\omega) - Z_{out}(i\omega)J(i\omega)$$

$$P = \text{Re}(V_{out}^* J) = \text{Re} \left( \frac{Z^* V_0^*}{Z^* + Z_{out}^*} \frac{V_0}{Z + Z_{out}} \right)$$

$$= \frac{|V_0|^2}{|Z + Z_{out}|^2} \text{Re}(Z)$$


Hence the maximum power transfer  $P_{\max} = \frac{|V_0|^2}{4\text{Re}(Z_{out})^2}$   
can be obtained under the impedance matching condition:

Impedance matching condition  $Z = Z_{out}^*$


When  $Z$  is real:  $Z = Z_{out}$
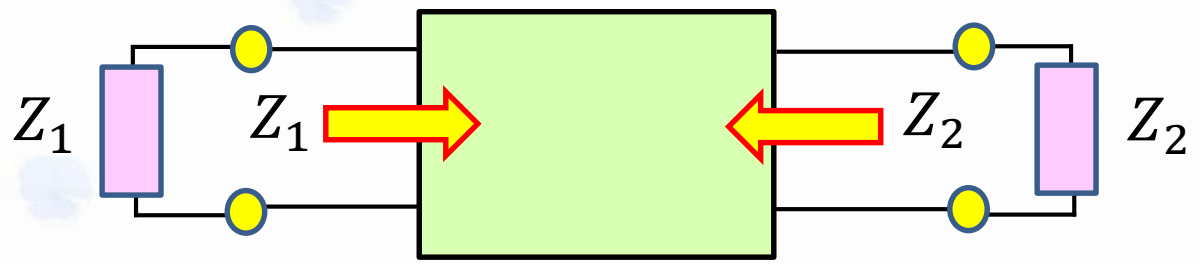
### 3.2.3 Image parameters (matching with 4-terminal circuits)

If the 4-terminal parameters can be tuned to give the situation as




That is

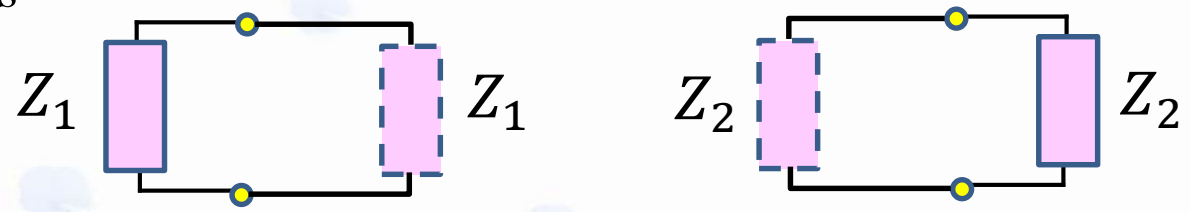

$Z_1$  and  $Z_2$  are called image impedances.



# Conditions for image parameters

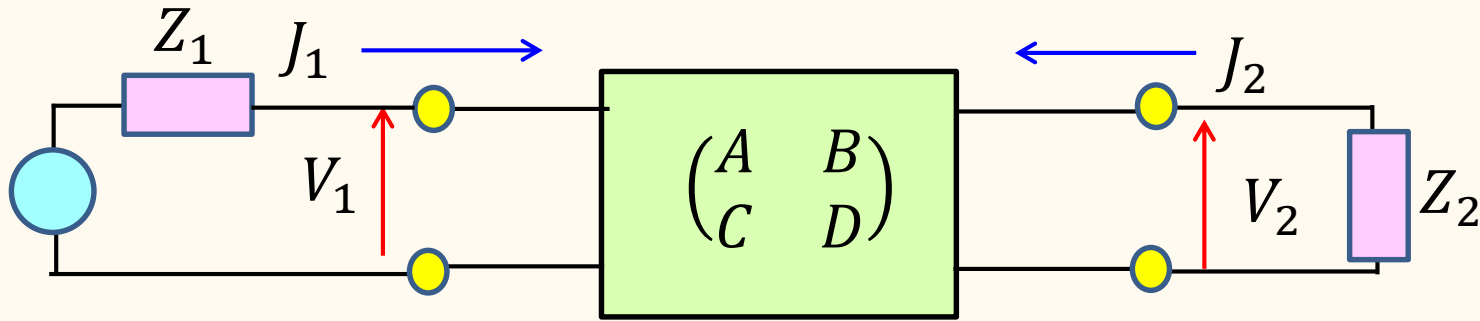

From definition:

$$\begin{cases} V_1 = AZ_2 - BJ_2, \\ J_1 = CV_2 - DJ_2 \end{cases}$$

$$V_2 = -J_2 Z_2$$

Image (mirror)  
condition



$$\begin{cases} Z_1 = \frac{V_1}{J_1} = \frac{AZ_2 + B}{CZ_2 + D} \\ Z_2 = \frac{DZ_1 + B}{CZ_1 + A} \end{cases}$$

When  $ABCD \neq 0$ ,

$$Z_1 = \sqrt{\frac{AB}{CD}}, \quad Z_2 = \sqrt{\frac{DB}{CA}}$$

# Image parameters

$$\frac{V_1}{V_2} = \sqrt{\frac{A}{D}}(\sqrt{AD} + \sqrt{BC}), \quad \frac{J_1}{-J_2} = \sqrt{\frac{D}{A}}(\sqrt{AD} + \sqrt{BC})$$

The 4-terminal interface costs some power loss:

$$e^\theta \equiv \sqrt{\frac{V_1 J_1}{-V_2 J_2}} = \sqrt{\frac{Z_1}{Z_2} \frac{J_1}{-J_2}} = \sqrt{\frac{Z_2}{Z_1} \frac{V_1}{V_2}} = \sqrt{AD} + \sqrt{BC}$$

$\theta$ : Image propagation constant  $\theta = \alpha + i\beta$  ( $\alpha, \beta \in \mathbb{R}$ )

$$\alpha = \frac{1}{2} \ln \left| \frac{V_1 J_1}{V_2 J_2} \right| \quad (\text{image attenuation constant}),$$

$$\beta = \frac{1}{2} \arg \left[ \frac{V_1 J_1}{-V_2 J_2} \right] \quad (\text{image phase shift})$$


# Image parameters

$$A = \sqrt{\frac{Z_1}{Z_2}} \cosh \theta, \quad B = \sqrt{Z_1 Z_2} \sinh \theta,$$

$$C = \frac{1}{\sqrt{Z_1 Z_2}} \sinh \theta, \quad D = \sqrt{\frac{Z_2}{Z_1}} \cosh \theta$$

$Z_1, Z_2, \theta$ : Image parameters
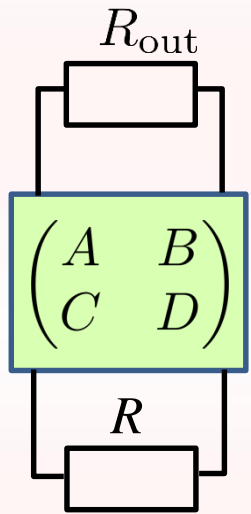
# 3.2.4 Impedance matching with two terminal-pair circuits




$ABCD \neq 0$        $R_{out} = \sqrt{\frac{AB}{CD}}, \quad R = \sqrt{\frac{BD}{AC}}$   
 $A = D = 0$        $R_{out} = \frac{AR + B}{CR + D}, \quad R = \frac{DR_{out} + B}{CR_{out} + A}$   
 $\rightarrow RR_{out} = B/C$

$B = C = 0$        $R_{out}/R = A/D$



Matching transformer

$n = \sqrt{\frac{R}{R_{out}}}$

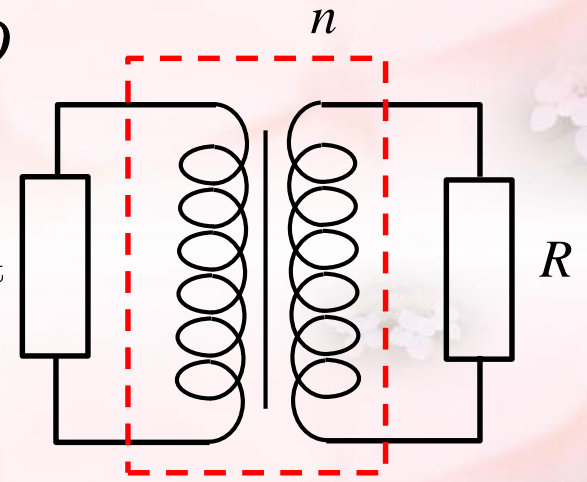

## 3.2.5 Fidelity and distortion in wave transformation

When a linear response  $w(t) = \mathcal{L}\{u(t)\}$  is just a time delay with  $\tau_0$ , that is

$$w(t) = A_0 u(t - \tau_0) \quad \therefore W(i\omega) = A_0 e^{-i\omega\tau_0} U(i\omega),$$

$$\Xi(i\omega) = A_0 e^{-i\omega\tau_0}$$

**No distortion** conditions are: (1)  $|\Xi(i\omega)| = A_0$ , (2)  $\arg[\Xi(i\omega)] = -\omega\tau_0$

In other words the conditions can be described as

(1)  $A_0$  does not depend on frequency: **No filter effect**

(2)  $\phi(\omega) \equiv \arg[\Xi(i\omega)]$ ,  $\tau(\omega) \equiv -\frac{d\phi(\omega)}{d\omega}$  :group delay  $\tau(\omega) = \tau_0$

**No dispersion in group delay**

# Effect of distortion in amplitude

(1) Sinusoidal amplitude distortion (amplitude modulation)

$$A(\omega) = a_1 \cos(\tau_1 \omega) + a_0, \quad \phi(\omega) = -\tau_0 \omega$$

$$\begin{aligned} w(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} A(\omega) U(i\omega) e^{i(\omega t + \phi(\omega))} d\omega \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} d\omega U(i\omega) \{a_1 \cos(\tau_1 \omega) + a_0\} e^{i\omega(t - \tau_0)} \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} d\omega U(i\omega) \left[ a_0 + \frac{a_1}{2} (e^{i\tau_1 \omega} + e^{-i\tau_1 \omega}) \right] e^{i\omega(t - \tau_0)} \\ &= a_0 u(t - \tau_0) + \frac{a_1}{2} [u(t - \tau_0 + \tau_1) + u(t - \tau_0 - \tau_1)] \end{aligned}$$

Paired echo

# Effect of distortion in group delay

Sinusoidal group delay distortion

$$A(\omega) = A_0, \quad \phi(\omega) = -\tau_0\omega + b_1 \sin(\tau_1\omega)$$


$$\exp[ib_1 \sin(\tau_1\omega)] \approx 1 + \frac{ib_1}{2i} (e^{i\tau_1\omega} - e^{-i\tau_1\omega})$$

$$w(t) = A_0[u(t - \tau_0) + \frac{b_1}{2} \{u(t - \tau_0 + \tau_1) - u(t - \tau_0 - \tau_1)\}]$$


Paired echo with inverted sign

# Distortion (paired echo)

Cosine Amplitude Distortion




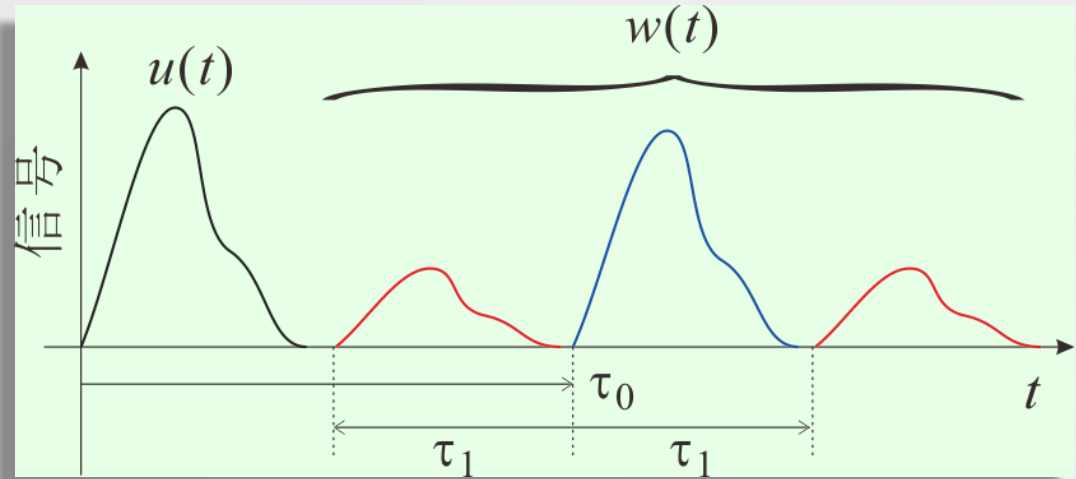


Sine Delay Distortion

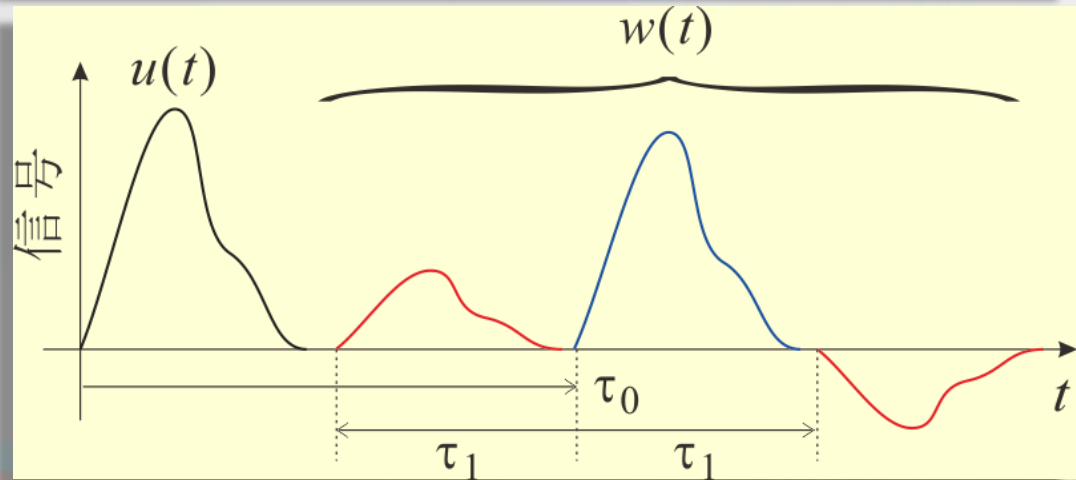



## 3.2.6 Filter Circuit

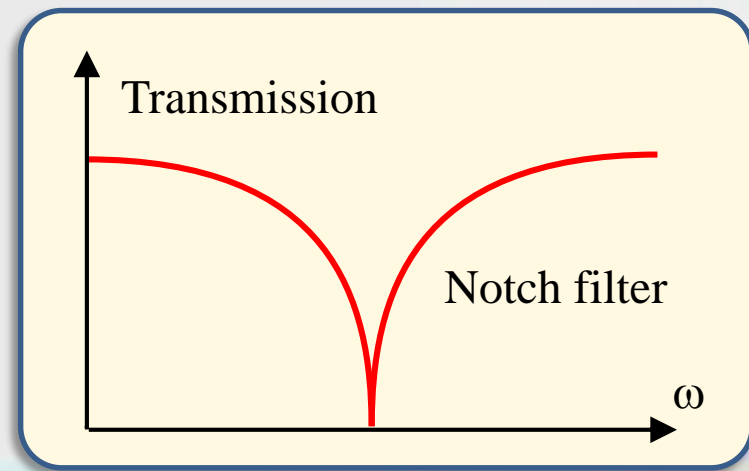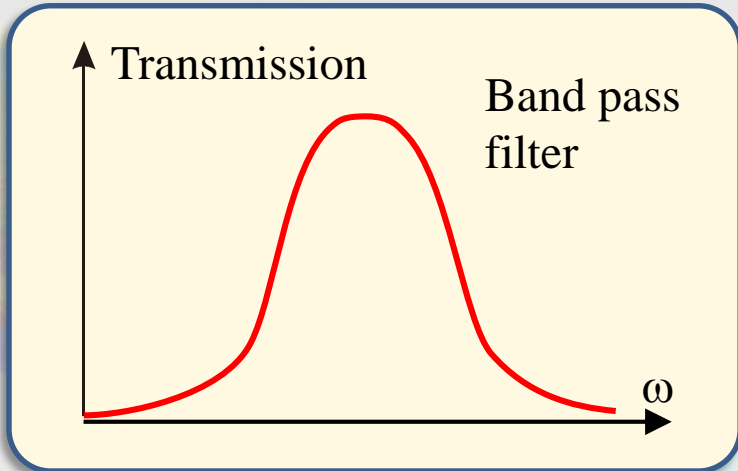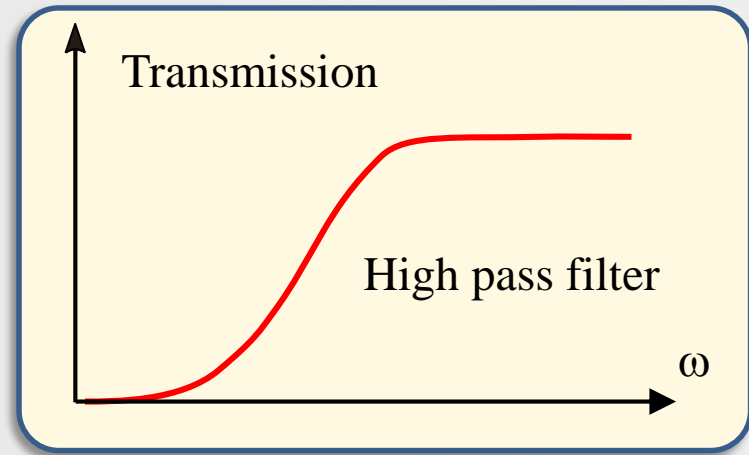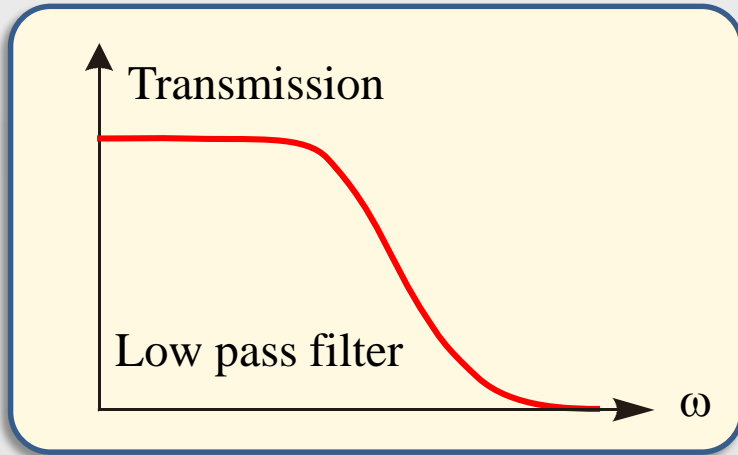


# Terms for Filters

$$\Xi(i\omega) = \underline{A(\omega)} e^{i\phi(\omega)}$$


Transmission

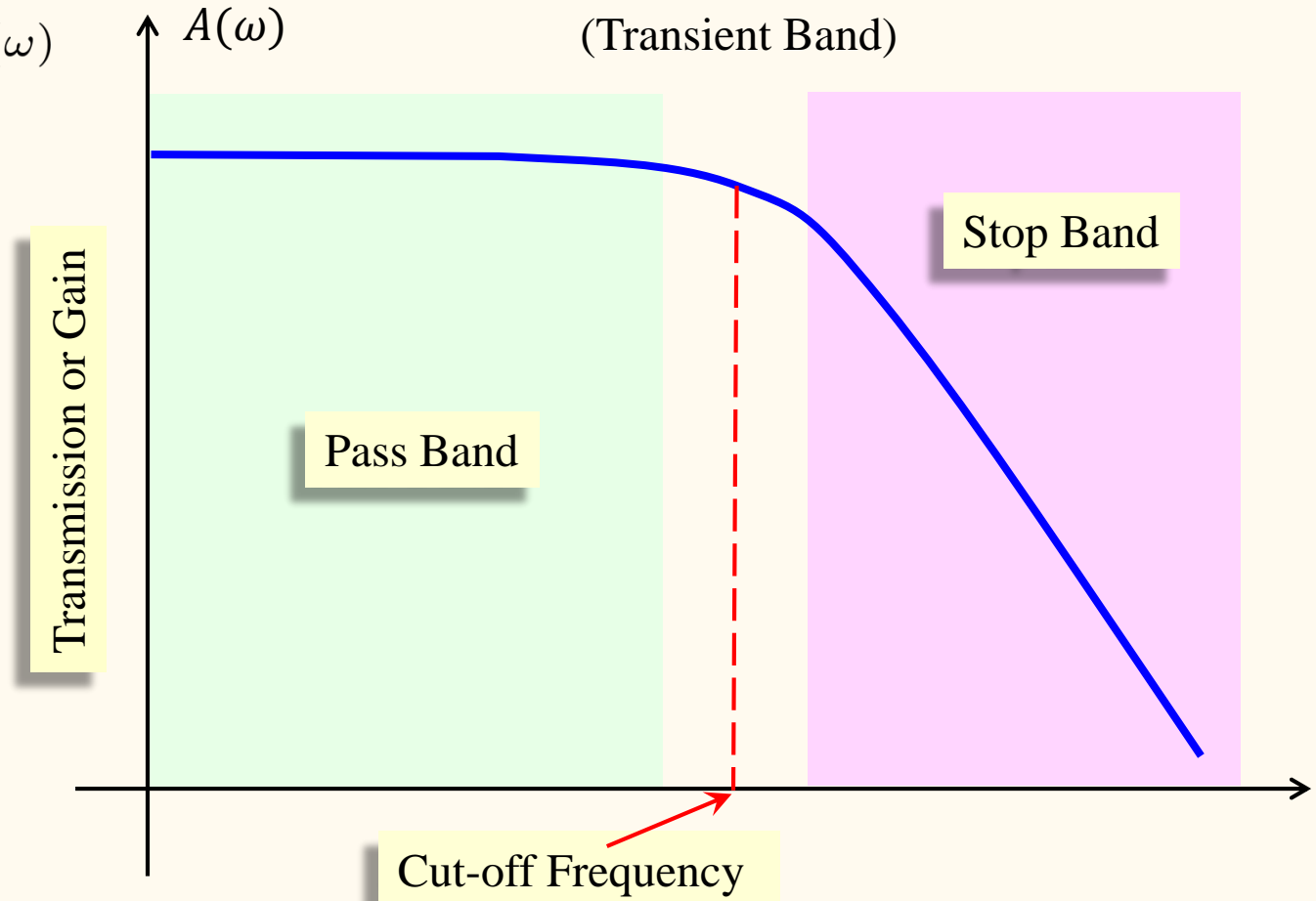$A(\omega)$  is sometimes called as “gain”



# Can an ideal filter exist?

Ideal low pass filter

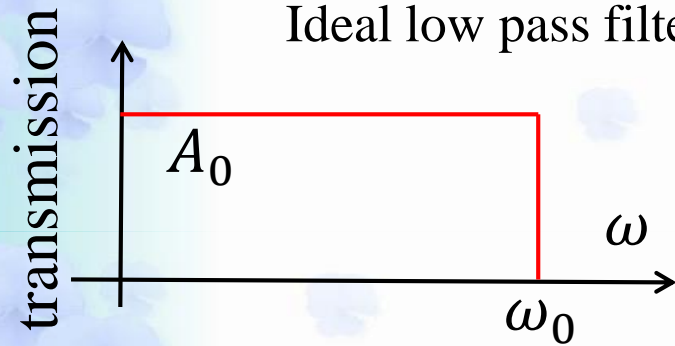

$$\Xi(i\omega) = H(\omega_0 - |\omega|)$$


Transfer function is written as Heaviside function

$w(t)$ : output to  $\delta$ -function input at  $t=0$


$$\begin{aligned}\frac{w(t)}{A_0} &= \int_{-\omega_0}^{\omega_0} e^{i\omega t} \frac{d\omega}{2\pi} \\ &= \int_{-\omega_0}^{\omega_0} \frac{d\omega}{2\pi} \cos \omega t = 2f_0 \frac{\sin \omega_0 t}{\omega_0 t} \\ &= 2f_0 \text{sinc}(2f_0 t)\end{aligned}$$

The output begins  $t < 0$  hence breaks the causality.

No ideal low pass filter can exist.

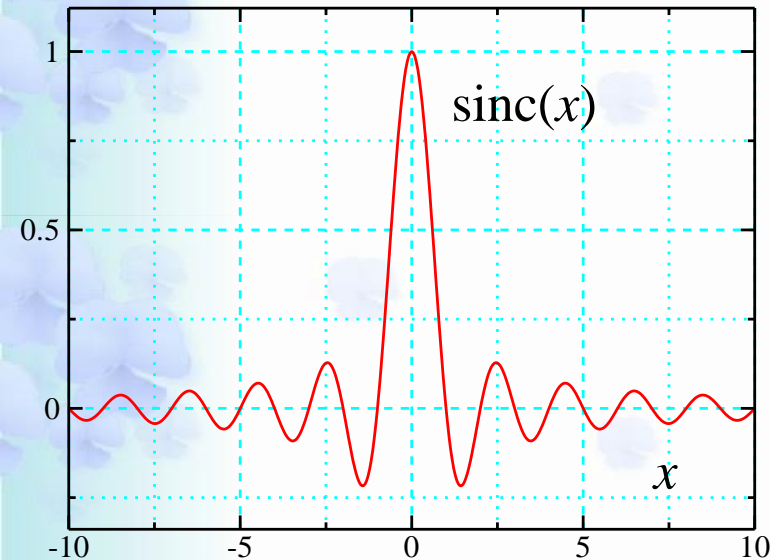

# Transmission

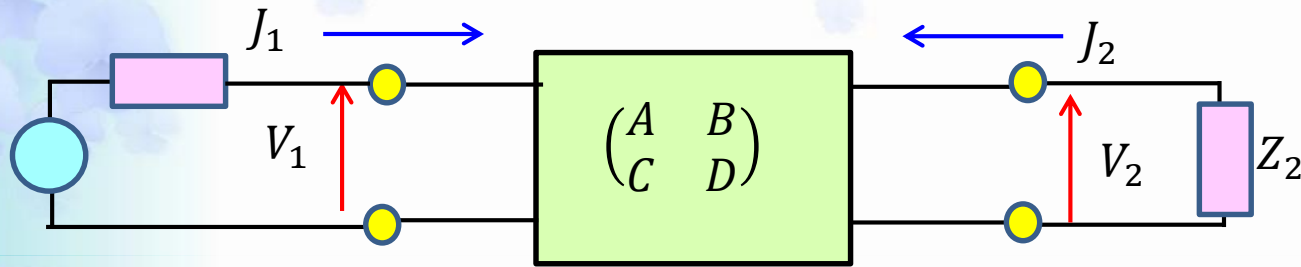

Voltage transmission coefficient:

$$T(i\omega) \equiv \frac{V_2(i\omega)}{V_1(i\omega)}$$

$$\log T = \log |T| + i \arg T = -\alpha - i\beta$$


attenuation      phase shift

Square root power transmission coefficient

$$S_B \equiv \sqrt{\frac{P_0}{P_2}} = \frac{R_2 A + B + C R_1 R_2 + D R_1}{2\sqrt{R_1 R_2}}$$

Sometimes called as “gain”

# An example: Constant K type filter

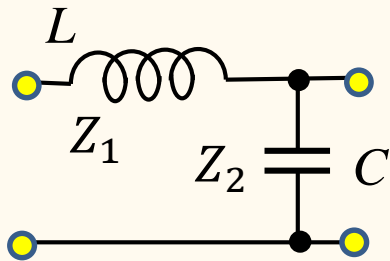

definition

$$Z_1 Z_2 = R^2 = K$$

:constant

$$Z_1 Z_2 = \frac{L}{C} = R^2 \quad \therefore \sqrt{\frac{L}{C}} = R$$


Image parameters are

$$Z_{01} = R\sqrt{1 - \omega^2 LC}, \quad Z_{02} = \frac{R}{\sqrt{1 - \omega^2 LC}},$$

$$\coth \theta = \sqrt{1 - \frac{1}{\omega^2 LC}} \equiv \sqrt{1 - \frac{1}{\Omega^2}}$$


$$\theta = \alpha + i\beta$$
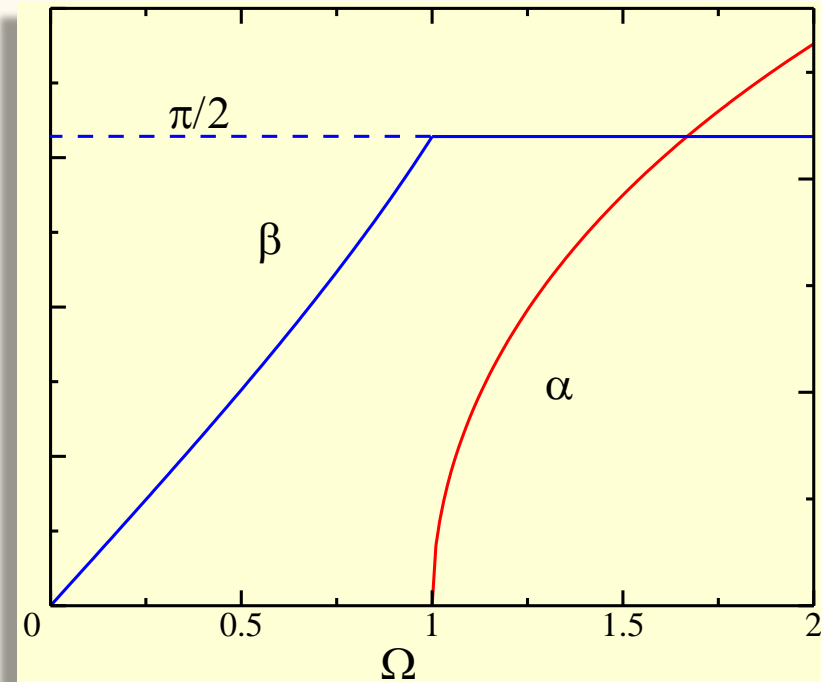
$$\begin{aligned} \cosh(\alpha + i\beta) &= \cosh \alpha \cos \beta + i \sinh \alpha \sin \beta \\ &= \sqrt{1 - \Omega^2} \end{aligned}$$



# Butterworth Filter

$$G^2(i\omega/\omega_0) = |H(i\omega)|^2 = \frac{1}{1 + (\omega/\omega_0)^{2n}}$$

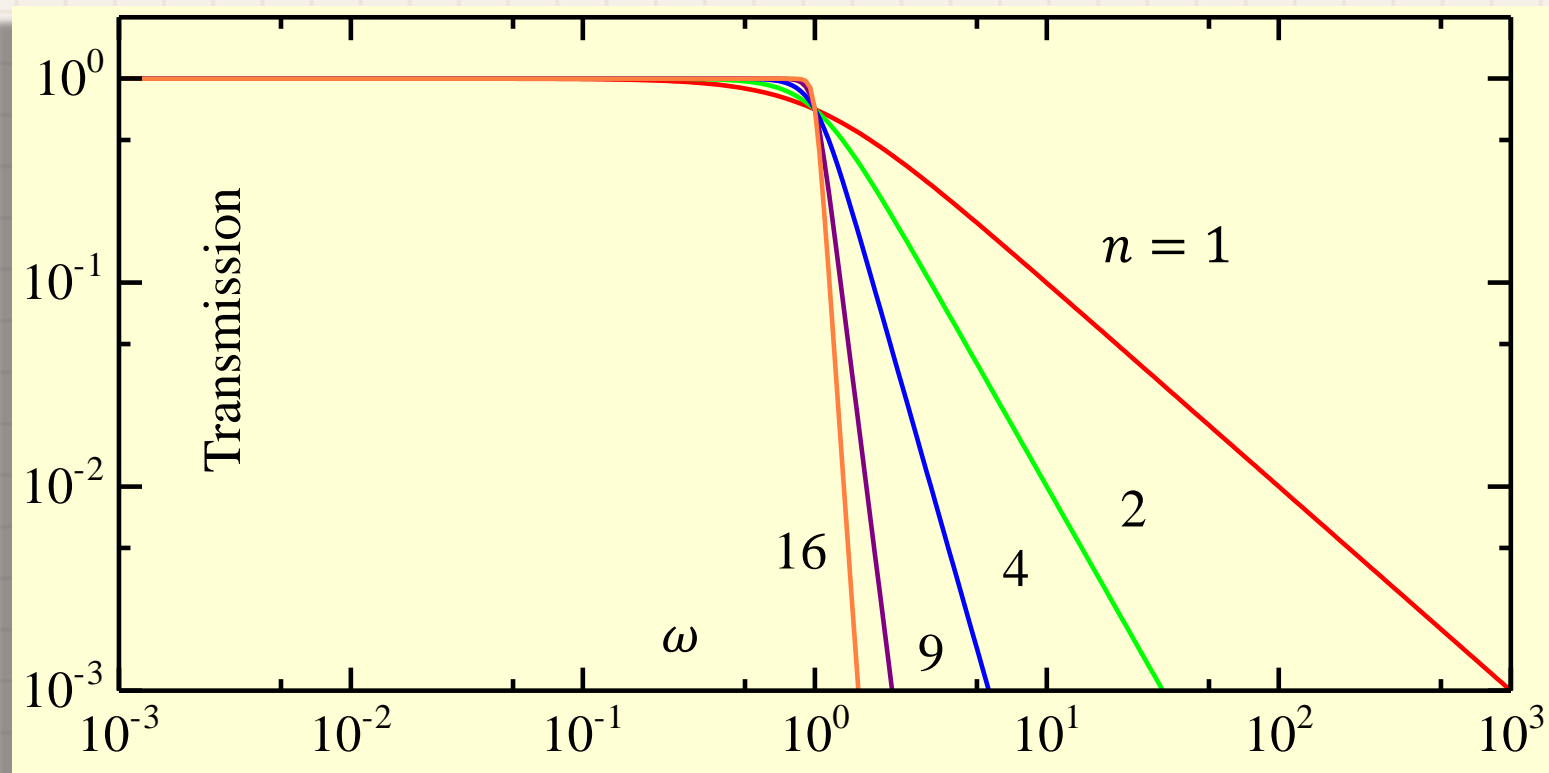



# Bessel Filter

## Inverse Bessel Polynomial

$$B_0 = 1, \quad B_1(s) = s + 1$$

$$B_n(s) = (2n - 1)B_{n-1}(s) + B_{n-2}(s)s^2$$

$$\Xi(s) = \frac{B_n(0)}{B_n(s)}$$

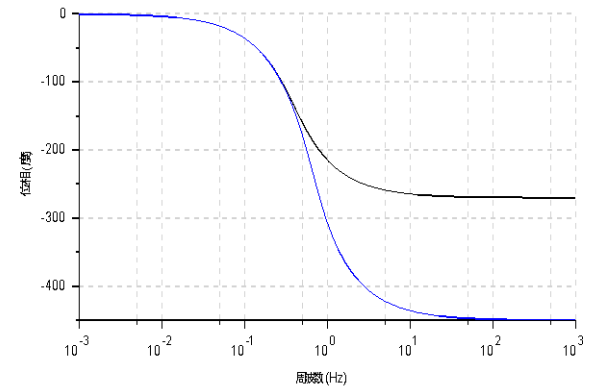
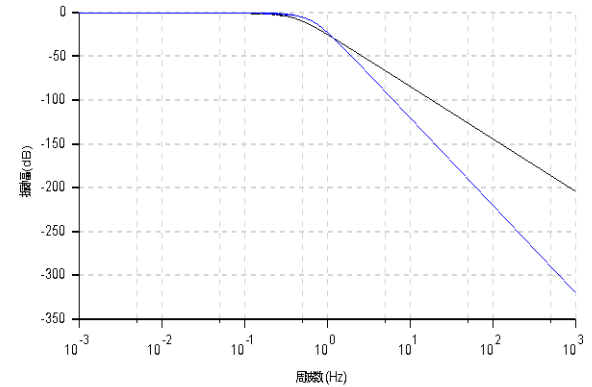


# Chebyshev Filter

$$G_n(i\Omega) = |H_n(i\Omega)| = \frac{1}{\sqrt{1 + \epsilon^2 T_n^2(\Omega)}}$$

$\epsilon$ : Ripple coefficient

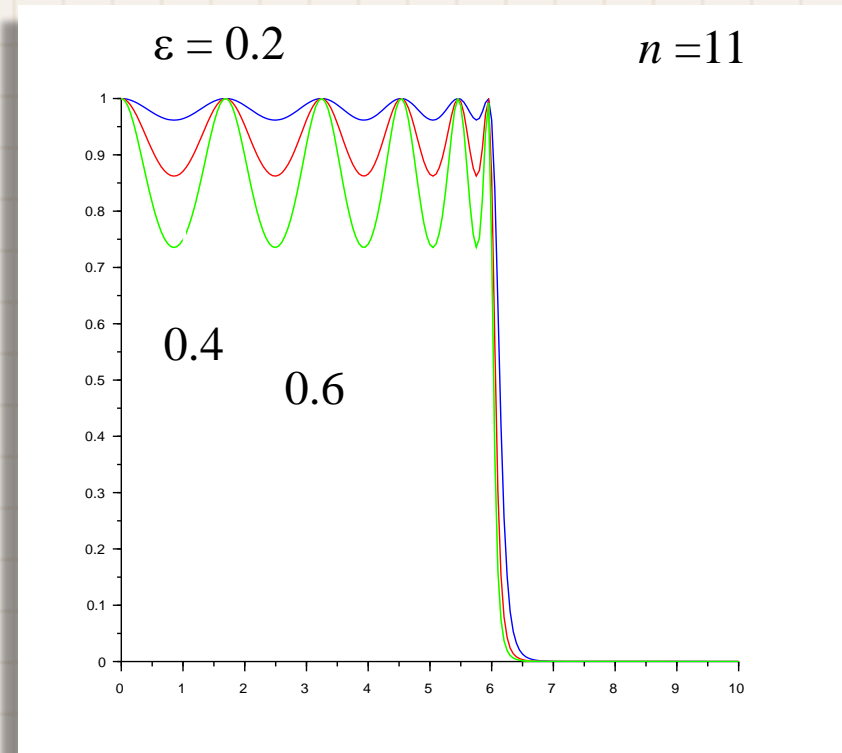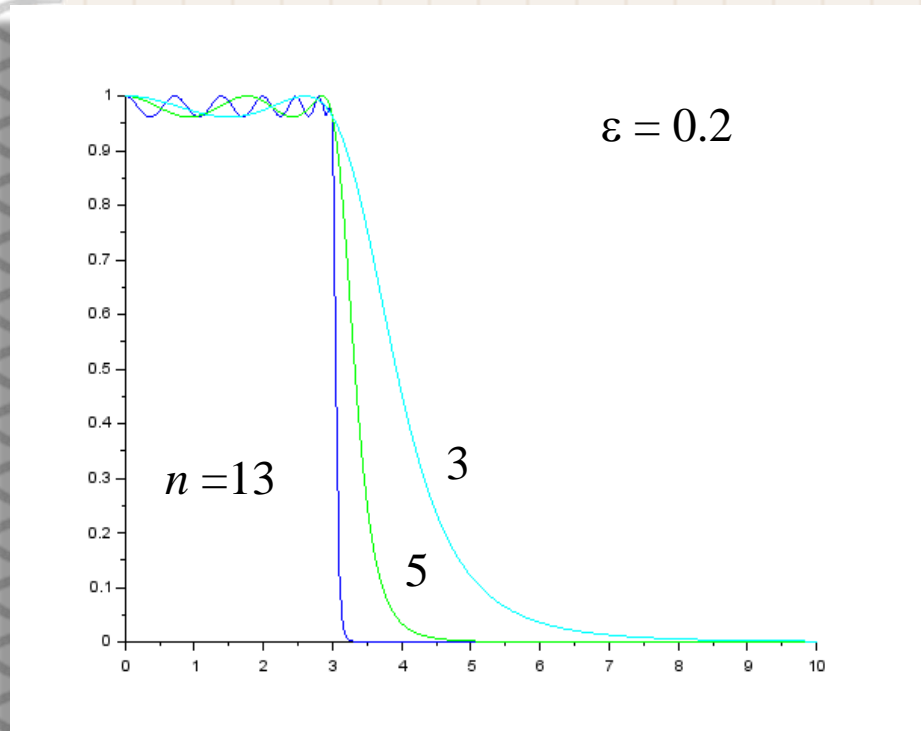$T_n$ :  $n$ -th order Chebyshev polynomial





# Packaged Filters



Web selection [page](#)


<https://ww3.minicircuits.com/WebStore/RF-Filters.html>

Mini-Circuits


Band Pass

19.2 – 23.6MHz 50Ohm
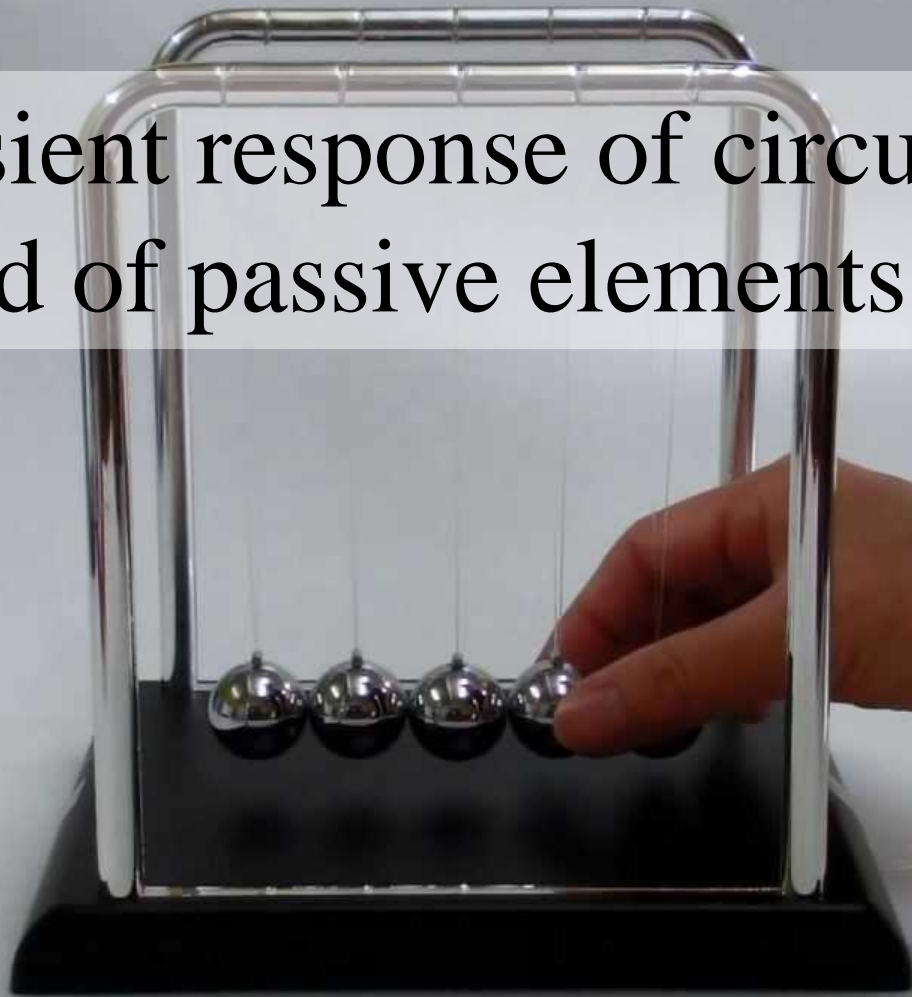
### 3.3 Transient response of circuits composed of passive elements



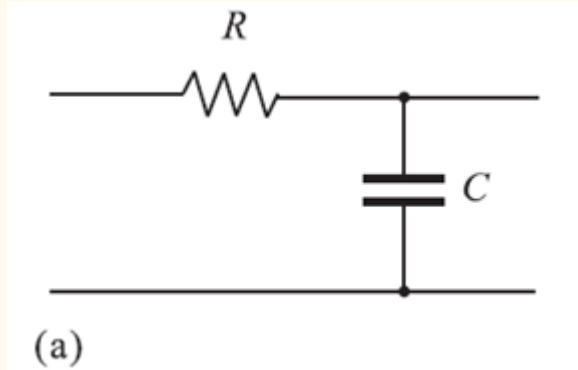
### 3.3.1 Classification with the number of storages



(a) Single energy storage

$$\Xi(s) = \frac{1}{1 + s/s_0}$$

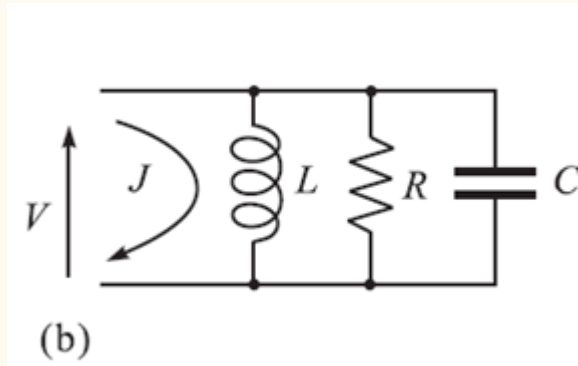


(b) Double energy storage

$$\Xi(s) = \frac{1}{b + s + as^{-1}}$$

Number of storages: order of polynomial in the denominator of rational expression for transfer function
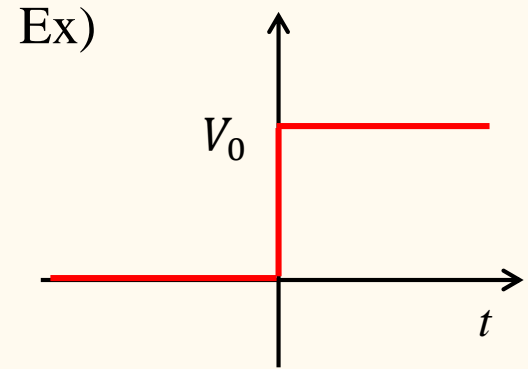
# Ex) Transient response to step function input

Responses are obtained as  $w(t) = \mathcal{F}^{-1}\{\Xi(i\omega)U(i\omega)\} = \int_{-\infty}^{\infty} \Xi(i\omega)U(i\omega)e^{i\omega t} \frac{d\omega}{2\pi}$




Heaviside function

$$H(x) = \begin{cases} 0 & x < 0 \\ 1/2 & x = 0 \\ 1 & x > 0 \end{cases}$$

Fourier transform

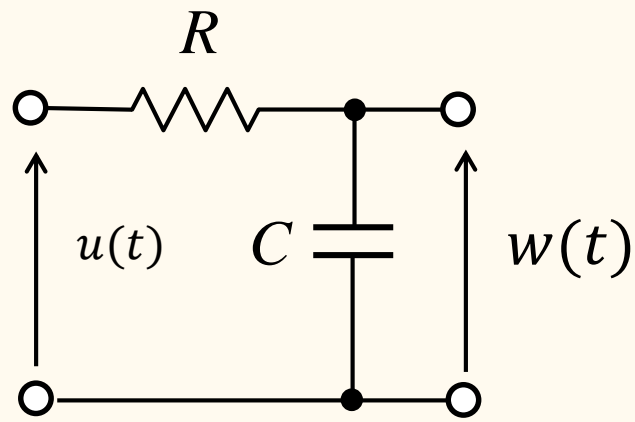
$$\mathcal{F}\{H(t)\} = \frac{1}{i\omega} + \pi\delta(\omega)$$



$$g(t) = \int_{-\infty}^{\infty} \frac{e^{i\omega t}}{1+i\omega} \left[ \frac{1}{i\omega} + \pi\delta(\omega) \right] \frac{d\omega}{2\pi}$$

$$= \int_{-\infty}^{\infty} \frac{e^{i\omega t}}{(i-\omega)\omega} \frac{d\omega}{2\pi} + \frac{1}{2}$$
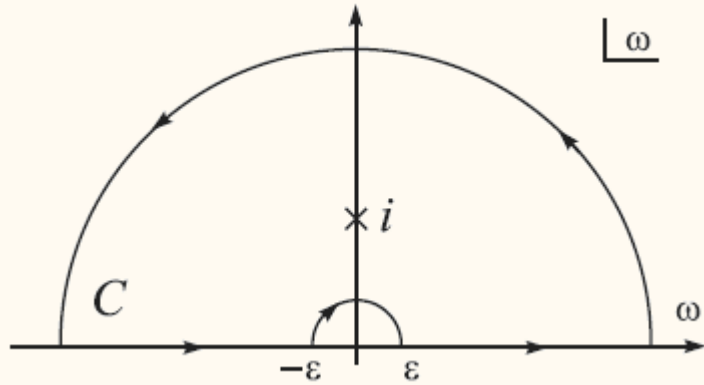
# Ex) Transient response to step function input




$$\int_{-\infty}^{\infty} \frac{e^{i\omega t}}{(i - \omega)\omega} \frac{d\omega}{2\pi}$$

$$= -2\pi i \frac{e^{-t}}{2\pi i} - \lim_{\epsilon \rightarrow 0} \left[ \int_{\pi}^0 \frac{e^{i\epsilon e^{i\theta} t}}{\epsilon e^{i\theta} (\epsilon e^{i\theta} - i)} \frac{i\epsilon e^{i\theta} d\theta}{2\pi} \right]$$

$$= -e^{-t} - \frac{1}{2}$$

$$\therefore g(t) = -e^{-t}$$

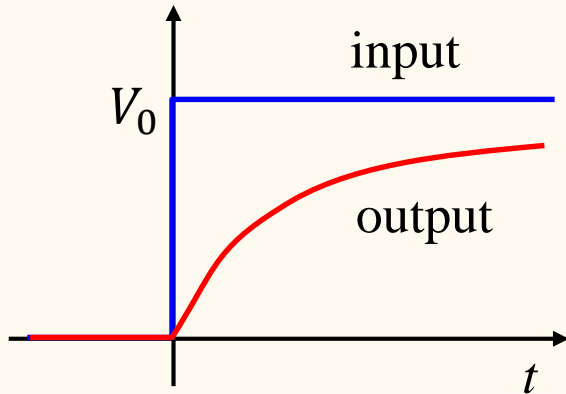

From the initial condition and renormalization of  $t$  we obtain

$$V = V_0 \left[ 1 - \exp\left(-\frac{t}{CR}\right) \right]$$

# Introduction of freeware: Scilab

**Download Scilab**  
Scilab 6.0.1 - Windows 64 bits • 175.96 MB  
Other Systems

Open source software for numerical computation

Scilab 6.0.0 Console

File Edit Control Applications ?

File Browser

myScripts

myScripts  
compute.sce  
myData.csv

plot3d

Graphic window number 0

Y 0

2 0 2

News 12/21/2012 - Seasons Greetings 09/14/2018 - Back to School - Training on C

Discover Scilab Cloud

*Tired of exchanging Excel spreadsheets for your scientific & engineering applications?*

Discover the capabilities of Scilab Cloud for the deployment of web applications:

- Centralize your data and algorithms
- Simplify and control your deployment

Scilab Cloud is a **new professional solution** developed by the Scilab Team.

Discover Scilab

- What is Scilab ?
- Features
- Xcos

Scilab versions

- Scilab 6.0.1 (Feb 18)
- Scilab 5.5.2
- System requirements

Showcases

- Gallery
- ScilabTEC '15 presentations
- Previous ScilabTEC Presentations

Get started

New to Scilab?

Here is a tutorial to get you started:

- Overview
- First steps
- Plotting

Get help

Scilab Enterprises is developing the software Scilab, and offering professional services:

- Training,
- Support,
- Development.

<https://www.scilab.org/>


MATLAB clone but free!

Graphical linear response analysis: Scicos

Convenient set of commands for linear response analysis


# Transfer function analysis with Scilab

$$\Xi(s) = \frac{1}{1 + s}$$

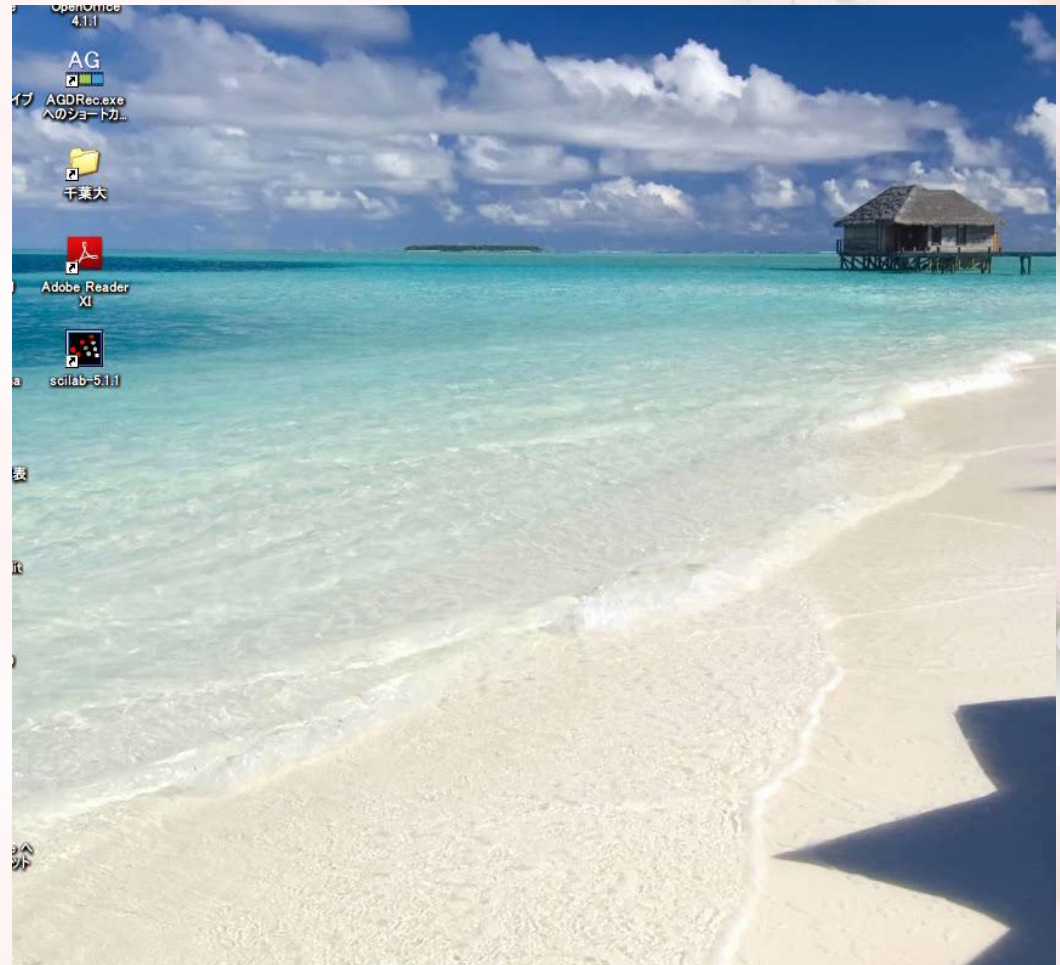

# Transient response: Use of Scilab


$$\Xi(s) = \frac{1}{1+s}$$

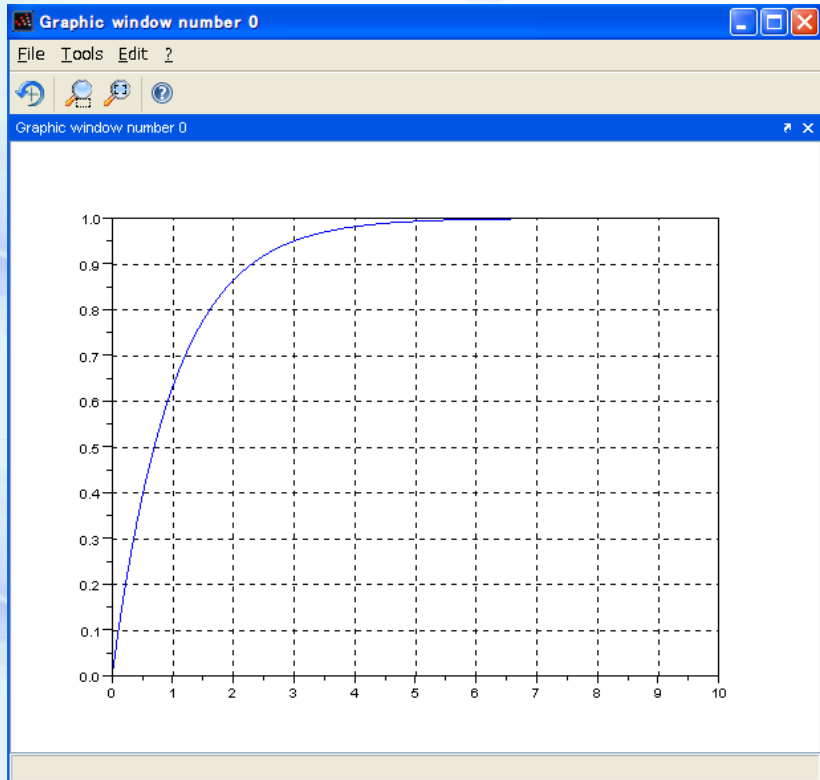

```
-->s=poly(0,'s');  
  
-->G=1/(1+s);  
  
-->sys=syslin('c',G);  
  
-->t=linspace(0,10,100);  
  
-->y=csim('step',t,sys);  
  
-->plot(t,y)  
  
-->xgrid()
```



# Transient response: Use of Scilab

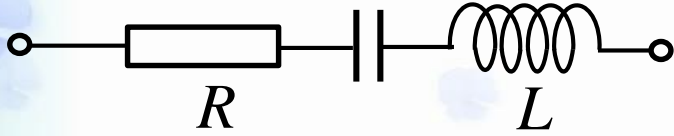

$$Y(s) = \frac{Cs}{LCs^2 + CRs + 1}$$

```
-->G=s/(1+s+2*s*s);  
  
-->sys=syslin('c',G);  
  
-->y=csim('step',t,sys);  
  
-->plot(t,y)
```

