




電子回路論第5回

Electric Circuits for Physicists #5

東京大学理学部・理学系研究科
物性研究所
勝本信吾


Shingo Katsumoto

Chapter 4 Amplification circuits

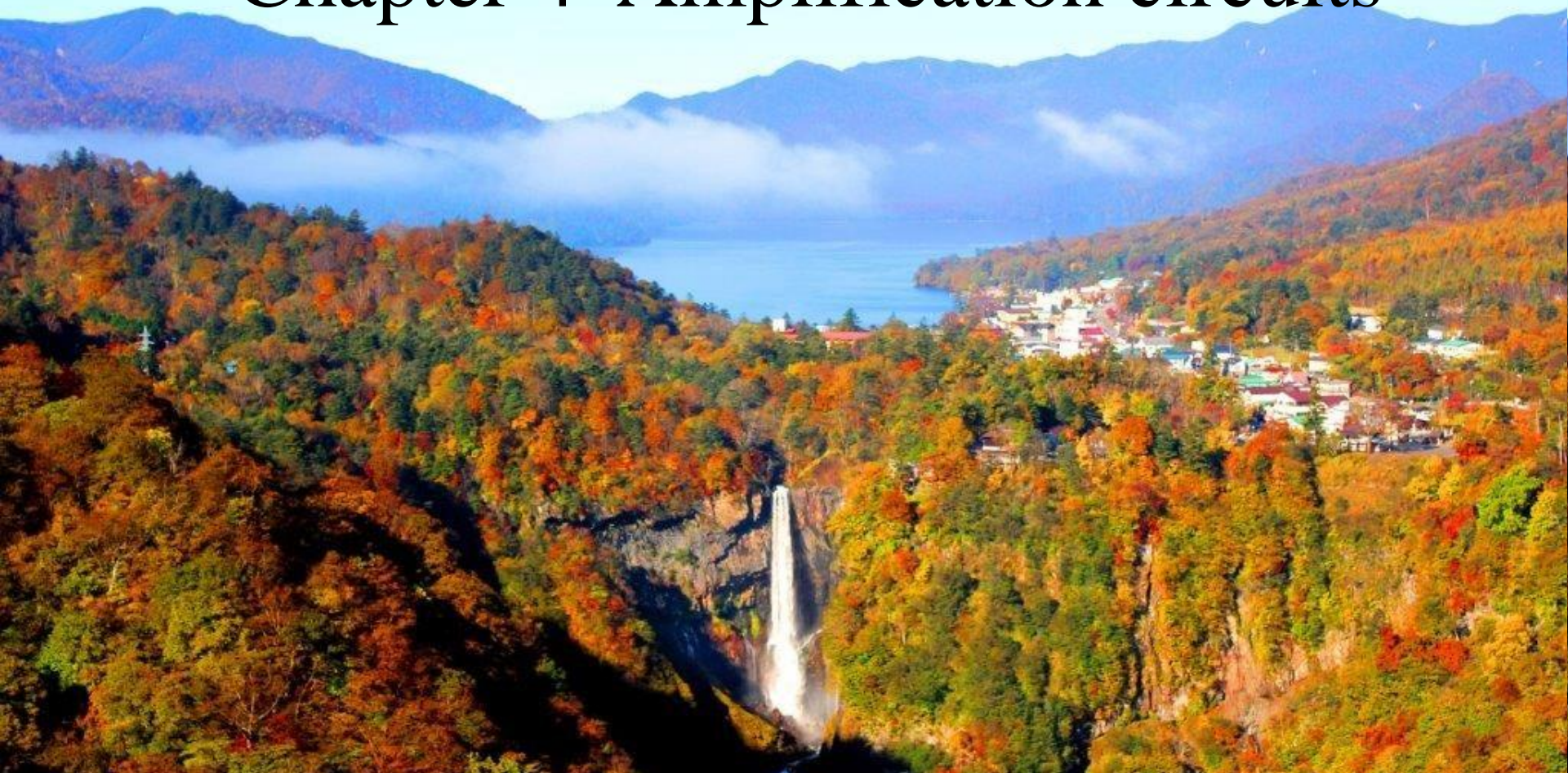


Linear amplifier

passive
filter

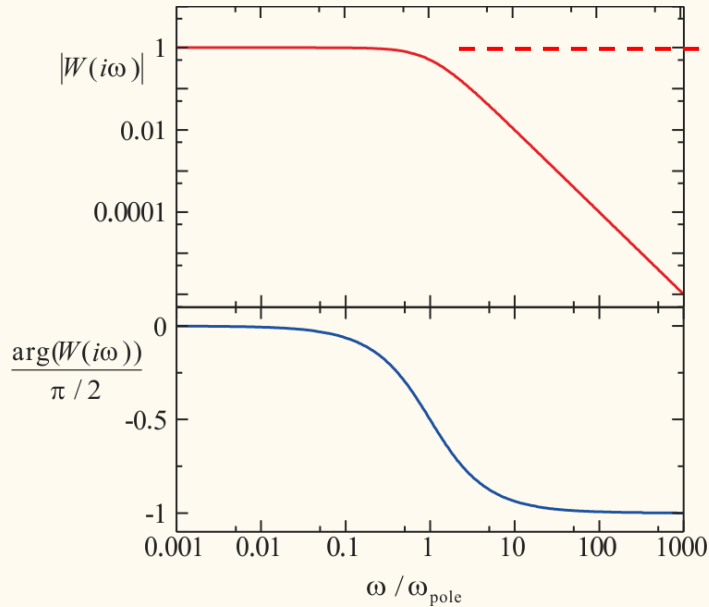


maximum gain = 1
gain $> 1 \rightarrow$ amplifier

four terminal circuit model




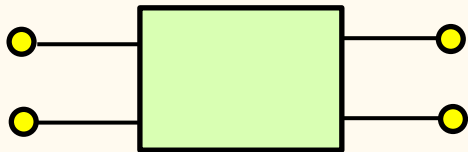


Circuit symbol

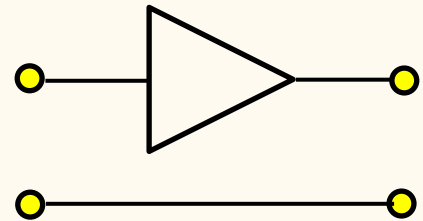

Which quantity is “amplified”?

Controlled power source models

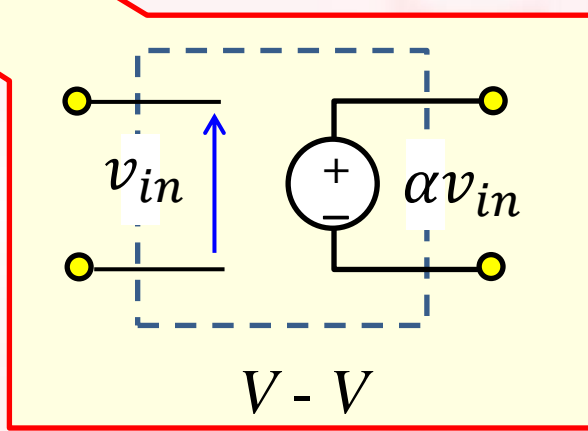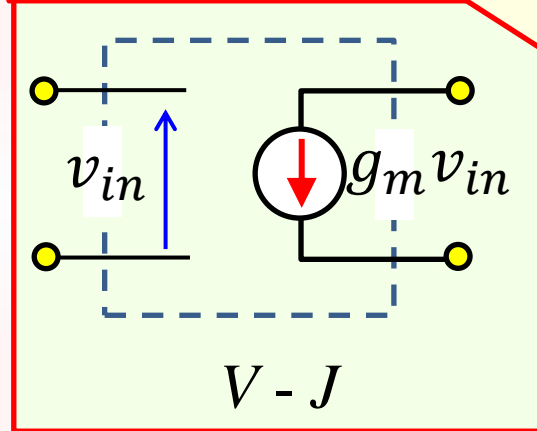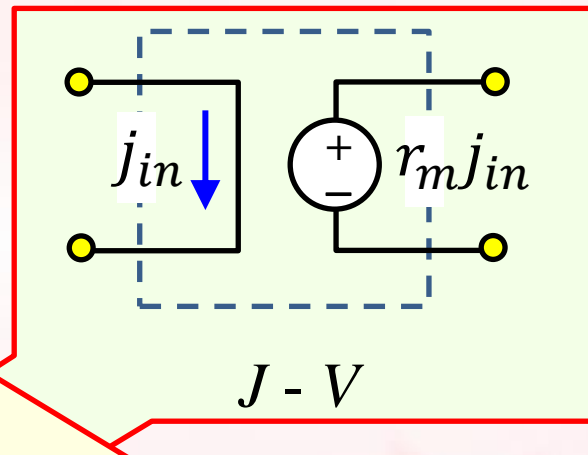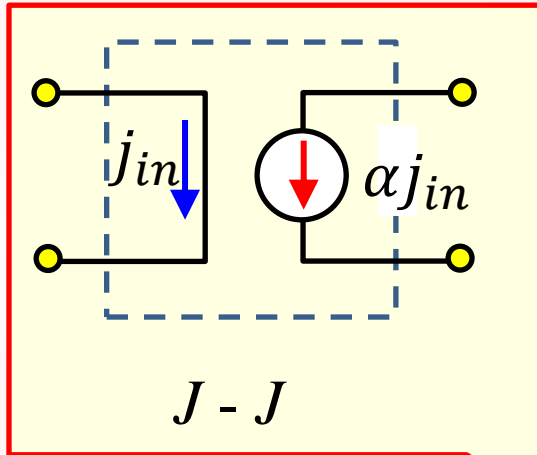

Off-diagonal: $J-V$, $V-J$

$$v_{out} = r_m j_{in}$$

$$j_{out} = g_m v_{in}$$

Transducers

r_m : trans (mutual) resistance

g_m
: trans (mutual) conductance


Diagonal: $J-J$, $V-V$

$$j_{out} = \alpha j_{in}$$

$$v_{out} = \alpha v_{in}$$

Amplifiers with gain = $|\alpha|$

Gain, and “Unit” for gain

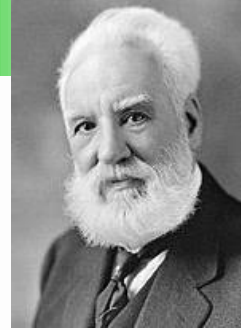

Voltage gain: $\left| \frac{v_{out}}{v_{in}} \right|$ Current gain: $\left| \frac{j_{out}}{j_{in}} \right|$ Power gain: $\left| \frac{v_{out}j_{out}}{v_{in}j_{in}} \right|$

When we say “the gain of the amplifier ...”, the gain usually means power gain.

quantity Q , unit Q_0 : Q in log scale: $L = \log_{10} \frac{Q}{Q_0}$

Alexander Graham Bell
(B, bel) 1847 - 1922

cf. deca- 10 dB : (decibel)

1/10

From: G. Bell

$$G = 10 \times \log_{10} \left(\frac{v_{out}}{v_{in}} \right)^2 = 20 \log_{10} \frac{v_{out}}{v_{in}}$$


dB units: dBm (1mW: 0dBm), dBv (1V: 0dBv), etc.

Linear response and transfer function diagram

Linear response:

$$W(s) = \Xi(s)U(s)$$


$U(s)$

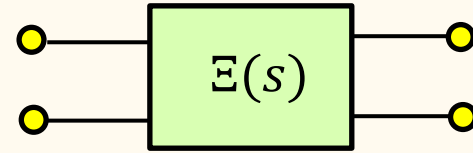


$W(s)$

Cascade connection of linear response systems:

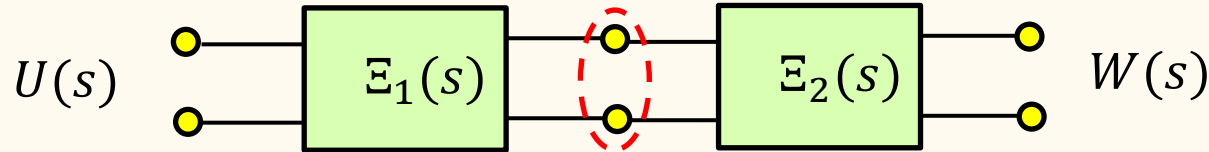
$$W(s) = \Xi_{\text{tot}}(s)U(s) = \Xi_2(s)[\Xi_1(s)U(s)] = [\Xi_2(s)\Xi_1(s)]U(s)$$



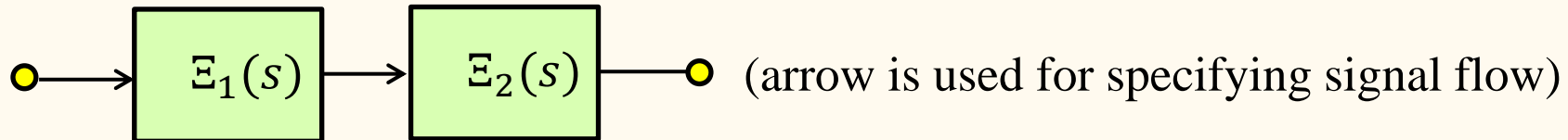Parallel lines can be expressed as a single line. Such diagram representation can be applied to any linear response system.



Feedback

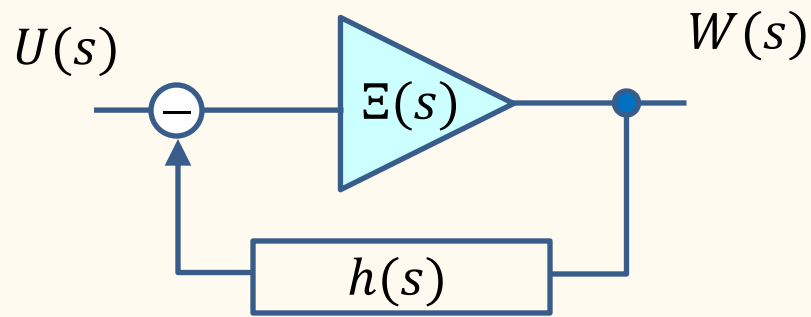


Feedforward \longleftrightarrow Feedback

$$W(s) = \Xi(s)U(s)$$


$$W(s) = \Xi(s)[U(s) - h(s)W(s)]$$

$$W(s) = \frac{\Xi(s)}{1 + \Xi(s)h(s)}U(s) \stackrel{\text{def}}{=} G(s)U(s)$$


node:

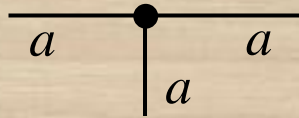

extraction:

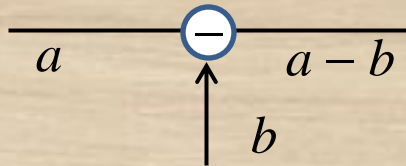

summation:

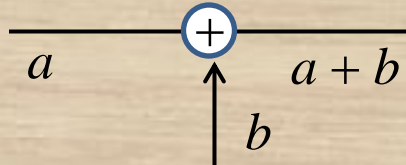

$|1 + \Xi(s)h(s)| > 1$: Negative feedback,
 < 1 : Positive feedback


Why negative feedback?

$$|\Xi(s)| \gg 1 \rightarrow G(s) \approx \frac{1}{h(s)}$$

Can be very stable, linear. Easy to calculate.

Condition for negative feedback

$|1 + \Xi(s)h(s)| > 1$: Negative feedback
 < 1 : Positive feedback

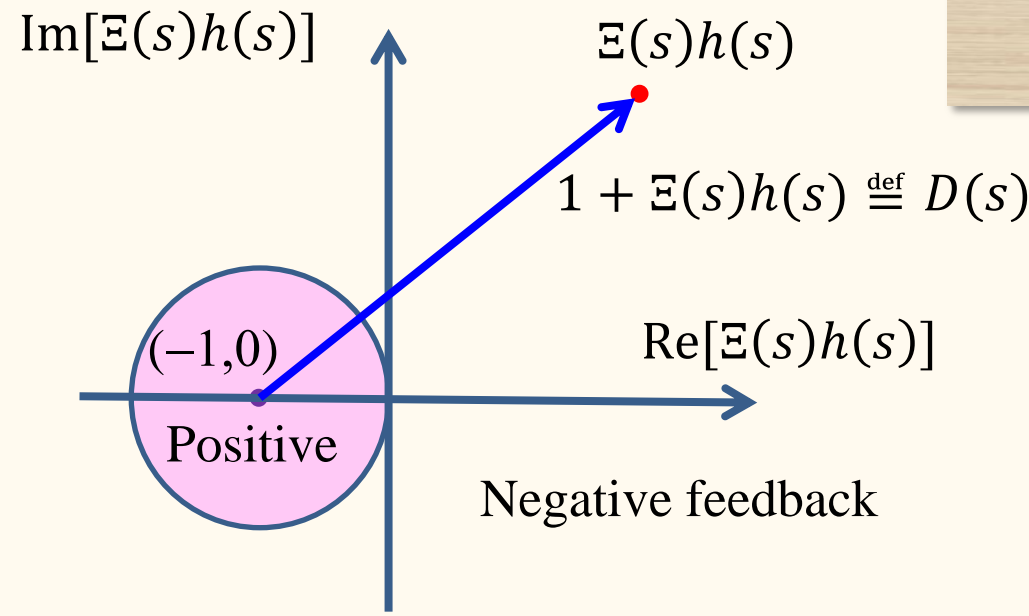

$$\begin{cases} D(s) = 0 & (\Xi(s)h(s) = -1) \\ G(s) = \infty \end{cases}$$

Output without input: oscillation point

If $\Xi(s)h(s) = -1$ has solutions, the circuit may be unstable.

How can we judge?



Criteria

(Routh-Hurwitz, **Nyquist**,
Liapunov, ...)

Stability of linear response systems with poles

Rational representation of a transfer function

$$\Xi(s) = B \frac{(s - \beta_1) \cdots (s - \beta_m)}{(s - \alpha_1) \cdots (s - \alpha_n)} \quad \{\alpha_j\} : \text{Poles}$$

Partial fraction expansion (ignore zeros)

$$\sim \frac{B_1}{s - \alpha_1} + \frac{B_2}{s - \alpha_2} + \cdots + \frac{B_n}{s - \alpha_n}$$

$$= \sum_{j=1}^n \frac{B_j}{s - s_j} \quad \{B_j\} : \text{Residues}$$

With inverse Laplace transform

$$\xi(t) = \sum_{j=1}^n B_j \exp(\alpha_j t)$$

For $\xi(t)$ to be finite with $t \rightarrow +\infty$ all the real parts of α_j should be negative.

For a linear system to be stable, all the poles of the transfer function should be in the left half of the complex plane.

Zeros and poles of $D(s)$

Assumption 1: $\Xi(s), \Xi(s)h(s)$ are stable \rightarrow Poles are on the left half plane of s .

Assumption 2: $\Xi(i\omega), \Xi(i\omega)h(i\omega) \rightarrow 0$ for $|\omega| \rightarrow \infty$ (a cut of frequency should exist)

$$\Xi(s) = \frac{Q(s)}{P(s)}, \quad h(s) = \frac{q(s)}{p(s)} : P(s), Q(s), p(s), q(s) \text{ polynomials}$$

$$\deg(P) > \deg(Q), \deg(p) \geq \deg(q)$$

$$D(s) = 1 + \Xi(s)h(s) = \frac{P(s)p(s) + Q(s)q(s)}{P(s)p(s)} \quad \begin{array}{l} P(s)p(s) \text{ should be dominant} \\ \text{in determining the order} \end{array}$$

$$D(s) = D_0 \frac{(s - \beta_1) \cdots (s - \beta_n)}{(s - \alpha_1) \cdots (s - \alpha_n)} \quad \begin{array}{l} \text{The same order} \end{array}$$

The numerator and the denominator are in the same order in s .

Zeros and poles of $D(s)$

$$D(s) = D_0 \frac{(s - \beta_1) \cdots (s - \beta_n)}{(s - \alpha_1) \cdots (s - \alpha_n)}$$


$\{\beta_i\}$: Zeros of $D(s)$ \rightarrow Poles of $G(s)$

Then we say that $\exists \beta_i \in$ right half plane of $s \rightarrow$ The circuit is unstable.


Taking the argument we write:

$$\arg(D) = \sum_{i=1}^n \arg(s - \beta_i) - \sum_{i=1}^n \arg(s - \alpha_i)$$

Left half plane

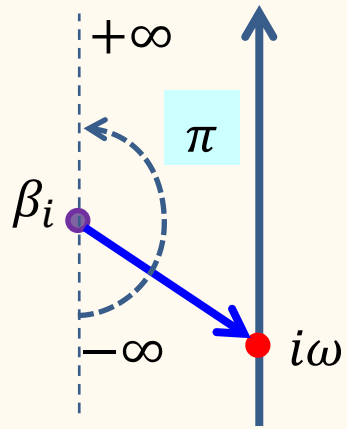

Right half plane

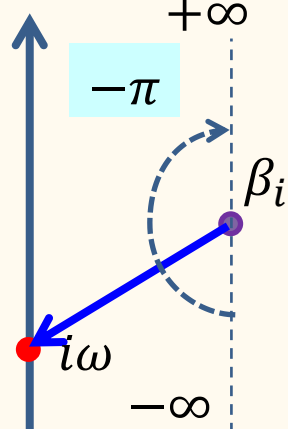

Imagine you are on the imaginary axis $s = i\omega$.
And $\omega: -\infty \rightarrow +\infty$.


Number of zeros on the right half plane: m
All the poles should be on the left plane
from the assumption 1.

$$\Delta \arg(D) = (n - m)\pi - m\pi - n\pi = -2m\pi$$


Nyquist plot and criterion



Harry Nyquist
(1889–1976)

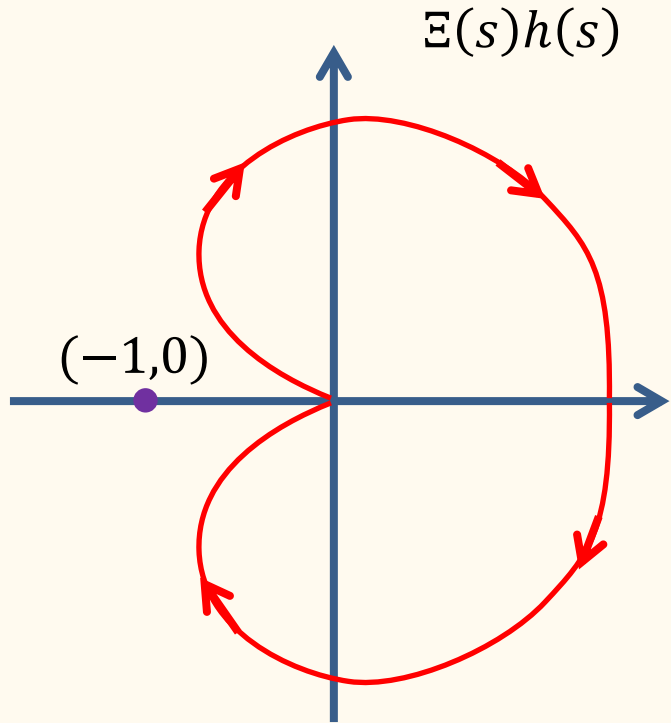


$\Delta \arg(D) = 0$
Stable

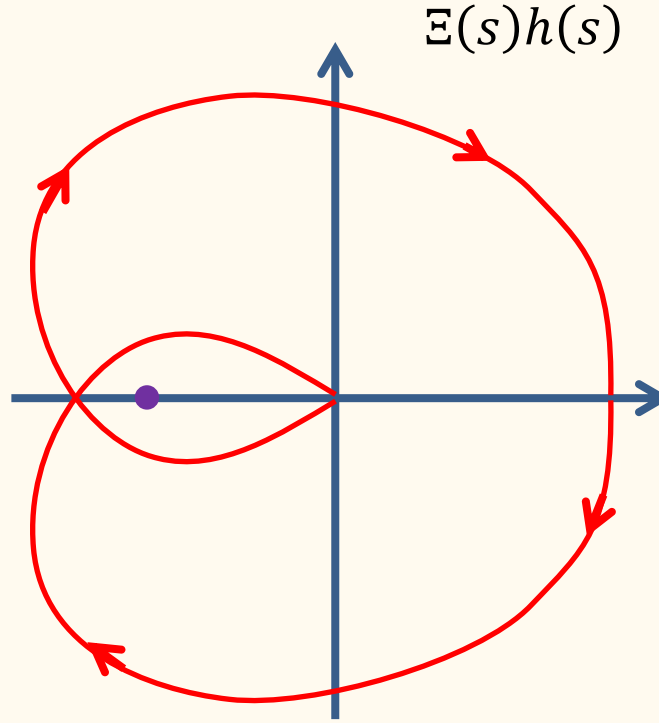


$\Delta \arg(D) = -4\pi$
Unstable

Operational amplifier (OP amp.)

circuit symbol

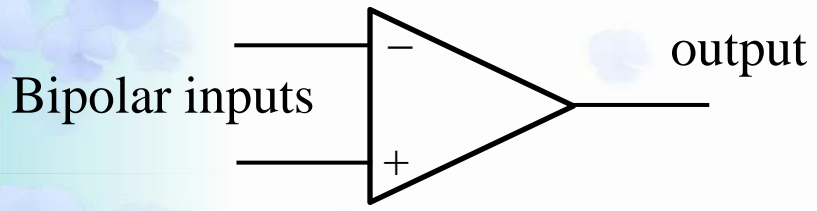

can be used for both

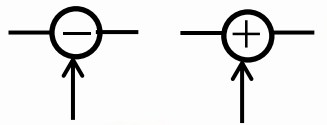


- Differential amplifier
- Input impedance $\sim \infty$
- Open loop gain $A_o \gg 1$
- Output resistance ≈ 0

$$V_{out} = A_o(V_+ - V_-)$$

$$A_o \gg 1 \therefore \underline{V_- \approx V_+ = 0}$$

Virtual short circuit

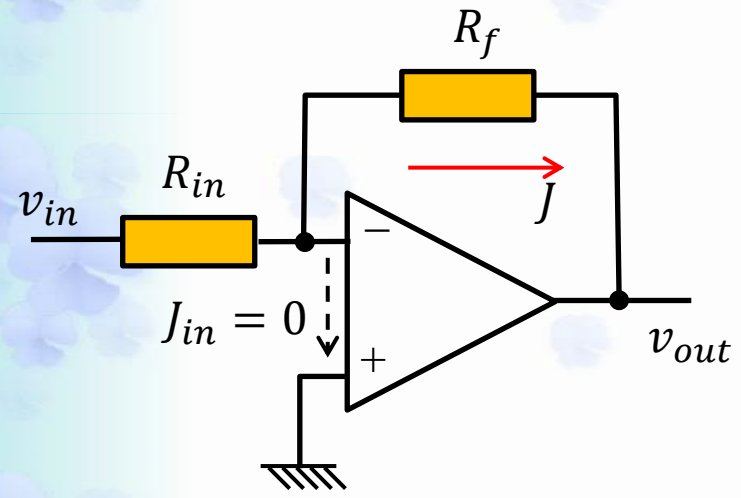

$$J = -\frac{v_{out}}{R_f} = \frac{v_{in}}{R_{in}}$$

$$\therefore v_{out} = -\frac{R_f}{R_{in}} v_{in} \quad \text{Inverting amplifier}$$


OP amp. packages




(a)




(b)

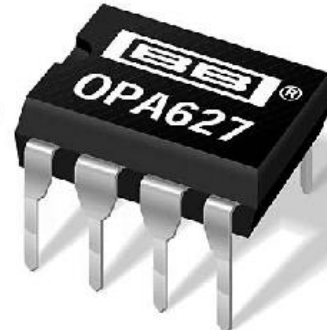

(c)

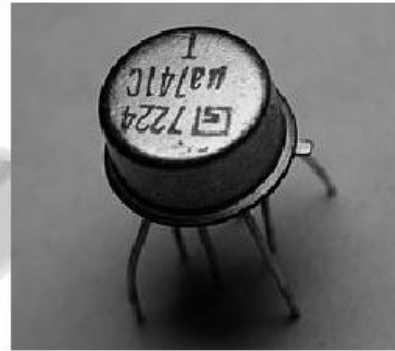


(d)

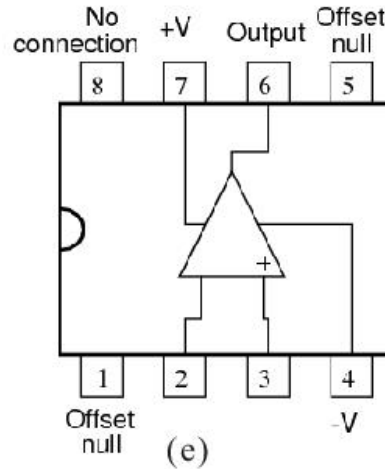


(e)

Various applications of OP amps

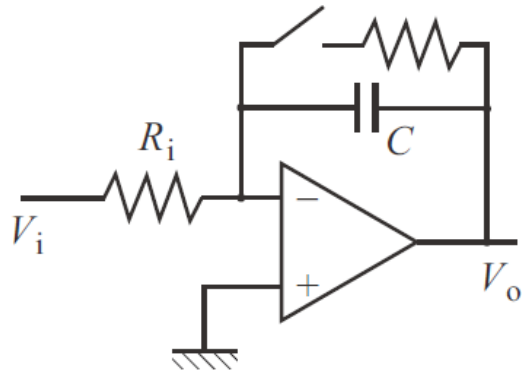
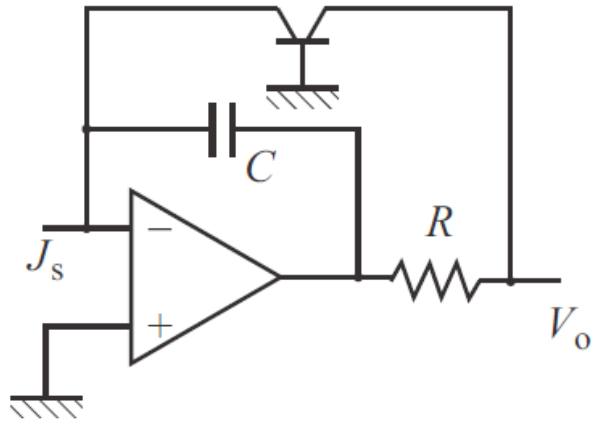
$$V_{\text{out}}(t) = -\frac{Q}{C} = -\frac{1}{C} \int_0^t \frac{V_i(\tau)}{R_i} d\tau \quad \text{Integration circuit}$$
$$= -\frac{1}{CR_i} \int_0^t V_i(\tau) d\tau$$



$$V_{\text{out}} = -V_{\text{BE}} = -\frac{k_B T}{e} \ln \left(\frac{J_s}{J_0} + 1 \right)$$

Logarithmic amplifier

Amplifiers with specialized function




Low Cost, DC to 500 MHz, 92 dB
Logarithmic Amplifier


Data Sheet

AD8307

Logarithmic amplifier

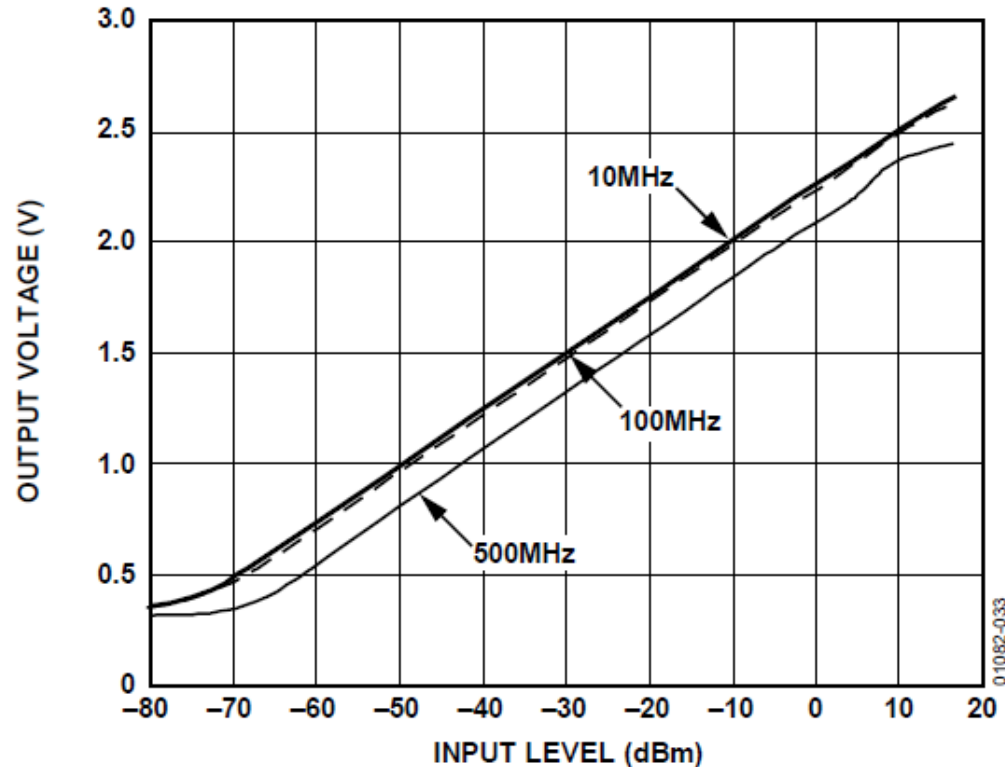

Voltage follower

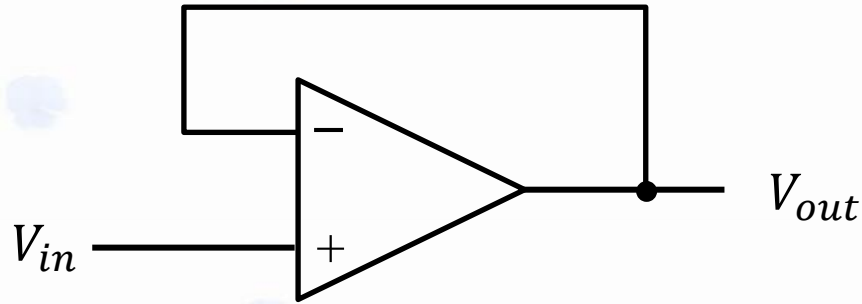


From virtual shortage, simply $V_{out} = V_{in}$

Very high input impedance, very low output impedance.



Impedance transformer

Instrumentation amplifier

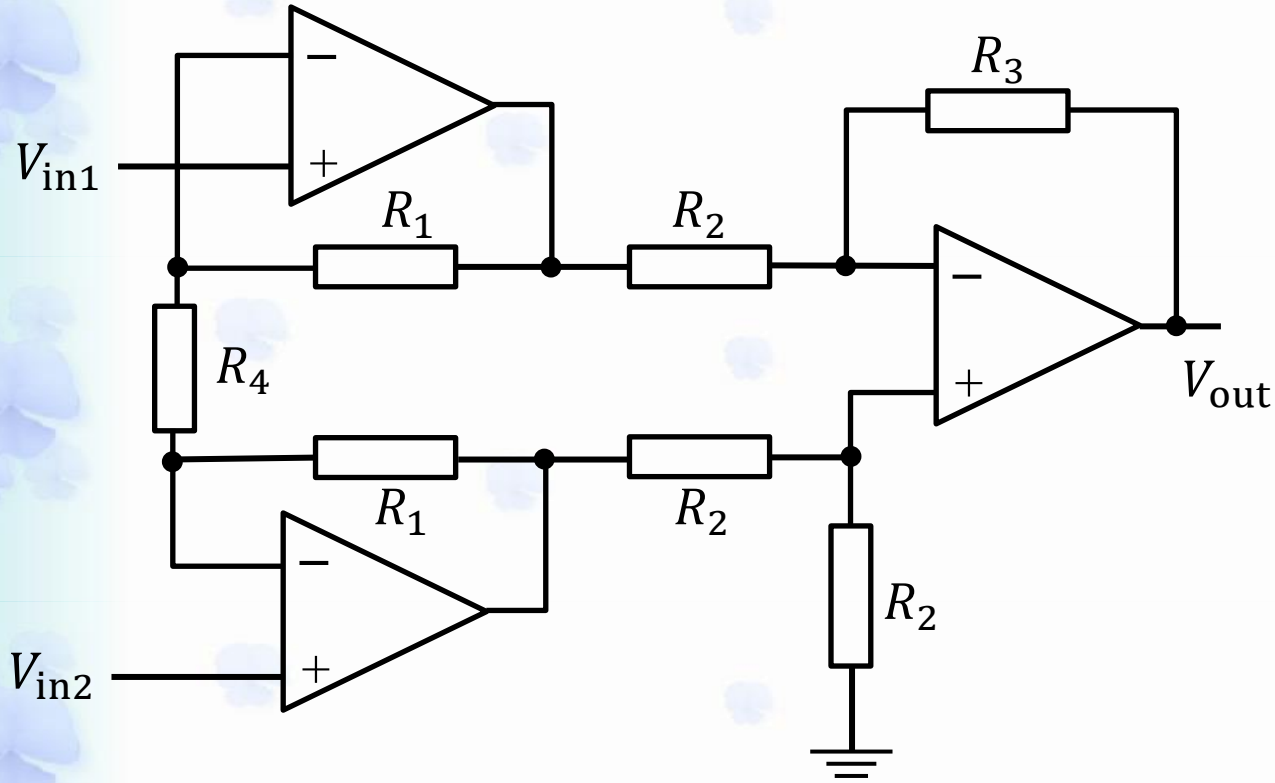


$$V_{out} = -\frac{R_3}{R_2} \frac{2R_1 + R_4}{R_4} (V_{in1} - V_{in2})$$

Instrumentation amplifier



INA114

Precision INSTRUMENTATION AMPLIFIER

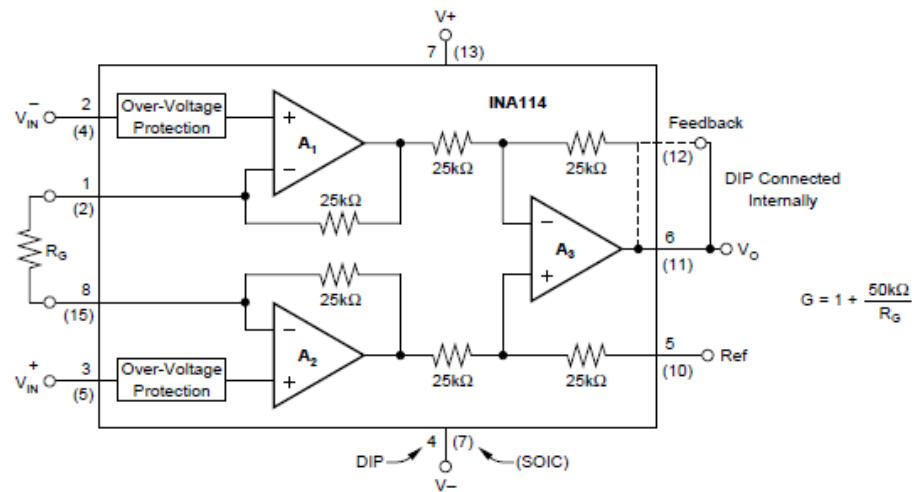



Ultralow Offset Voltage Operational Amplifier

Data Sheet

OP07

FEATURES

- Low V_{os} : 75 μV maximum
- Low V_{os} drift: 1.3 $\mu\text{V}/^\circ\text{C}$ maximum
- Ultrastable vs. time: 1.5 μV per month maximum
- Low noise: 0.6 μV p-p maximum
- Wide input voltage range: $\pm 14\text{ V}$ typical
- Wide supply voltage range: $\pm 3\text{ V}$ to $\pm 18\text{ V}$
- 125 $^\circ\text{C}$ temperature-tested dice

PIN CONFIGURATION


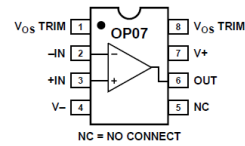


Figure 1.

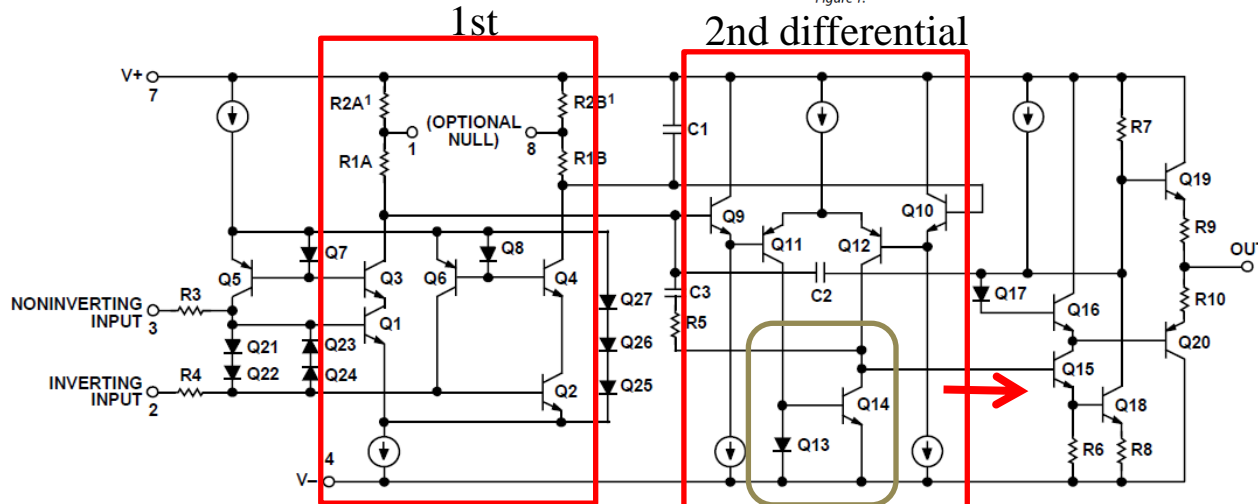


¹R2A AND R2B ARE ELECTRONICALLY ADJUSTED ON CHIP AT FACTORY FOR MINIMUM INPUT OFFSET VOLTAGE.

Figure 2. Simplified Schematic


Parameters

Parameter	Symbol	Conditions	Min	Typ	Max	Unit
INPUT CHARACTERISTICS						
T_A = 25°C						
Input Offset Voltage ¹	V _{OS}			60	150	μV
Long-Term V _{OS} Stability ²	V _{OS} /Time			0.4	2.0	μV/Month
Input Offset Current	I _{OS}			0.8	6.0	nA
Input Bias Current	I _B			±1.8	±7.0	nA
Input Noise Voltage	e _n p-p	0.1 Hz to 10 Hz ³		0.38	0.65	μV p-p
Input Noise Voltage Density	e _n	f ₀ = 10 Hz		10.5	20.0	nV/√Hz
		f ₀ = 100 Hz ³		10.2	13.5	nV/√Hz
		f ₀ = 1 kHz		9.8	11.5	nV/√Hz
Input Noise Current	I _n p-p			15	35	pA p-p
Input Noise Current Density	I _n	f ₀ = 10 Hz		0.35	0.90	pA/√Hz
		f ₀ = 100 Hz ³		0.15	0.27	pA/√Hz
		f ₀ = 1 kHz		0.13	0.18	pA/√Hz
Input Resistance, Differential Mode ⁴	R _{IN}		8	33		MΩ
Input Resistance, Common Mode	R _{INCM}			120		GΩ


Common mode rejection ratio
(CMRR)

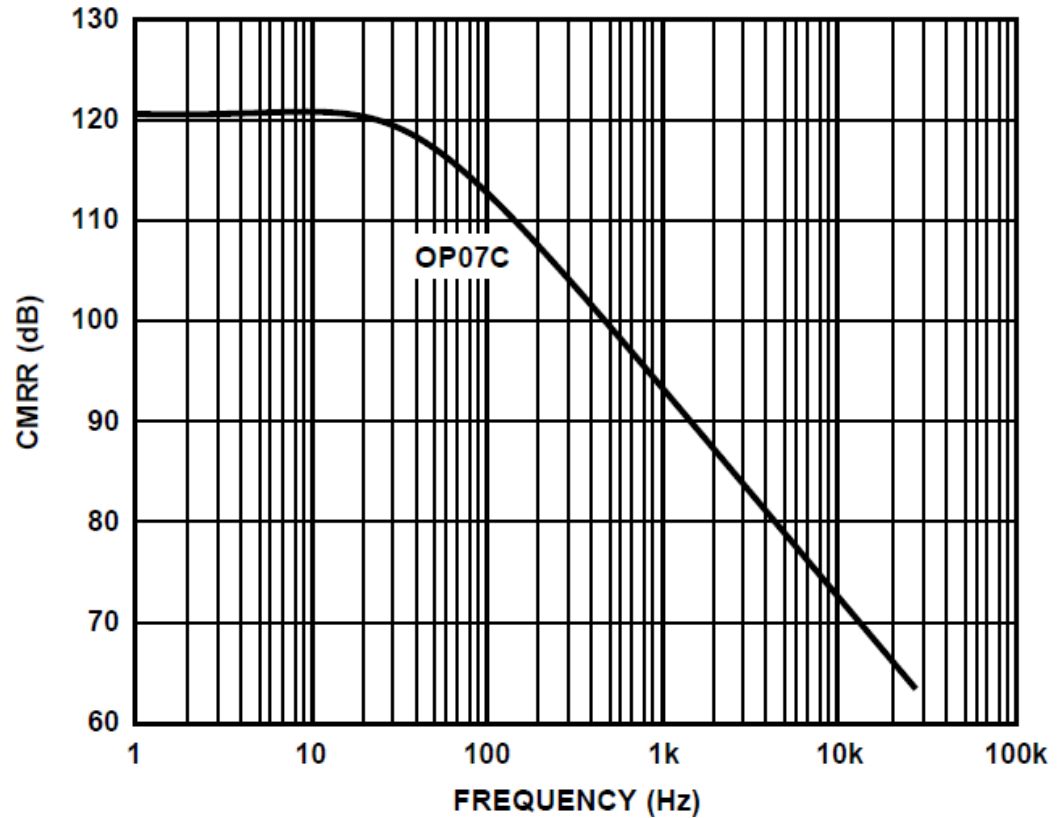

OP amp. data sheet

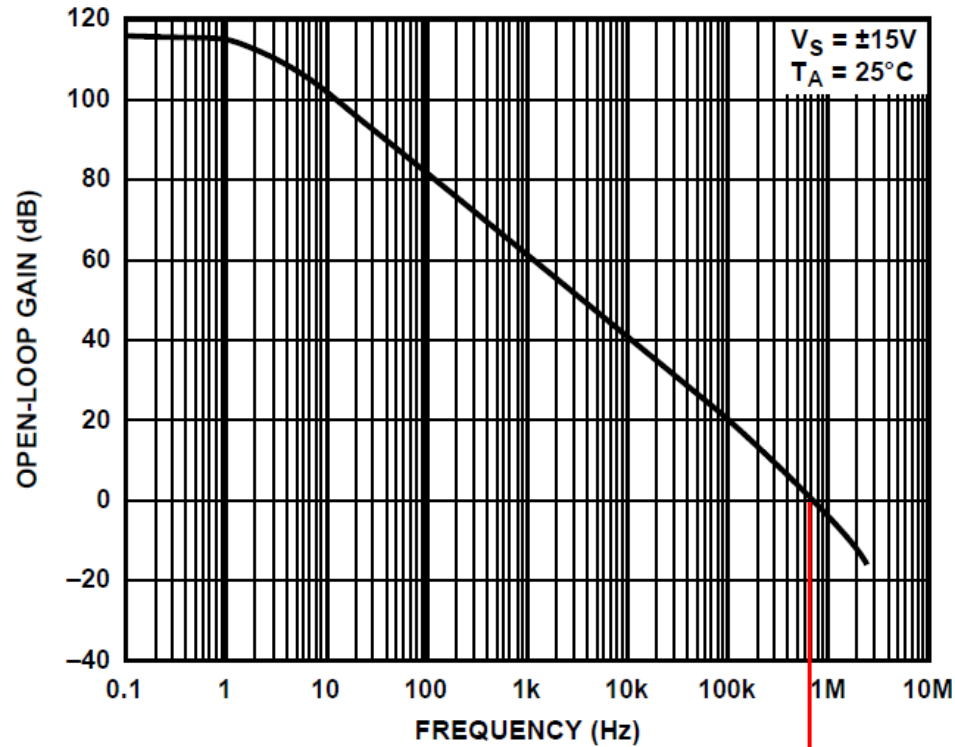


Unity gain frequency

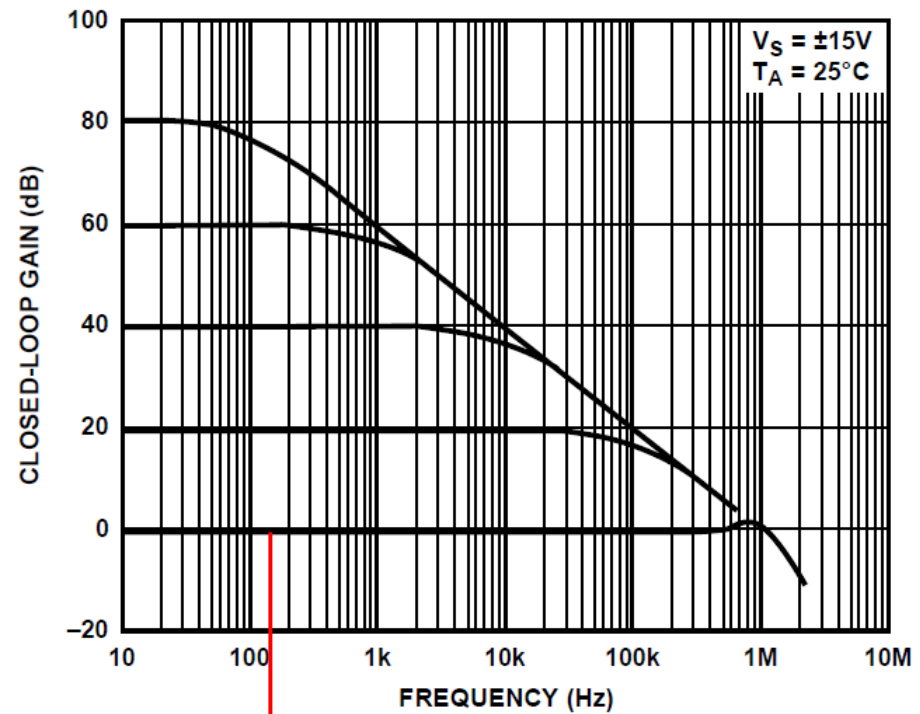


Voltage follower

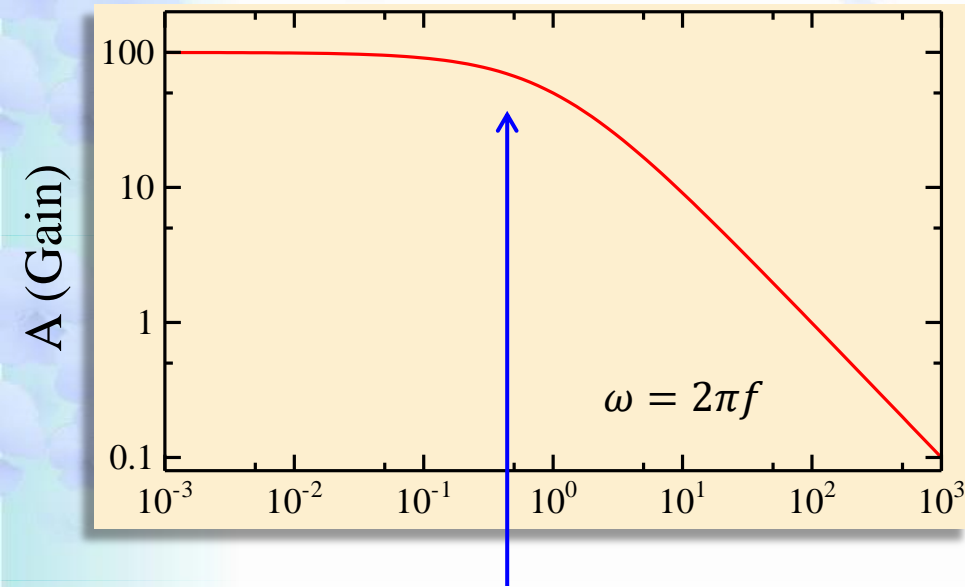Frequency dependent characteristics of OP amps




Cut-off frequency $\omega_T = 2\pi f_T$

Phase rotates by $\pi/2$

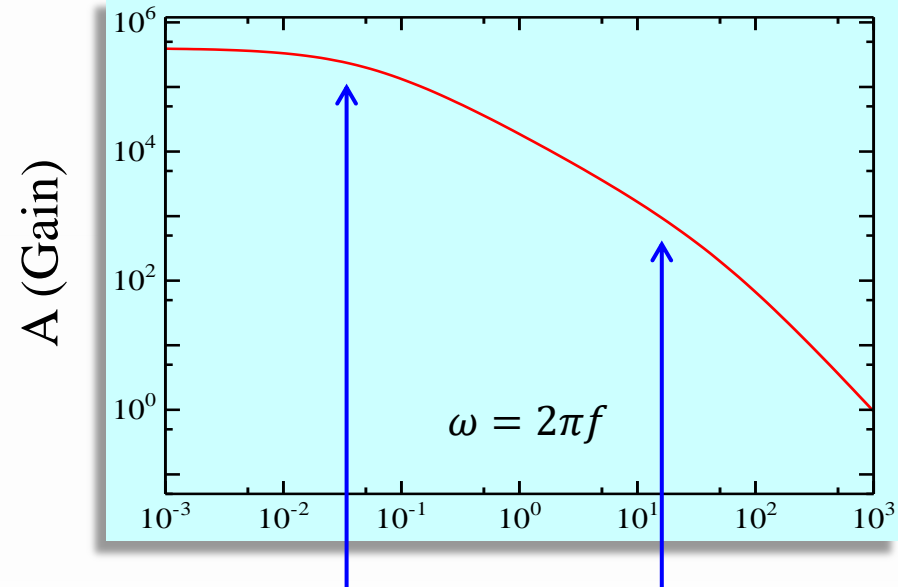

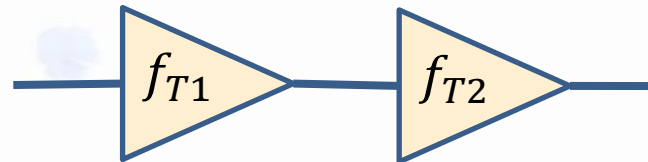
Multiple cut-off frequency:
Phase rotates more than π



If gain is larger than 1 at
phase shift π :

Dangerous!



Phase compensation

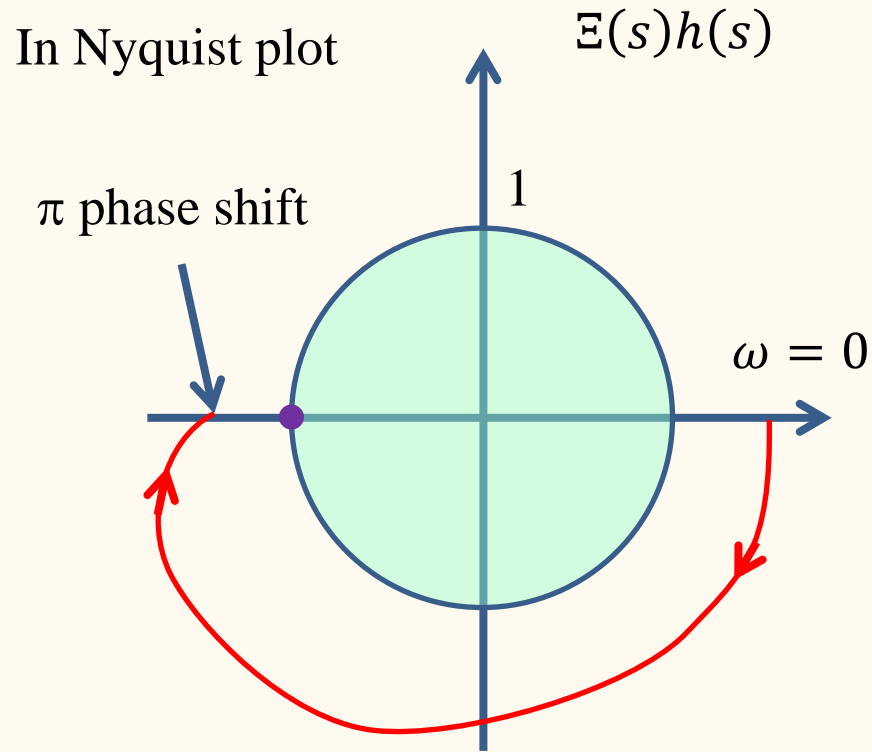



Why dangerous?

π phase shift: negative feedback \rightarrow
positive feedback



Phase compensation

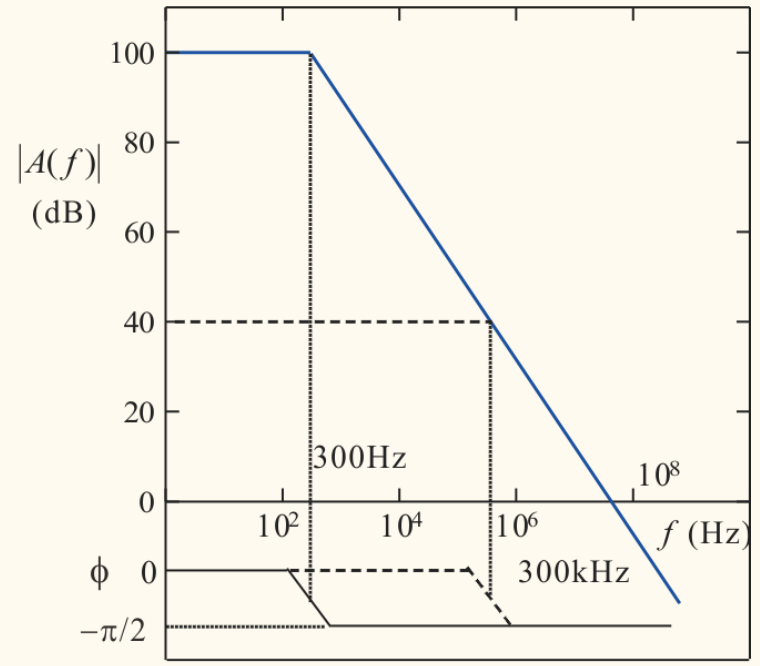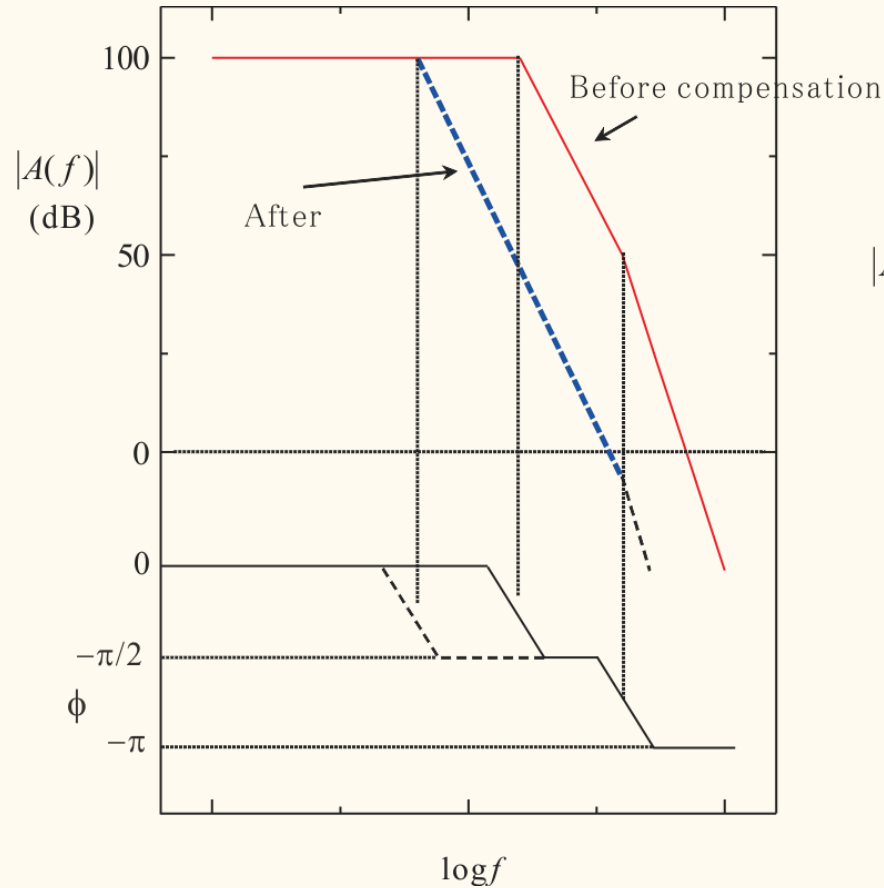


Phase compensation

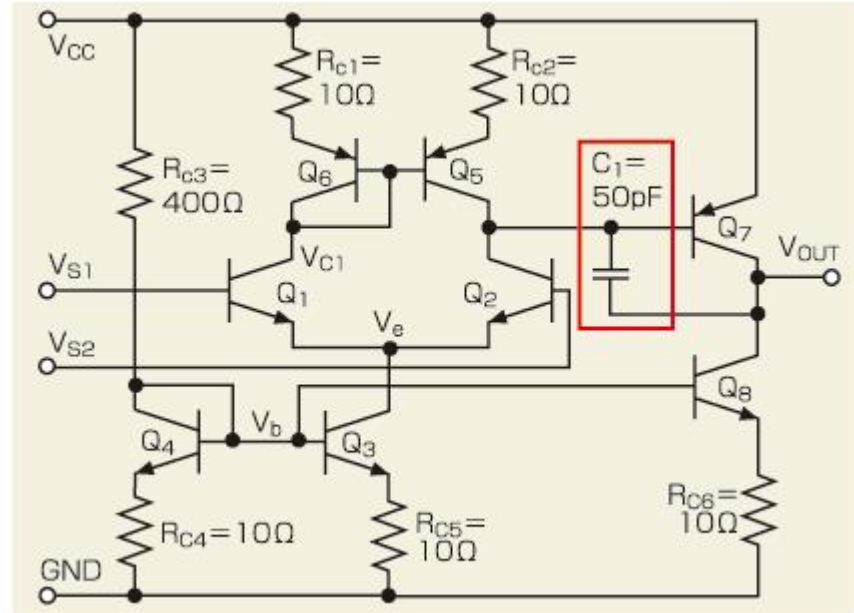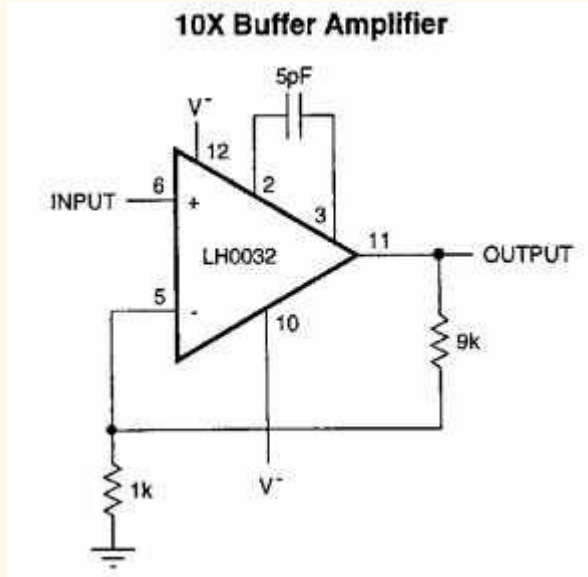

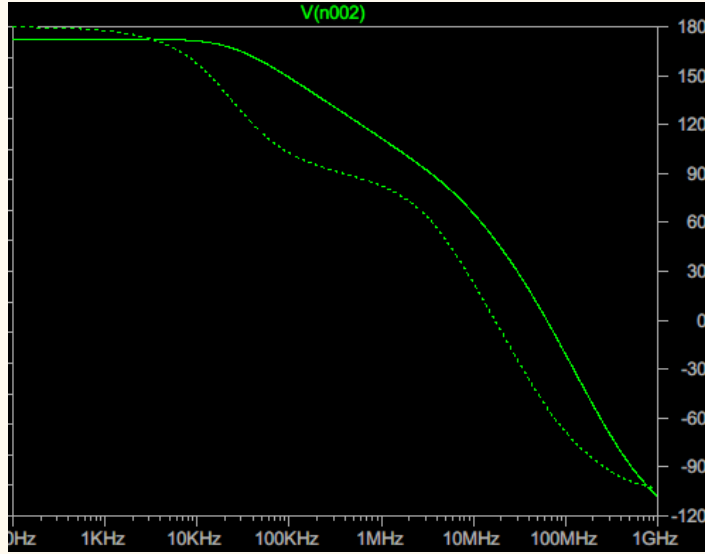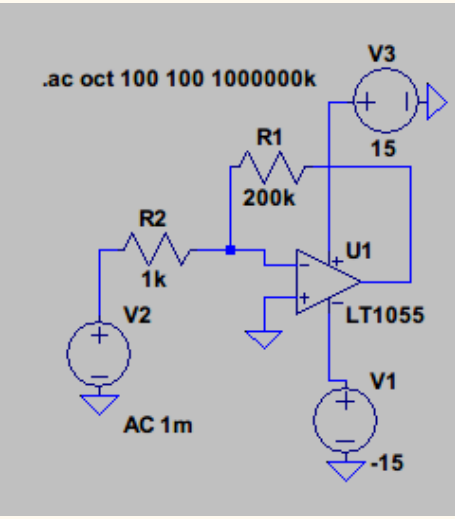Inverting amplifier and cut-off frequency (LT Spice simulation)




$$A = 200 \quad f_T = 30\text{kHz}$$

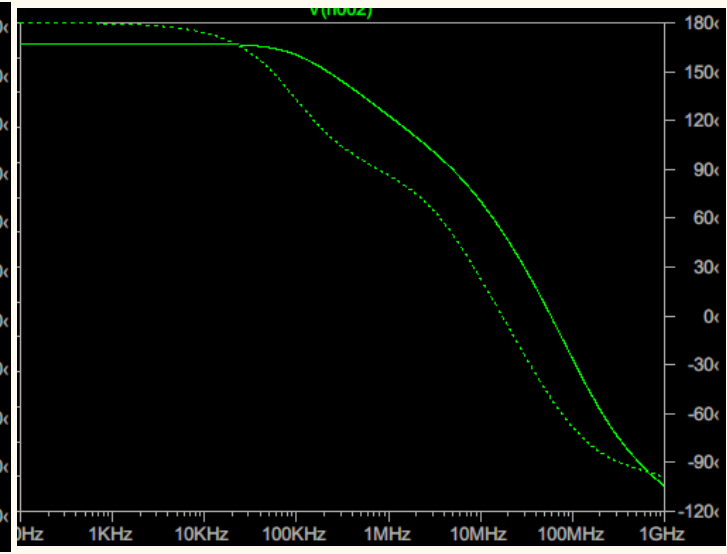


$$A = 50 \quad f_T = 90\text{kHz}$$

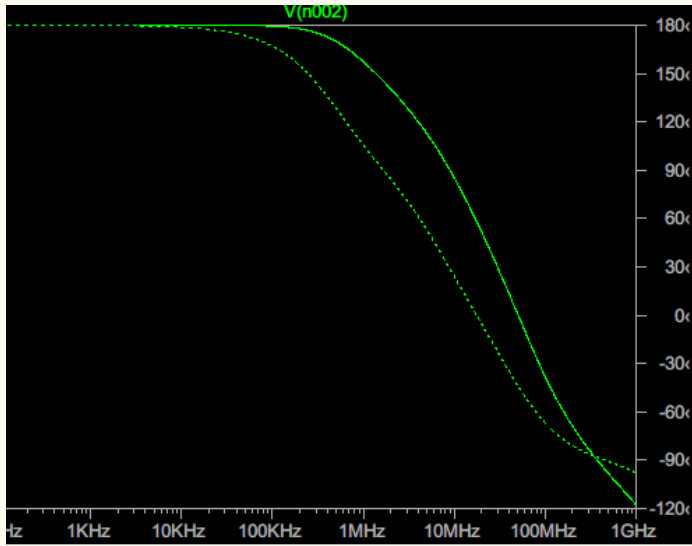Inverting amplifier and cut-off frequency (LT Spice simulation)






$$A = 10 \quad f_T = 300\text{kHz}$$

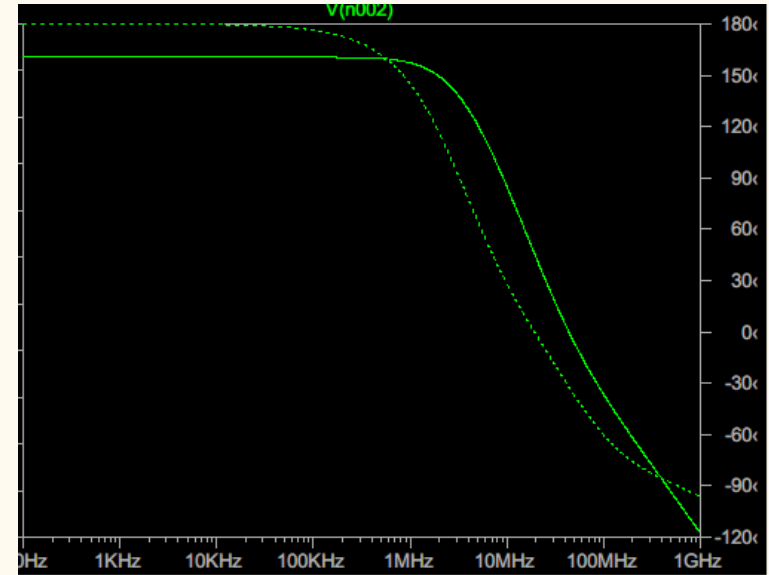


$$A = 2 \quad f_T = 2\text{MHz}$$


Oscillation in an OP amp. circuit

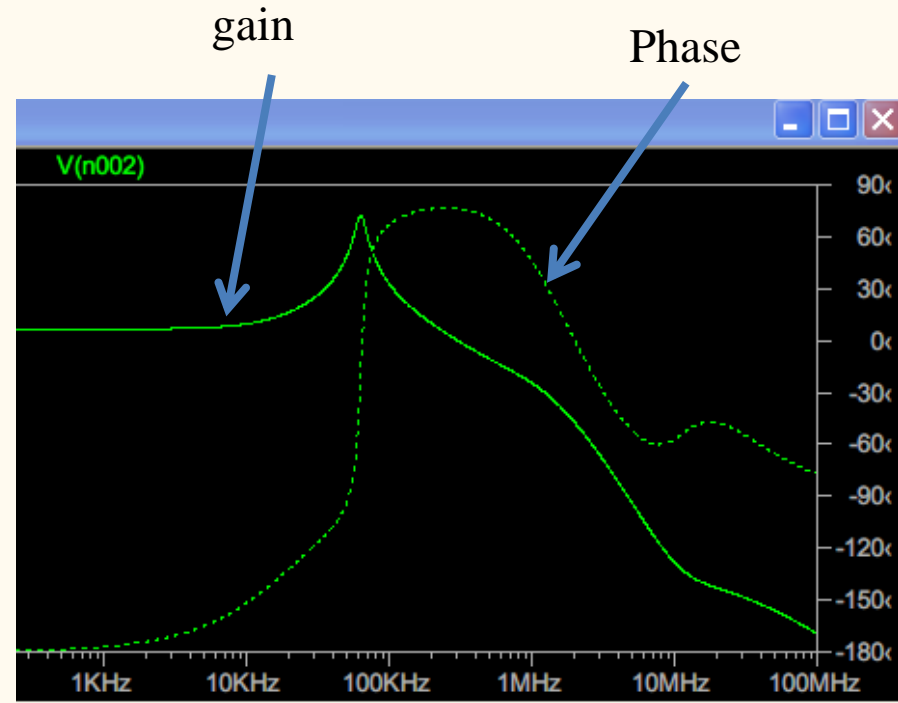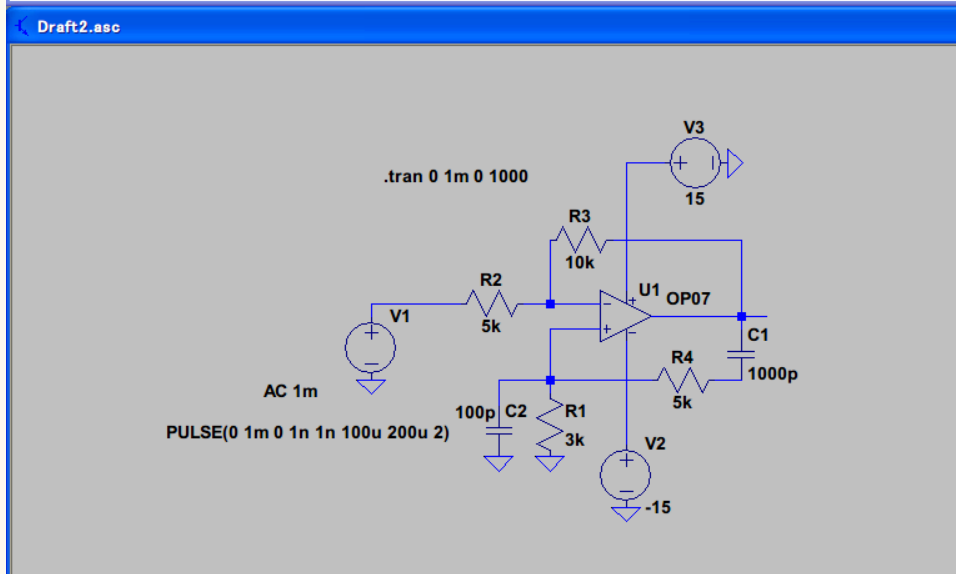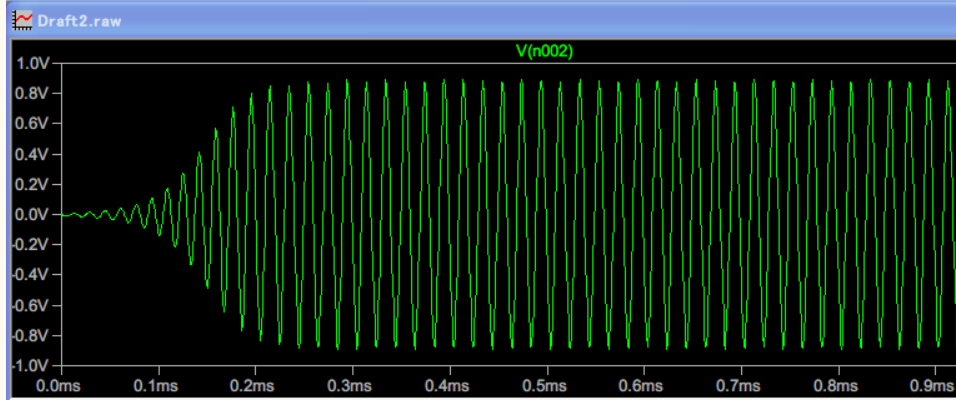

Use of OP amps at saturation voltages

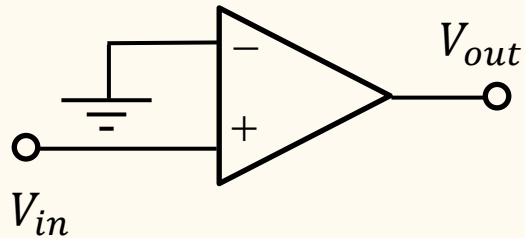


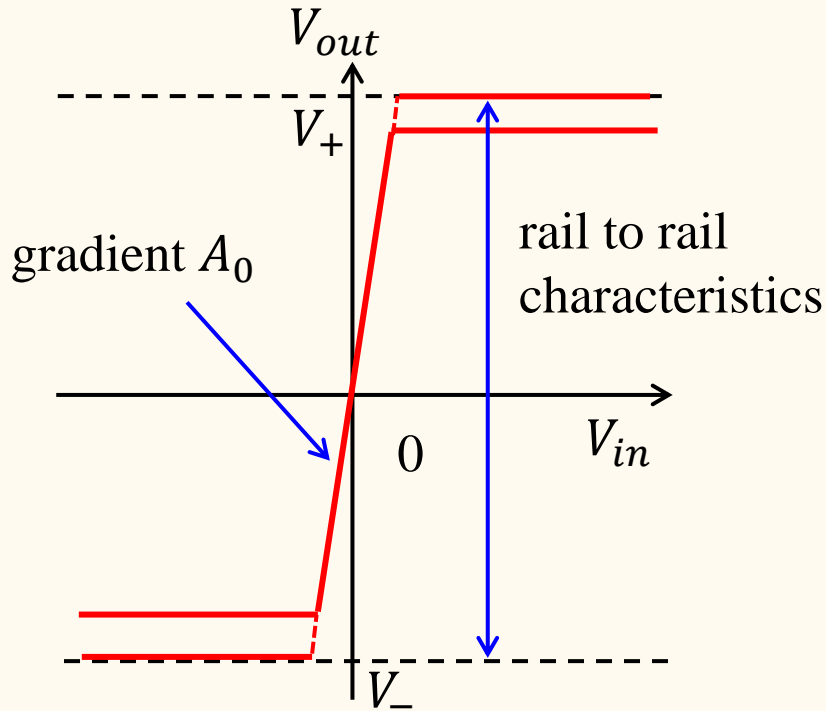Positive feedback is applied. V_{out} goes up to the highest voltage which the OP amp can reach for positive V_{in} .




Compare V_{in} with 0

Comparator

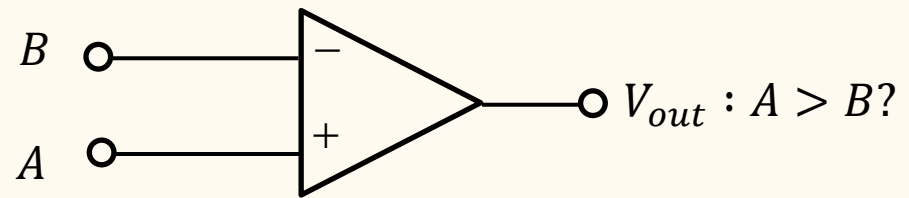

Hurwitz criterion (no proof)

Adolf Hurwitz
1859 - 1919

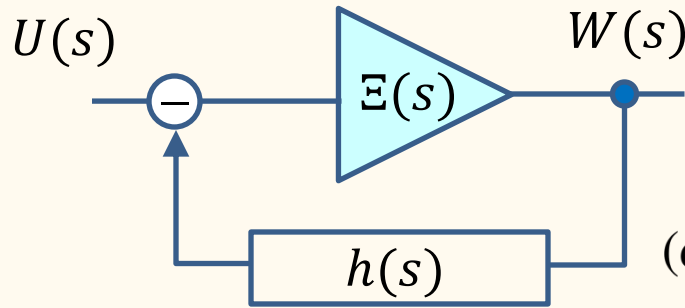

$$G(s) = \frac{\Xi(s)}{1 + h(s)\Xi(s)}$$

Pole equation:

$$\begin{aligned} \text{(denominator)} &= a_n s^n + a_{n-1} s^{n-1} + \dots + a_0 \\ &= a_n (s - p_1) \dots (s - p_n) = 0 \end{aligned}$$

$$\forall j = 0, 1, \dots, n : a_j > 0 \text{ (or } < 0)$$

Otherwise the system is unstable (no proof is given here).

Then we assume all $a_j > 0$.

Define Hurwitz matrix

$n \times n$

n is even (poles are paired).

$$H = \begin{pmatrix} a_{n-1} & a_{n-3} & a_{n-5} & \dots & 0 \\ a_n & a_{n-2} & a_{n-4} & \dots & 0 \\ 0 & a_{n-1} & a_{n-3} & \dots & 0 \\ 0 & a_n & a_{n-2} & \dots & 0 \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & a_0 \end{pmatrix}$$

Hurwitz criterion (no proof)

Hurwitz determinants $H_j \equiv |H[1, \dots, j; 1, \dots, j]|$

$$H_1 = a_{n-1}, \quad H_2 = \begin{vmatrix} a_{n-1} & a_{n-3} \\ a_n & a_{n-2} \end{vmatrix}, \quad H_3 = \begin{vmatrix} a_{n-1} & a_{n-3} & a_{n-5} \\ a_n & a_{n-2} & a_{n-4} \\ 0 & a_{n-1} & a_{n-3} \end{vmatrix}, \dots$$

Hurwitz criterion

$$H_j > 0 \quad (j = 2, \dots, n-1)$$

$H_1, H_n > 0$ is trivial from the assumption.

Another expression:

Divide the denominator to odd and even parts $O(s)$ and $E(s)$.
If the zeros of $O(s)$ and $E(s)$ are aligned on the imaginary axis alternatively, the system is stable.



A series of horizontal dashed lines spanning the width of the page, intended for writing or text entry. The lines are evenly spaced and extend across the central area of the document.

