



電子回路論第6回

Electric Circuits for Physicists #6

東京大学理学部・理学系研究科  
物性研究所  
勝本信吾

Shingo Katsumoto








<https://www.energymanagertoday.com/bell-labs-reinvented-energy-efficient-complex-0169126/>

# Bell labs is reinvented as an energy efficient complex

## Outline

Supplements to feedback circuit and system control


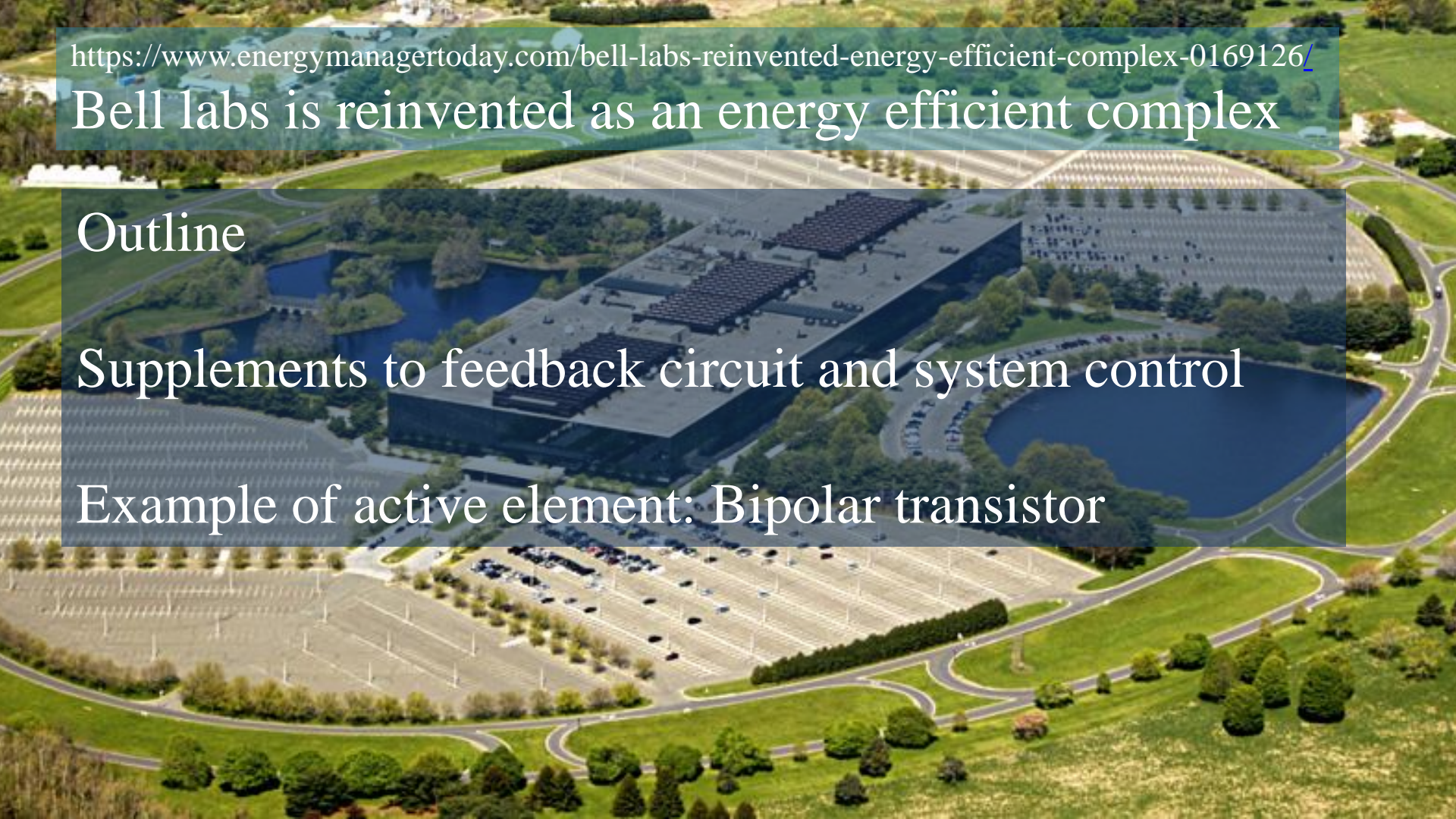
Example of active element: Bipolar transistor


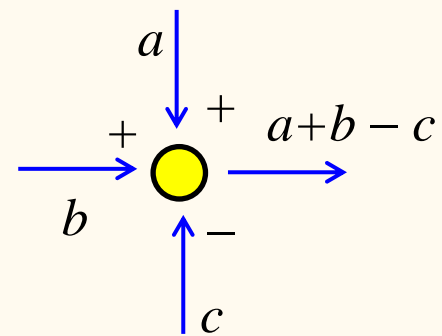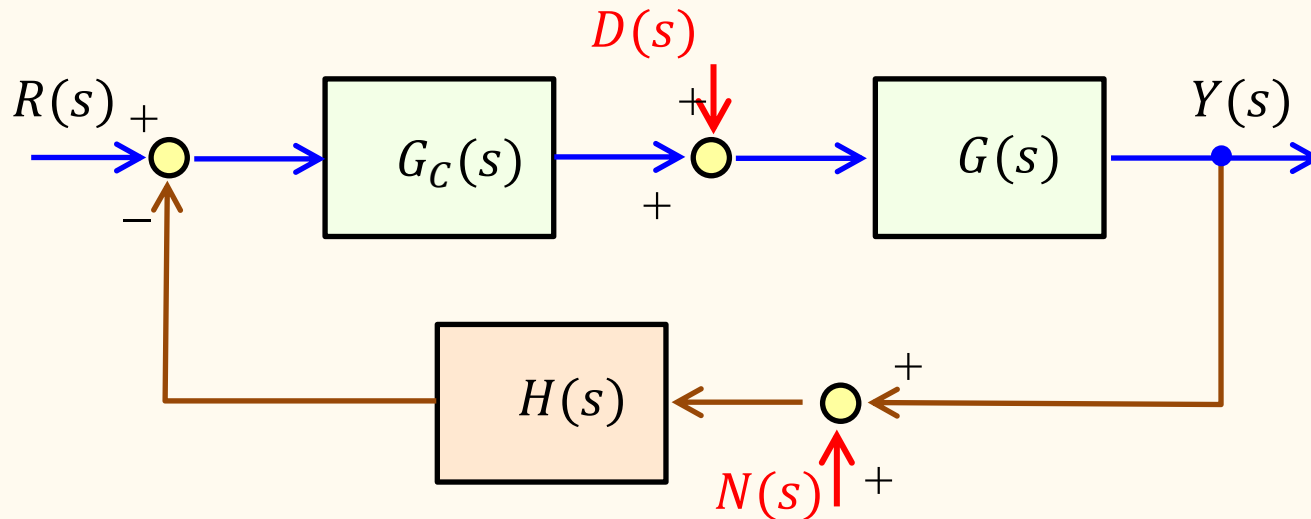
# Disturbance and noise on feedback circuits

Circuit treatment of fluctuations:

- Prepare external power sources
- Express them as transfer functions




$$Y(s) = \frac{G(s)}{F(s)} [G_C(s)R(s) + D(s) + G_C(s)H(s)N(s)]$$

$$F(s) \equiv 1 + G_C(s)G(s)H(s)$$
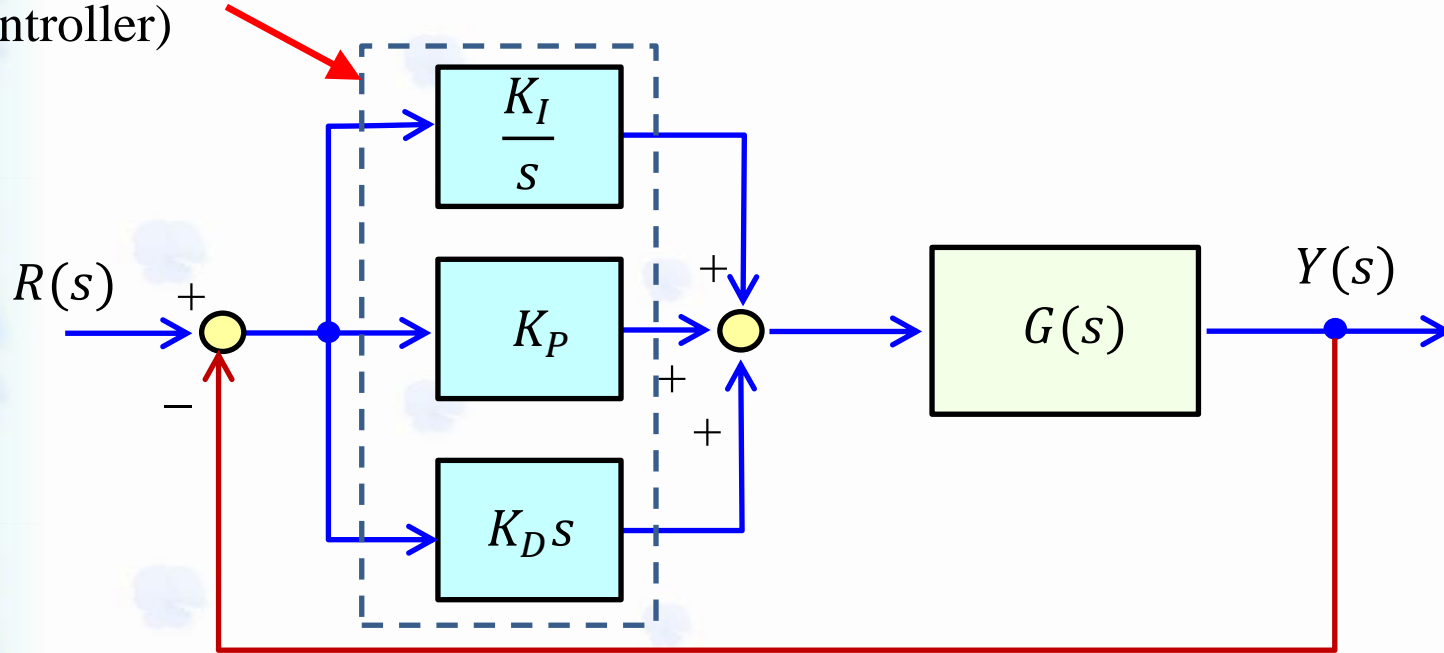
# PID control

Compensator  
(controller)

P: proportional, I: integral, D: derivative



$$G_c(s) = K_p + \frac{K_I}{s} + K_D s$$




# PID controllers

OMRON



- E5GC  
ねじ端子台タイプ  
スクリューレス  
クランプ端子台タイプ  
48×24mm
- E5CC  
ねじ端子台タイプ  
48×48mm
- E5EC  
ねじ端子台タイプ  
48×96mm
- E5AC  
ねじ端子台タイプ  
96×96mm

invensys  
EUROTHERM

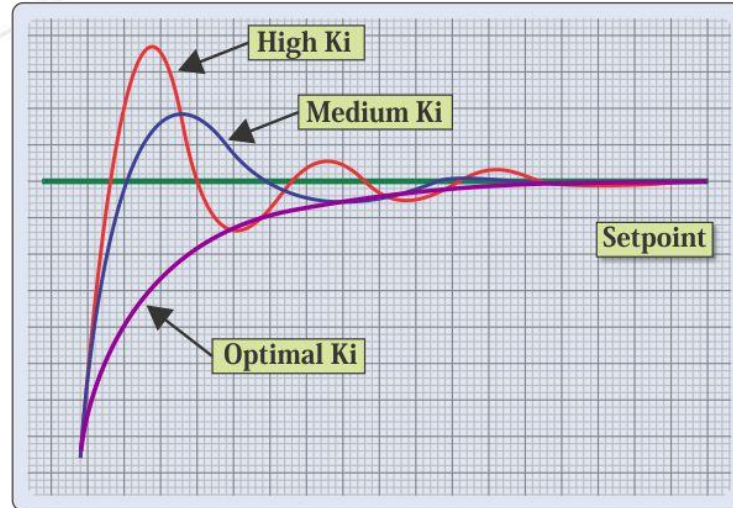



## 4.4 Example of active element: Transistors





John Bardeen, William Shockley,  
Walter Brattain 1948 Bell Labs.

Two types of transistors



Bipolar junction transistor

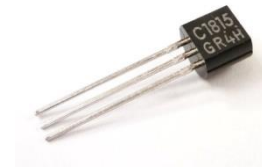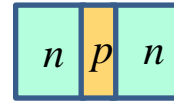

Field effect transistor

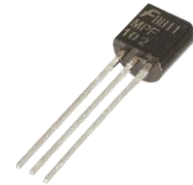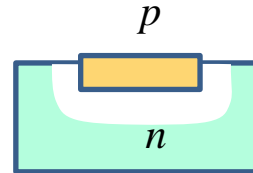


# Three types of semiconductors

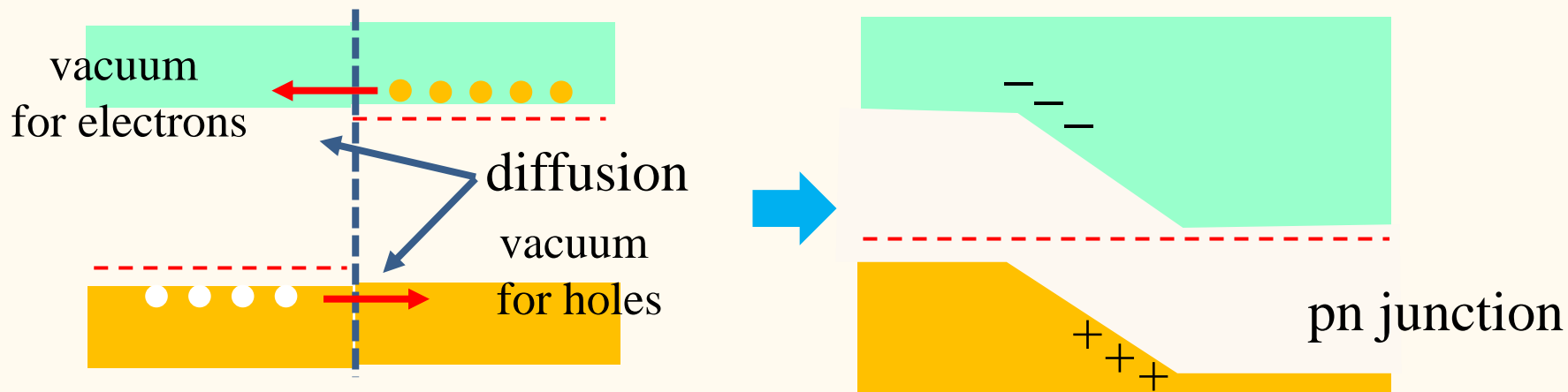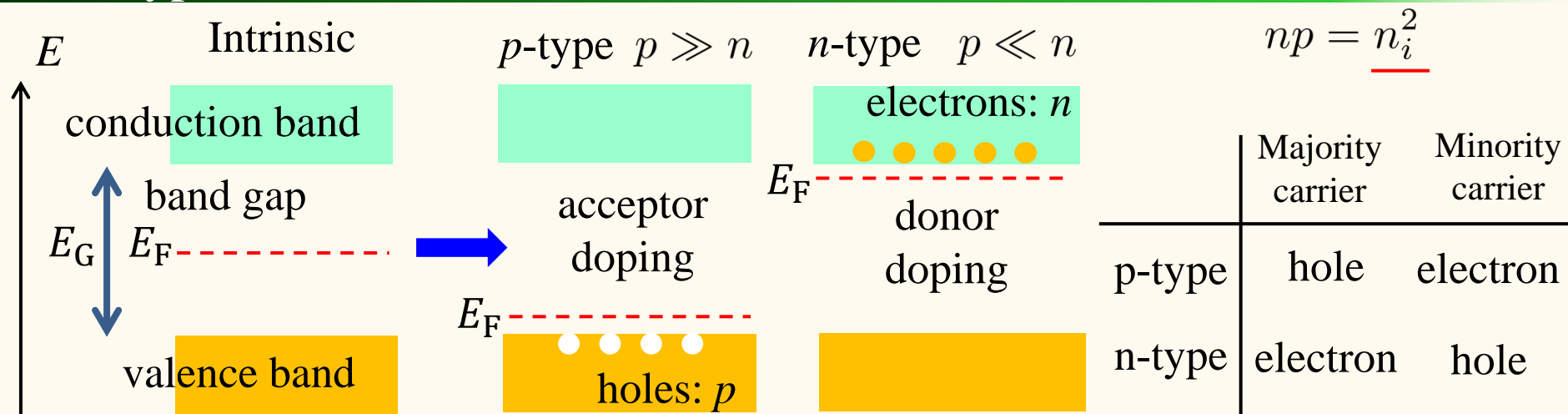



# *pn* junction thermodynamics

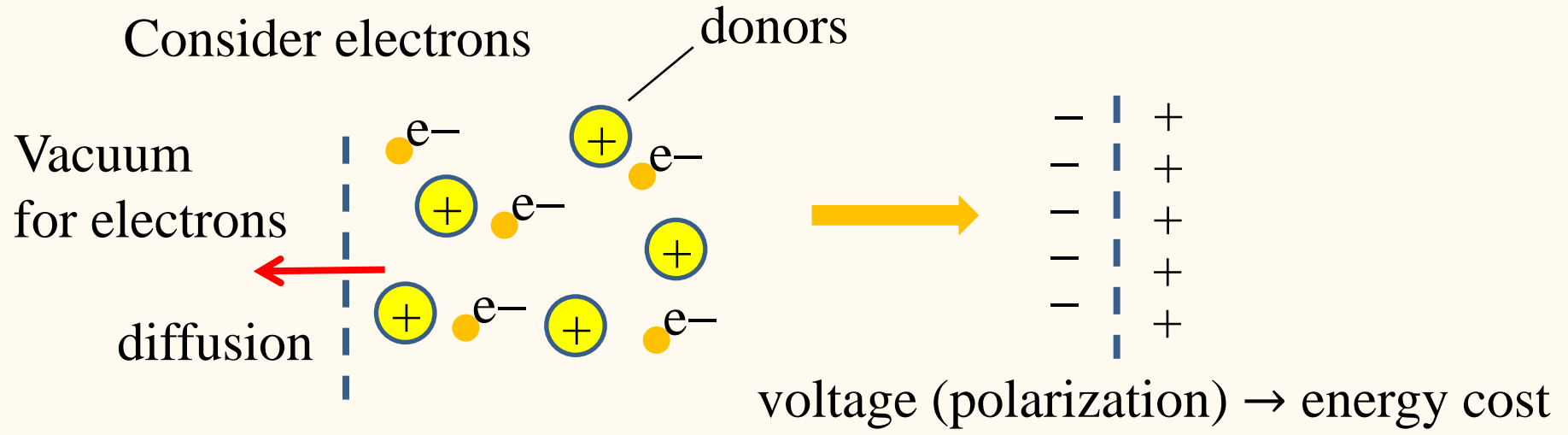

Helmholtz free energy:

$$F = U - TS$$

Voltage (internal energy cost)

Diffusion (entropy)

Minimization of  $F$  → Built-in (diffusion) voltage  $V_{bi}$

# Two kinds of “current” in semiconductors


$$F = U - TS$$

$U$  → drift current,  $-TS$  → diffusion current

**Drift current:** Motive force (electric field) gives rise to non-uniformity in the momentum space.

$$-e\mathbf{E} \cdot \frac{\partial f}{\partial \mathbf{p}} = -\frac{f - f_0}{\tau(\mathbf{p})}$$

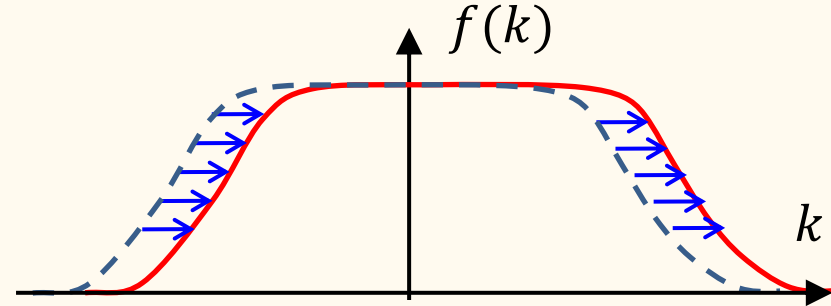**Diffusion current:** There are some origins (particle sink/source) to cause non-uniformity in the real space (spatial density), which causes flow of charges.




$f$ : distribution function in phase space

$$\frac{\mathbf{p}}{m} \cdot \frac{\partial f}{\partial \mathbf{r}}$$

$$\mathbf{j} = -eD \frac{\partial \rho(\mathbf{r})}{\partial \mathbf{r}}$$

$D$ : diffusion constant
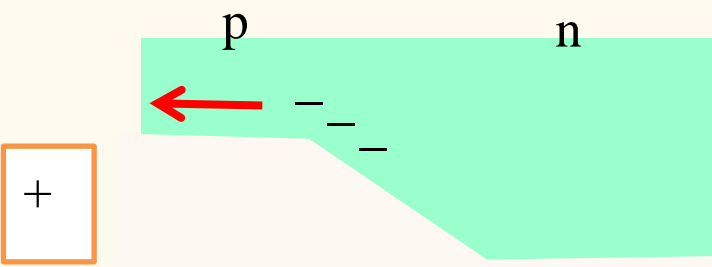
# 4.4.1 I-V characteristics of pn junctions




Forward bias

overcomes  $V_{bi}$


- : go

Shockley theory
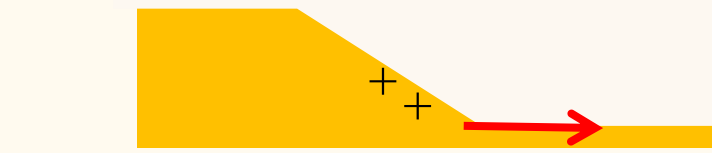
$$J = J_0 \left[ \exp \left( \frac{eV}{k_B T} \right) - 1 \right]$$




Minority carrier injection

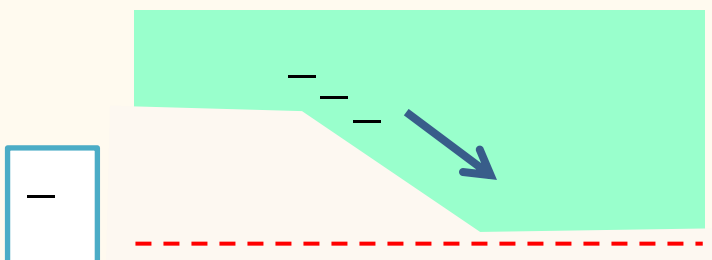


Reverse bias

enhances  $V_{bi}$

+ : no go

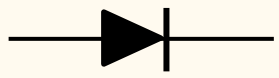

circuit symbol

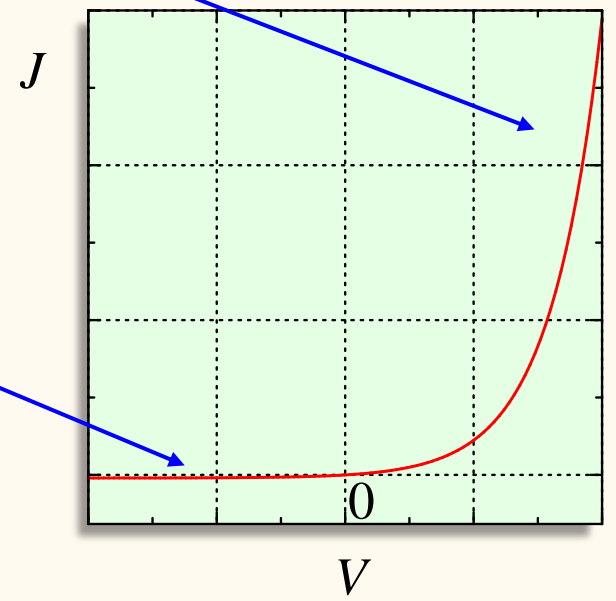





# Injection of minority carriers

$$J = e(v_n n_p + v_p p_n) \left[ \exp \frac{eV}{k_B T} - 1 \right]$$

minority carrier current

Barrier overflow

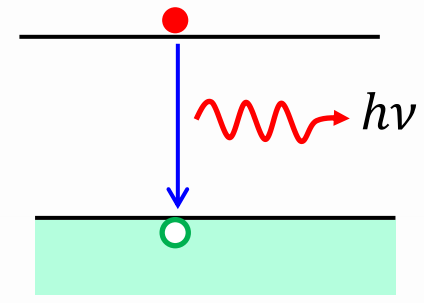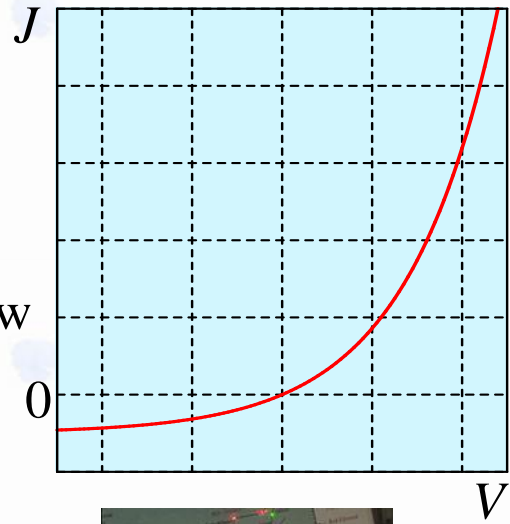

Fate of injected minority carriers:  
Radiative recombination

light emitting diode



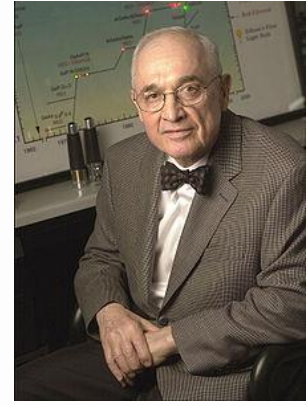
Photo: A. Mahmoud  
Isamu Akasaki



Photo: A. Mahmoud  
Hiroshi Amano


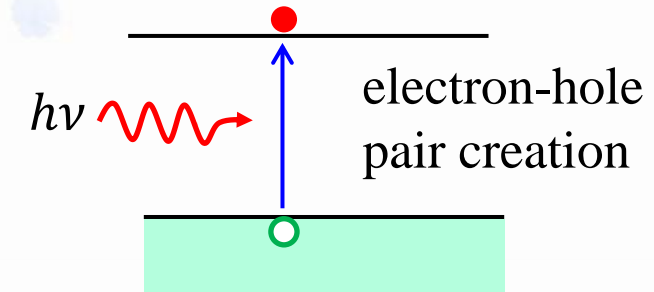


Photo: A. Mahmoud  
Shuji Nakamura

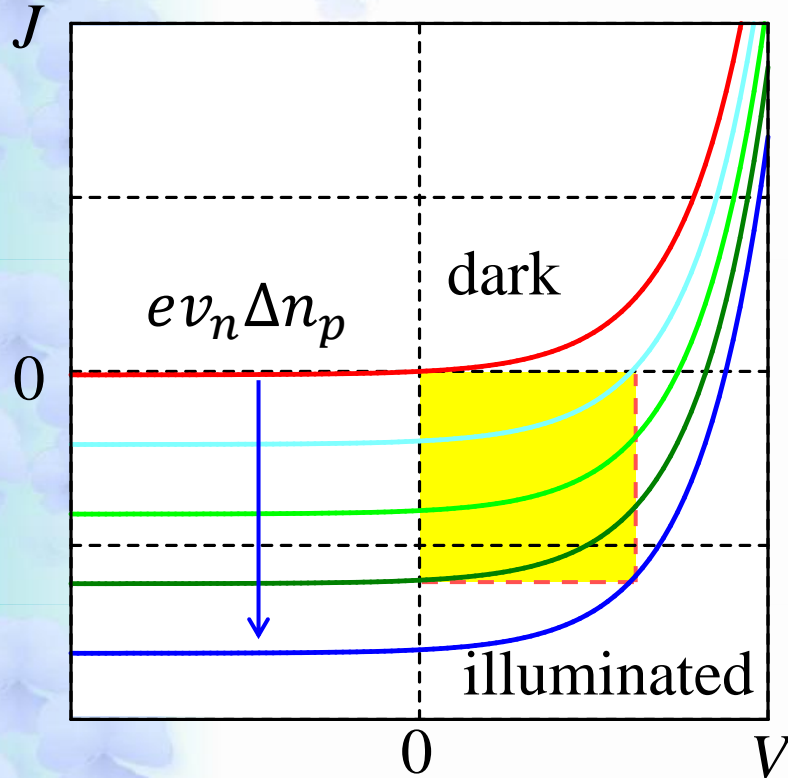

Nick Holonyak Jr.

# Solar cells (injection of minority carriers with light)



$$J_{e0} = ev_n n_p \left[ \exp \frac{eV}{k_B T} - 1 \right]$$

$$J_e = ev_n n_p \exp \frac{eV}{k_B T} - ev_n (n_p + \Delta n_p)$$

$$= J_{n0} - ev_n \Delta n_p$$


external injection

Minority carriers which diffuse to the junction region are swept out to the other side.

Gerald Pearson, Daryl Chapin → and Calvin Fuller at Bell labs. 1954




## 4.3.2 Bipolar transistors

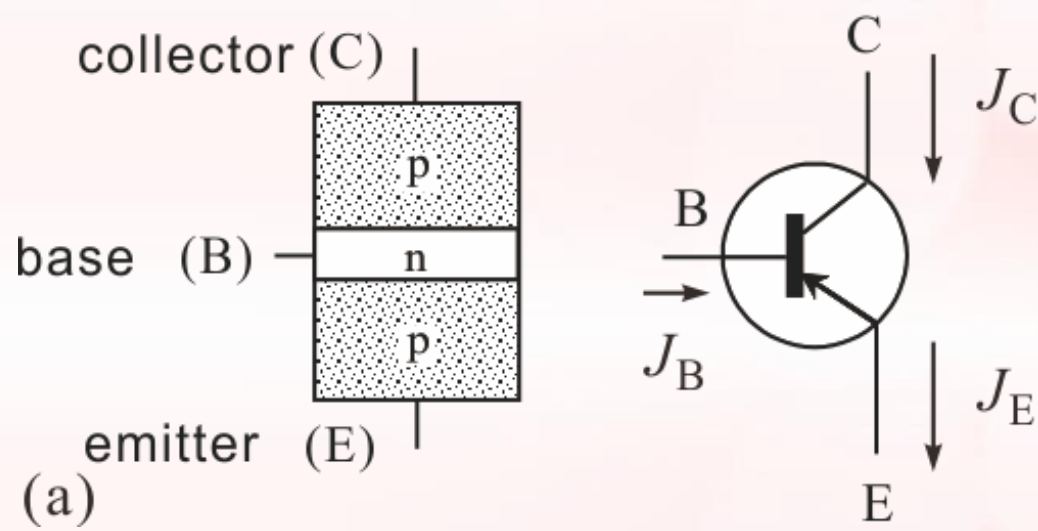

PNP type

$$L_B < L_h$$

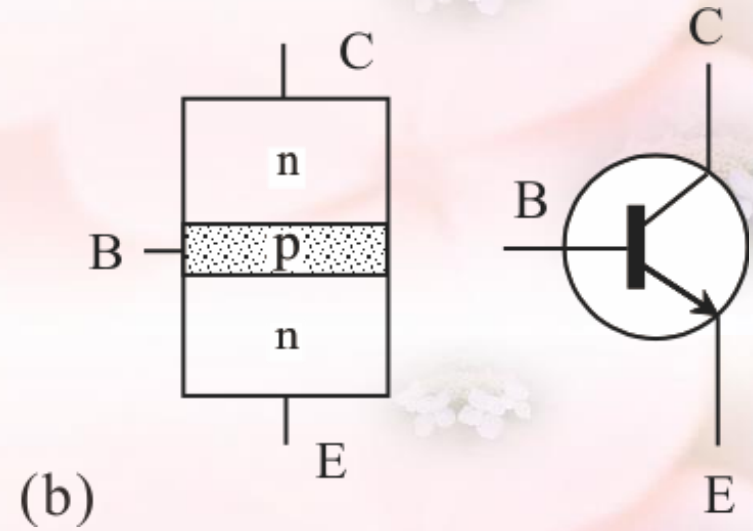


NPN type

$$L_B < L_e$$

Similar characteristics PNP and NPN: complementary



# Base-Collector characteristics

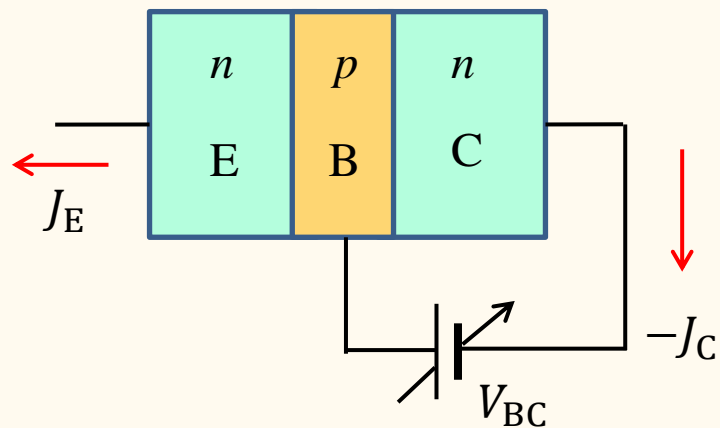


$J_C$  increases with  $V_{BC}$ .

Light illumination in solar cells




Emitter current

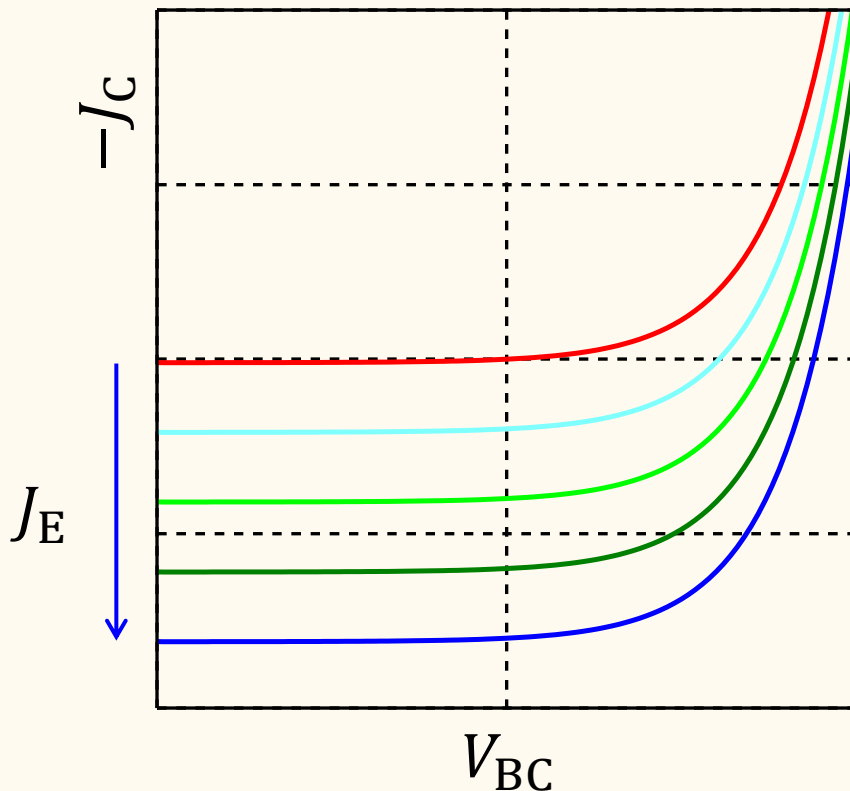


What is common?

Minority carrier injection
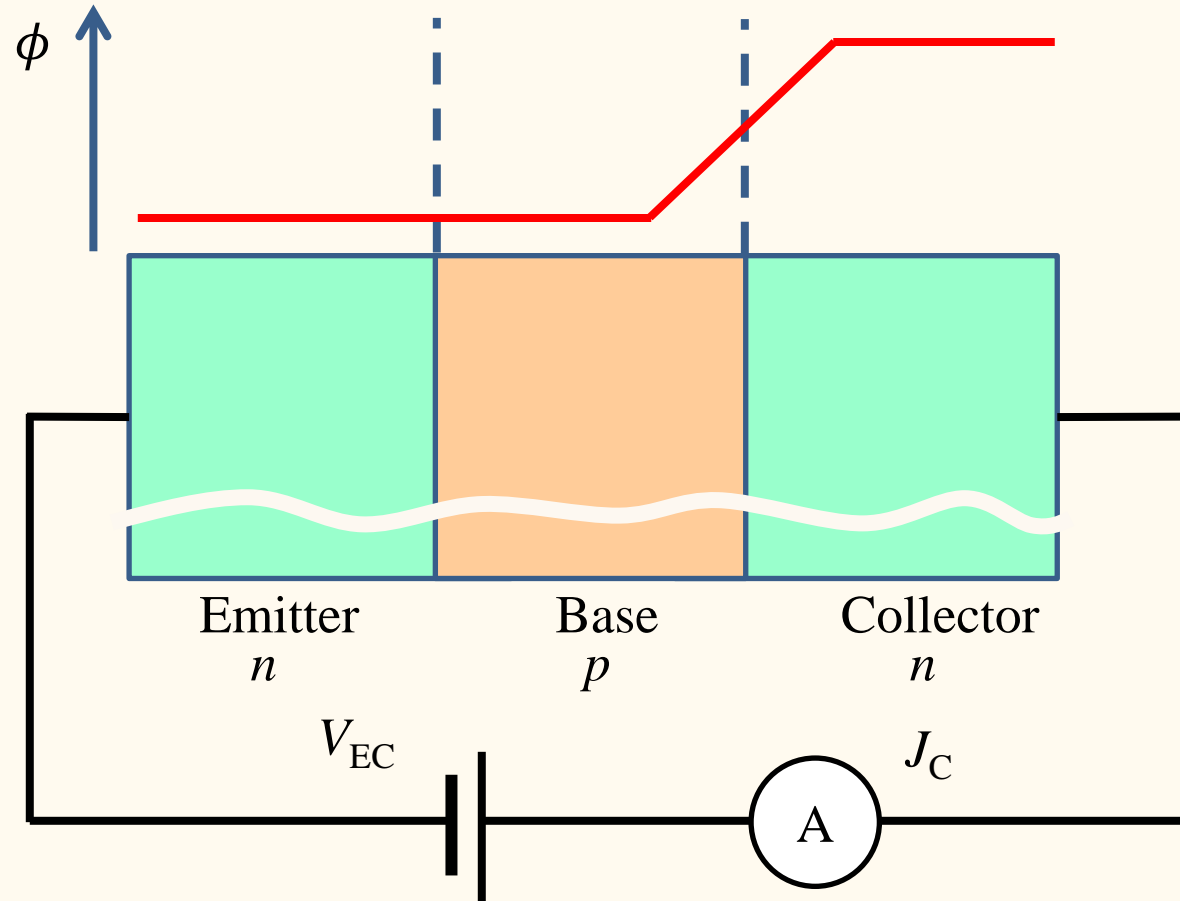
# How a bipolar transistor amplifies signal?





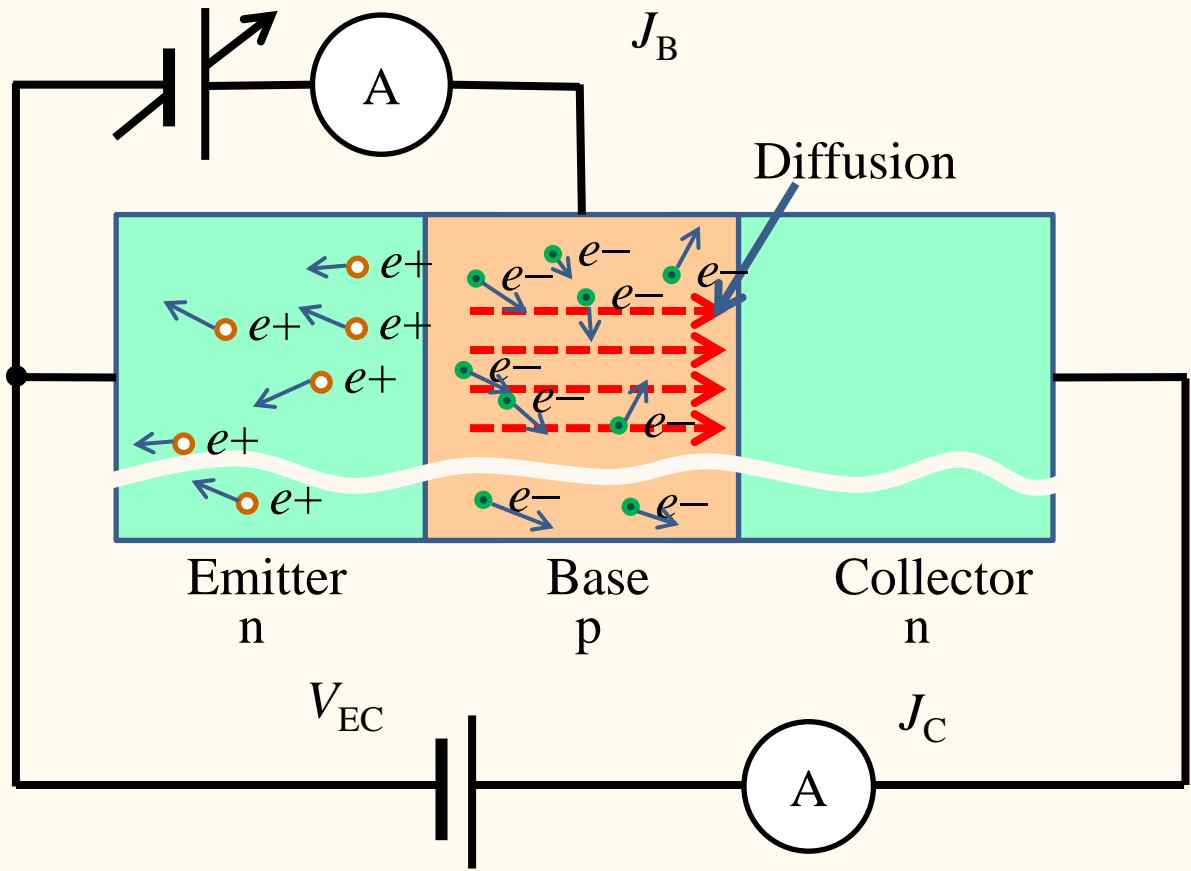
# How a bipolar transistor amplifies signal?






# Collector-Emitter characteristics

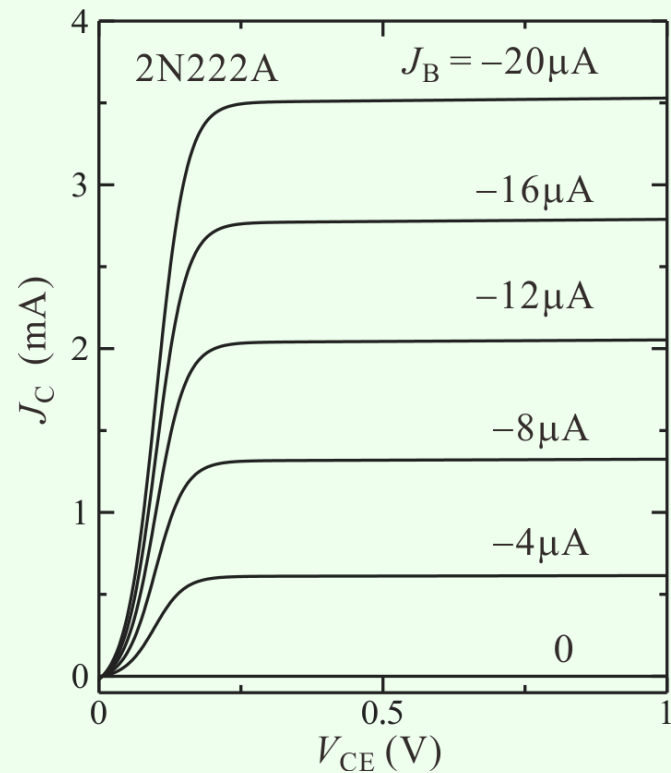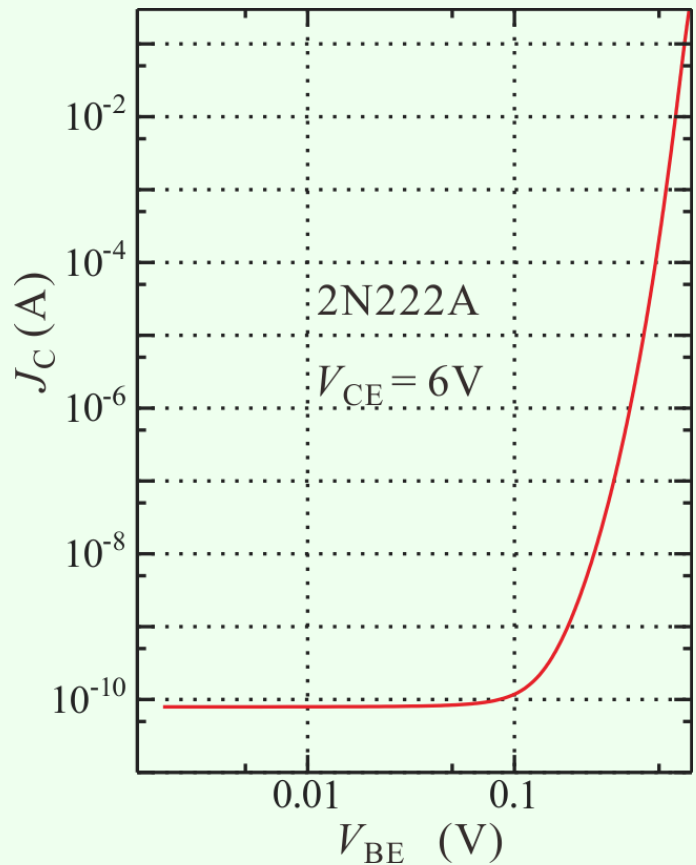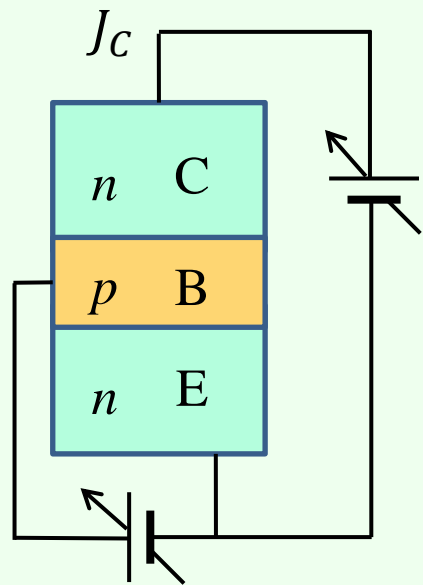

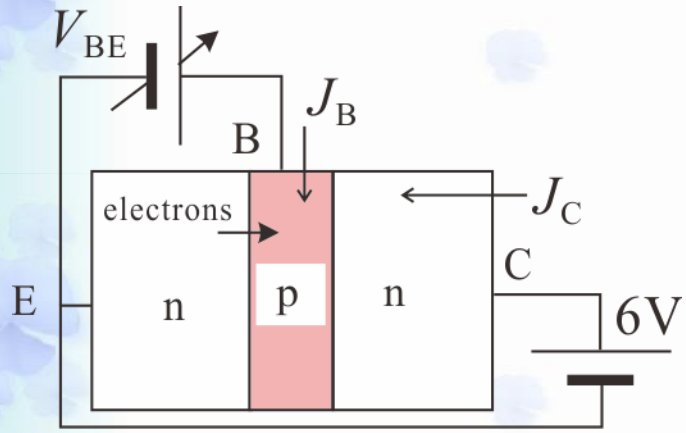
# Current amplification: Linearize with quantity selection




$$J_C = \underline{h_{FE}} J_B$$

Emitter-common current gain

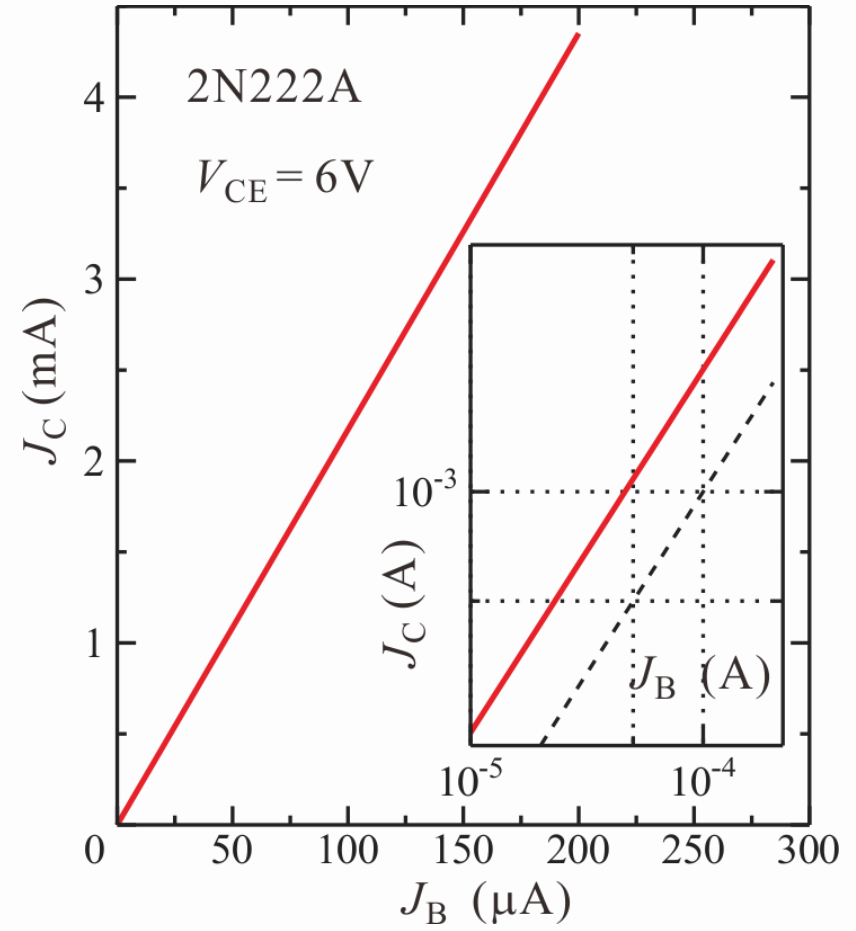

# Linear approximation of bipolar transistor


Hybrid matrix

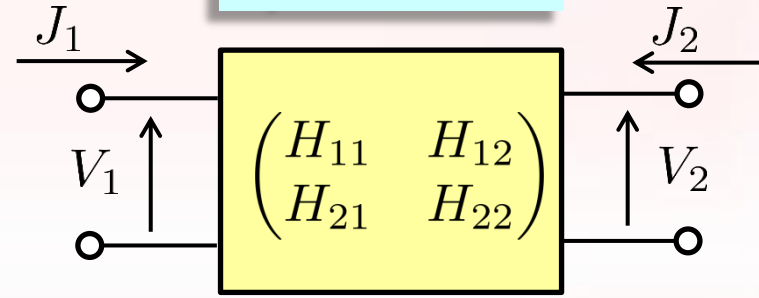

$$\begin{pmatrix} V_1 \\ J_2 \end{pmatrix} = \begin{pmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{pmatrix} \begin{pmatrix} J_1 \\ V_2 \end{pmatrix}$$

Linear approximation for non-linear devices:  
Take derivative to have local linear matrices.


h-parameters

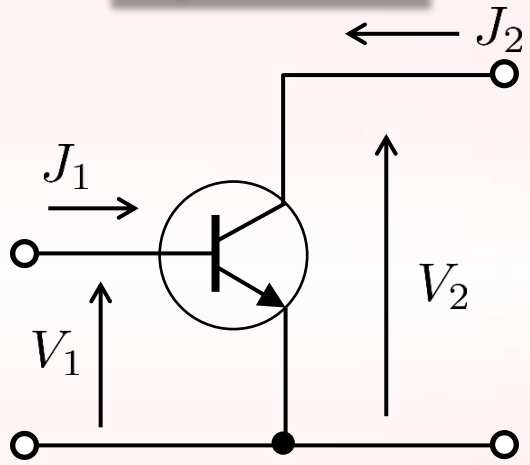

$$\begin{pmatrix} v_1 \\ j_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} j_1 \\ v_2 \end{pmatrix}$$

$$= \begin{pmatrix} h_i & h_r \\ h_f & h_o \end{pmatrix} \begin{pmatrix} j_1 \\ v_2 \end{pmatrix}$$

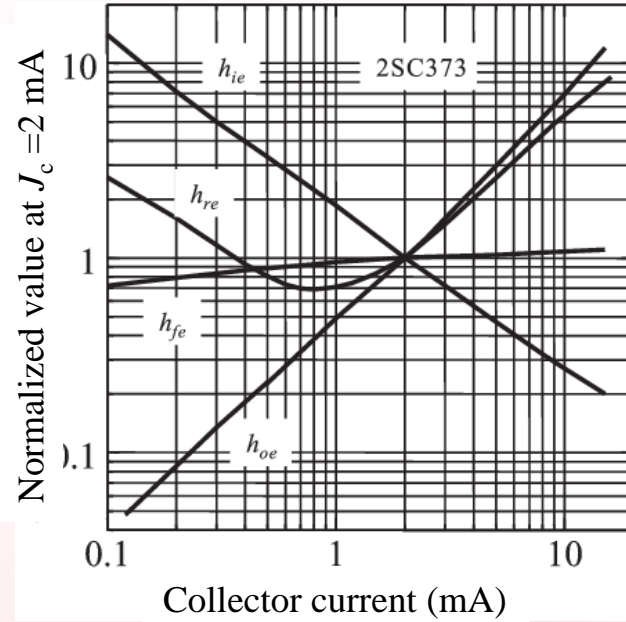
(lower case:  
local linear approximation)


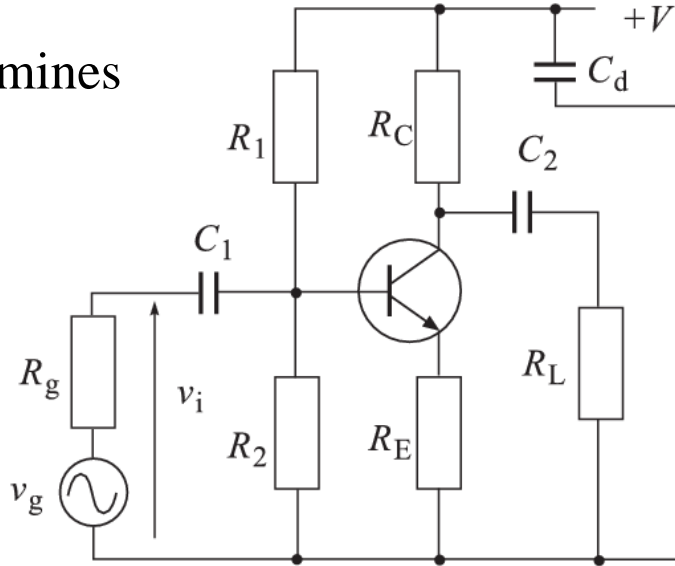
# Concept of bias circuits for non-linear devices

**Bias circuit** determines the action point.

Signal lines can be separated with reactive elements.




For small amplitude (high-frequency) circuits

All the capacitors can be viewed as short circuits.



For bias (dc) circuits

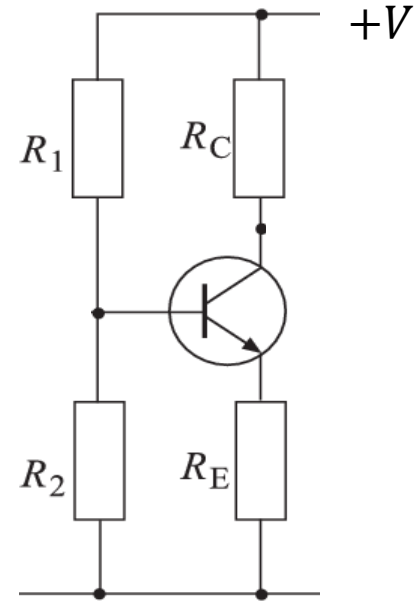All the capacitors can be viewed as break line.






# Concept of equivalent circuit

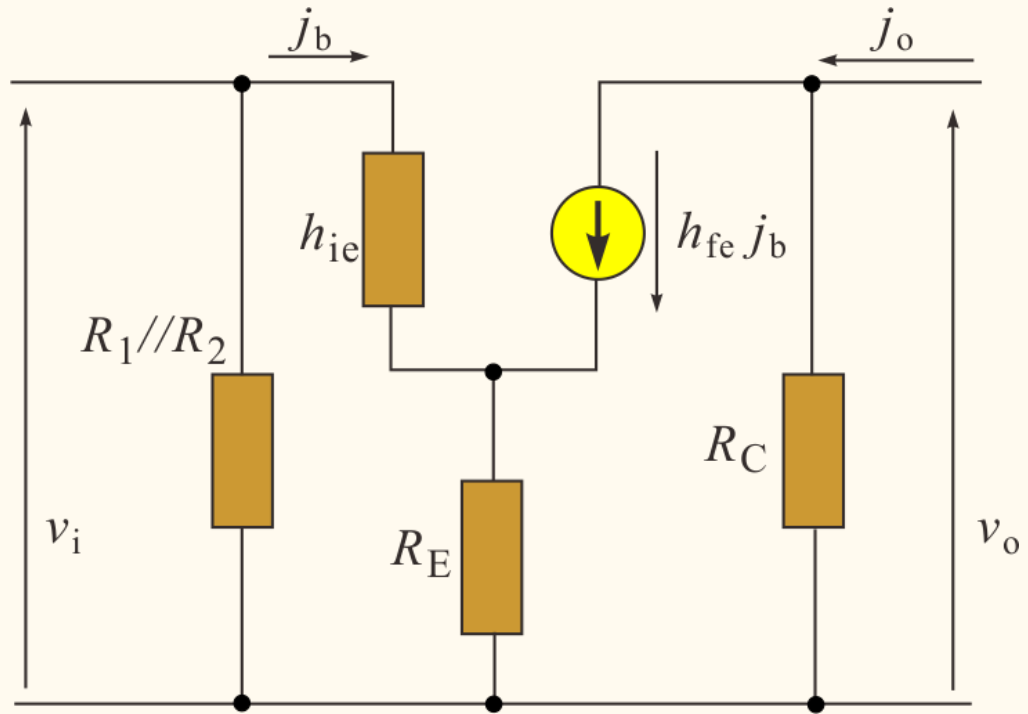
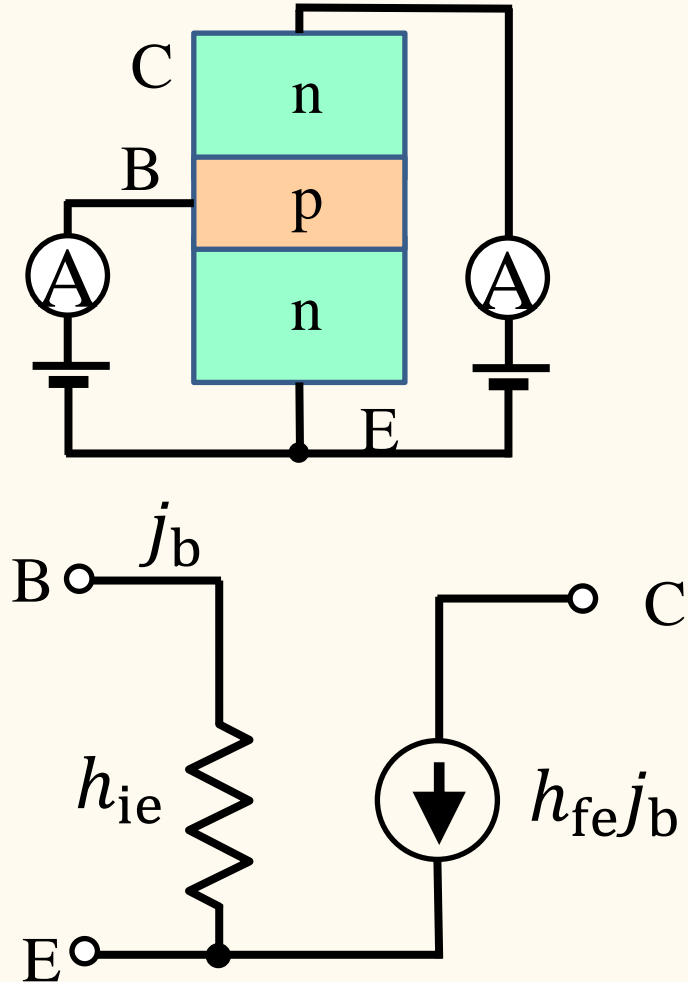


But resistors for bias circuit still work in signal circuit as long as they are not short circuited by capacitors.

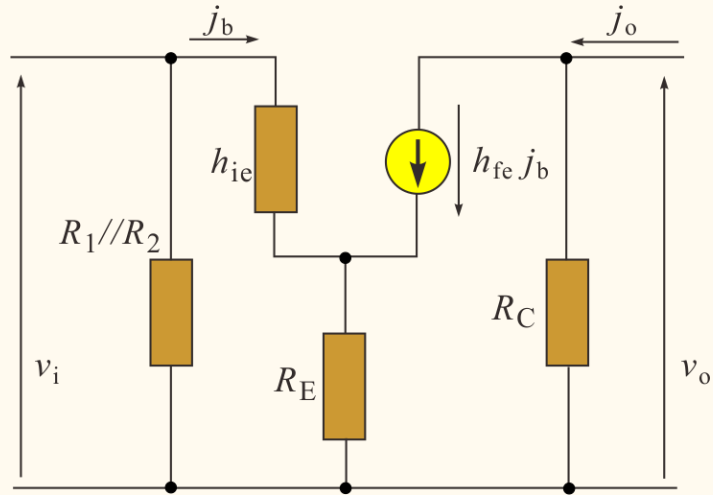
# Concept of equivalent circuit: Feedback?



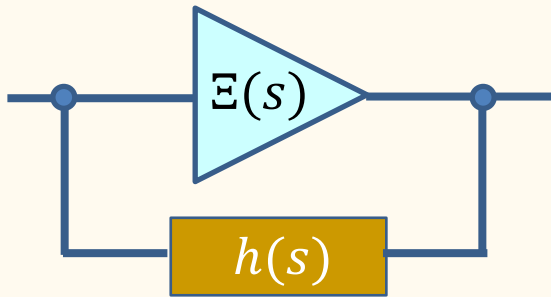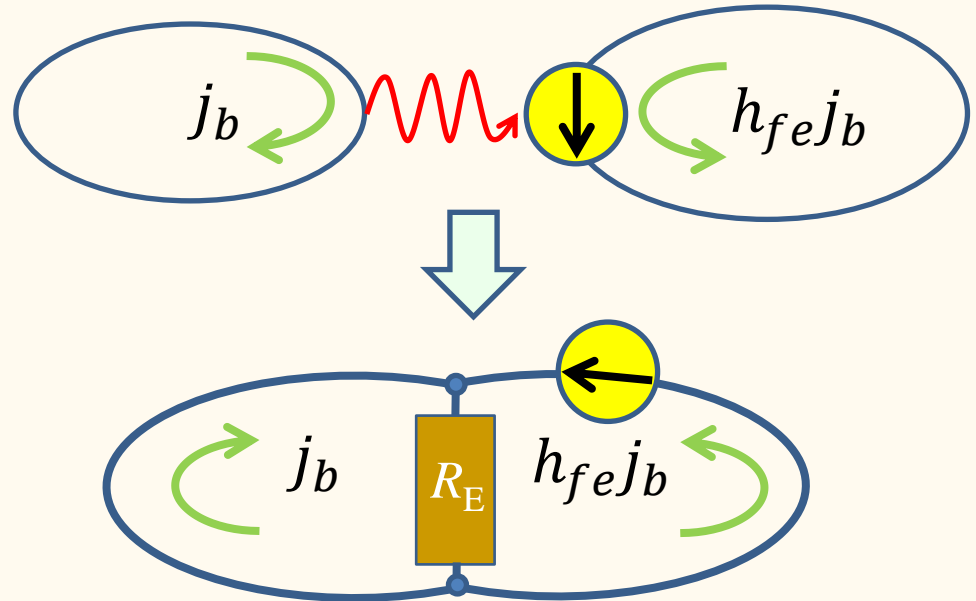In the case of current-current linear circuit, a way for feedback is to have a common part the current loops.



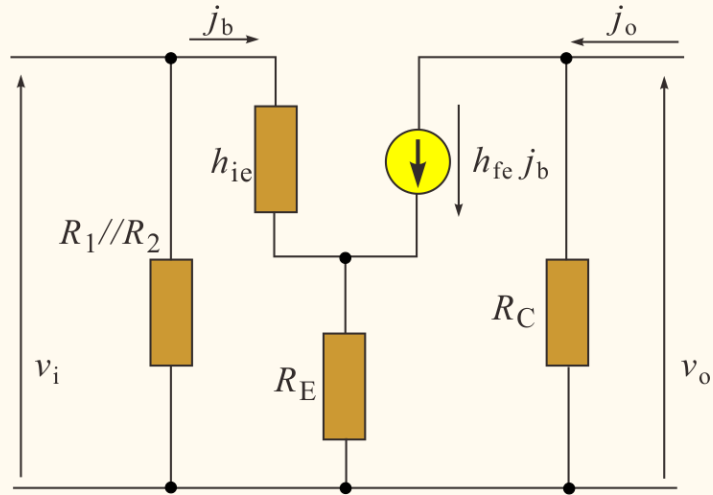
# Concept of equivalent circuit: Feedback?





In the case of current-current linear circuit, a way for feedback is to have a common part the current loops.
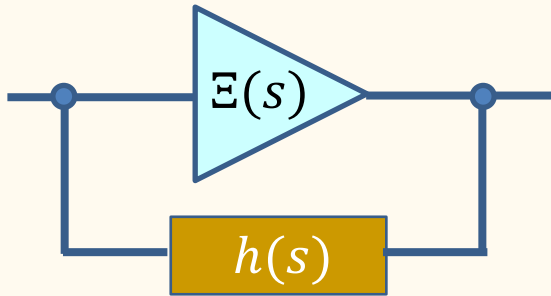
$$\begin{aligned}
 A &= \frac{v_o}{v_i} \\
 &= \frac{h_{fe} R_C}{h_{ie} + R_E(1 + h_{fe})} \\
 &\approx \frac{R_C}{R_E} \quad h_{fe} \gg 1
 \end{aligned}$$



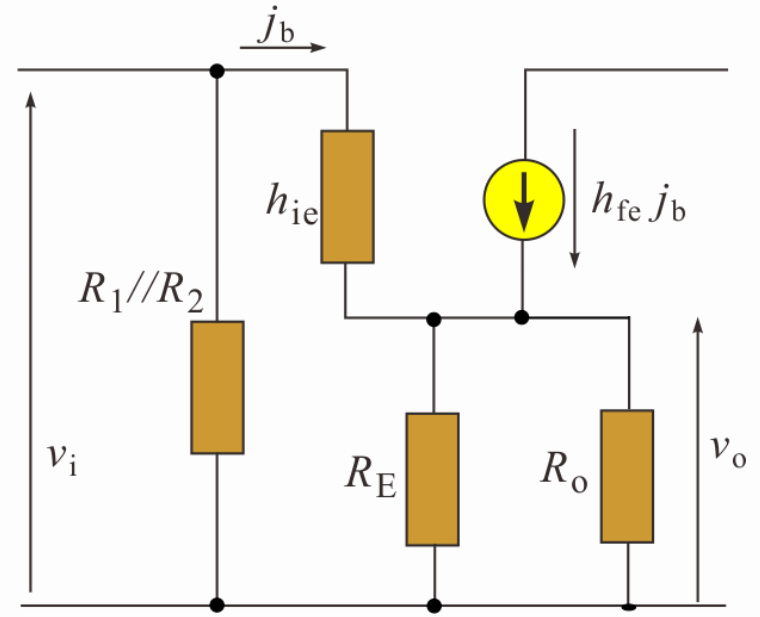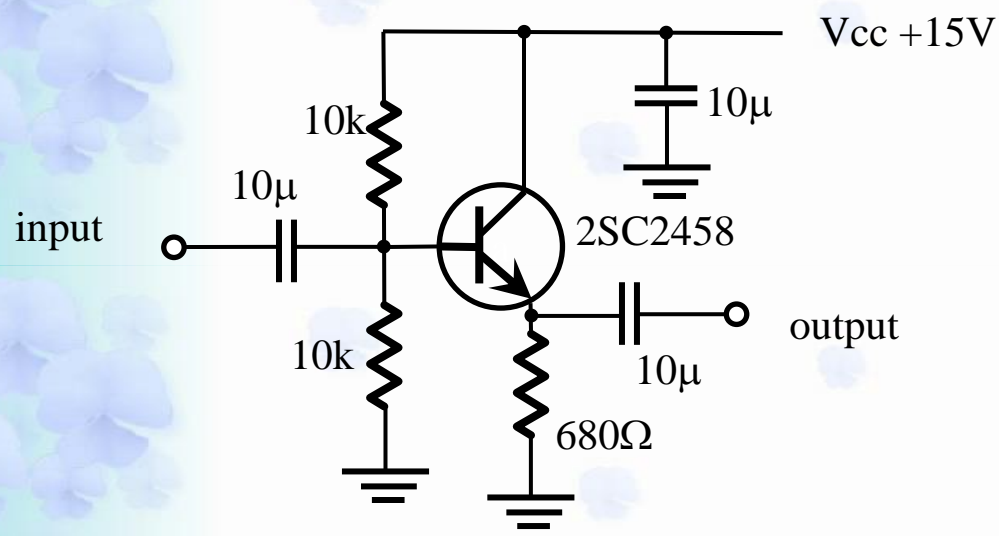
# Current amplification: Emitter follower



$$\frac{v_o}{v_i} = \frac{j_b(1 + h_{fe})(R_E \parallel R_o)}{j_b[h_{ie} + (1 + h_{fe})(R_E \parallel R_o)]}$$
$$\approx 1 \quad (h_{fe} \gg 1)$$

$v_o$  does not depend on load resistance  
 $\Rightarrow$  Very low output resistance

# Complementary transistors

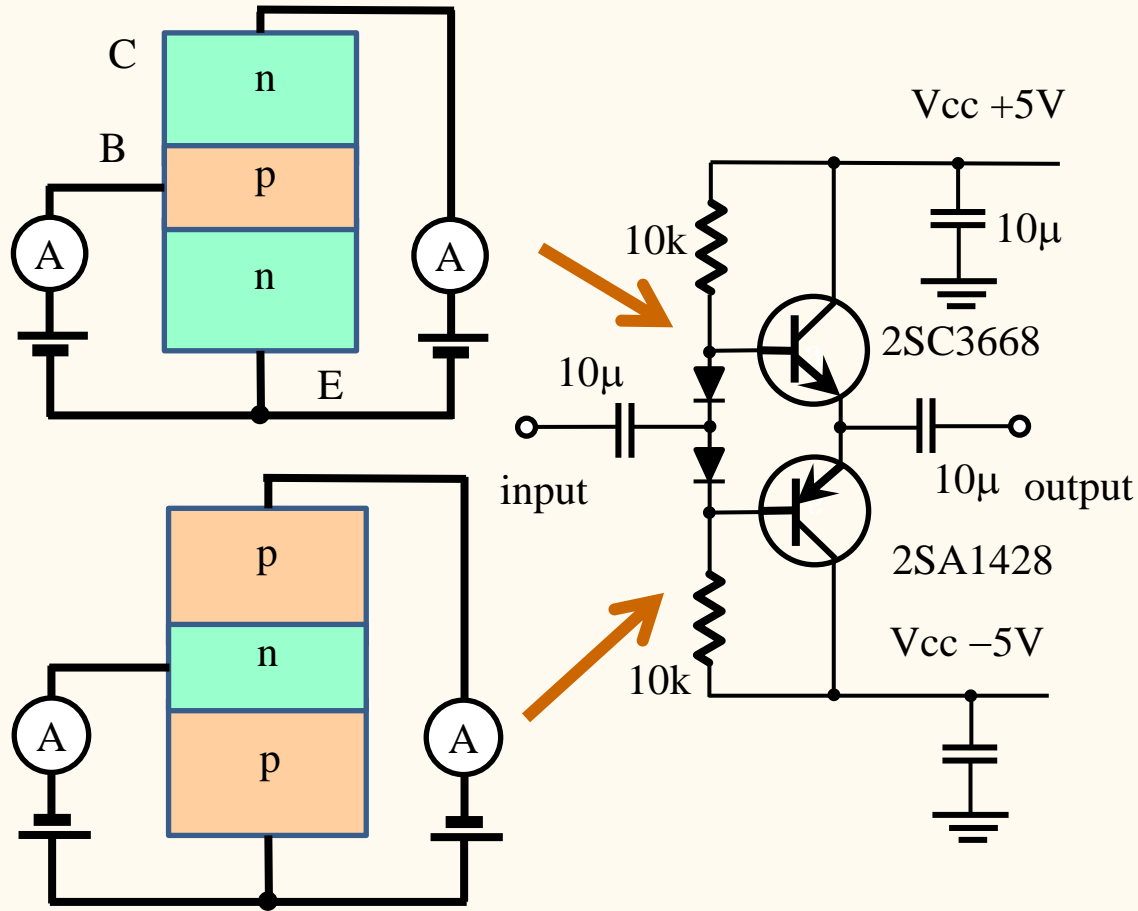

Symmetric characteristics:  
Complementary

Symmetric: Small collector current (idling current) for zero input.



# Example of transistor datasheet




Unit: mm

**TOSHIBA**

2SC1815(L)

TOSHIBA Transistor Silicon NPN Epitaxial Type (PCT process)

## 2SC1815(L)

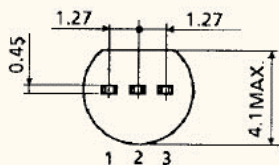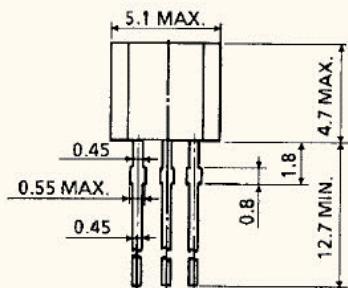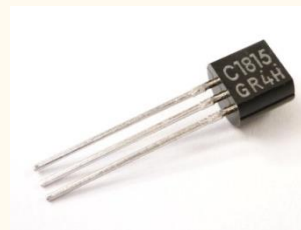

1. EMITTER
2. COLLECTOR
3. BASE

JEDEC TO-92

JEITA SC-43

TOSHIBA 2-5F1B

Audio Frequency Voltage Amplifier Applications  
Low Noise Amplifier Applications

- High breakdown voltage, high current capability  
:  $V_{CEO} = 50 \text{ V (min)}$ ,  $I_C = 150 \text{ mA (max)}$
- Excellent linearity of  $h_{FE}$   
:  $h_{FE} (2) = 100 \text{ (typ.)}$  at  $V_{CE} = 6 \text{ V}$ ,  $I_C = 150 \text{ mA}$   
:  $h_{FE} (I_C = 0.1 \text{ mA})/h_{FE} (I_C = 2 \text{ mA}) = 0.95 \text{ (typ.)}$
- Low noise:  $NF = 0.2\text{dB (typ.)}$  ( $f = 1 \text{ kHz}$ ).
- Complementary to 2SA1015 (L). (O, Y, GR class).


# Example of transistor datasheet (2SC1815(L))

## Electrical Characteristics (Ta = 25°C)


Characteristics		Symbol	Test Condition	Min	Typ.	Max	Unit
Collector cut-off current		$I_{CBO}$	$V_{CB} = 60\text{ V}, I_E = 0$	—	—	0.1	$\mu\text{A}$
Emitter cut-off current		$I_{EBO}$	$V_{EB} = 5\text{ V}, I_C = 0$	—	—	0.1	$\mu\text{A}$
DC current gain		$h_{FE(1)}$ (Note)	$V_{CE} = 6\text{ V}, I_C = 2\text{ mA}$	70	—	700	
		$h_{FE(2)}$	$V_{CE} = 6\text{ V}, I_C = 150\text{ mA}$	25	100	—	
Saturation voltage	Collector-emitter	$V_{CE(sat)}$	$I_C = 100\text{ mA}, I_B = 10\text{ mA}$	—	0.1	0.25	V
	Base-emitter	$V_{BE(sat)}$	$I_C = 100\text{ mA}, I_B = 10\text{ mA}$	—	—	1.0	
Transition frequency		$f_T$	$V_{CE} = 10\text{ V}, I_C = 1\text{ mA}$	80	—	—	MHz
Collector output capacitance		$C_{ob}$	$V_{CB} = 10\text{ V}, I_E = 0, f = 1\text{ MHz}$	—	2.0	3.5	pF
Base intrinsic resistance		$r_{bb'}$	$V_{CE} = 10\text{ V}, I_E = -1\text{ mA}, f = 30\text{ MHz}$	—	50	—	$\Omega$
Noise figure		NF (1)	$V_{CE} = 6\text{ V}, I_C = 0.1\text{ mA}$ $R_G = 10\text{ k}\Omega, f = 100\text{ Hz}$	—	0.5	6	dB
		NF (2)	$V_{CE} = 6\text{ V}, I_C = 0.1\text{ mA}$ $R_G = 10\text{ k}\Omega, f = 1\text{ kHz}$	—	0.2	3	

Note:  $h_{FE(1)}$  classification O: 70~140, Y: 120~240, GR: 200~400, BL: 350~700
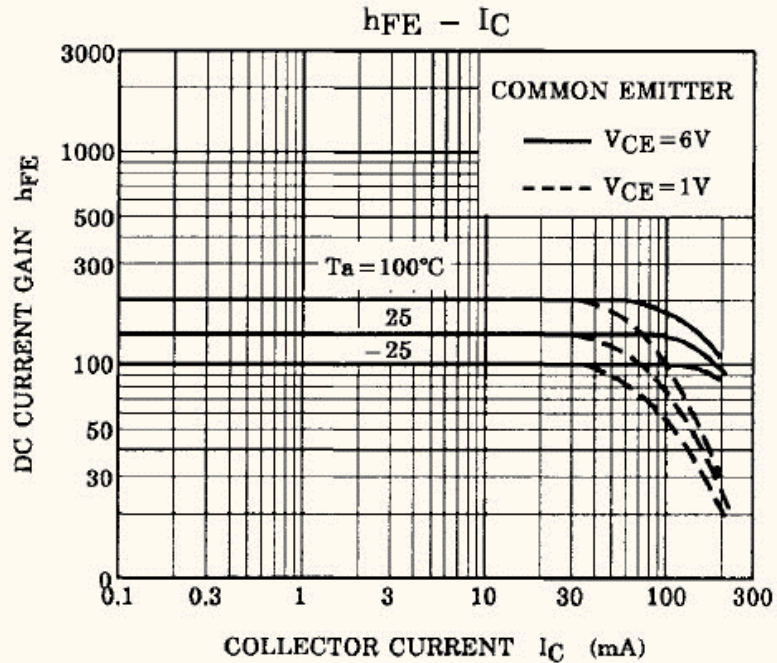
# Example of transistor datasheet (2SC1815(L))



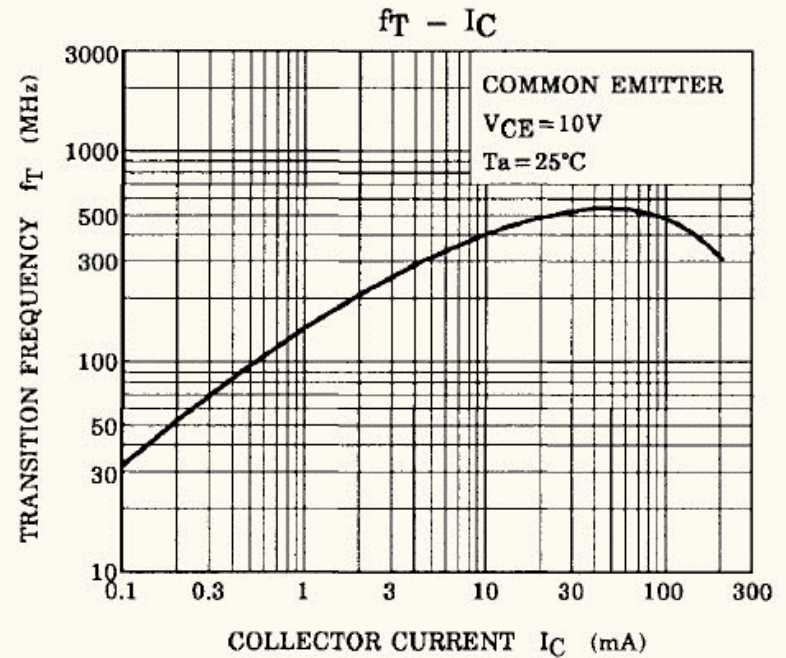$h_{fe}$  linear model availability  
in the range of  $I_C$ .



Cut-off frequency as a function of  $I_C$

# Simulation example

$$\begin{aligned}\Delta V_C &= R_2 \Delta J_C \approx R_2 \Delta J_E \\ &= R_2 \frac{\Delta V_E}{R_4} = \frac{R_2}{R_4} \Delta V\end{aligned}$$

