



電子回路論第7回

Electric Circuits for Physicists #7

東京大学理学部・理学系研究科
物性研究所
勝本信吾

Shingo Katsumoto

Outline

4.5 Field Effect Transistors (FETs)

Ch.5 Distributed constant circuits

5.1 Transmission lines

5.1.1 Coaxial cables


5.1.2 Lecher lines

5.1.3 Micro-strip lines


5.2 Wave propagation through transmission lines

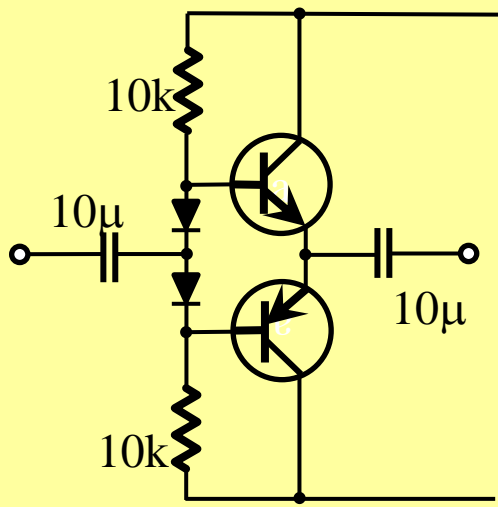5.2.2 Connection and termination of transmission lines


Combination of op-amp and discrete transistors



Complementary
push-pull

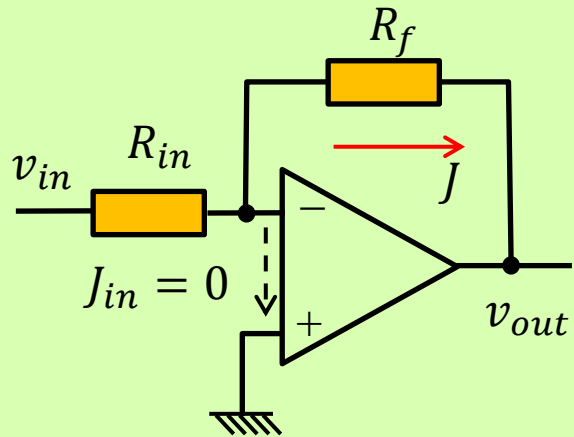


Inversion
amplifier

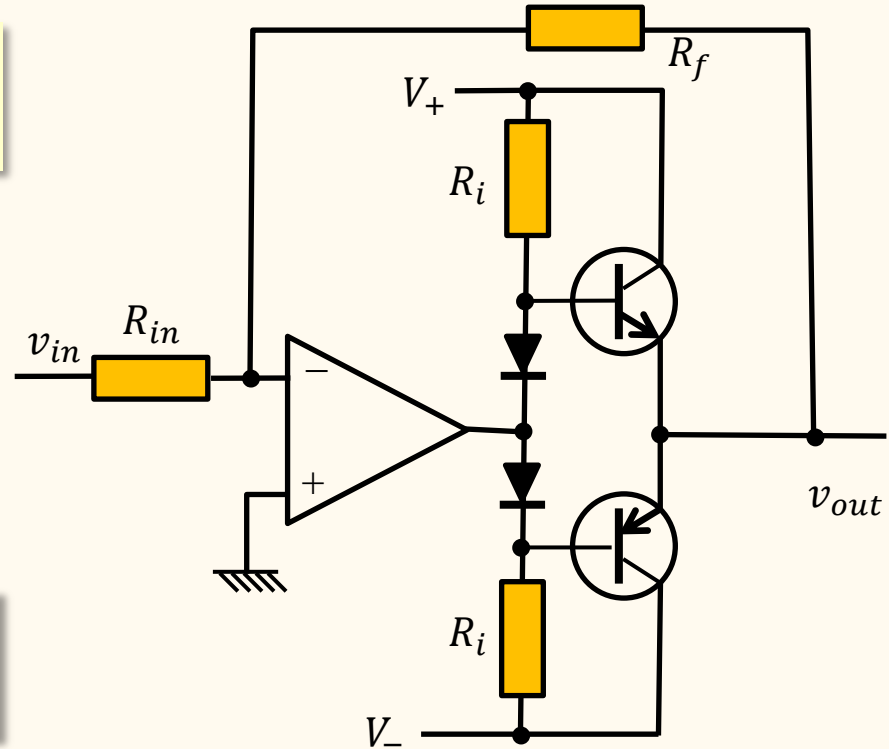

Voltage, current booster

pn-junction in reverse bias region

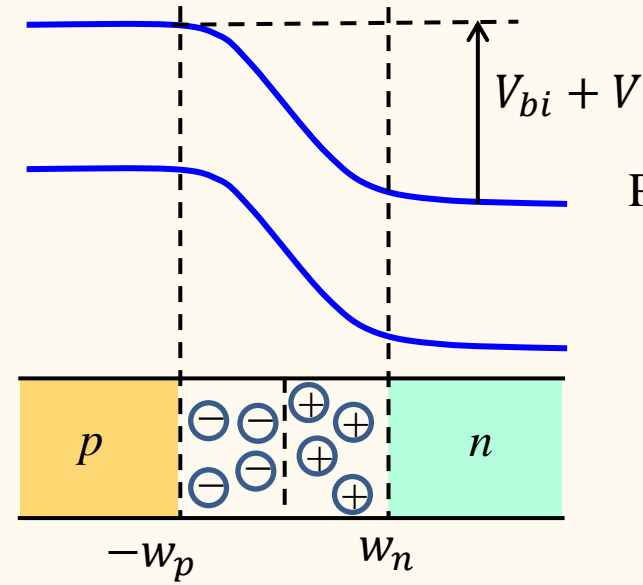

Built-in potential \rightarrow Depletion layer

Poisson equation
$$\frac{d^2\phi}{dx^2} = -aq(x) \quad (a \equiv (\epsilon\epsilon_0)^{-1})$$

Space charge density:
$$\begin{cases} q = -eN_A & (-w_p \leq x \leq 0), \\ q = eN_D & (0 \leq x \leq w_n) \end{cases}$$


Boundary condition:
$$\phi(-w_p) = 0, \quad \phi(-\infty) = 0$$

$$\left. \frac{d\phi}{dx} \right|_{-w_p} = 0, \quad \phi(w_n) = V + V_{bi}, \quad \left. \frac{d\phi}{dx} \right|_{w_n} = 0$$

Solution:

$$\phi(x) = \begin{cases} (aeN_A/2)(x + w_p)^2 & (-w_p \leq x \leq 0), \\ V + V_{bi} - (aeN_D/2)(x - w_n)^2 & (0 \leq x \leq w_n) \end{cases}$$

Varicap diode

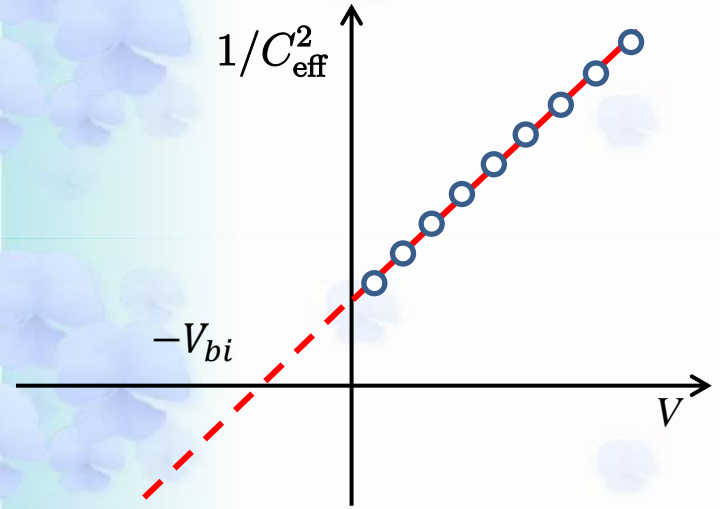


$$w_d = w_p + w_n = A\sqrt{V + V_{bi}}$$

Reverse bias voltage widens depletion layer.

$$\frac{1}{C_{\text{eff}}^2} = \frac{2}{\epsilon\epsilon_0 e N_D} (V + V_{bi})$$




Varicap diode


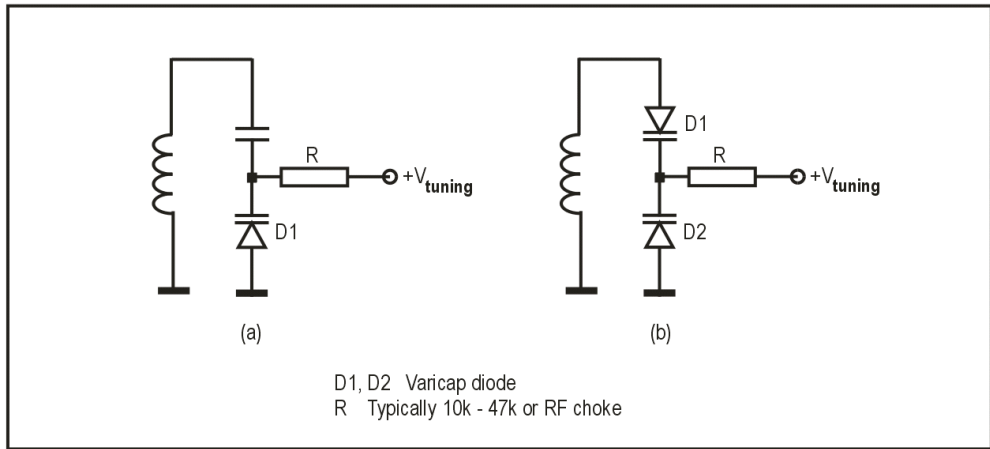


Frequency modulation (FM), Phase lock loop (PLL)


4.4 Field effect transistor (FET)

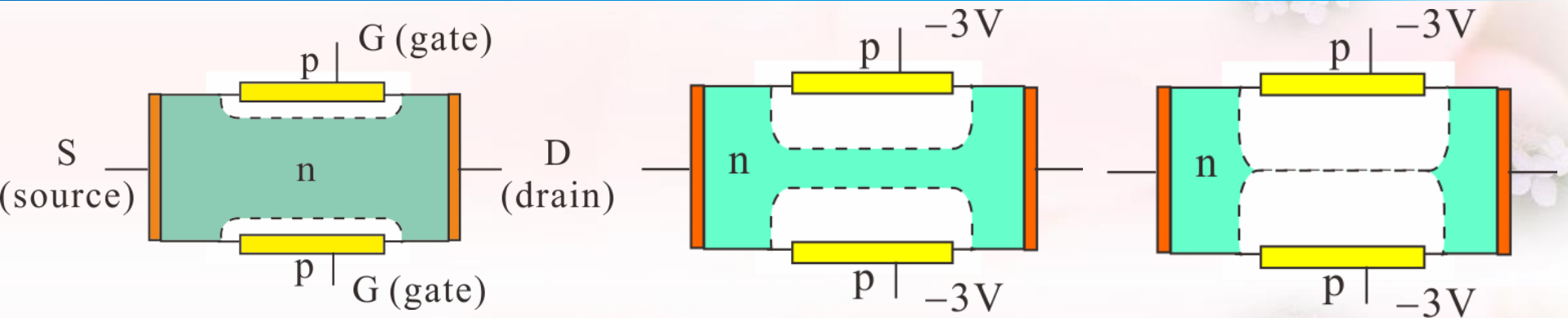


Circuit symbols

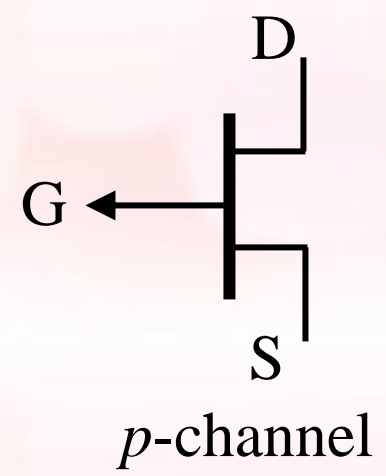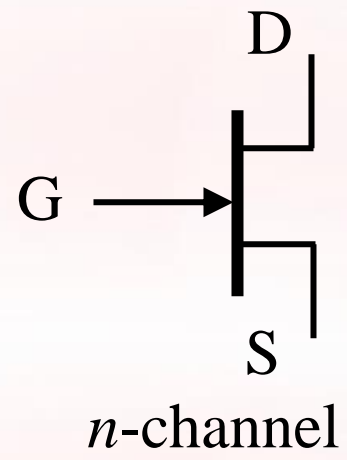

Static characteristics of FET

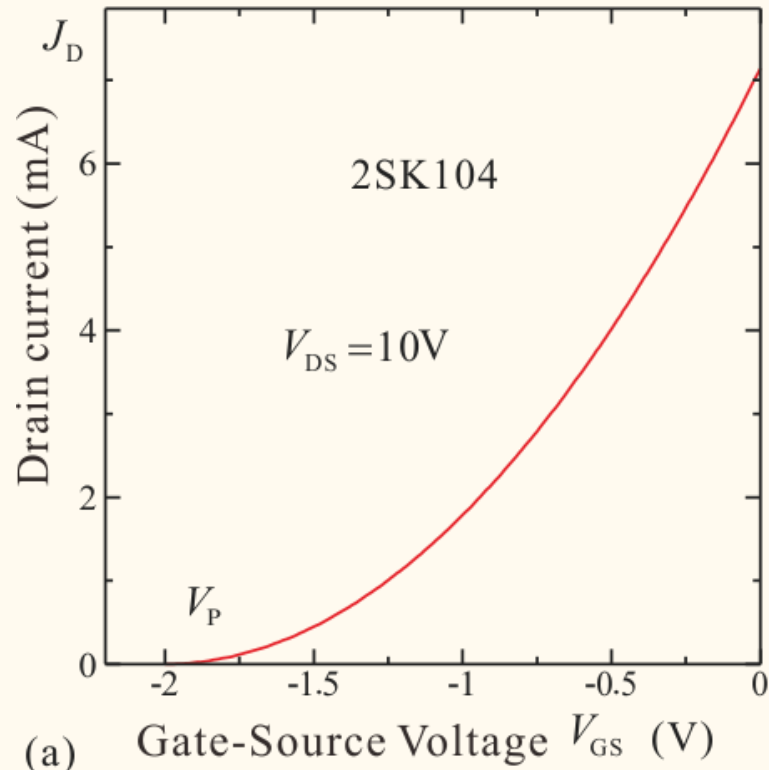

(a)

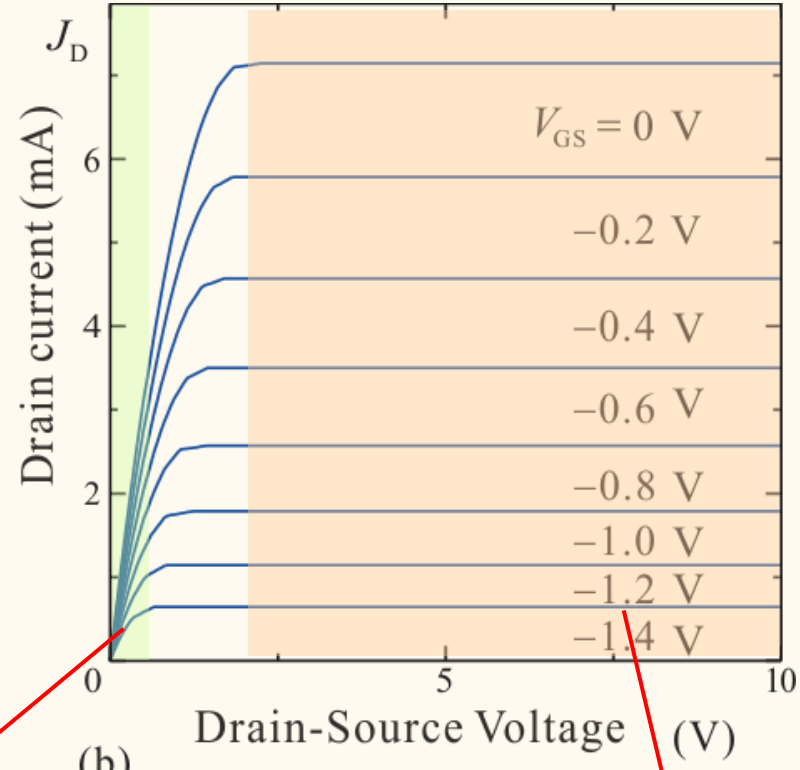


(b)

Ohmic area

Space charge limited area

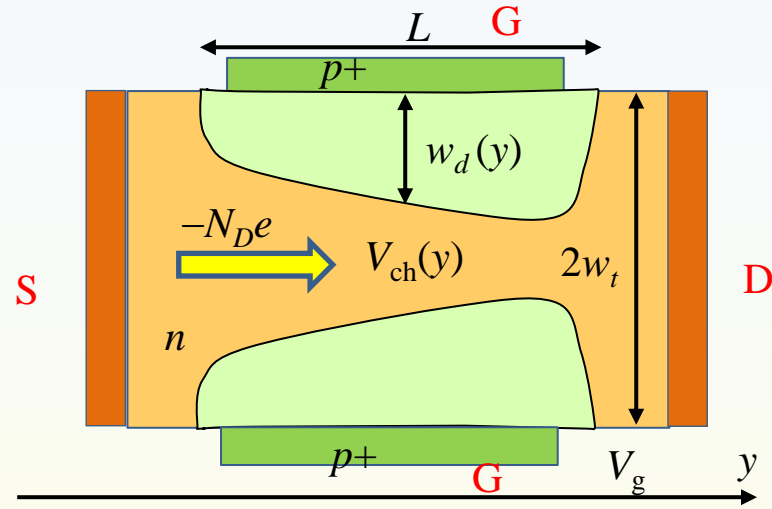Space-charge limitation of source-drain current



Travel distance (y)
dependent potential

$$V(y) = V_g + V_{vi} - V_{ch}(y)$$

Depletion layer width

$$w_d(y) = \sqrt{\frac{2\epsilon\epsilon_0 V(y)}{eN_D}}$$

$$J_{ch} = \underbrace{eN_D}_{\text{conductivity}} \underbrace{\mu_n}_{\text{electric field}} \underbrace{\frac{dV_{ch}}{dy}}_{\text{channel width}} \cdot 2[w_t - w_d(y)]W$$



$$J_{ch}L = \int_0^L J_{ch} dy = 2eN_D\mu_n W \int_0^L (w_t - w_d) \frac{dV}{dy} dy = 2w_t eN_D\mu_n W \int_{V_0}^{V_L} \left(1 - \frac{w_d}{w_t}\right) dV$$

$$w_d(V_c) = w_t \quad \therefore V_c = \frac{eN_D w_t^2}{2\epsilon\epsilon_0}$$

Approx. for
 $w_d < w_t/2$

$$J_{ch} = \frac{2N_D e \mu_n W w_t}{L} \left[V_L - V_0 + \frac{2}{3\sqrt{V_c}} (V(V_0)^{3/2} - V(V_L)^{3/2}) \right]$$

Static characteristics of FET

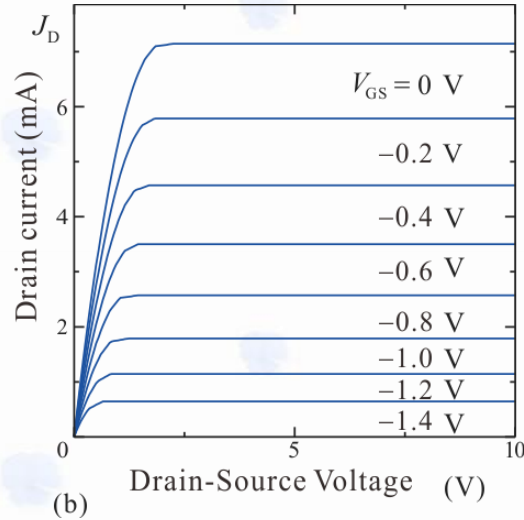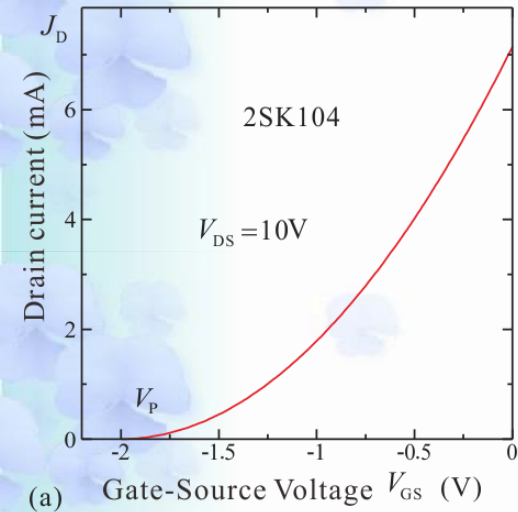

$$J_G \simeq 0, \quad J_D = f(V_G, V_{DS})$$

$$g_m \equiv \left(\frac{\partial J_D}{\partial V_{GS}} \right)_{V_{DS}=\text{const.}}$$

transconductance

$$r_d \equiv \left(\frac{\partial V_{DS}}{\partial J_D} \right)_{V_{GS}=\text{const.}}$$

drain resistance

Local linear approximation:
$$j_d = g_m v_{gs} + \frac{v_{ds}}{r_d}$$



$$v_{ds} = \underbrace{-r_d g_m}_{\text{Amplification factor (voltage gain)}} v_{gs} + r_d j_d$$

$$\mu \equiv r_d g_m$$



Biasing circuits for FETs: Fixed bias circuit

Local linear approximation \rightarrow action point (the center of parameters)

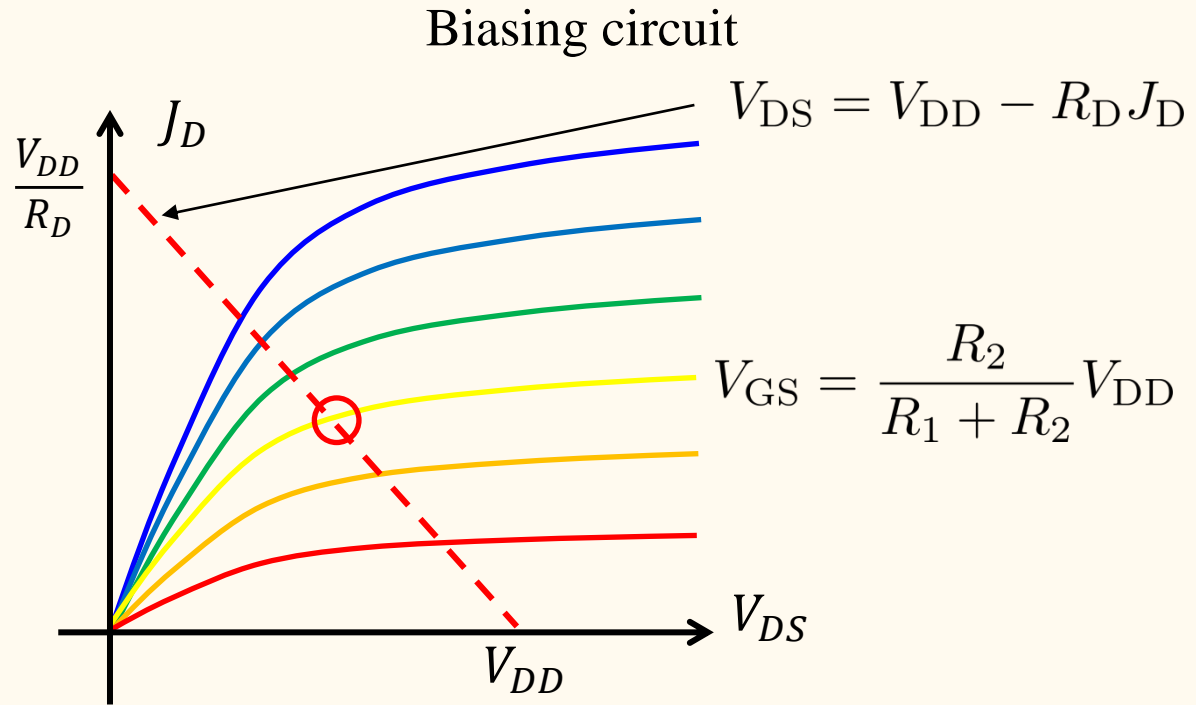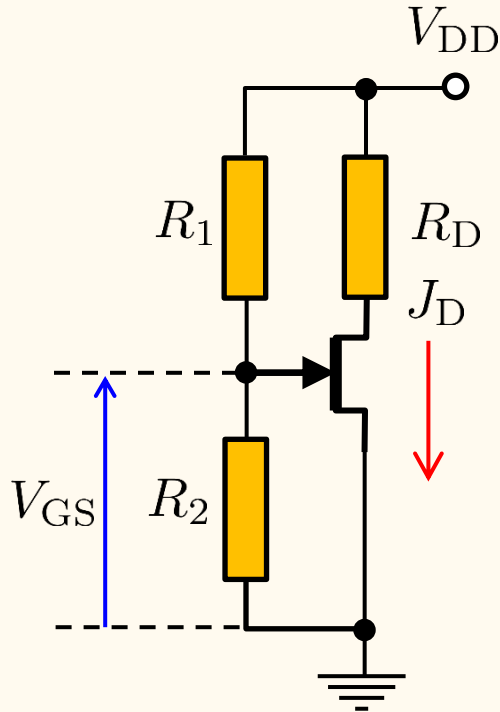
The action point is determined by resistors and dc power sources.







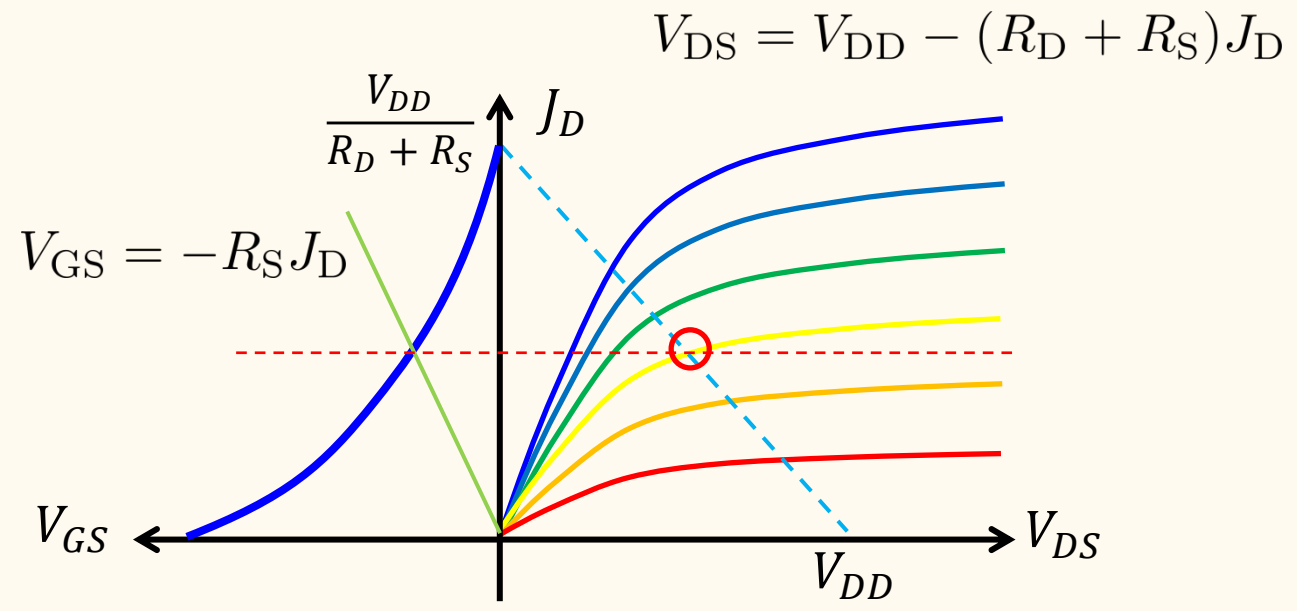
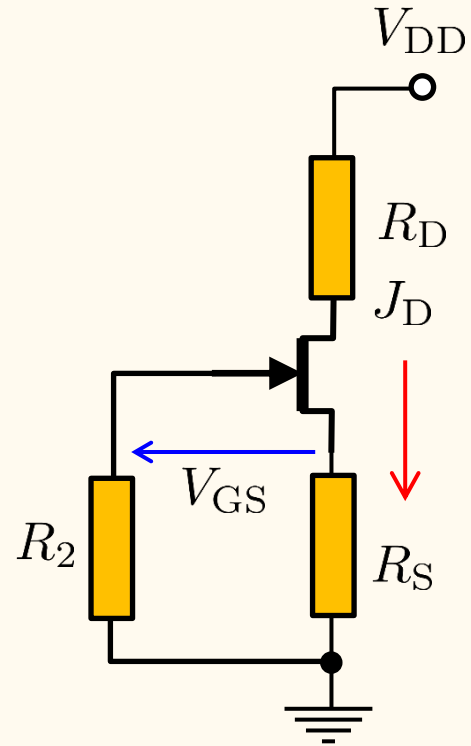
Biasing circuits for FETs: Self-biasing circuit




Equivalent signal circuits for FET

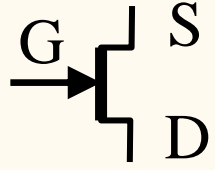

$$\mu = r_d g_m$$

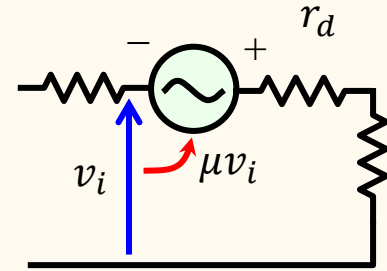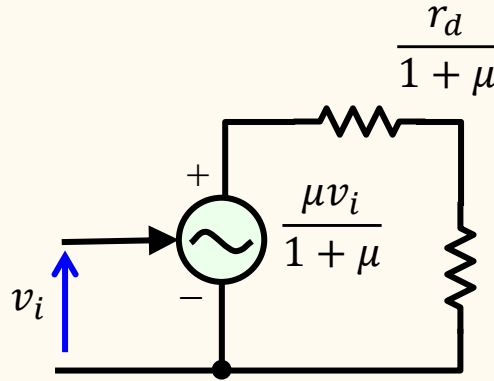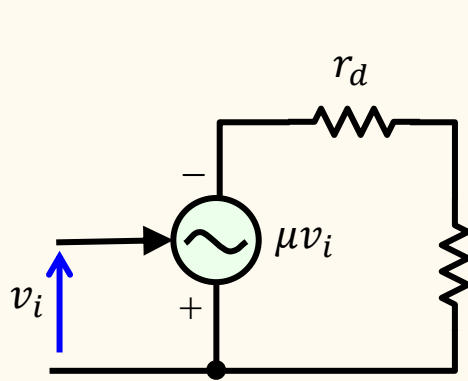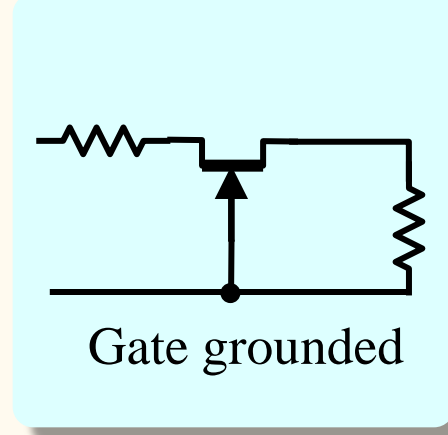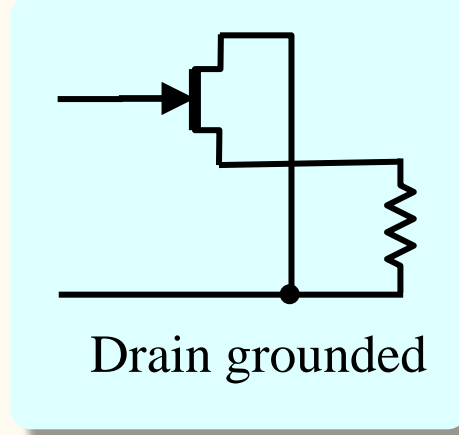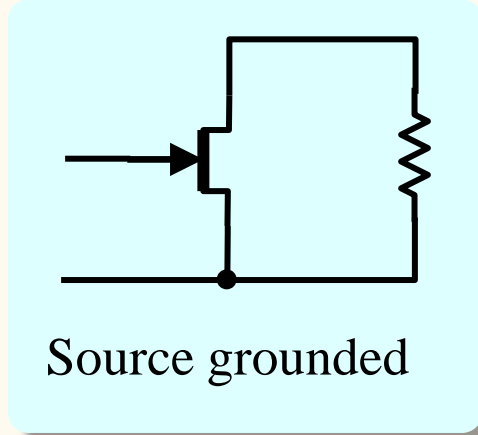

Example of source-grounded FET amplifier

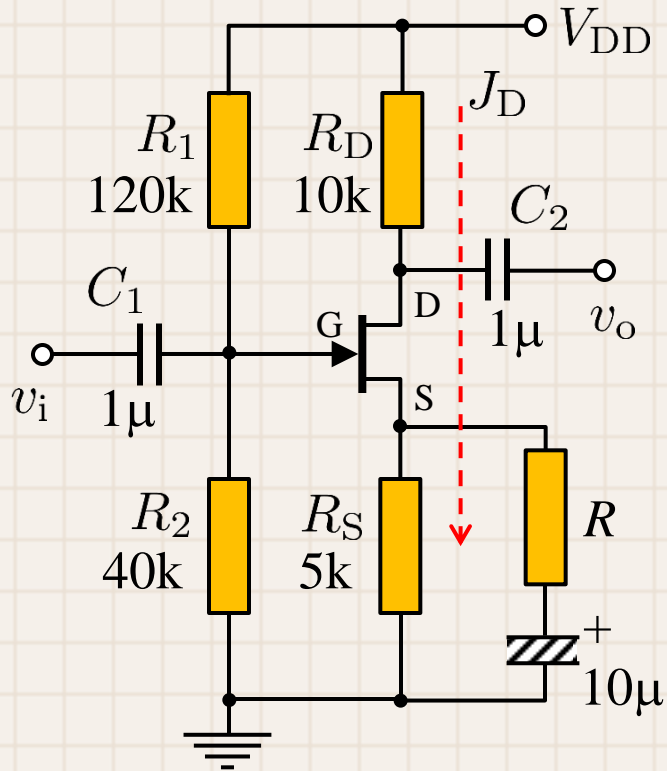


R_S is working as a negative feedback circuit.

$$\begin{cases} \delta V_{GS} = \delta V_G - R_S \delta J_D \\ \delta V_{DS} = -\mu(\delta V_G - R_S \delta J_D) \quad \text{ignore } r_d \\ \delta V_D = \delta V_{DS} + R_S \delta J_D \end{cases}$$

$$\delta V_D = \frac{-\mu R_D}{R_D + R_S(1 - \mu)} \delta V_G \approx \boxed{\frac{R_D}{R_S}} \delta V_G \quad A_v$$



Voltage gain A_v (dB)

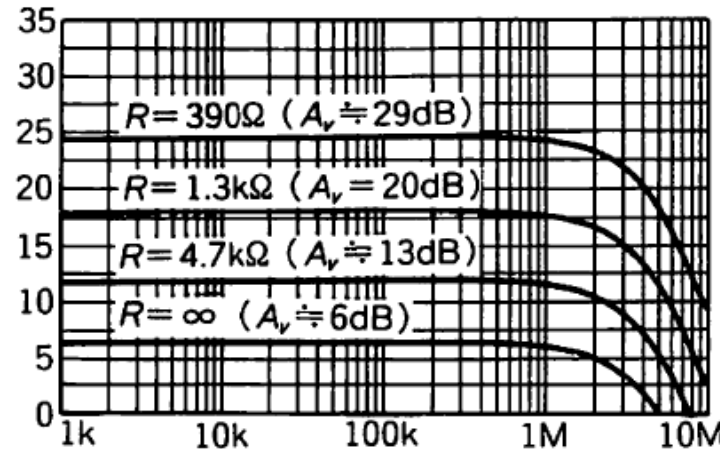


f (Hz)

Simulation by LTSpice

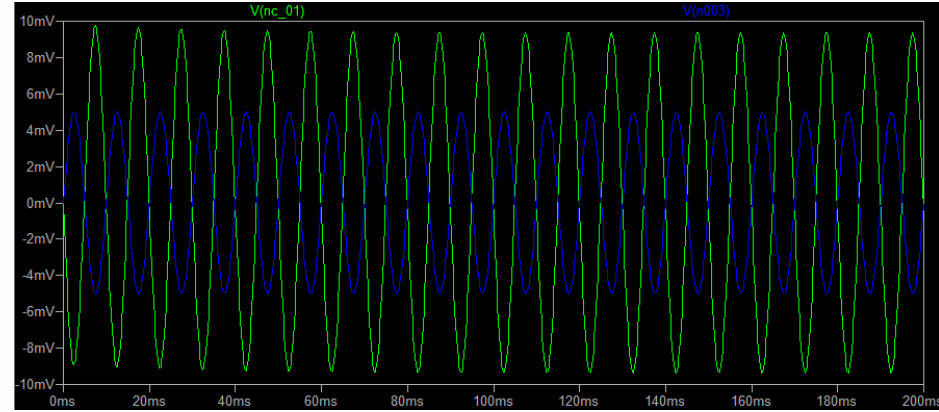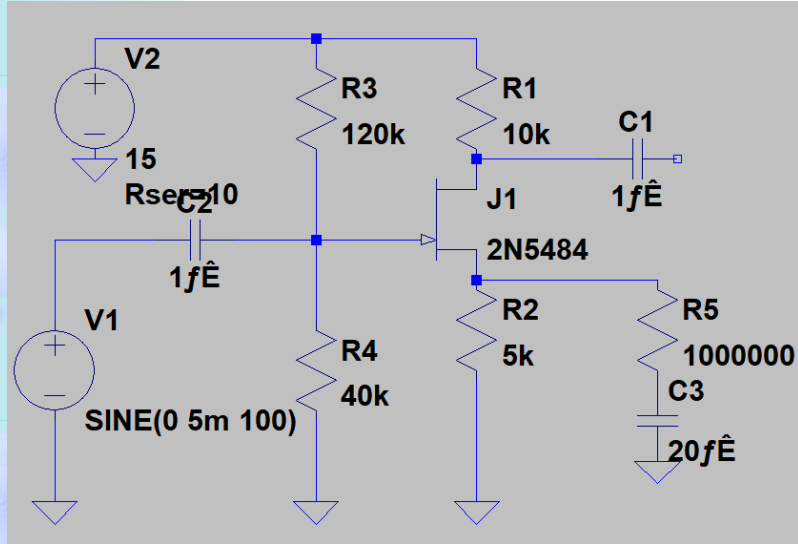
$$R_5 = 1 \times 10^6 \Omega \quad A_V \approx 2$$




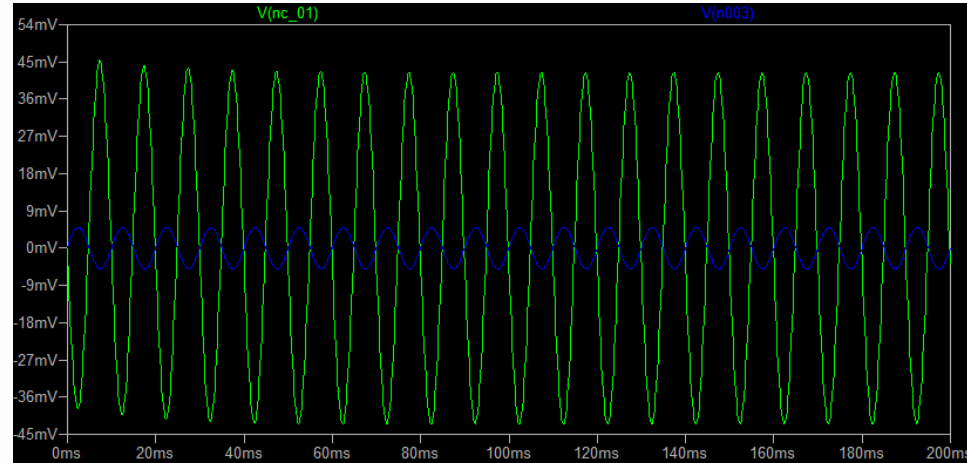
$$R_5 = 1 \times 10^3 \Omega \quad A_V \approx 9$$





Metal-Semiconductor (MES) FET

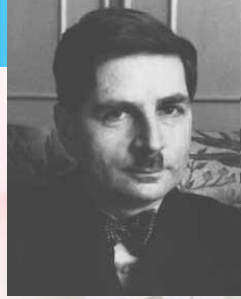


Walter Schottky
1886-1976

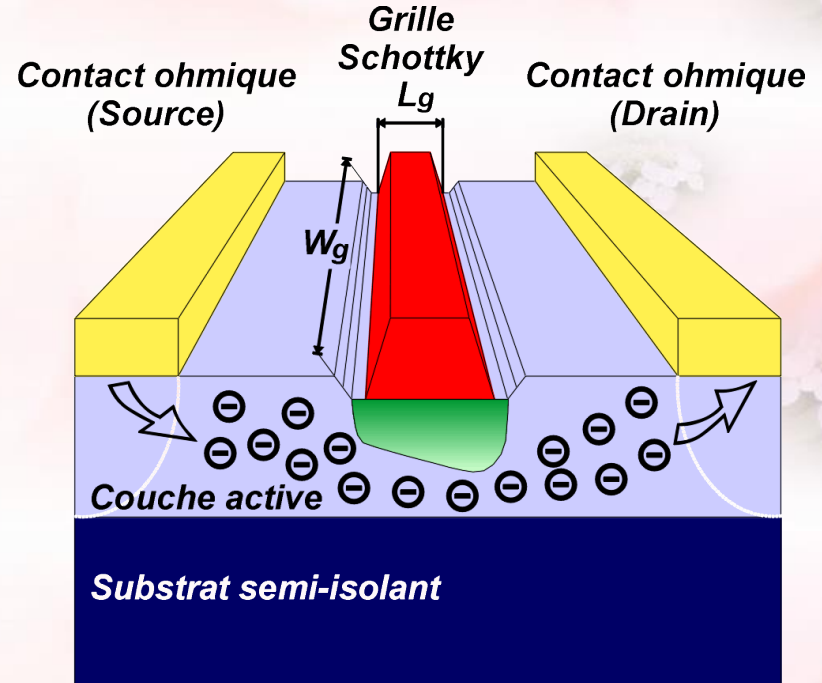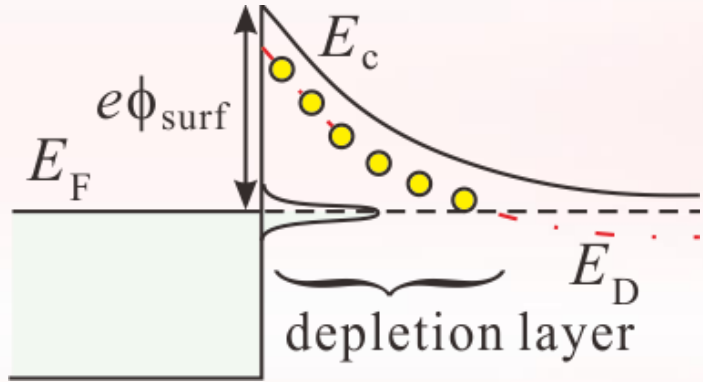

Metal-Oxide-Semiconductor (MOS) FET

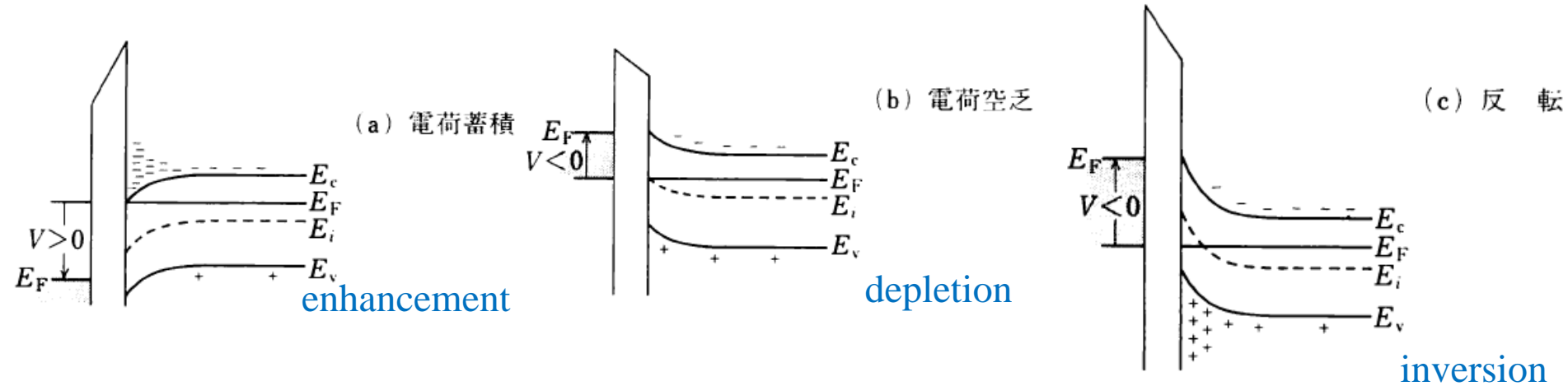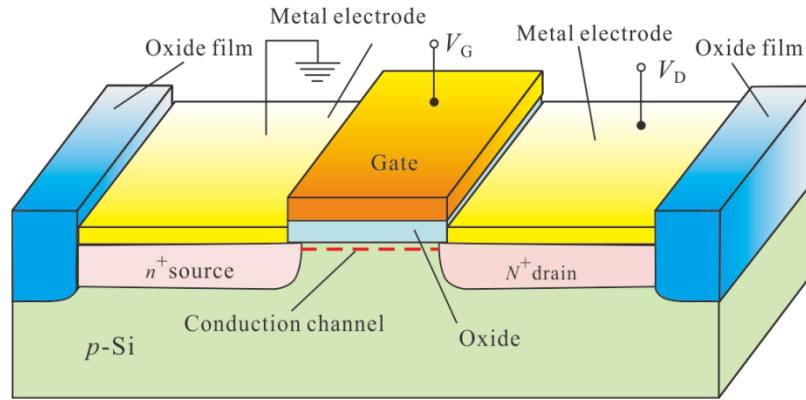


Complementary MOS logic gates

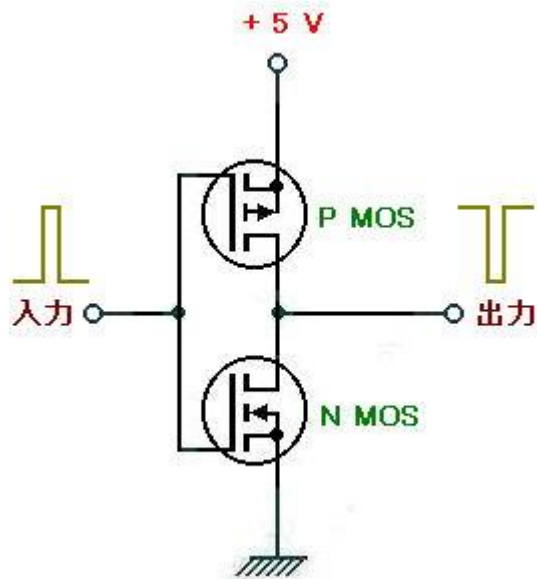

Simplified
CMOS inverter
circuit

Low leakage
current

Single gate input
both on/off switch

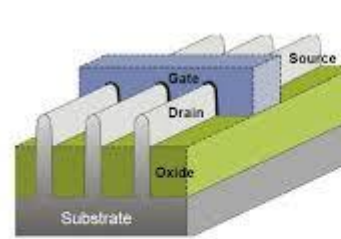

14-nm FinFET by UMC




14-nm FinFET by Intel

FinFET structure

MOSFET switching characteristics

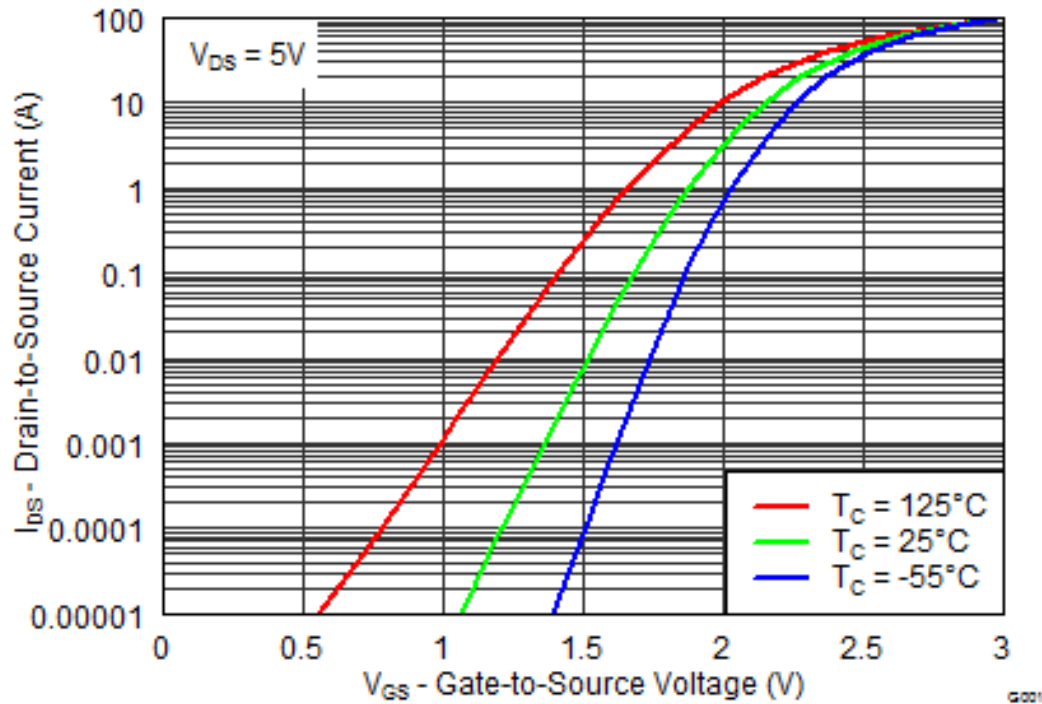From datasheet CSD87381P power MOSFET (Texas instr.).



More than 7 orders change in J_D within 3 V change of V_{GS} .

Summary of chapter 4 Amplification circuit

Feedback (feedforward) Transfer function diagram
Stability criteria

Operational amplifier

Elements for amplification Bipolar transistors (Semiconductor physics)
(non-linear treatment. Field effect transistors
Bias circuits + signal circuits.)

OP amp selection


BT input

High precision
Low voltage noise
Large power output

FET input

Low bias current/ High input
impedance
Low power consumption

Ch.5 Distributed constant circuits

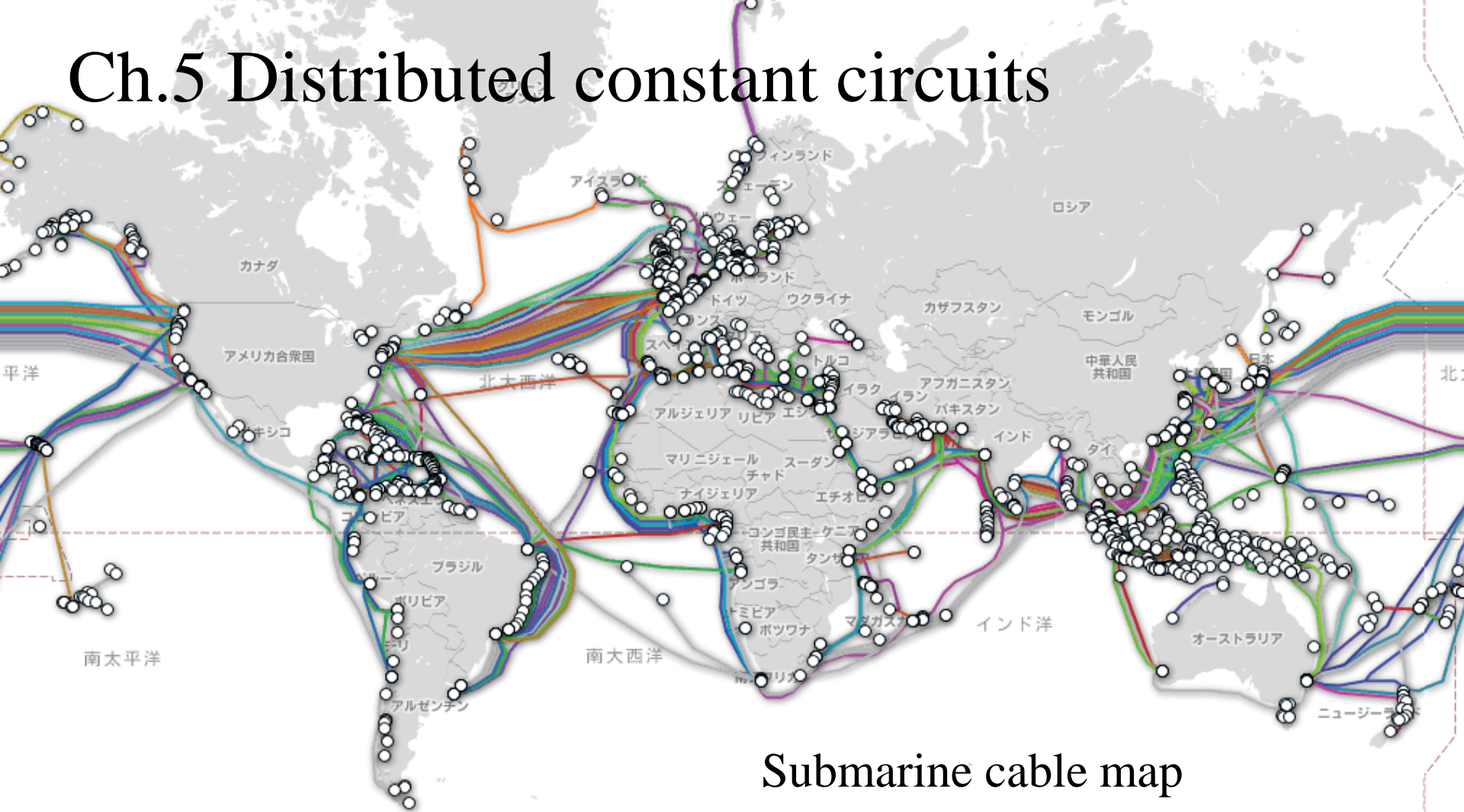


Submarine cable map

Distributed constant circuit concept

1. In what case we need to consider distributed constant circuits?

Characteristic sizes of devices \gtrsim wavelength of electromagnetic signal


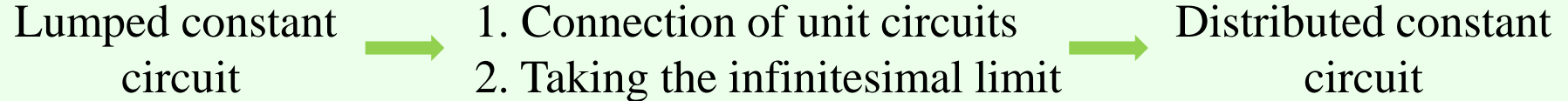
2. A typical scheme to make the shift for distributed circuit




3. Distributed constant circuits : transmission lines

Coaxial cables, Lecher lines, micro-strip lines, waveguides, optical fibers


5.1.1 Coaxial cable

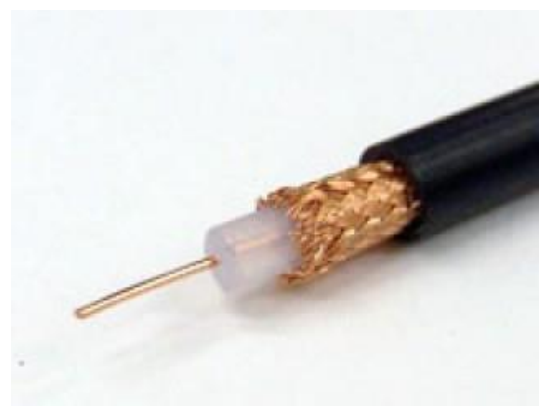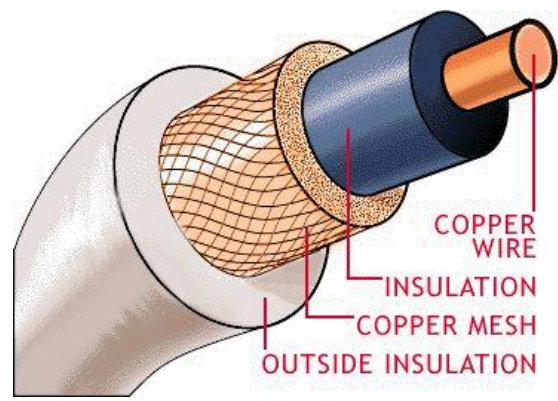

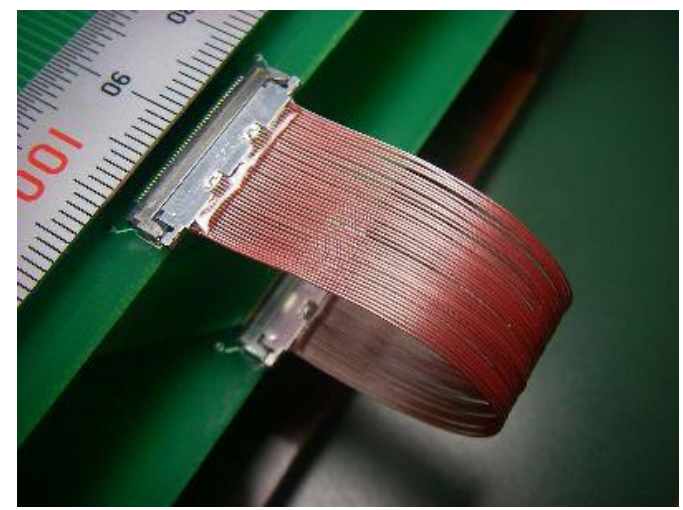Thin coaxial cable AWG50 ($\phi 25\mu\text{m}$)




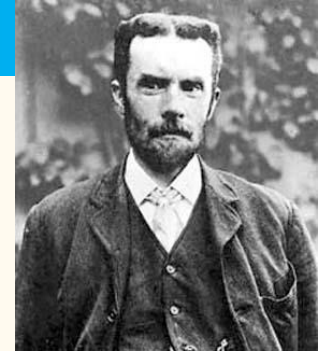Transmission line as a series of infinitesimal terminal-pairs




Oliver Heaviside
1850- 1925

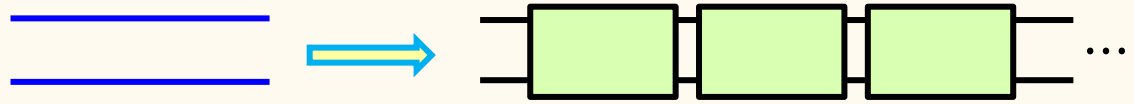Transmission line → divide into four terminal circuits



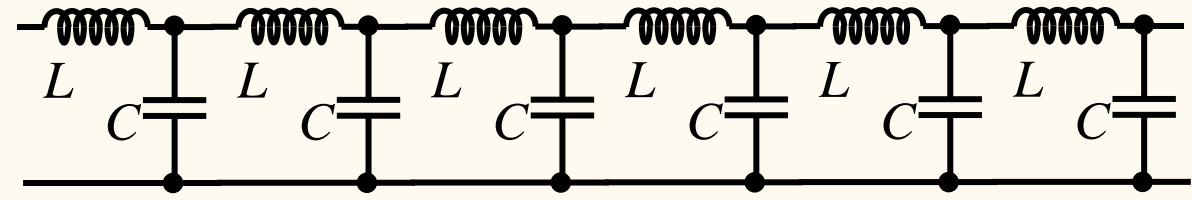Each unit should have delay. Ignore energy dissipation.




Then take the infinitesimal limit

Width → 0, Number → ∞

$$dV = -JZdx, \quad dJ = -VYdx$$

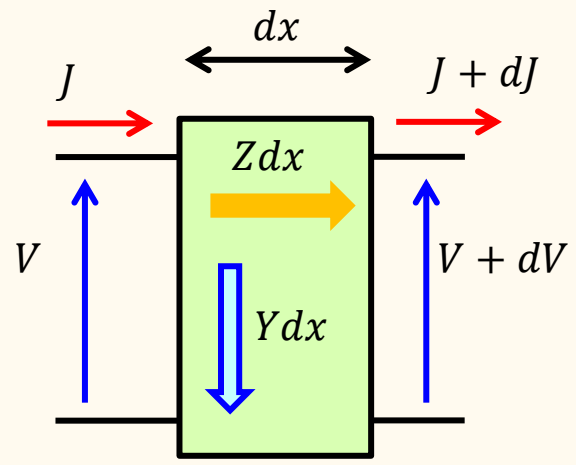Z, Y : Impedance, Admittance per unit length



Characteristic impedance

$$\frac{d^2 V}{dx^2} = YZV, \quad \frac{d^2 J}{dx^2} = YZJ \quad : \text{telegraphic equation}$$

$$J(x, t) = J(0, t) \exp(\pm \kappa x), \quad V(x, t) = V(0, t) \exp(\pm \kappa x) \quad \kappa \equiv \sqrt{YZ}$$

–: Progressive, +: Retrograde


Impedance: $\frac{V}{J} = \mp \frac{Z}{\kappa} = \mp \sqrt{\frac{Z}{Y}}$

Pure reactance $Y = i\omega C$, $Z = i\omega L$ for L and C model

$$\kappa = \sqrt{-\omega^2 LC} = i \frac{\omega}{\omega_0}, \quad \omega_0 \equiv \frac{1}{\sqrt{LC}} \quad (\text{physical dimension: velocity})$$

Characteristic impedance: $Z_0 = \sqrt{\frac{L}{C}}$

Maxwell theory for coaxial cable

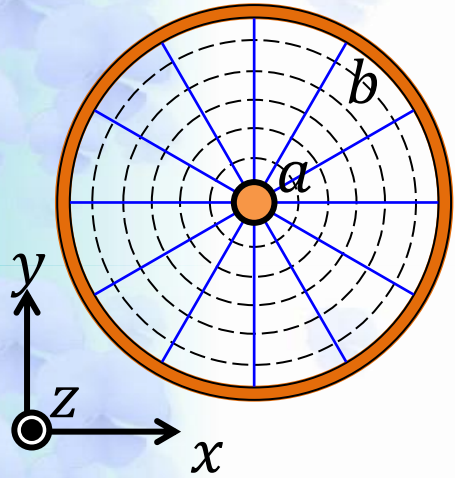

a : inner metal radius, b : radius of outer cylinder,
 ϵ : insulator dielectric constant, μ : magnetic permeability

$$E = E_0(x, y)e^{i\omega t - \gamma z}, \quad H = H_0(x, y)e^{i\omega t - \gamma z}$$

From Maxwell equations

$$(\omega^2 \epsilon \mu + \gamma^2) \begin{pmatrix} E_x \\ E_y \end{pmatrix} = \begin{pmatrix} -\gamma \partial_x & -i\omega \mu \partial_y \\ -\gamma \partial_y & i\omega \mu \partial_x \end{pmatrix} \begin{pmatrix} E_z \\ H_z \end{pmatrix},$$

$$(\omega^2 \epsilon \mu + \gamma^2) \begin{pmatrix} H_x \\ H_y \end{pmatrix} = \begin{pmatrix} i\omega \mu \partial_y & -\gamma \partial_x \\ -i\omega \mu \partial_x & -\gamma \partial_y \end{pmatrix} \begin{pmatrix} E_z \\ H_z \end{pmatrix}.$$

In TEM (transverse electric and magnetic) mode: $E_z = H_z = 0$

For the fields along x and y to survive, $\omega^2 \epsilon \mu + \gamma^2 = 0 \quad \therefore \gamma = \pm i\omega \sqrt{\epsilon \mu}$

Propagation velocity $v = \frac{\omega}{\omega \sqrt{\epsilon \mu}} = \frac{1}{\sqrt{\epsilon \mu}}$

Maxwell theory for coaxial cable

In TEM mode: $\text{rot}_{xy} \mathbf{H} = 0$, $\text{rot}_{xy} \mathbf{E} = 0 \rightarrow$ potentials \mathcal{U} , \mathcal{V} are available.

That is $\mathbf{E} = \nabla_{xy} \mathcal{U} / \sqrt{\epsilon}$, $\mathbf{H} = \nabla_{xy} \mathcal{V} / \sqrt{\mu}$

$$\frac{\partial \mathcal{U}}{\partial x} = \frac{\partial \mathcal{V}}{\partial y}, \quad \frac{\partial \mathcal{U}}{\partial y} = -\frac{\partial \mathcal{V}}{\partial x} \quad \text{Cauchy-Riemann condition}$$

$f(w) = \mathcal{U} + i\mathcal{V}$ is an analytic function of $w = x + iy$

Characteristic impedance: $Z_0 = \frac{V}{J} = \frac{\mathcal{U}_a - \mathcal{U}_b}{J\sqrt{\epsilon}} \quad \mathcal{U}_{a,b} : \text{potential at } a, b$

This expression represents the equivalence of distributed constant circuit model and the Maxwell theory for coaxial cable.

Capacitance part

$$V = \frac{q}{\epsilon} \int_a^b \frac{dr}{2\pi r} = \frac{q}{2\pi\epsilon} \log \frac{b}{a} = \frac{q}{C} \quad \therefore C = \frac{2\pi\epsilon}{\log(b/a)}$$

Maxwell theory for coaxial cable

Inductance part

Core current J , shield current $-J$ $H(r) = \frac{J}{2\pi r}, \quad B(r) = \frac{\mu J}{2\pi r}$


Flux per length: $\Phi = \int_a^b dr B(r) = \frac{\mu J}{2\pi} \log \frac{b}{a}$

Self inductance per length: $L = \frac{\mu}{2\pi} \log(b/a)$



$$Z_0 = \sqrt{\frac{L}{C}} = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \log\left(\frac{b}{a}\right)$$

cf. Characteristic impedance of the vacuum $Z_0 = \sqrt{\frac{\mu_0}{\epsilon_0}} \approx 376\Omega$


Coaxial cable 2

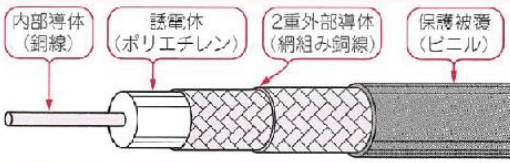

(a)

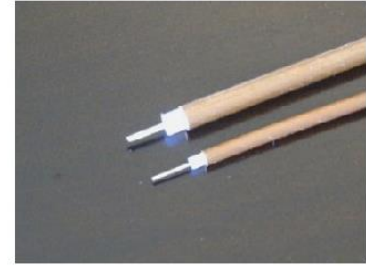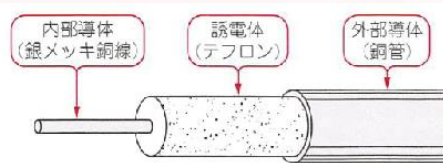

(b)

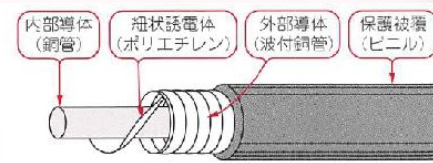

(c)

図12 同軸ケーブルの型名 (JIS C3501)



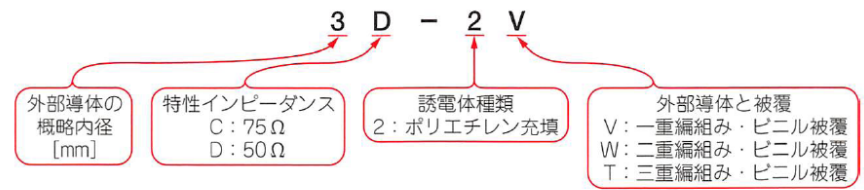


図13 MIL規格での同軸ケーブル型名の例

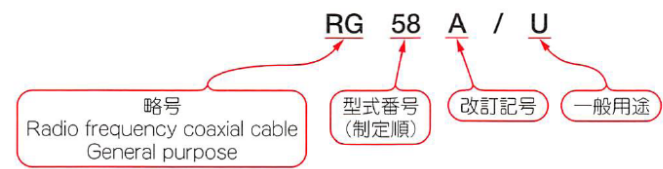

Coaxial connectors

図22 同軸コネクタの構造(概念図)

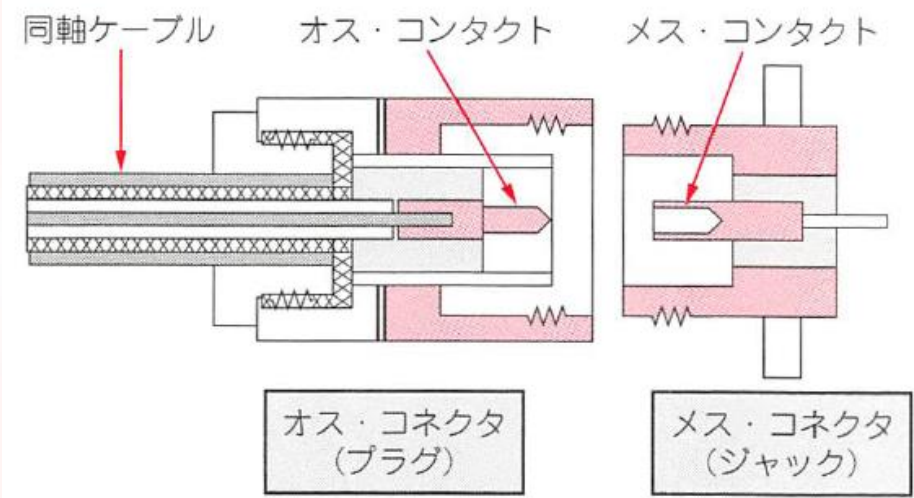

代表的な同軸コネクタの最高使用周波数例


形式	外部導体内径	最高使用周波数
BNC	約 7 mm	2 ~ 4 GHz
N	約 7 mm	10 ~ 18 GHz
7 mm	7 mm	~ 18 GHz
SMA	4.15 mm	18 GHz
3.5 mm	3.5 mm	26.5 GHz
K	2.92 mm	40 GHz
2.4 mm	2.4 mm	50 GHz
V	1.85 mm	65 GHz
W	1.1 mm	110 GHz
1.0 mm	1.0 mm	110 GHz

Coaxial connectors

写真2 N型コネクタ



(a) フランジ付きジャック

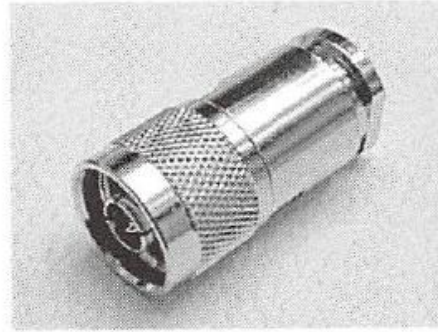


(b) プラグ




(c) プラグ[(b)を分解]


写真3 BNC型コネクタ

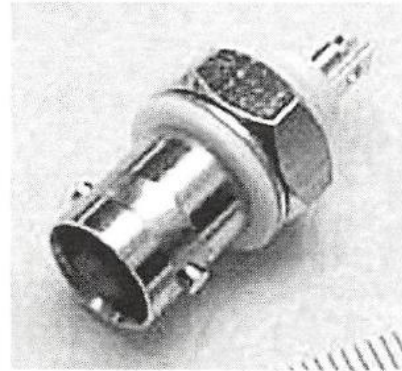

(a) 絶縁型ジャック
(高周波に向かない)

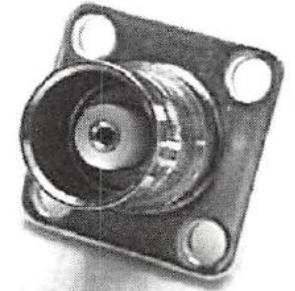

(b) フランジ付きジャック

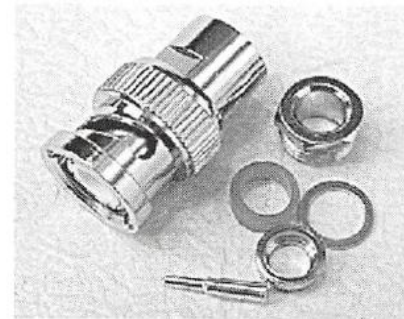


(c) プラグ

Coaxial connectors 2


SMA-type

写真4 SMA型コネクタ

jack

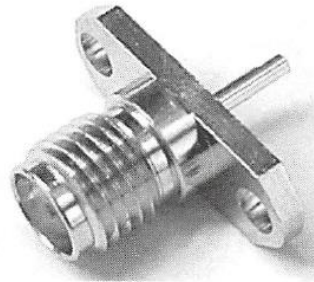

(a) ジャック

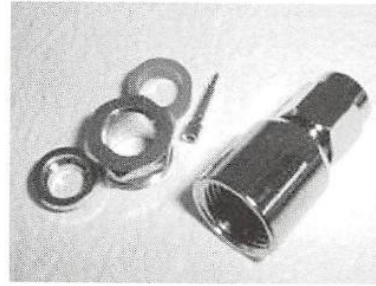


(b) プラグ


plug

K-type

写真6 K型コネクタ

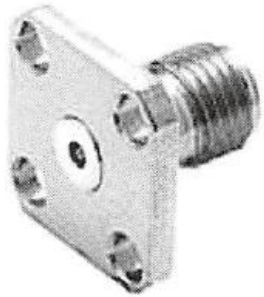


(a) ジャック

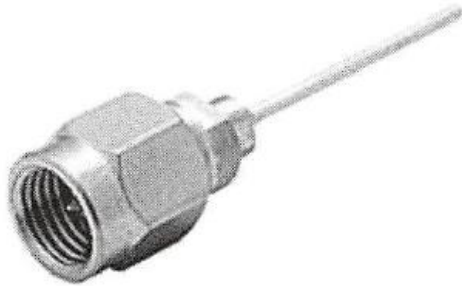


(b) プラグ

V-type

写真7 V型コネクタ

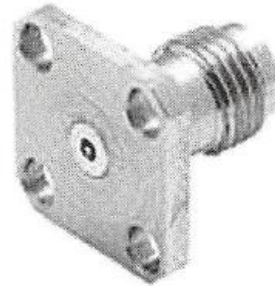

(a) ジャック

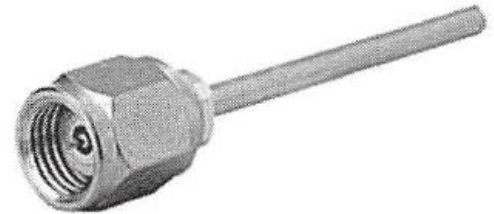

(b) プラグ

LEMO cables and connectors

MFBモデル



MSBモデル





<http://www.lemo.com/>


High-energy physics experiment,
etc.

Transmission lines with TEM mode

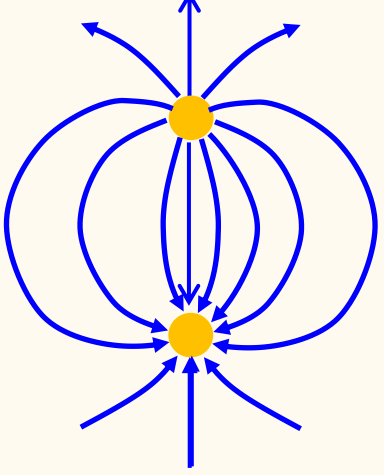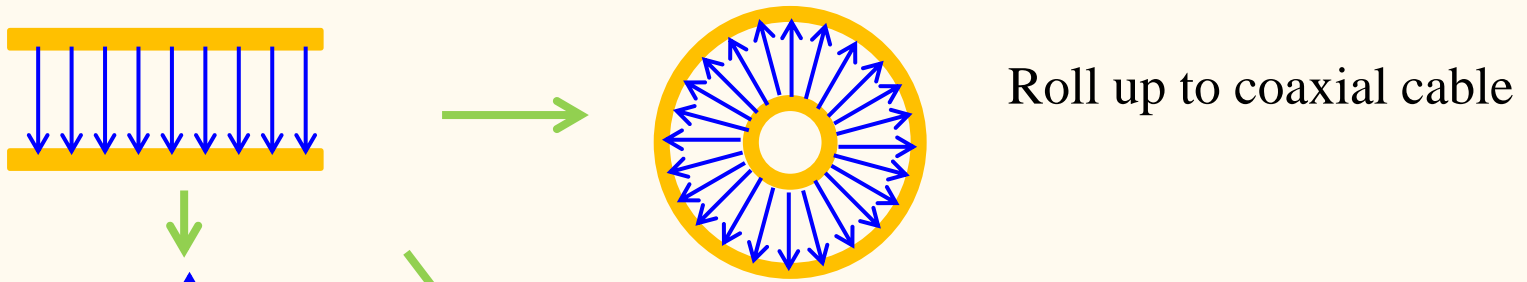Transmission lines with **two conductors** are “families”.
Electromagnetic field confinement with parallel-plate capacitor




Shrink to dipole (Lecher line)

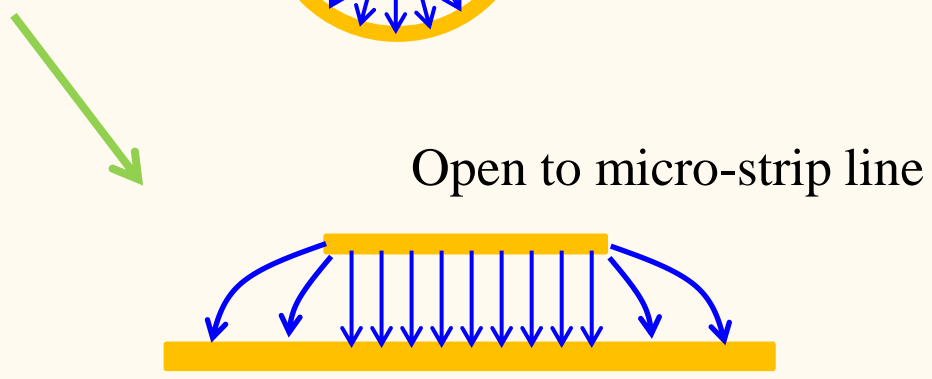


Commonly

TEM is the primary mode.

Lecher line

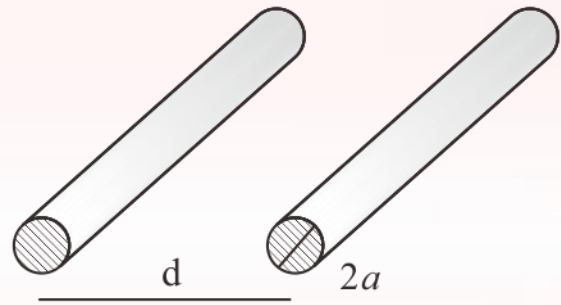

(a)

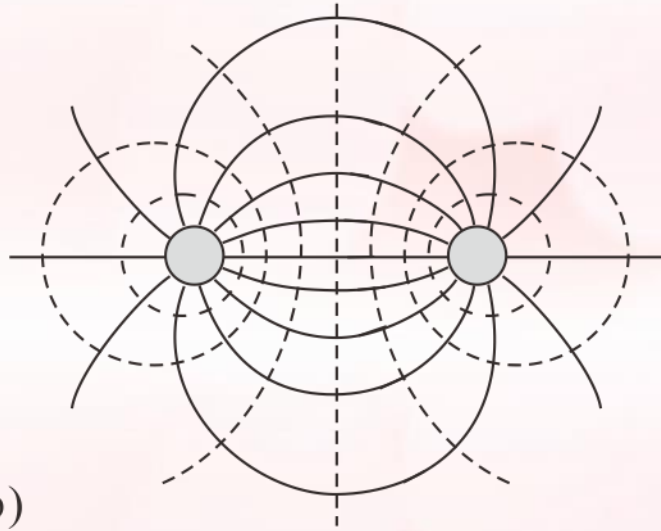


(b)




(c)

$$\phi_1 = -\phi_2 = \frac{J\sqrt{\mu}}{2\pi} \log \frac{d}{a} \qquad Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{1}{\pi} \log \frac{d}{a}$$


Micro strip line

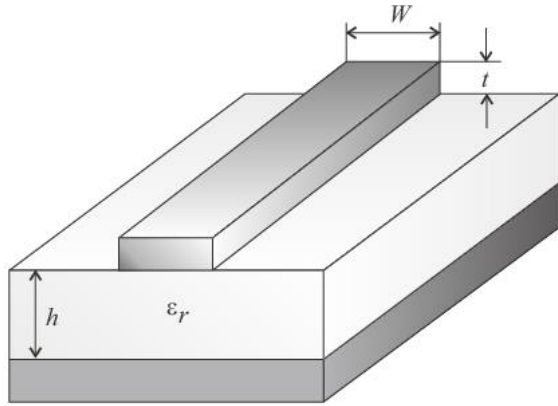

(a)

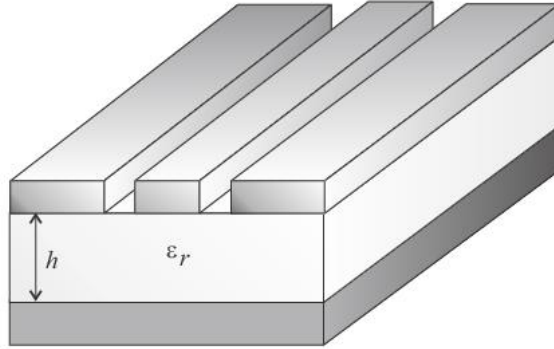

(b)

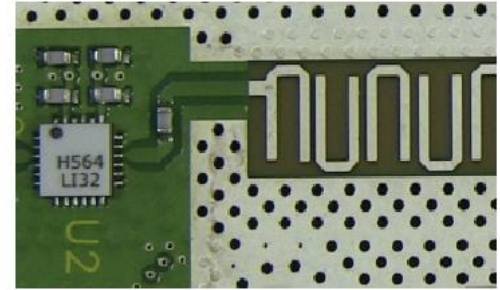

(c)


Wide ($W/h > 3.3$) strip

$$Z(W, h, \epsilon_r) = \frac{Z_{F0}}{2\sqrt{\epsilon_r}} \left\{ \frac{W}{2h} + \frac{1}{\pi} \log 4 + \frac{\epsilon_r + 1}{2\pi\epsilon_r} \log \left[\frac{\pi e}{2} \left(\frac{W}{2h} + 0.94 \right) \right] \frac{\epsilon_r - 1}{2\pi\epsilon_r^2} \log \frac{e\pi^2}{16} \right\}^{-1}$$

Narrow ($W/h < 3.3$) strip

$$Z(W, h, \epsilon_r) = \frac{Z_{F0}}{\pi\sqrt{2(\epsilon_r + 1)}} \left\{ \log \left[\frac{4h}{W} + \sqrt{\left(\frac{4h}{W} \right)^2 + 2} \right] - \frac{1}{2} \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(\log \frac{\pi}{2} + \frac{1}{\epsilon_r} \log \frac{4}{\pi} \right) \right\}$$

Waveguide

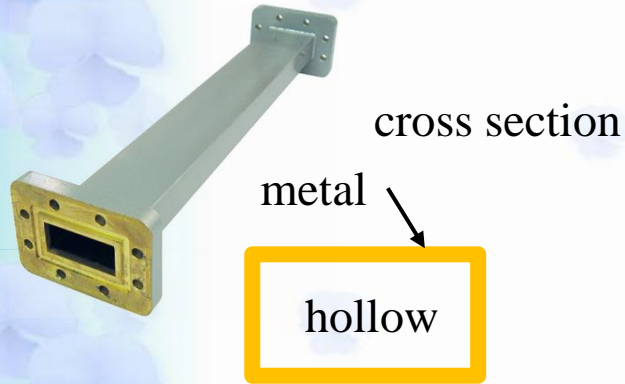

Electromagnetic field is confined into a simply-connected space.



TEM mode cannot exist.

Maxwell equations give


$$\left[\frac{\partial^2}{\partial x^2} + \frac{\partial^2}{\partial y^2} \right] E_z = -(\omega^2 \epsilon \mu + \gamma^2) E_z,$$

$$\left[\frac{\partial^2}{\partial x^2} + \frac{\partial^2}{\partial y^2} \right] H_z = -(\omega^2 \epsilon \mu + \gamma^2) H_z.$$



Helmholtz equation

$E_z = 0$: TE mode,


$H_z = 0$: TM mode

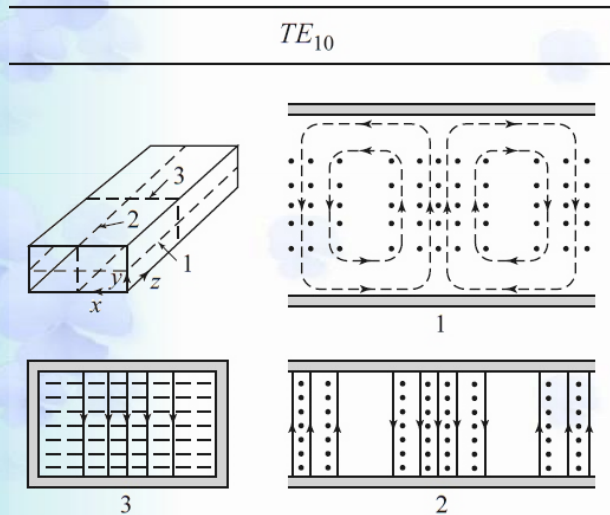


Optical fiber

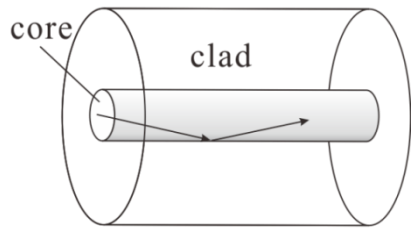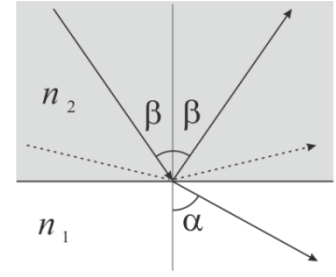

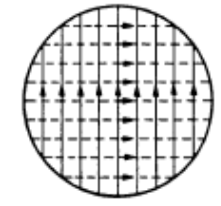
Difference in dielectric constant
step-type optical fiber




HE₁₁

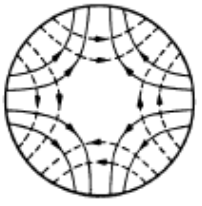

HE₂₁

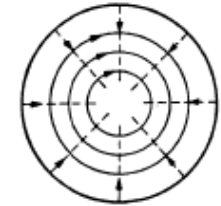


TE₀₁

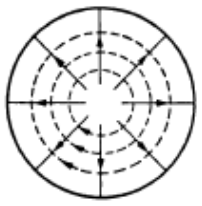


TM₀₁


no dispersion

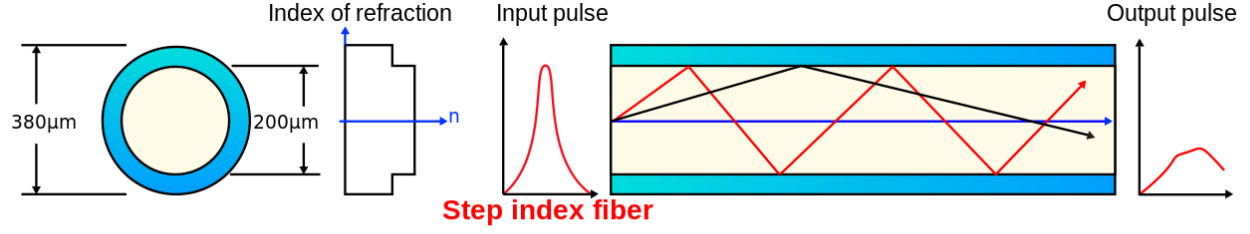

Step index fiber

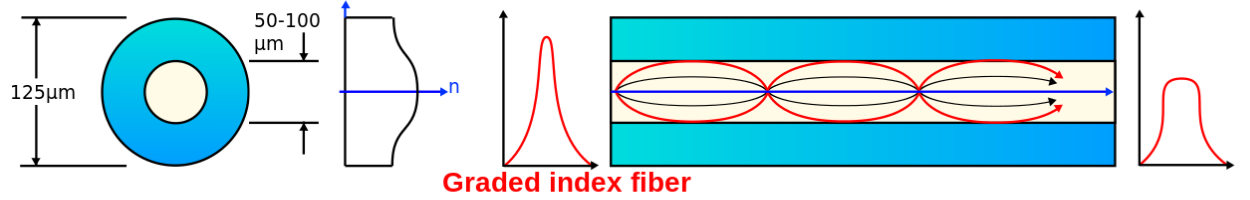


Graded index fiber

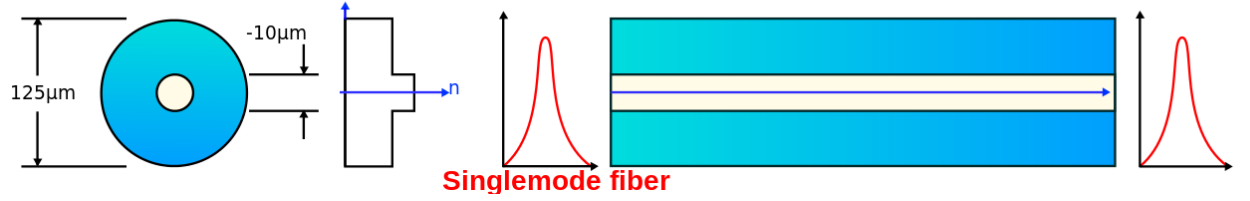

Singlemode fiber

Connection and termination

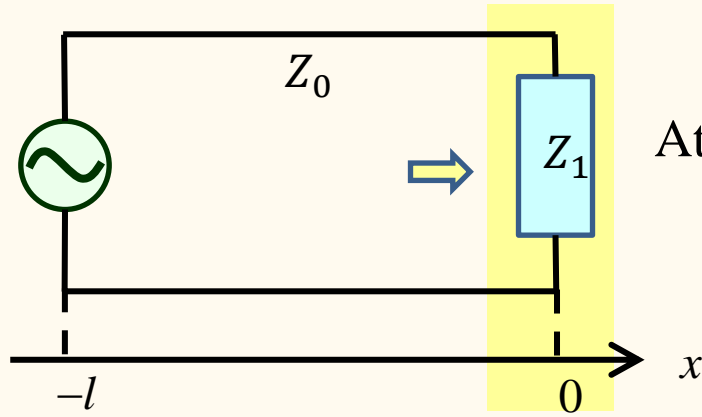

At $x = 0$:

$$J = \underbrace{J_+}_{\text{progressive}} + \underbrace{J_-}_{\text{retrograde}} \quad (\text{definition right positive})$$

$$V = V_+ + V_- = Z_0(J_+ - J_-)$$

$$Z_1 = \frac{V}{J} = \frac{J_+ - J_-}{J_+ + J_-} Z_0$$

Termination of a transmission line with length l and characteristic impedance Z_0 at $x = 0$ with a resistor Z_1 .

Reflection coefficient is $r = \frac{V_-}{V_+} = -\frac{J_-}{J_+} = \frac{Z_1 - Z_0}{Z_1 + Z_0}$

Comment: Sign of Ohm's law in transmission lines reflects direction of waves (depends on the definitions).


- $Z_1 = Z_0$: no reflection, *i.e.*, impedance matching
- $Z_1 = +\infty$ (open circuit end) : $r = 1$, *i.e.*, free end
- $Z_1 = 0$ (short circuit end) : $r = -1$, *i.e.*, fixed end

Connection and termination

Finite reflection \rightarrow Standing wave

Voltage-Standing Wave Ratio (VSWR):

$$\frac{1 + |r|}{1 - |r|}$$

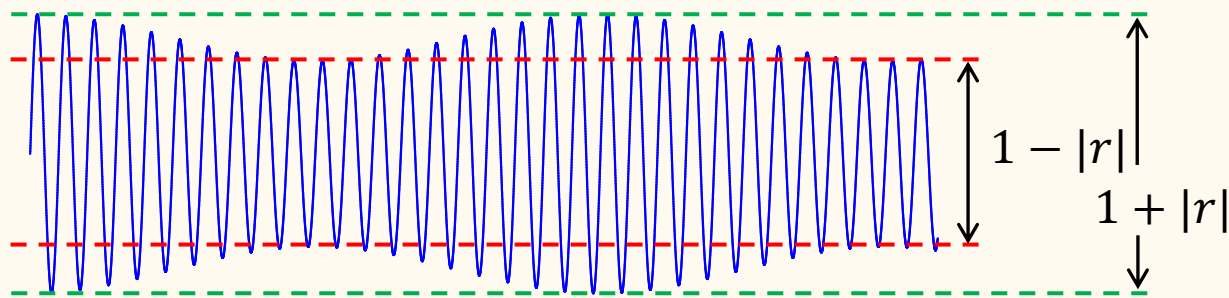

$$\left. \begin{aligned} \text{At } x = -l \quad V &= V_{+0} \exp(\kappa l) + V_{-0} \exp(-\kappa l) = [J_{+0} \exp(\kappa l) - J_{-0} \exp(-\kappa l)] Z_0 \\ J &= J_{+0} \exp(\kappa l) + J_{-0} \exp(-\kappa l) \end{aligned} \right\}$$


Then at $x = -l$ (at power source), the right hand side can be represented by

$$Z_l = \frac{V}{J} = \frac{J_{+0} e^{\kappa l} - J_{-0} e^{-\kappa l}}{J_{+0} e^{\kappa l} + J_{-0} e^{-\kappa l}} Z_0$$

Reflection coefficient:
$$r_l = \frac{V_-}{V_+} = \frac{V_{0-} \exp(-\kappa l)}{V_{0+} \exp(\kappa l)} = r \exp(-2\kappa l)$$

SWR measurement

SWR Meters:

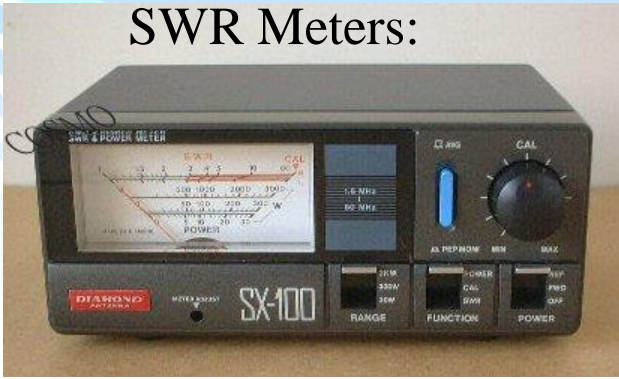


desktop types



cross-meter



handy type

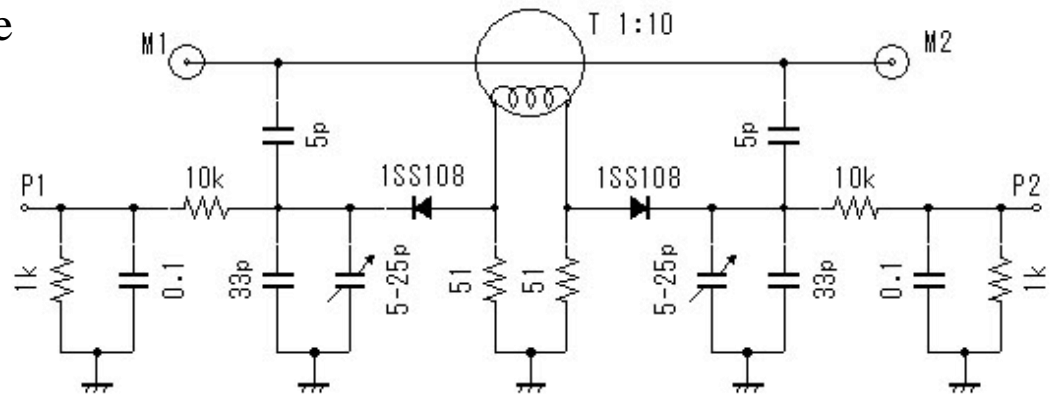

directional coupler