
電子回路論第9回 Electric Circuits for Physicists #9

東京大学理学部・理学系研究科 物性研究所 勝本信吾 Shingo Katsumoto

Outline


Various transmission lines Termination and connection Smith chart S-matrix (S-parameters)

An example FET power matching

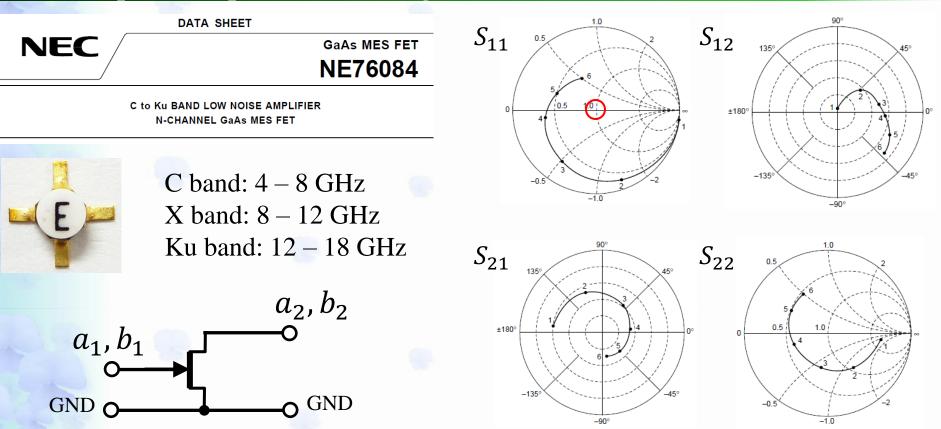

 S_{12} and S_{21} are normalized with some constants

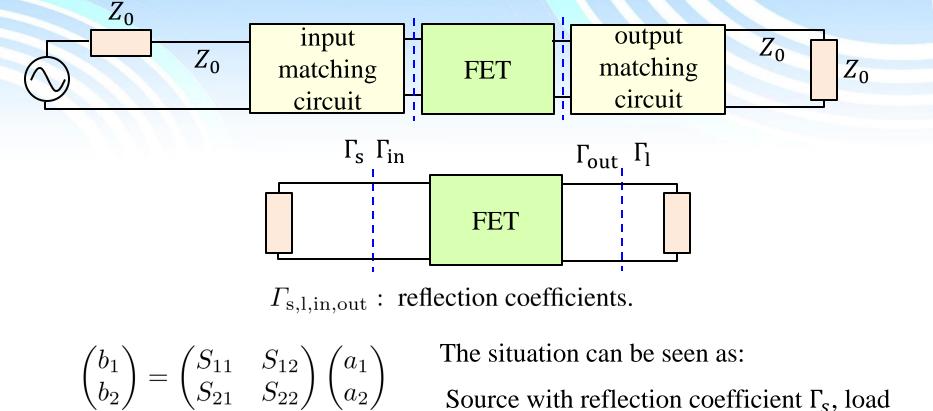S parameter representation and matching circuits



FET S-matrix

with reflection coefficient Γ_l are connected.

Power matching with S-parameters


That is
$$\Gamma_{s} \longrightarrow a_{1} \longrightarrow b_{2} \longrightarrow \Gamma_{l} \qquad \frac{a_{1}}{b_{1}} = \Gamma_{s}, \quad \frac{a_{2}}{b_{2}} = \Gamma_{l}$$

Then the total coefficients are $\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_{l}}{1 - S_{22}\Gamma_{l}}, \quad \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_{s}}{1 - S_{11}\Gamma_{s}}$
The power matching conditions are $\Gamma_{l} = \Gamma_{out}^{*}, \quad \Gamma_{s} = \Gamma_{in}^{*}$
The quadratic equation gives $\Gamma_{s} = \frac{B_{1} \pm \sqrt{B_{1}^{2} - 4|M|^{2}}}{2M}, \quad \Gamma_{l} = \frac{B_{2} \pm \sqrt{B_{2}^{2} - 4|N|^{2}}}{2N}$
 $B_{1} = 1 + |S_{11}|^{2} - |S_{22}|^{2} - |\det S|^{2}, \quad B_{2} = 1 - |S_{11}|^{2} + |S_{22}|^{2} - |\det S|^{2}, \quad N = S_{22} - S_{11}^{*}\det S, \quad M = S_{11} - S_{22}^{*}\det S$

Then the problem is reduced to tune the passive circuits to Γ_s and Γ_l

A simplified way to make impedance matching

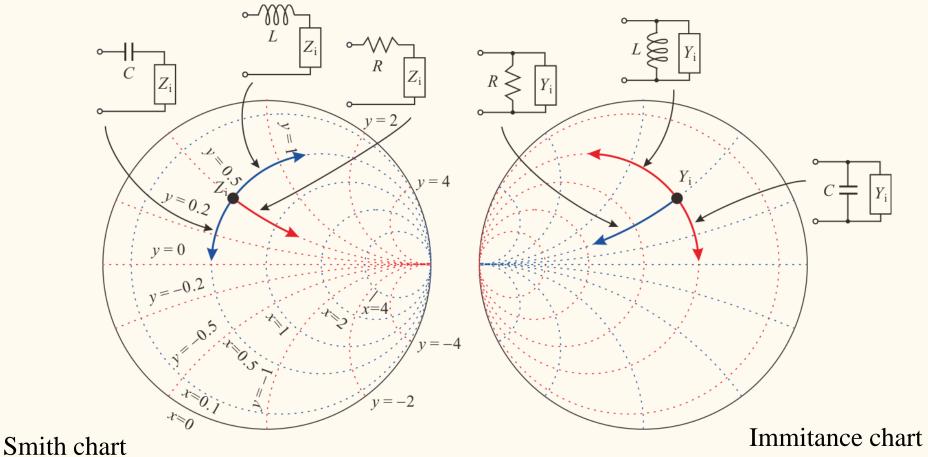Series and parallel connection of passive elements and traces on charts



6.1.2 Wiener-Khintchine theorem


Autocorrelation function $C(\tau) = \overline{\langle x(t)x(t+\tau) \rangle}$

$$= \overline{\sum_{n,m} \langle [a_n \cos \omega_n t + b_n \sin \omega_n t] [a_m \cos \omega_m (t + \tau) + b_m \sin \omega_m (t + \tau)] \rangle}$$
$$= \frac{1}{2} \sum_n \overline{\langle a_n^2 + b_n^2 \rangle} \cos \omega_n \tau = \sum_n \overline{\langle \mathscr{P}_n \rangle} \cos \omega_n \tau$$
$$= \int_0^\infty G(\omega) \cos \omega \tau \frac{d\omega}{2\pi}$$

$$C(\tau) = \int_0^\infty G(\omega) \cos \omega \tau \frac{d\omega}{2\pi}$$
$$G(\omega) = 4 \int_0^\infty C(\tau) \cos \omega \tau d\tau$$


Wiener-Khintchine theorem

An example of impedance matching

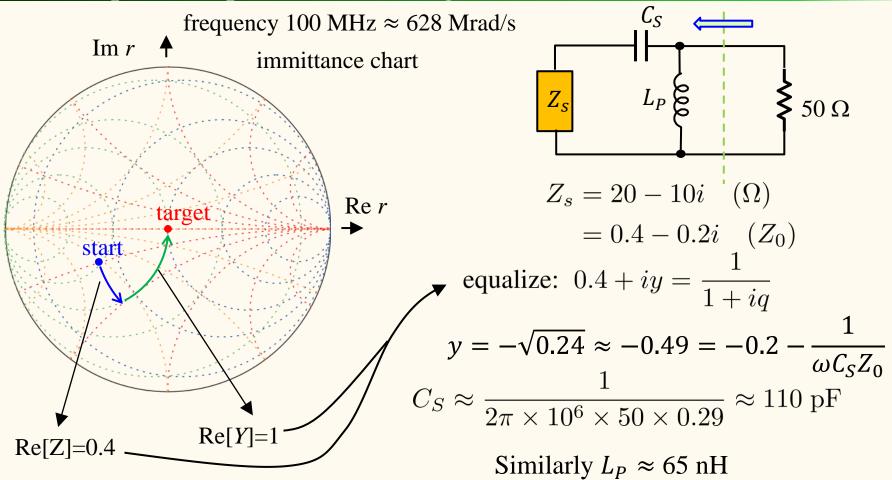


Introduction of useful freeware Smith v4.0 (present version 4.1)


http://fritz.dellsperger.net/smith.html

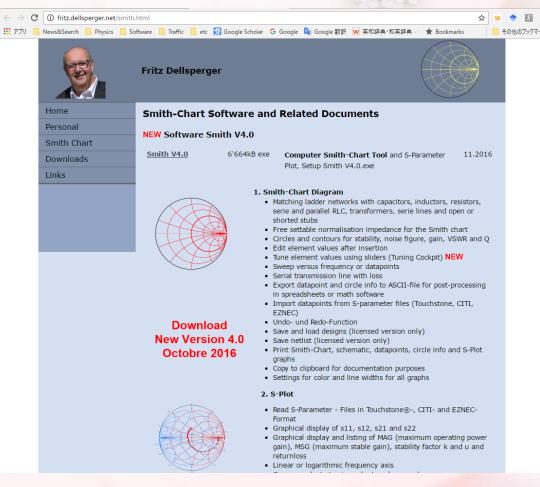

Impedance matching with Smith v4 (1)

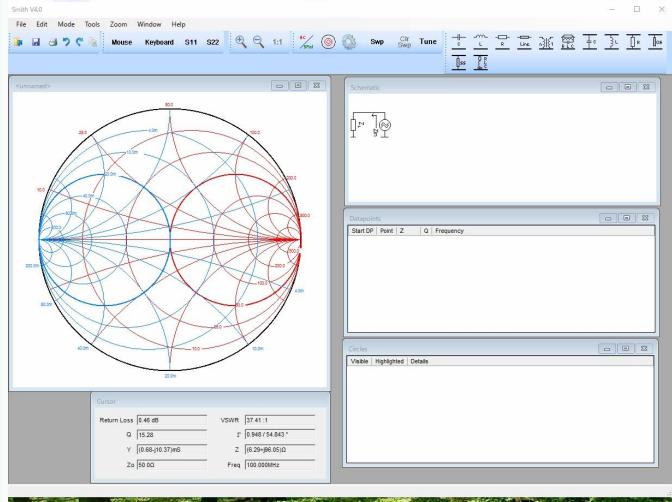

Impedance matching with Smith V4 (2)

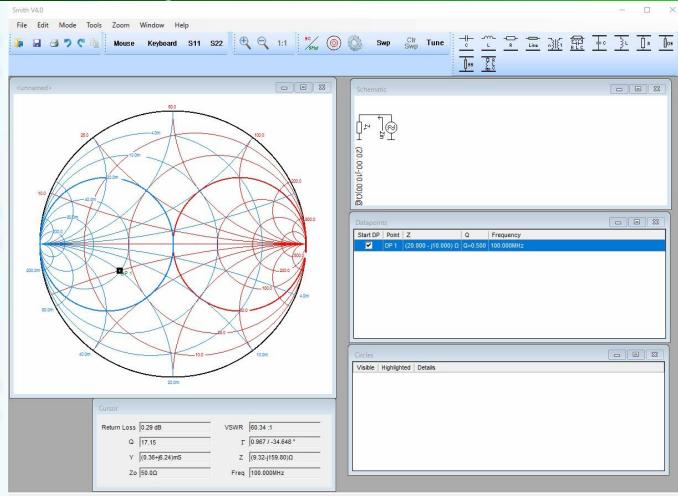

Introduction of useful freeware Qucs 0.0.19



Latest News

Latest stable release: 0.0.19	Official SourceForge repository
Source	GitHub Mirror
Windows Ubuntu OS X	<u>Qucs Wiki</u>

22 January 2017 Released Qucs 0.0.19, News

- 18 September 2015 Publication "Ques: An introduction to the new simulation and compact device modelling features implemented in release 0.0.19/0.0.19Src2 of the popular GPL circuit simulator.", 13th MOS-AK Workshop, Graz.(A). The presentation slides by Mike Brinson are available <u>online</u>.
- 19 January 2015 Enabled automatic generation and deployment of Doxygen source

Qucs: Quite Universal Circuit Simulator


http://qucs.sourceforge.net/


The Ques project was begun by Michael Margraf in Germany in 2004.

- Based on SPICE simulation language.
- Free but no restriction in the number of nodes, etc.
- Can read S-parameter files. Have Sparameter analysis options.
- In that sense, better than LTSpice.


Introduction of useful freeware Qucs 0.0.19

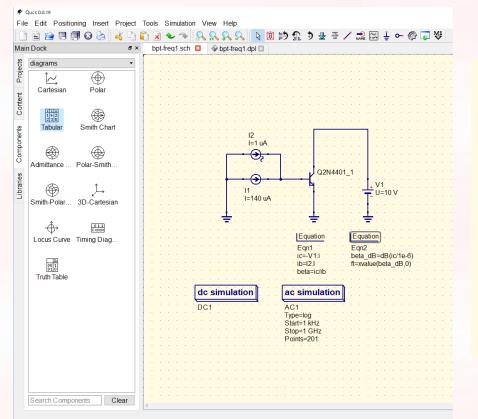Example: Frequency characteristics of a bipolar transistor




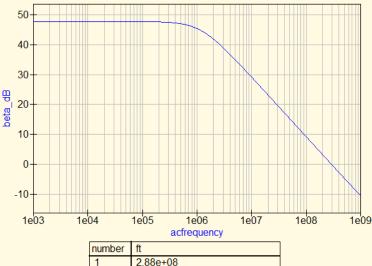

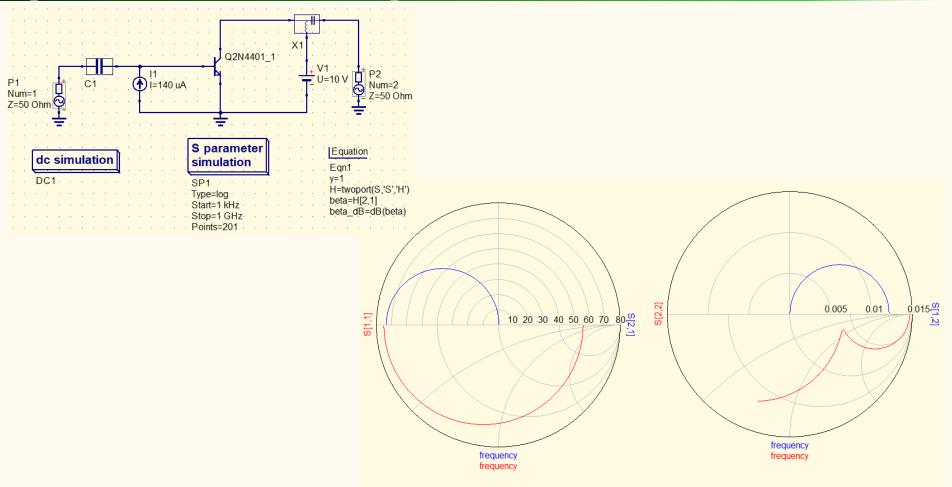S-parameter simulation of a bipolar transistor with Qucs



Simulation of matching circuit

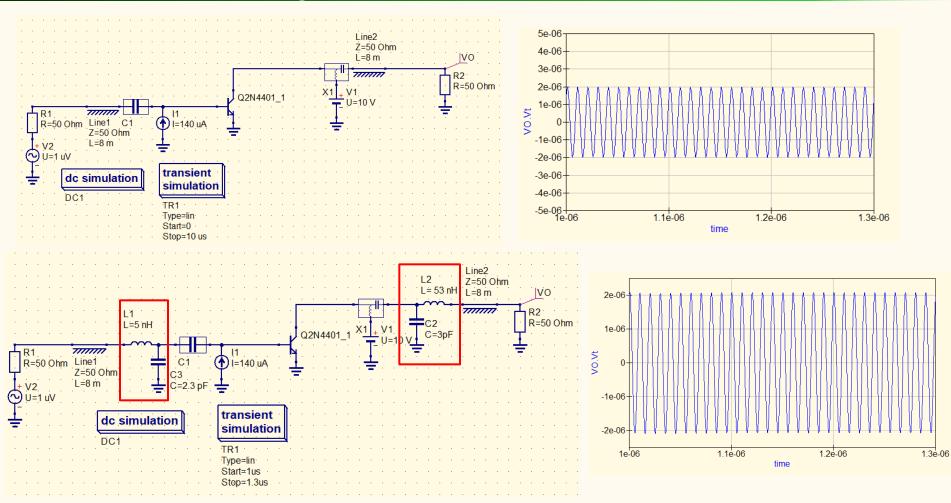

Propagation of a wave: Impedance match: complete absorption (propagation without reflection) Mismatch: wave reflection

Impedance match/mismatch is an important concept applicable to a broad area of physics.

> Antenna: should be matched to the vacuum.

EM wave propagation simulation: boundary is shunted with the characteristic impedance of vacuum.


- \blacktriangleright Optics: impedance mismatch \rightarrow disagreement in refractive index
- > Plasma: should be matched to electrodes for excitation.
- > Phonon impedance mismatch at low temperatures: Kapitza resistance
- > Sound insulated booth: should have sound impedance mismatch.

5.4 Non TEM mode transmission lines

LC model:
$$Z = i\omega L$$
,
 $Y = i\omega C$

The inductance represents magnetic fields circulating the core and the capacitance electric fields directing from the core to the shield.
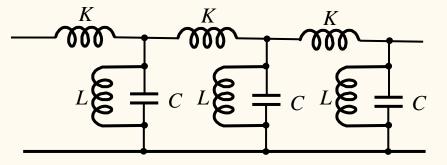
$$Z_0 = \sqrt{\frac{L}{C}}$$
 : real, dispersionless (linear ω -k relation)



C: capacitance per unit length*L*: inductance per inverse unit length*K*: inductance per unit length

Non-linear ω -term in Z or $Y \rightarrow$ dispersion (longitudinal components)

$$Y = i\omega C + \frac{1}{i\omega L}$$

5.4 Non TEM mode gives mass to the transmission mode

$$-k^{2} = YZ = \left(i\omega C + \frac{1}{i\omega L}\right)i\omega K = -CK\omega^{2} + \frac{K}{L}$$

Constant finite mass: $E = \hbar \omega \propto k^2$ (Schrodinger eq.: Parabolic partial differential equation) Coupling between linear dispersions: mass mechanism (*cf.* Higgs)

$$\frac{1}{\sqrt{LC}} = \omega_0 \text{ unchanged with } dx \to 0 \qquad Z = i\omega K, \quad Y = \frac{1 - (\omega/\omega_0)^2}{i\omega L} \text{ then}$$

$$\hbar\omega_0 = m^* c^{*2} \qquad \omega \qquad ik = \kappa = \sqrt{YZ} = i\sqrt{\frac{K}{L}\left[\left(\frac{\omega}{\omega_0}\right)^2 - 1\right]}$$

$$ik = \kappa = \sqrt{YZ} = i\sqrt{\frac{K}{L}\left[\left(\frac{\omega}{\omega_0}\right)^2 - 1\right]}$$

$$k = \eta\sqrt{(\omega/\omega_0)^2 - 1}, \quad \eta^2 \equiv (K/L)$$

5.4 Non TEM mode gives mass to the transmission mode

 $\hbar\omega_0 = m^* c^{*2}$

ω

 ω_0

 $\omega = c^* k$


k

$$\omega \gg \omega_0 \to k \sim \eta \frac{\omega}{\omega_0}$$
 No dispersion
velocity $c^* = \frac{\omega}{k} = \frac{\omega_0}{\eta} = \frac{1}{\sqrt{KC}}$
 $\omega \sim \omega_0 \quad \omega = \omega_0 + \delta \omega \quad \to k^2 \approx 2\eta^2 \frac{\delta \omega}{\omega_0}$

$$\therefore \epsilon \equiv \hbar \delta \omega = \frac{\hbar k^2}{2(\eta^2/\omega_0)} = \frac{\hbar^2 k^2}{2m^*} \left(m^* \equiv \frac{\hbar \eta^2}{\omega_0} \right)$$

$$E_0 = \hbar\omega_0 = \frac{\hbar\eta^2}{\omega_0} \cdot \left(\frac{\omega_0}{\eta}\right)^2 = m^* c^{*2}$$

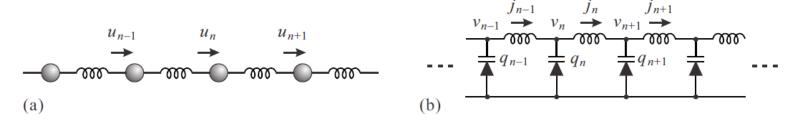5.5 Non-linear LC transmission line and Toda lattice




Toda lattice is a typical non-linear system with exact (soliton) solutions. It is defined as follows:


The springs in (a) have Toda-potential: $\phi(r) = \frac{a}{b}e^{-br} + ar$ (ab > 0)Equation of motion: $m\frac{d^2u_n}{dt^2} = -a\exp[-b(u_{n+1} - u_n)] + a\exp[-b(u_n - u_{n-1})]$ For relative shift $m\frac{d^2r_n}{dt^2} = a(2e^{-br_n} - e^{-br_{n+1}} - e^{-br_{n-1}})$

Force of a spring: $f = -\phi'(r) = a(e^{-br} - 1)$

Solitons in Toda lattice

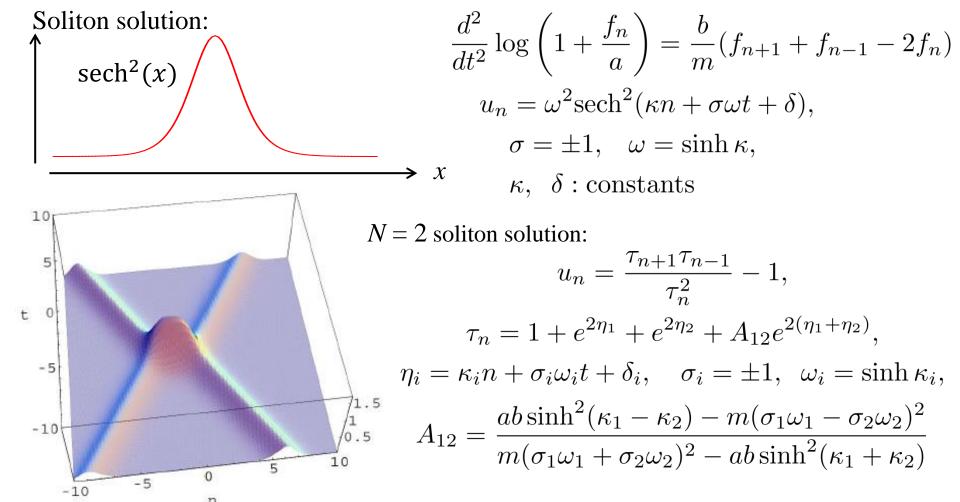

Non-linear capacitance: Varicap

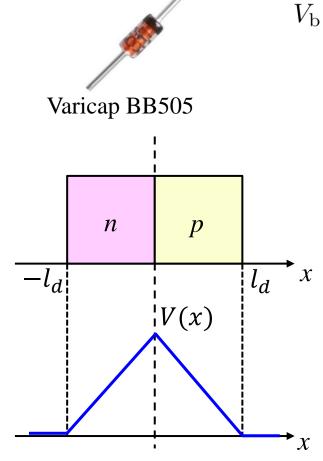

$$= \frac{en}{\epsilon} \int_{-l_d}^0 2(x+l_d) dx + \frac{en}{\epsilon} \int_0^{l_d} 2(l_d-x) dx = \frac{2enl_d^2}{\epsilon}$$
$$V + V_{\rm b} = \frac{2en}{\epsilon} \left(l_d + \frac{Q}{nS} \right)^2$$
$$\therefore C = \frac{dQ}{dV} = \sqrt{\frac{\epsilon}{2en}} \frac{nS}{\sqrt{V+V_{\rm b}}}$$
$$V + V_{\rm b} = V_0 + \delta V \quad \delta V \to V$$

L-Varicap transmission line

$$L\frac{dJ_n}{dt} = v_n - v_{n-1},$$

$$\frac{dq_n}{dt} = J_{n-1} - J_n,$$

$$q_n = \int_0^{v_n} C(V)dV, \quad C(V) = \frac{Q(V_0)}{F(V_0) + V - V_0}$$

$$q_n = Q(V_0) \log\left[1 + \frac{V_n}{F(V_0)}\right] + \text{const.}$$

$$\frac{d^2}{dt^2} \log\left[1 + \frac{V_n}{F(V_0)}\right] = \frac{1}{LQ(V_0)}(V_{n-1} + V_{n+1} - 2V_n)$$

Solitons in non-linear circuit


International Journal of Bifurcation and Chaos, Vol. 9, No. 4 (1999) 571–590 © World Scientific Publishing Company


CIRCUIT IMPLEMENTATIONS OF SOLITON SYSTEMS*


ANDREW C. SINGER Department of Electrical and Computer Engineering, University of Illinois, Urbana, IL 61801, USA

ALAN V. OPPENHEIM Department of Electrical Engineering, MIT, Cambridge, MA 02139, USA

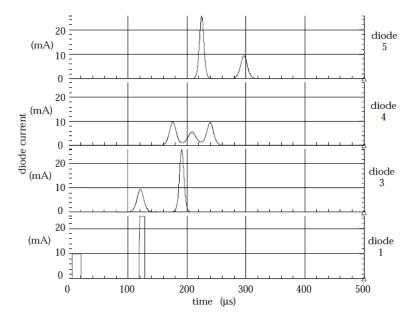Received May 27, 1998; Revised October 6, 1998



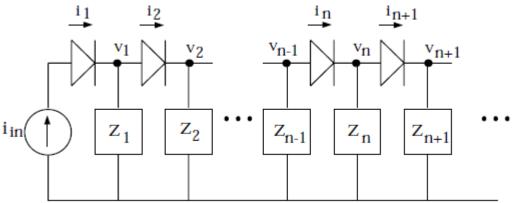

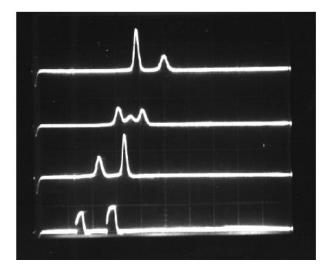

Toda lattice circuit, Soliton circuit


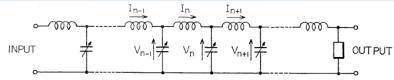


Fig. 1. A nonlinear network equivalent to a one-dimensional anharmonic lattice. The circuit elements have an inductance $L=22 \ \mu\text{H}$ or capacitance $C(V)=27 \ V^{-0.48} \text{ pF}$.

J. Phys. Soc. Japan 28 (1970) 1366~1367

Studies on Lattice Solitons by Using Electrical Networks

Ryogo HIROTA and Kimio SUZUKI

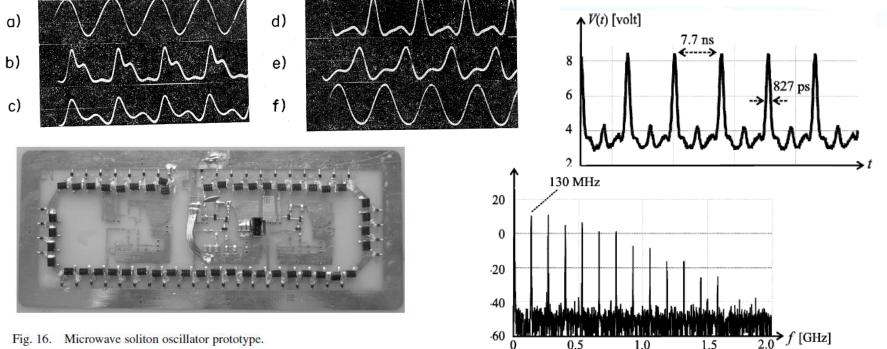

Ch.6 Noises and Signals

Chapter 6 Noises and Signals

Outline

6.1 Fluctuation 6.1.1 Fluctuation-Dissipation theorem 6.1.2 Wiener-Khintchine theorem 6.1.3 Noises in the view of circuits 6.1.4 Nyquist theorem 6.1.5 Shot noise 6.1.6 1/f noise 6.1.7 Noise units 6.1.8 Other noises

6.2 Noises from amplifiers6.2.1 Noise figure6.2.2 Noise impedance matching

Electric circuits transport 1) Information; 2) Electromagnetic power, on some physical quantities like voltages, current, ...

Noises: stochastic (uncontrollable, unpredictable by human) variation in other words, fluctuation in such a quantity.

Internal noise: Intrinsic noise: Thermal noise (Johnson-Nyquist noise), Shot noise Noise related to a specific physical phenomenon Avalanche, Popcorn, Barkhausen, etc. 1/f noise: Name for a group of noises with spectra 1/f.

External noise: EMI, microphone noise, etc.

6.1 Fluctuation

Quantity *x*, fluctuation $\delta x = x - \bar{x}$ $\overline{(\delta x)^2} = \overline{(x - \bar{x})^2} = \overline{x^2} - \bar{x}^2$ $(\overline{\delta x} = 0)$

g(x): distribution function of x

Fourier transform:
$$u(q) = \mathscr{F}\{g(x)\} = \int_{-\infty}^{\infty} g(x)e^{ixq}\frac{dx}{\sqrt{2\pi}}$$


u(q) : characteristic function of the distribution From Taylor expansion, *n*-th order moment can be obtained as

$$\overline{x^n} = \frac{\sqrt{2\pi}}{i^n} \left[\frac{d^n}{dq^n} u(q) \right]_{q=0}$$


Moments to high orders \rightarrow reconstruction of g(x)

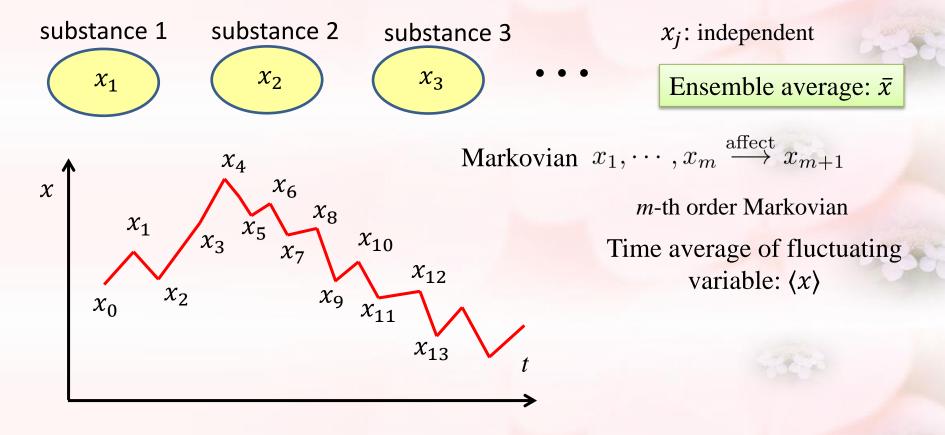
6.1 Fluctuation

In electric circuits we need to consider two kinds of averages:



Random process to distribution

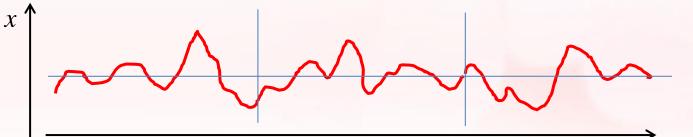

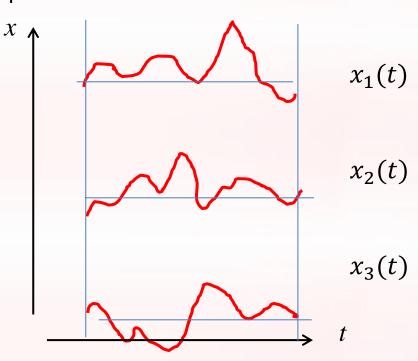

The averaging interval should be longer than m in m-th order Markovian.

1

Power spectrum

(Power)

Consider probability sets in the interval [0,T] with set index *j*.

$$\mathcal{P}_{jn} = (a_{nj}\cos\omega_n t + b_{nj}\sin\omega_n t)^2 \qquad \langle \mathcal{P}_n \rangle = \frac{1}{2} \langle a_n^2 + b_n^2 \rangle$$

: cross product terms are averaged out

Random process.

$$f(x) = \frac{1}{\sigma\sqrt{2\pi}} \exp\left[-\frac{x^2}{2\sigma^2}\right]$$

$$\overline{(\delta x)^2} = \sigma^2, \quad \overline{\left(\sum_{j=1}^m \delta x_j\right)^2} = m\sigma^2 \quad \text{Then} \quad \overline{\langle \mathscr{P}_n \rangle} = \sigma_n^2$$

Power spectrum $G(\omega)$

Frequency band width $\delta \omega$: separation between two adjacent frequencies

Power spectrum $G(\omega)$

Frequency band width $\delta \omega$: separation between two adjacent frequencies

$$\delta\omega = \omega_{n+1} - \omega_n = \frac{2(n+1)\pi}{T} - \frac{2n\pi}{T} = \frac{2\pi}{T}$$

$$G(\omega_n)\frac{\delta\omega}{2\pi} = \overline{\langle \mathscr{P}_n \rangle} \ (=\sigma_n^2)$$

$$\overline{\langle x^2(t) \rangle} = \sum_{n=1}^{\infty} \overline{\langle \mathscr{P}_n \rangle} \quad (\overline{x(t)} = 0)$$
$$= \sum_n G(\omega_n) \frac{\delta\omega}{2\pi} \to \int_0^\infty G(\omega) \frac{d\omega}{2\pi}$$

6.1.1 Fluctuation-Dissipation theorem



久保亮五 Ryogo Kubo 1920-1995



Harry Nyquist 1889-1976




Nobert Wiener 1894-1964



Aleksandr Khinchin 1894-1959

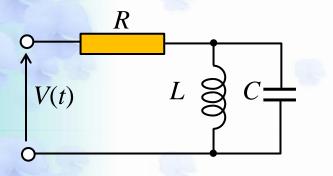Fluctuation-dissipation theorem in the language of circuit



$$\omega_0 \equiv 1/\sqrt{LC}$$

$$Z(i\omega) = \frac{R(\omega_0^2 - \omega^2) + i\omega_0^2 \omega L}{\omega_0^2 - \omega^2},$$

$$Y(i\omega) = \frac{\omega_0^2 - \omega^2}{R(\omega_0^2 - \omega^2) + i\omega_0^2 \omega L},$$

V(t) noise power spectrum $\rightarrow G_{v}(\omega)$

$$G_{\rm v}(\omega) = 4k_{\rm B}T{\rm Re}[Z(i\omega)] \qquad \text{Johnson-Nyquist noise} \\ = 4k_{\rm B}TR \qquad \text{Thermal noise}$$

White noise (noise with no frequency dependence) in the case of frequency independent resistance One of the representations for the fluctuation-dissipation theorem

6.1.2 Wiener-Khintchine theorem

Autocorrelation function

$$C(\tau) = \langle x(t)x(t+\tau) \rangle$$

= $\overline{\sum_{n,m}} \langle [a_n \cos \omega_n t + b_n \sin \omega_n t] [a_m \cos \omega_m (t+\tau) + b_m \sin \omega_m (t+\tau)] \rangle$
= $\frac{1}{2} \sum_n \overline{\langle a_n^2 + b_n^2 \rangle} \cos \omega_n \tau = \sum_n \overline{\langle \mathscr{P}_n \rangle} \cos \omega_n \tau$
= $\int_0^\infty G(\omega) \cos \omega \tau \frac{d\omega}{2\pi}$

$$C(\tau) = \int_0^\infty G(\omega) \cos \omega \tau \frac{d\omega}{2\pi}, \quad G(\omega) = 4 \int_0^\infty C(\tau) \cos \omega \tau d\tau$$

Wiener-Khintchine theorem