

電子回路論 第3回 2015年10月22日




Electric Circuit No.3  
2015.10.22  
Shingo Katumoto


# 4-terminal (2-terminal pair) circuits 4端子回路

Terminal pair (端子对)

Current: circulation, no net current

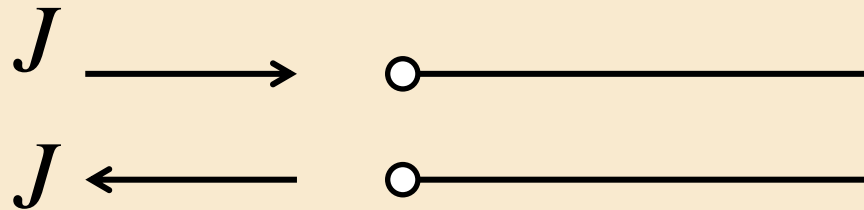


2-terminal pair (4-terminal) circuit

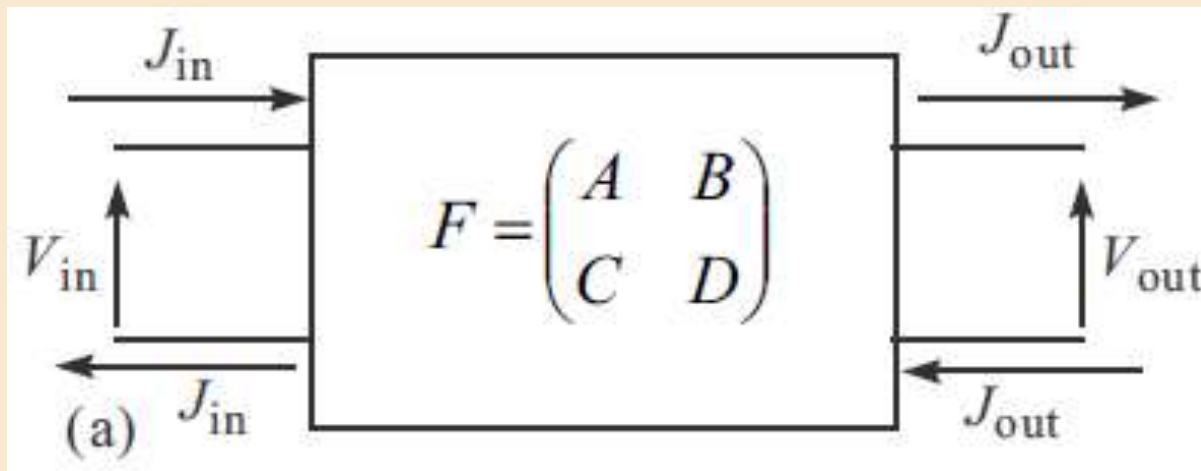

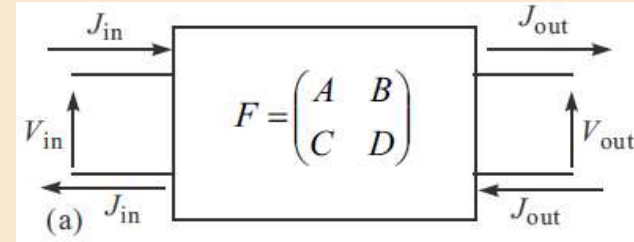
# F-matrix of 4-terminal circuit

$$\begin{pmatrix} V_{\text{in}} \\ J_{\text{in}} \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_{\text{out}} \\ J_{\text{out}} \end{pmatrix} \equiv F \begin{pmatrix} V_{\text{out}} \\ J_{\text{out}} \end{pmatrix}$$




$$A = \left( \frac{V_{\text{in}}}{V_{\text{out}}} \right)_{J_{\text{out}}=0}, \quad B = \left( \frac{V_{\text{in}}}{J_{\text{out}}} \right)_{V_{\text{out}}=0}, \quad C = \left( \frac{J_{\text{in}}}{V_{\text{out}}} \right)_{J_{\text{out}}=0}, \quad D = \left( \frac{J_{\text{in}}}{J_{\text{out}}} \right)_{V_{\text{out}}=0}.$$
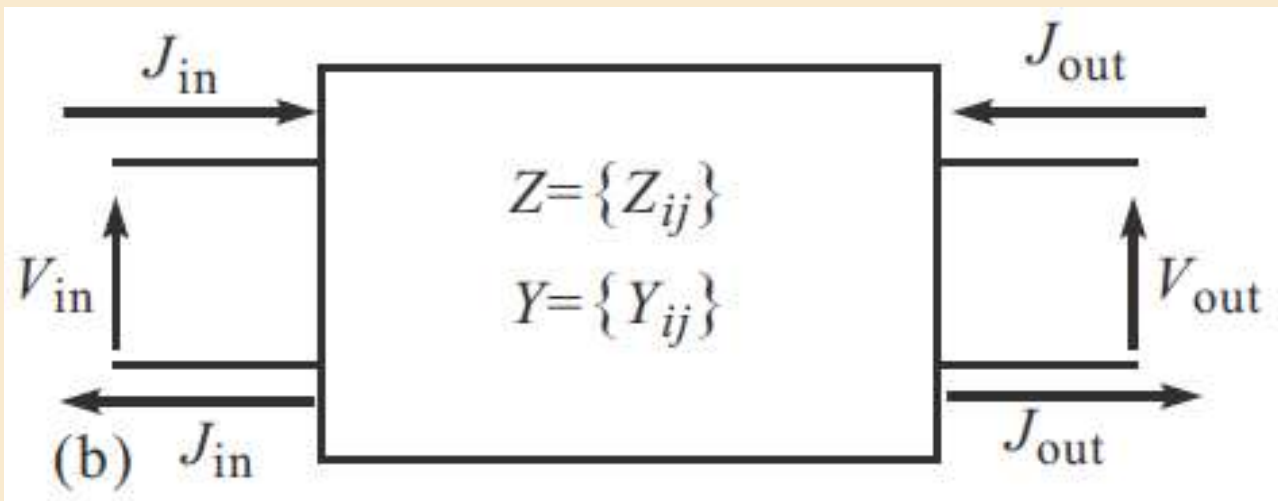
$$\begin{pmatrix} V_{\text{out}} \\ J_{\text{out}} \end{pmatrix} = \begin{pmatrix} K_{11} & K_{12} \\ K_{21} & K_{22} \end{pmatrix} \begin{pmatrix} V_{\text{in}} \\ J_{\text{in}} \end{pmatrix} \equiv K \begin{pmatrix} V_{\text{in}} \\ J_{\text{in}} \end{pmatrix}$$







# Impedance matrix, Admittance matrix

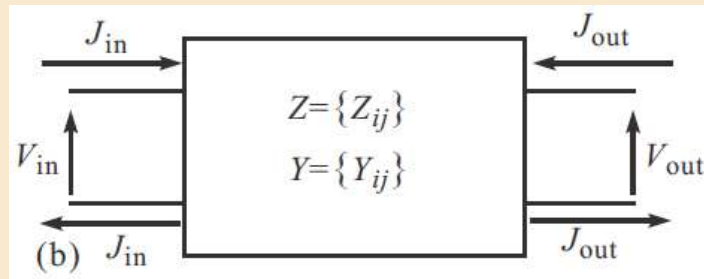


$$\begin{pmatrix} V_{in} \\ V_{out} \end{pmatrix} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} \begin{pmatrix} J_{in} \\ J_{out} \end{pmatrix} \equiv Z \begin{pmatrix} J_{in} \\ J_{out} \end{pmatrix}$$
$$\begin{pmatrix} J_{in} \\ J_{out} \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} V_{in} \\ V_{out} \end{pmatrix} \equiv Y \begin{pmatrix} V_{in} \\ V_{out} \end{pmatrix}$$

# Examples with impedances

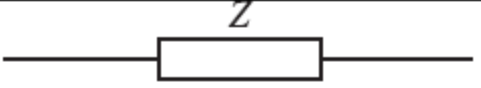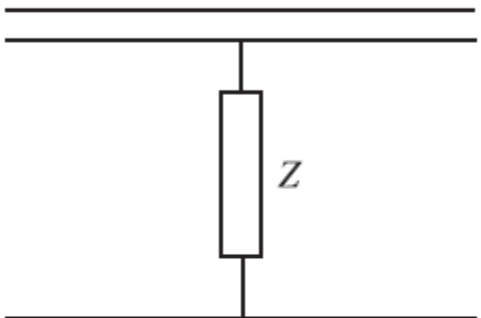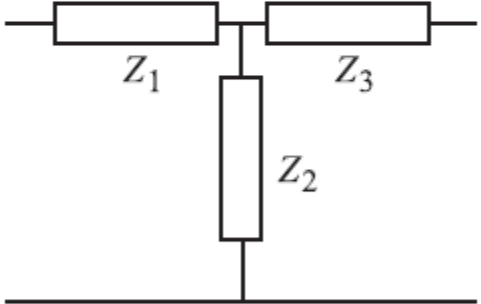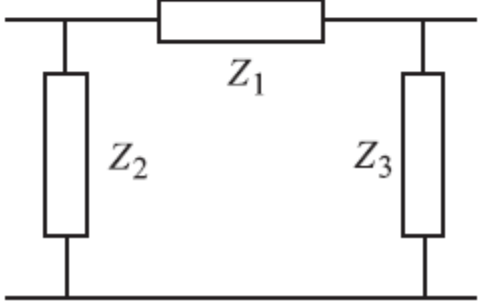	A	B	C	D
	1	$Z$	0	1
	1	0	$\frac{1}{Z}$	1
	$1 + \frac{Z_1}{Z_2}$	$\frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$	$\frac{1}{Z_2}$	$1 + \frac{Z_3}{Z_2}$
	$1 + \frac{Z_1}{Z_3}$	$Z_1$	$\frac{Z_1 + Z_2 + Z_3}{Z_2 Z_3}$	$1 + \frac{Z_1}{Z_2}$


# Connections of 4-terminal circuits

Cascade

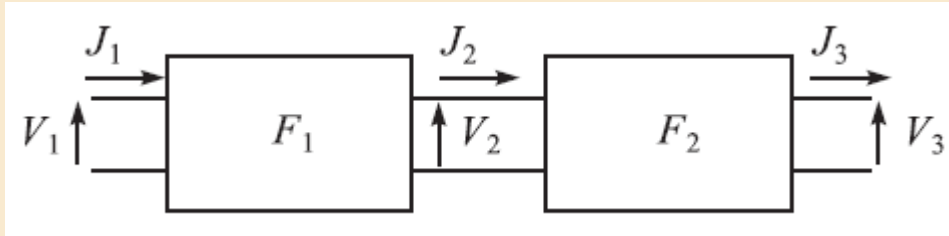


$$F_{\text{tot}} = \prod_{i=1}^N F_i$$

Series

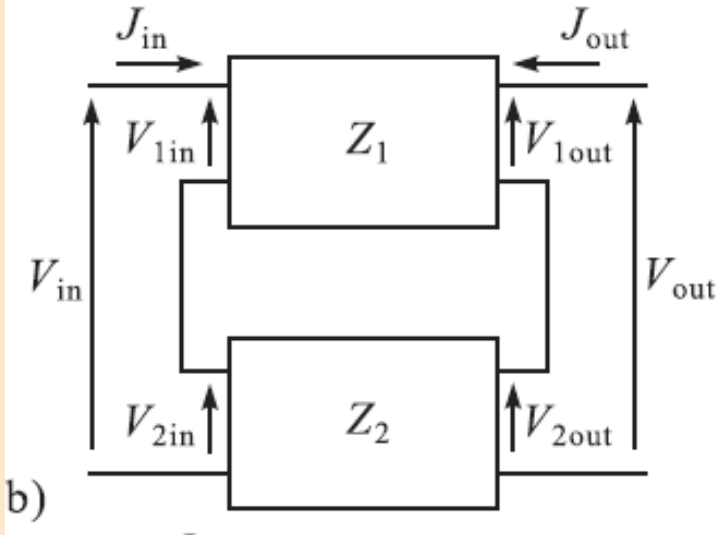

$$Z_{\text{tot}} = \sum_{i=1}^N Z_i$$


Parallel

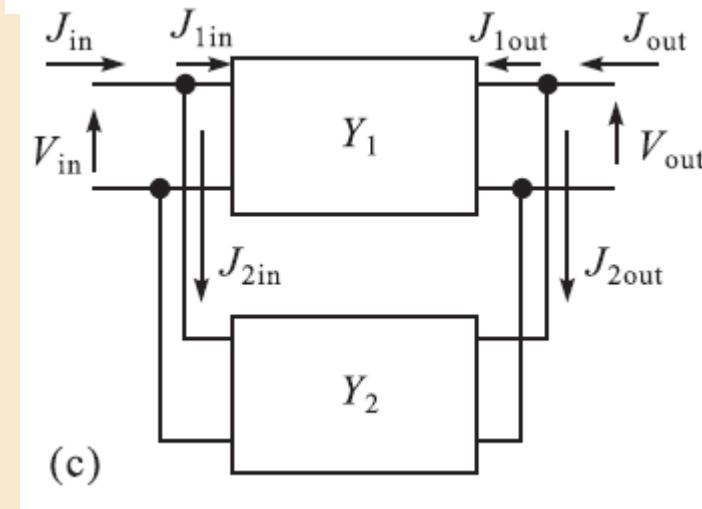


$$Y_{\text{tot}} = \sum_{i=1}^N Y_i$$

# Theorems for terminal-pair circuits


## Superposition theorem

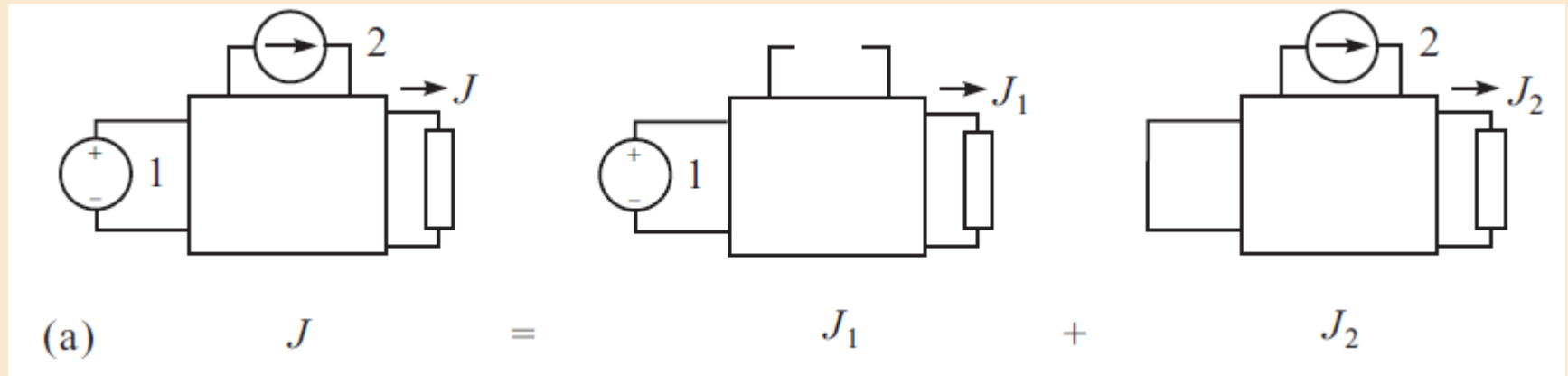

## Ho-Thevenin's theorem

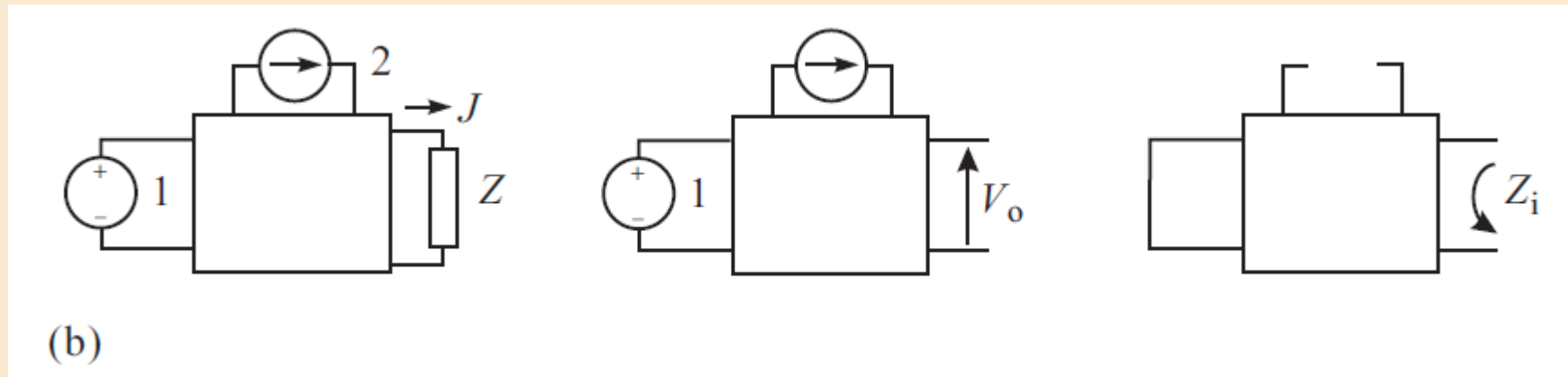

# Norton's theorem

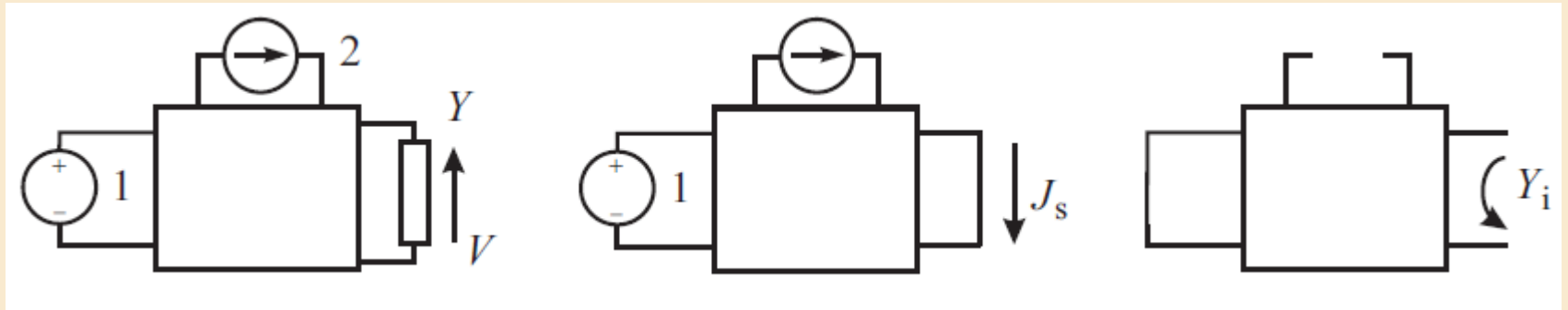

$$V = \frac{J_s}{Y + Y_i}$$



# Duality 双対性


直列接続	並列接続
開放	短絡
電場	磁場
キルヒホッフの第2法則	キルヒホッフの第1法則
電圧	電流
インピーダンス	アドミッタンス
抵抗	コンダクタンス
静電容量	インダクタンス
鳳-テブナンの定理	ノートンの定理

# Duality

Series	Parallel
Open	Short
Voltage	Current
Impedance	Admittance
Capacitance	Inductance
Electric field	Magnetic field
Resistance	Conductance
Ho-Thevenin	Norton
Kirchhoff's 2 <sup>nd</sup> law	Kirchhoff's 1 <sup>st</sup> law

# Resistance bridge 抵抗ブリッジ

Wheatstone bridge

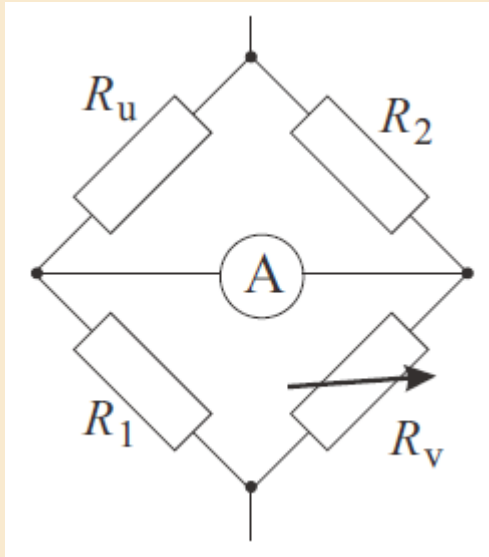


AVS-47 Resistance bridge

Not a “bridge” circuit!



# Schering Bridge

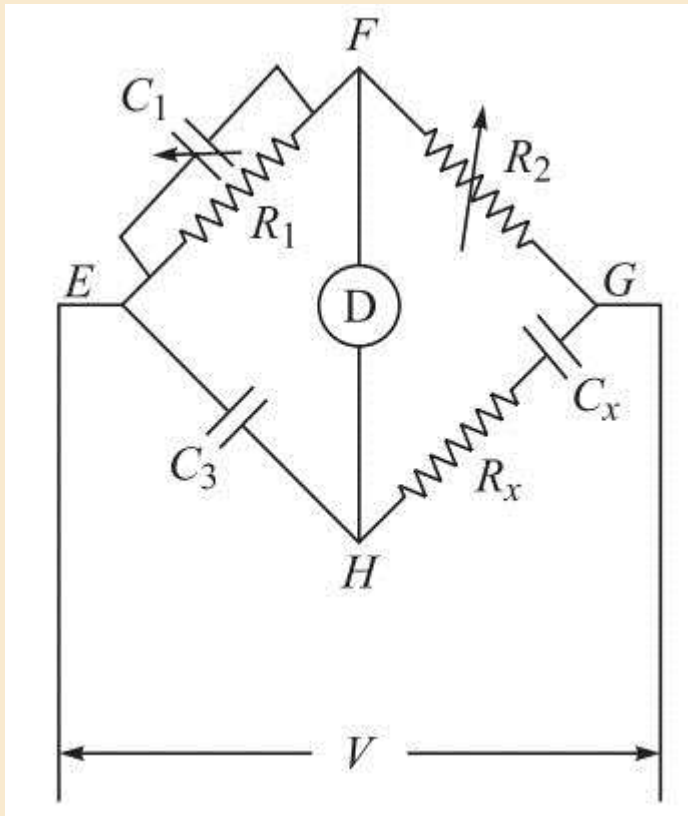



$$Z_1 Z_x = Z_2 Z_3, \quad Z_x = Z_2 Z_3 Y_1$$

$$Z_x = R_x + \frac{1}{i\omega C_x}, \quad Z_2 = R_2, \quad Z_3 = \frac{1}{i\omega C_3}, \quad Y_1 = \frac{1}{R_1} + i\omega C_1$$

$$R_x + \frac{1}{i\omega C_x} = R_2 \frac{1}{i\omega C_3} \left( \frac{1}{R_1} + i\omega C_1 \right)$$

$$R_x = \frac{R_2 C_1}{C_3}, \quad C_x = \frac{R_1}{R_2} C_3$$

# Hartshorn bridge

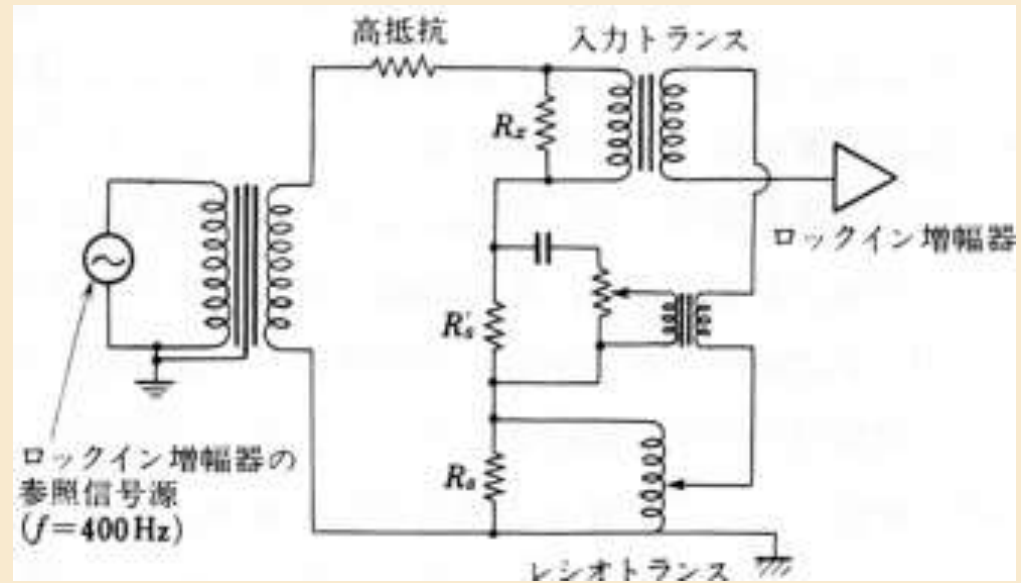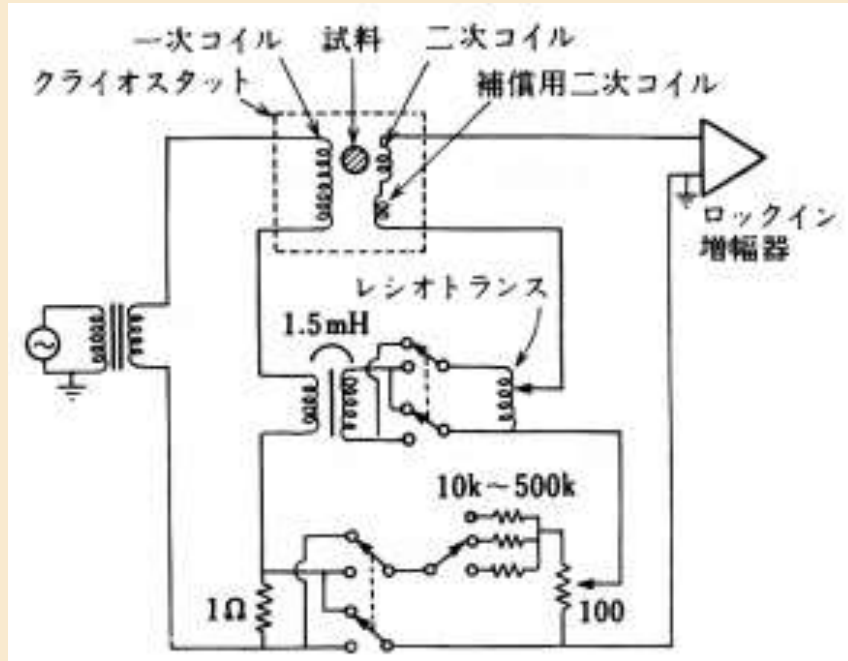

# Capacitance bridge キャパシタンスブリッジ



General Radio  
3-terminal  
Capacitance bridge

Agilent E4981A



# 2.4 General Properties of Resonance and Resonance Circuits

## 2.4.1 Resonance Phenomena

Harmonic oscillator:  $\frac{dq}{dt} = -\omega_0^2 q$


Kirchhoff's law

$$L \frac{dJ_L}{dt} = -L \frac{d^2 q_L}{dt^2} = \frac{q}{C} = RJ_R = R \frac{dq_R}{dt}$$




$$dq_L + dq_R + dq = 0$$

$$\frac{d^2 q}{dt^2} + \frac{1}{CR} \frac{dq}{dt} + \frac{1}{LC} q = \frac{d^2 q}{dt^2} + \frac{1}{\tau} \frac{dq}{dt} + \omega_0^2 q = 0$$

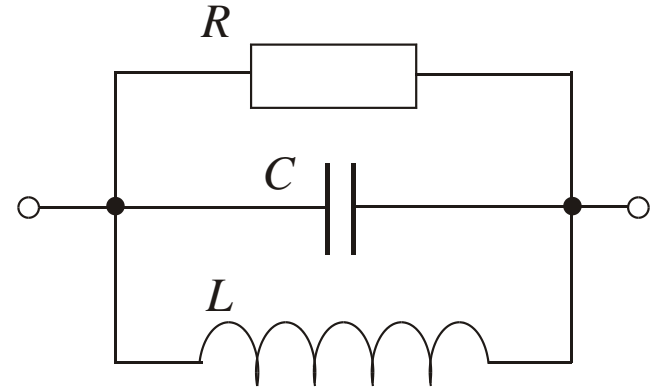
$$q = \exp(\lambda t) \quad \lambda = \frac{1}{2\tau} \left[ -1 \pm \sqrt{1 - 4(\omega_0 \tau)^2} \right] \approx -\frac{1}{2\tau} \pm i\omega_0 \quad (\omega_0 \tau \gg 1)$$



## 2.4.2 Resonance and Phase shift

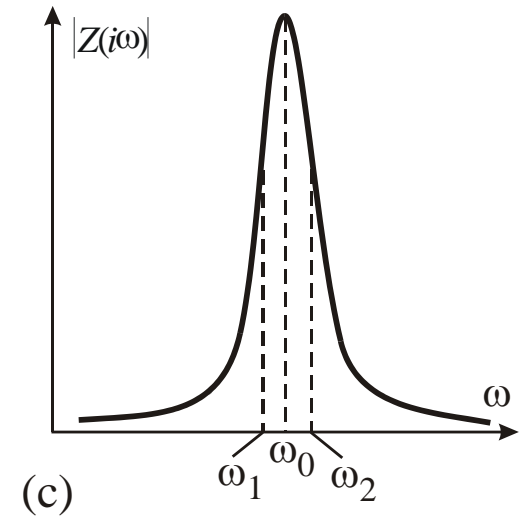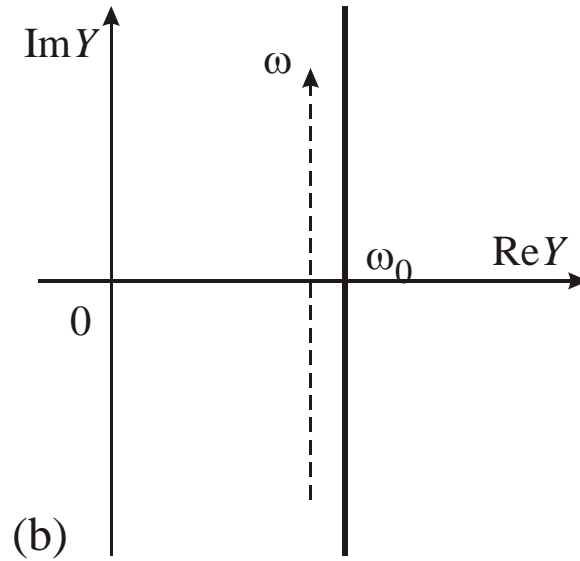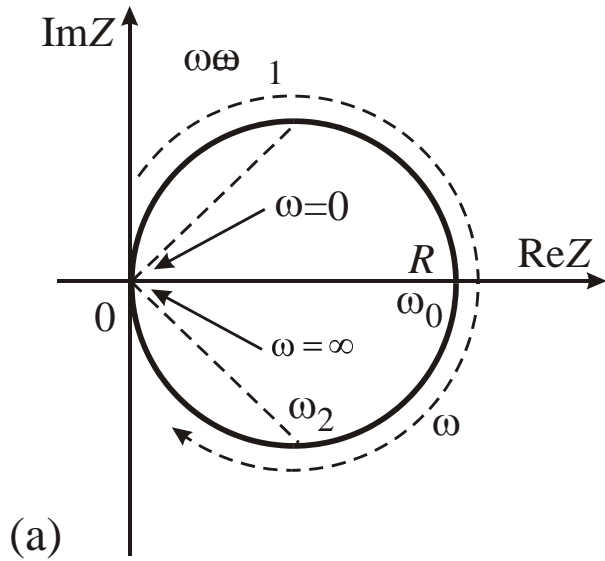

多聞丸

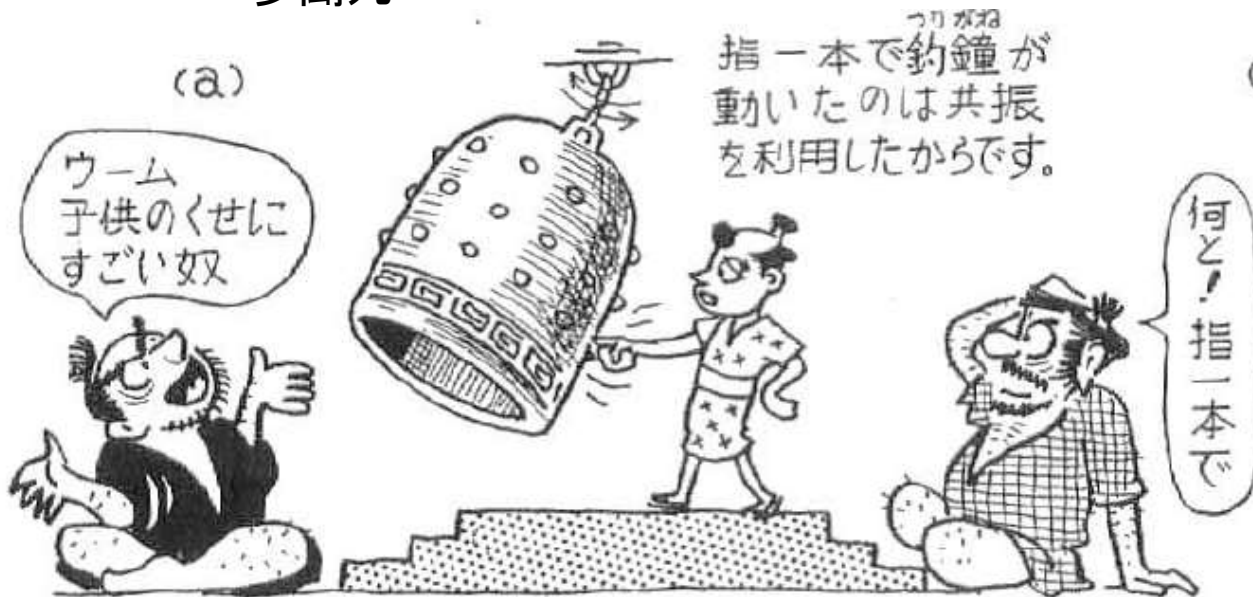

Resonance:  
Reactance = 0


Total Phase Shift  
Change:  $\pi$



# Kondo Resonance and Phase shift




Jun Kondo

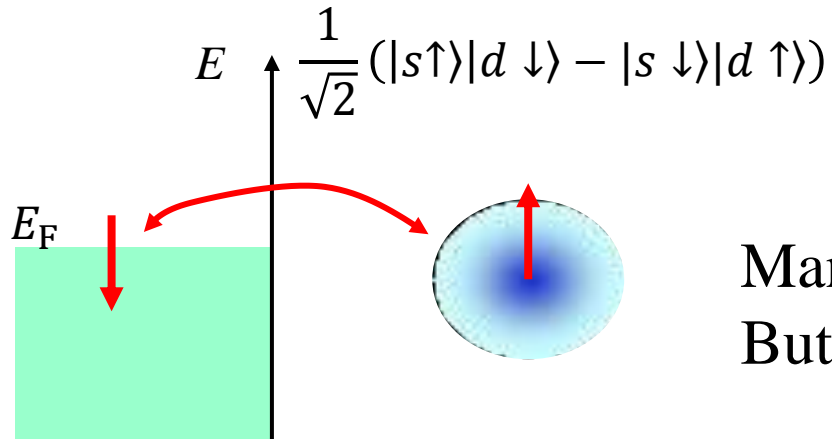


Many body resonance.  
But still has the phase shift of  $\pi/2$  !


Co atoms on Ag (111) surface

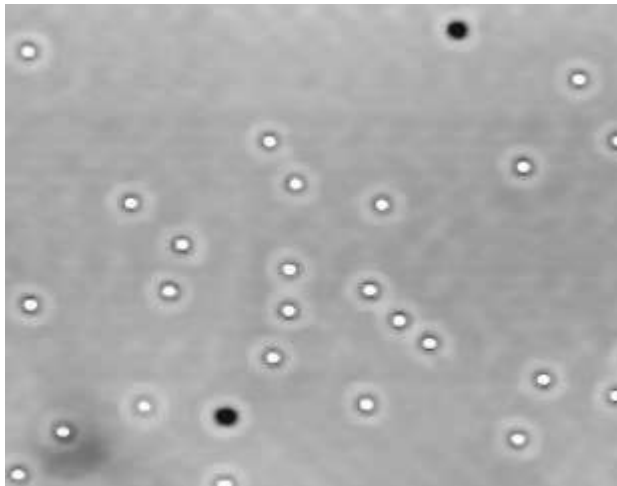

Co (magnetic)

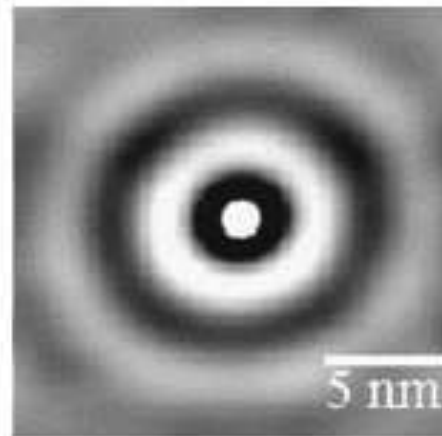


Defect (non-magnetic)

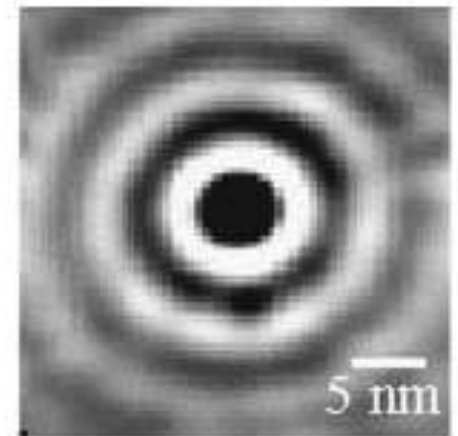

# Quartz crystal filter



(a)

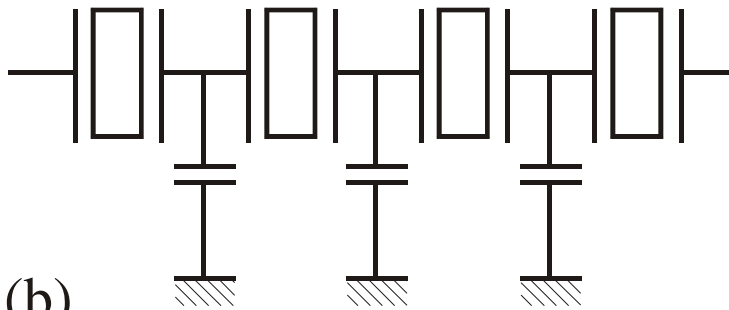

(b)

(c)

