

2015.12.3


Electric Circuit for Physicists

電子回路論 第8回


東京大学理学部・理学系研究科
物性研究所
勝本信吾

Shingo Katsumoto

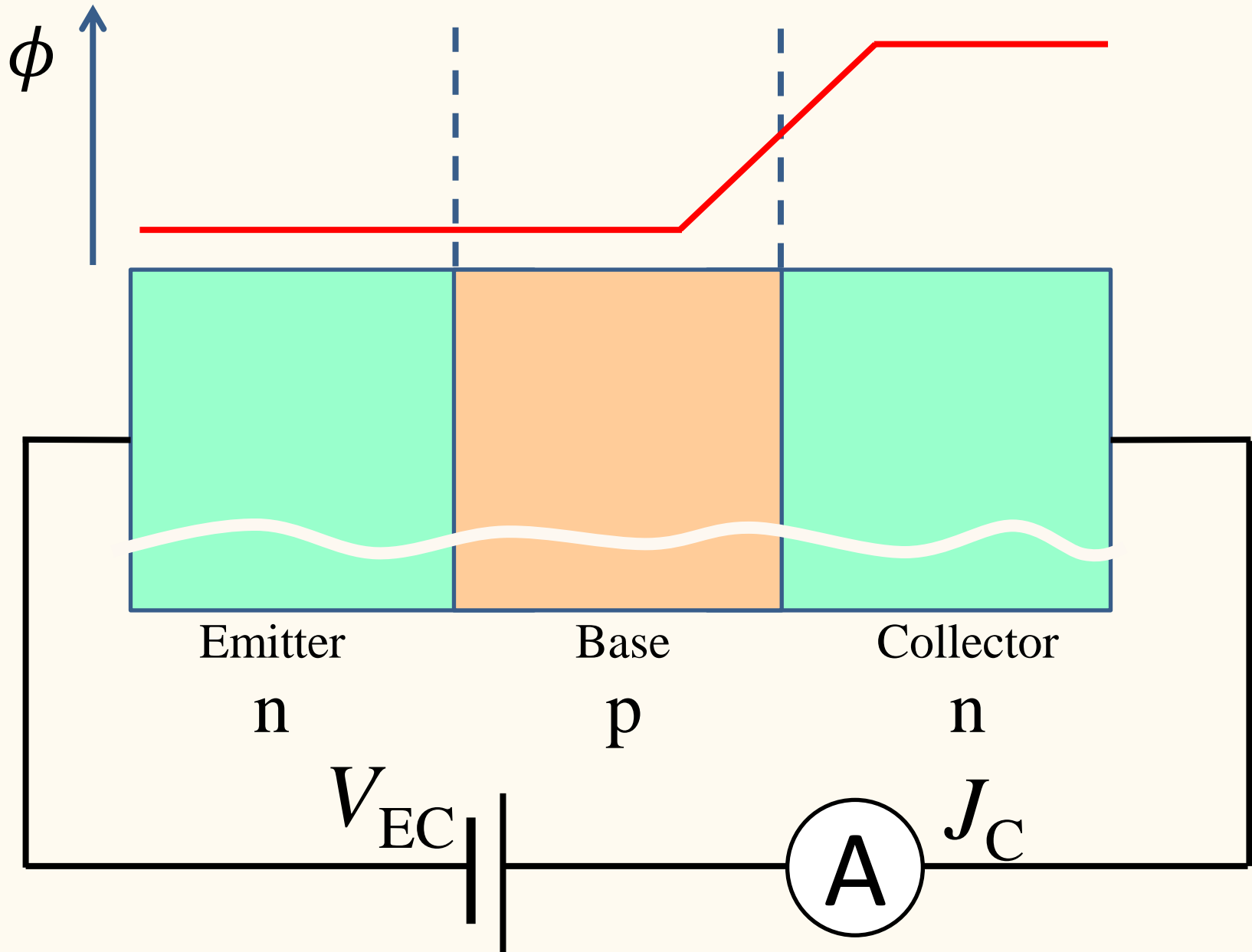
Review: How a bipolar transistor amplifies?





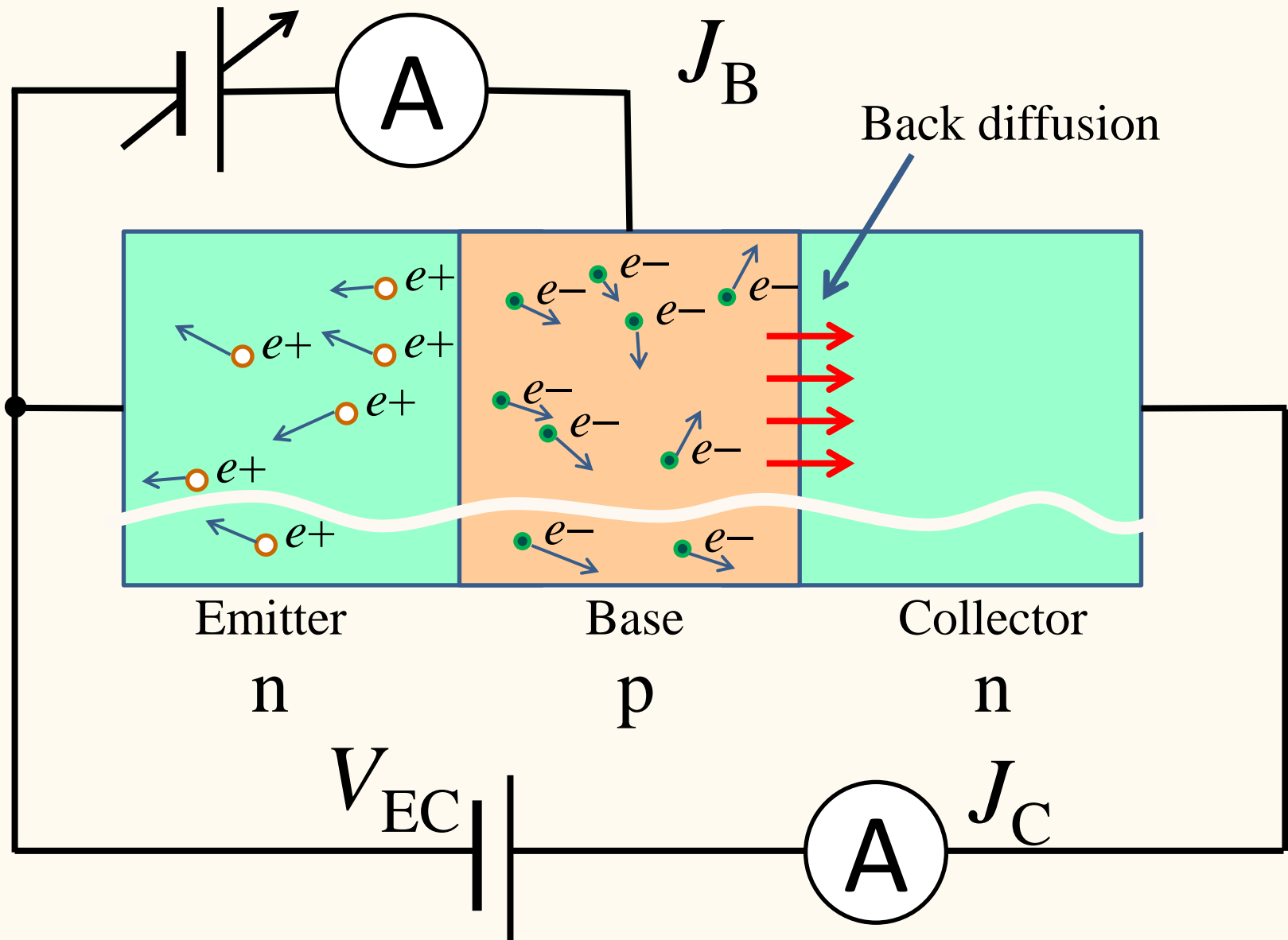
Review: How a bipolar transistor amplifies?



Concept of equivalent circuit

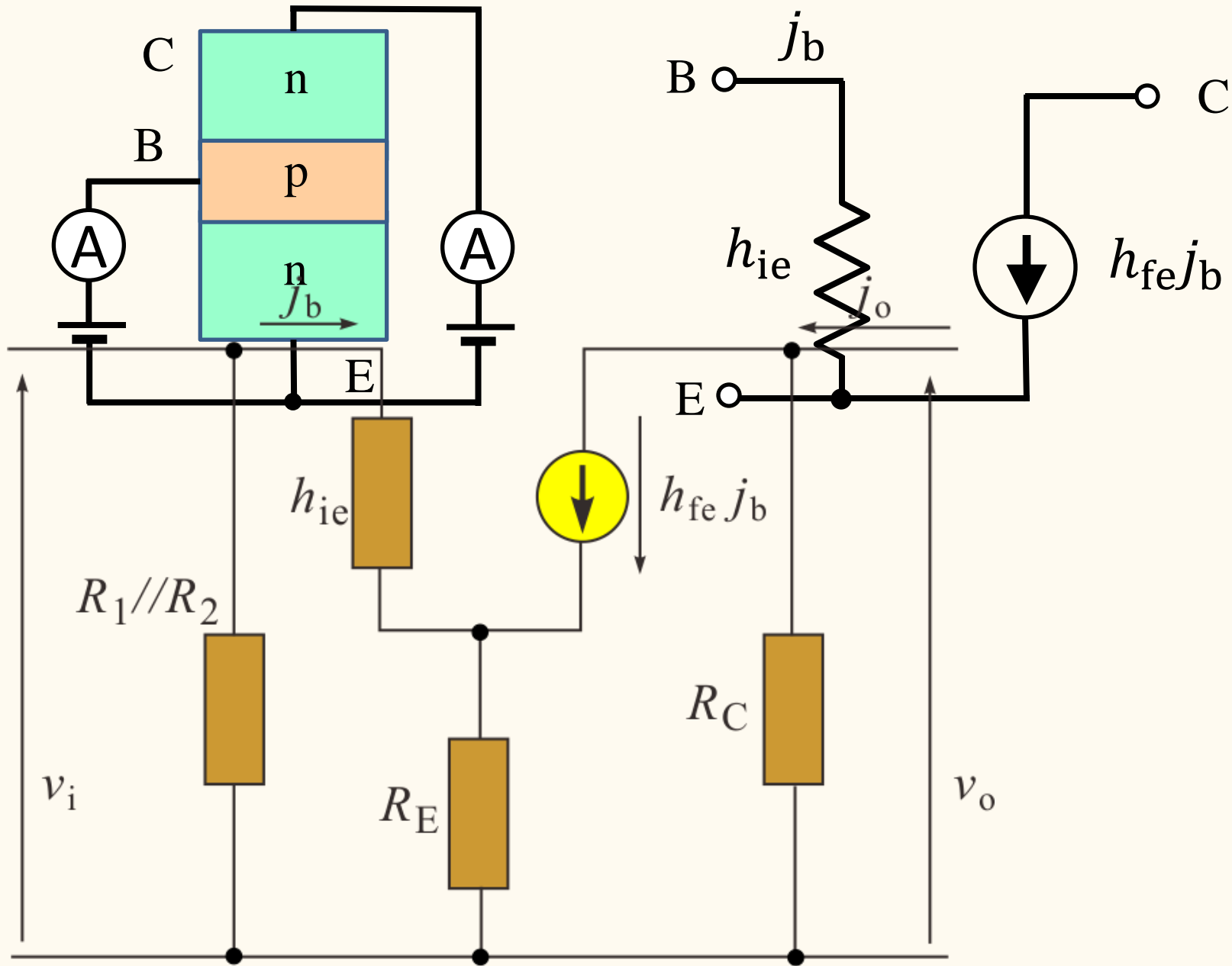


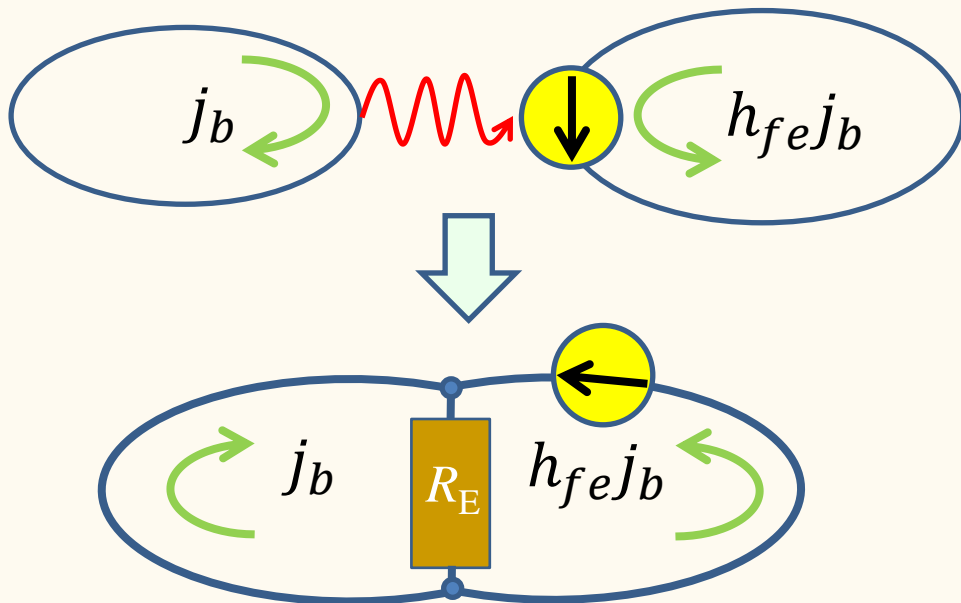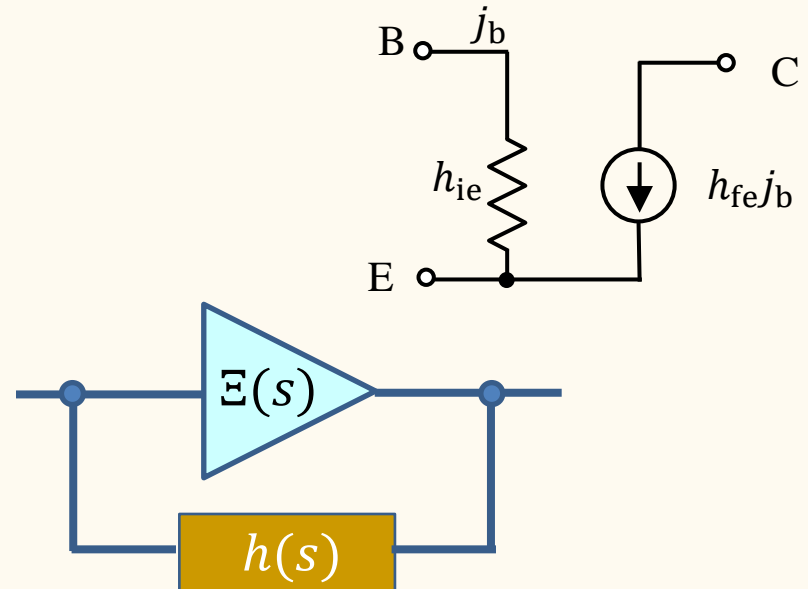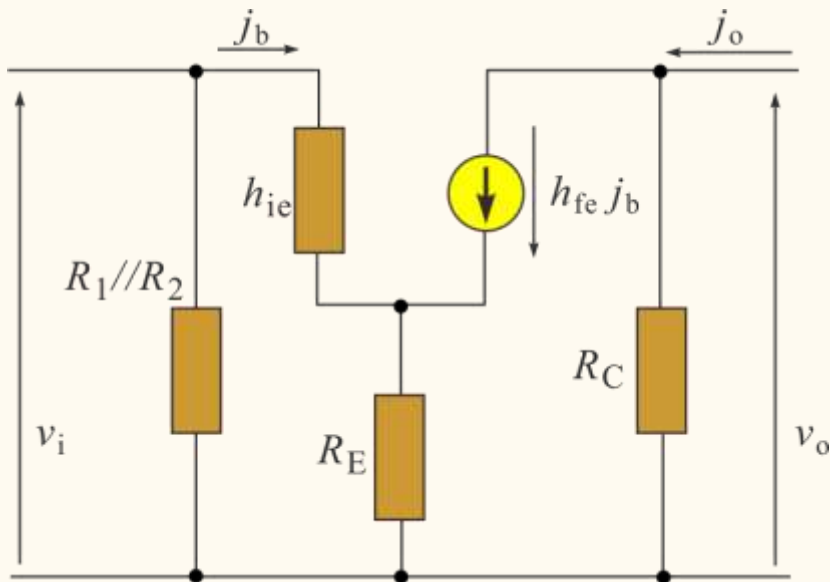Concept of equivalent circuit: Where is feedback?



$$\begin{aligned}
 A &= \frac{v_o}{v_i} \\
 &= \frac{h_{fe} R_C}{h_{ie} + R_E (1 + h_{fe})} \\
 &\approx \frac{R_C}{R_E} \quad h_{fe} \gg 1
 \end{aligned}$$


Current amplification: Emitter follower

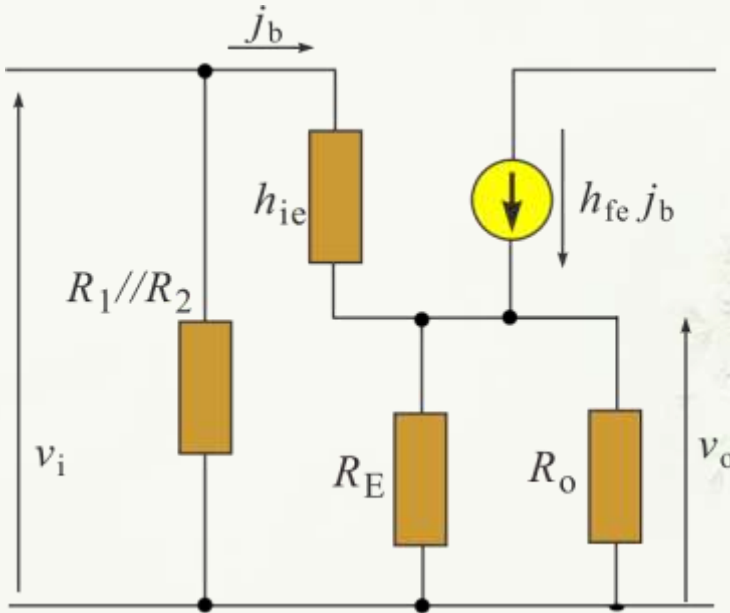




$$\frac{v_o}{v_i} = \frac{j_b(1 + h_{fe})(R_E \parallel R_o)}{j_b[h_{ie} + (1 + h_{fe})(R_E \parallel R_o)]}$$

$$\approx 1 \quad (h_{fe} \gg 1)$$

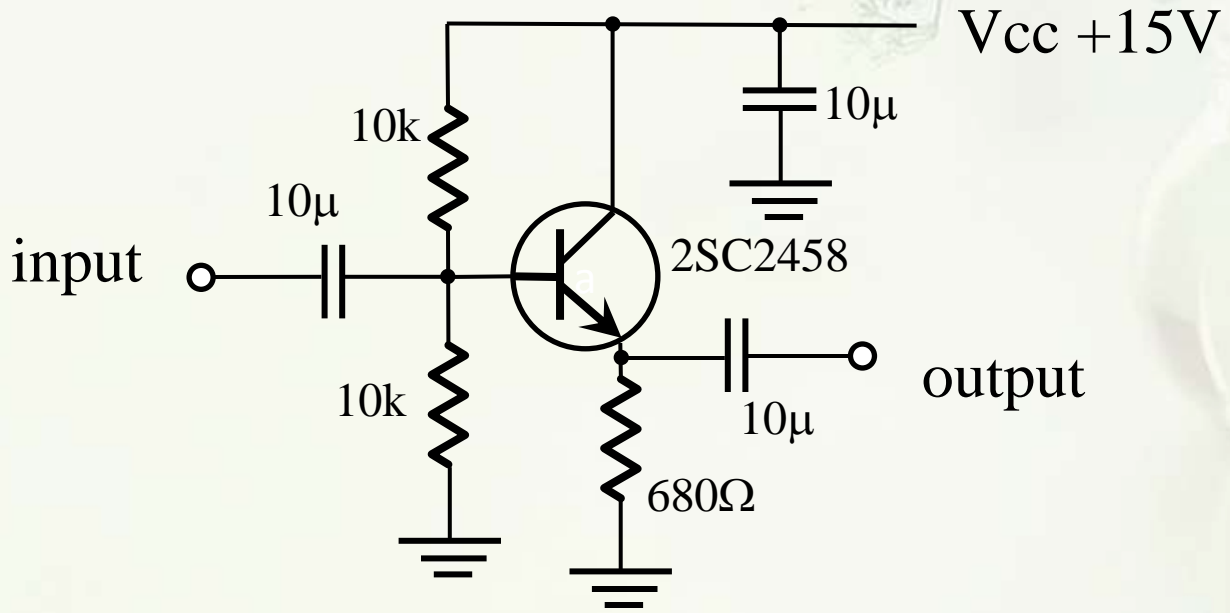v_o does not depend on load resistance
 \Rightarrow Very low output resistance



Complementary transistors

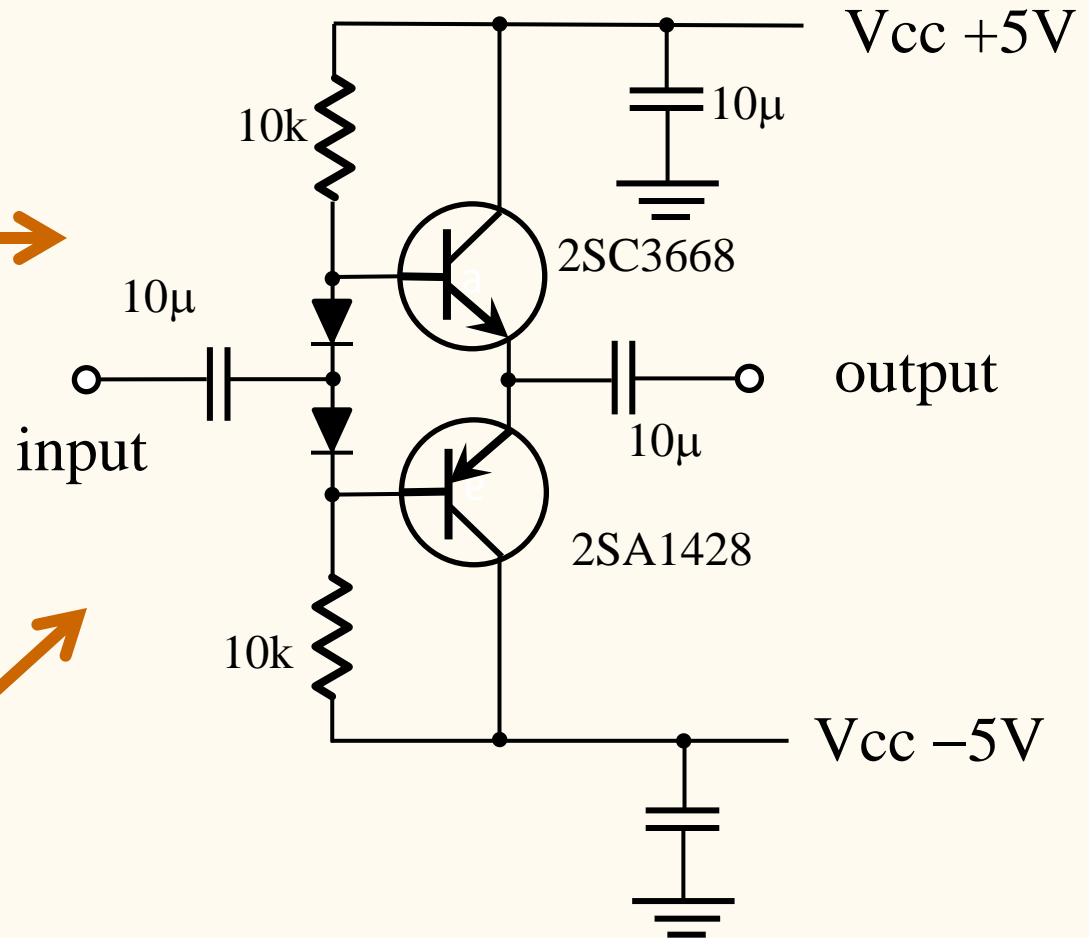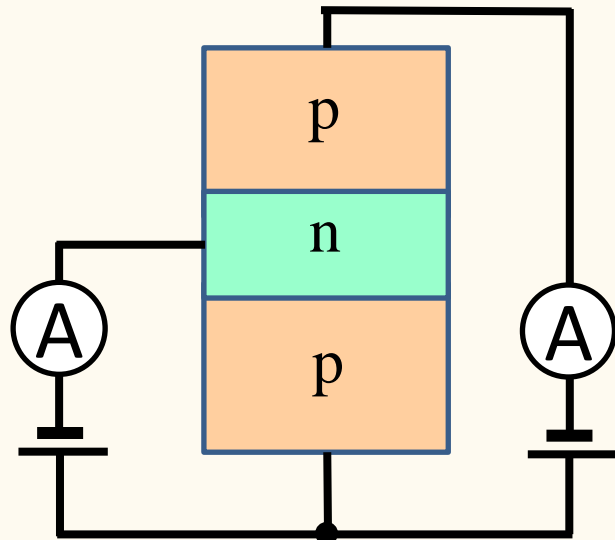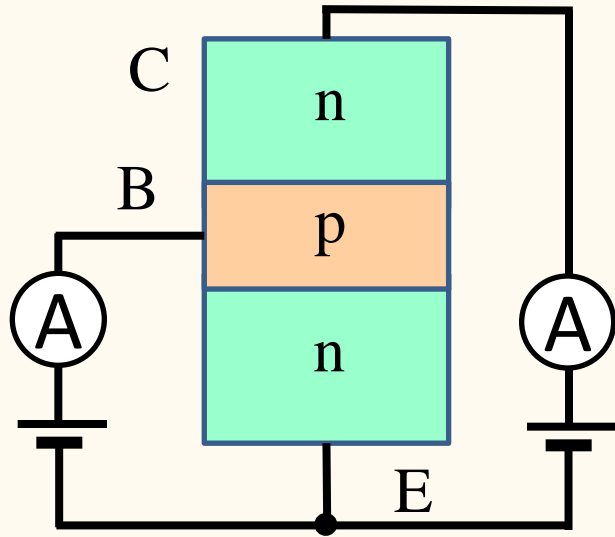

Symmetric characteristics: Complementary

Symmetric: Small collector current
(idling current) for zero input.

Example of transistor datasheet

TOSHIBA

2SC1815(L)

TOSHIBA Transistor Silicon NPN Epitaxial Type (PCT process)

2SC1815(L)


Unit: mm

Electrical Characteristics (Ta = 25°C)

Characteristics	Symbol	Test Condition	Min	Typ.	Max	Unit
Collector cut-off current	I_{CBO}	$V_{CE} = 60 \text{ V}, I_E = 0$	—	—	0.1	μA
Emitter cut-off current	I_{EBO}	$V_{EB} = 5 \text{ V}, I_C = 0$	—	—	0.1	μA
DC current gain	$h_{FE(1)}$	$V_{CE} = 6 \text{ V}, I_C = 2 \text{ mA}$	70	—	700	
	$h_{FE(2)}$	$V_{CE} = 6 \text{ V}, I_C = 150 \text{ mA}$	—	100	—	
Saturation voltage	Collector-emitter $V_{CE(sat)}$	$I_C = 100 \text{ mA}, I_B = 10 \text{ mA}$	—	0.1	0.25	V
	Base-emitter $V_{BE(sat)}$	$I_C = 100 \text{ mA}, I_B = 10 \text{ mA}$	—	—	1.0	
Transition frequency	f_T	$V_{CE} = 10 \text{ V}, I_C = 1 \text{ mA}$	80	—	—	MHz
Collector output capacitance	C_{ob}	$V_{CE} = 10 \text{ V}, I_E = 0, f = 1 \text{ MHz}$	—	2.0	3.5	pF
Base intrinsic resistance	r_{bb}	$V_{CE} = 10 \text{ V}, I_E = 1 \text{ mA}, f = 30 \text{ MHz}$	—	50	—	Ω
Noise figure	Complementary to 2SA1015(L) (OCY class).		—	0.5	6	dB
	JEDEC NF(1)	$R_G = 100 \Omega, f = 100 \text{ Hz}$	—	—	—	
	JEITA NF(2)	$V_{CE} = 6 \text{ V}, I_C = 0.1 \text{ mA}$	—	0.2	3	
	TOSHIBA	$R_G = 250 \Omega, f = 1 \text{ kHz}$	—	—	—	


Note: h_{FE} (1) classification O: 70~140, Y: 120~240, GR: 200~400, BL: 350~700

Example of transistor datasheet


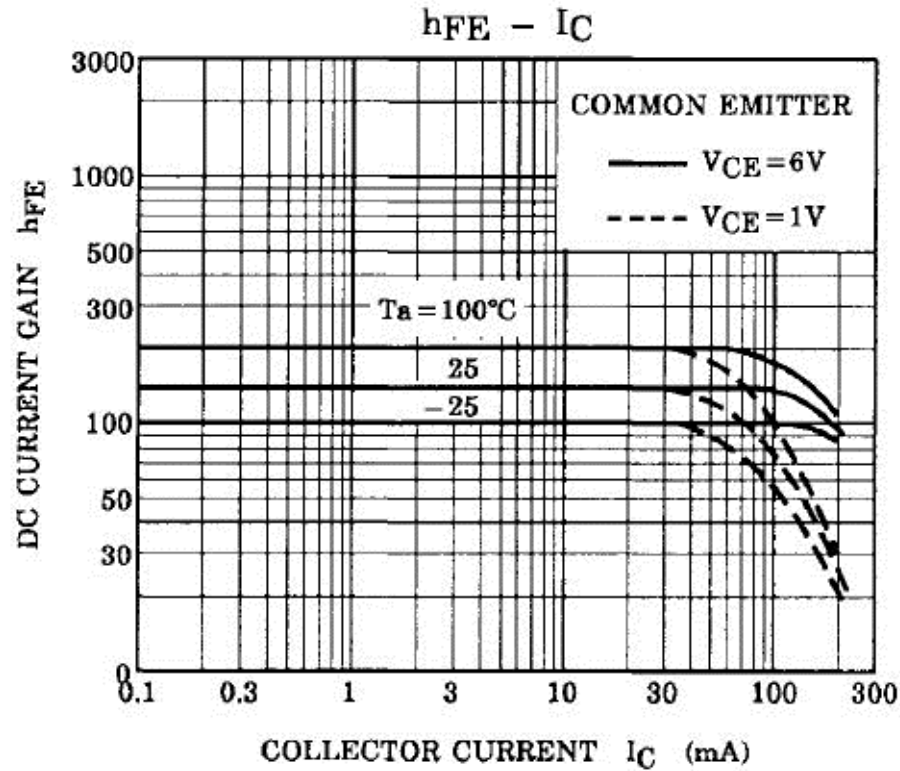


Cut-off frequency as a function of I_C

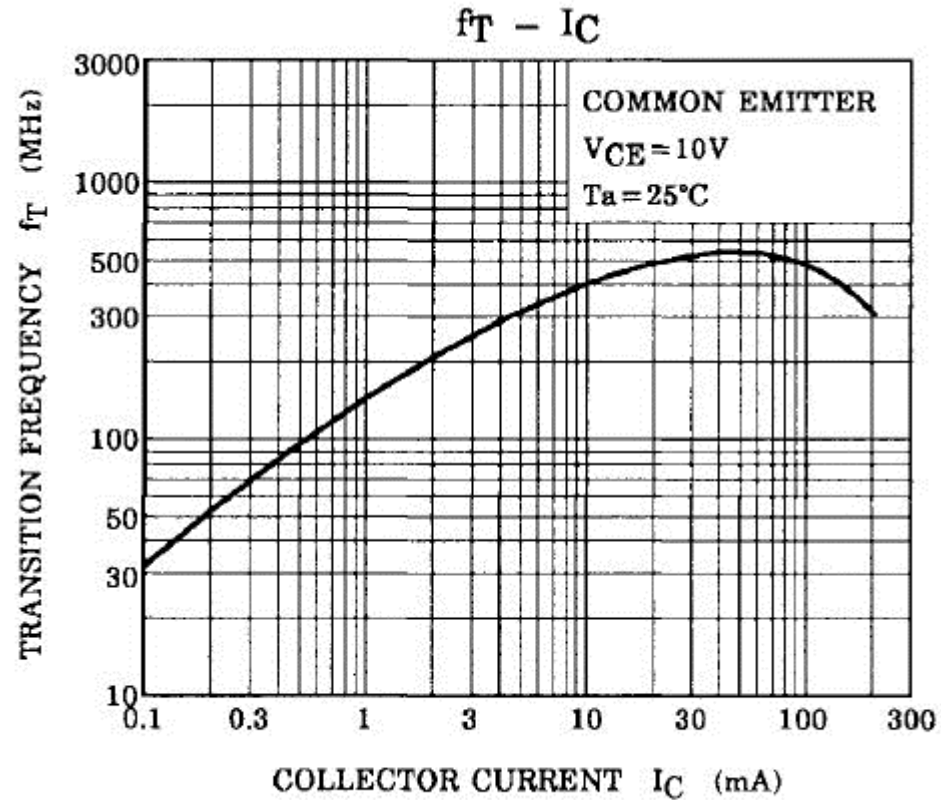h_{fe} linear model availability
in the range of I_C .




Example of transistor datasheet

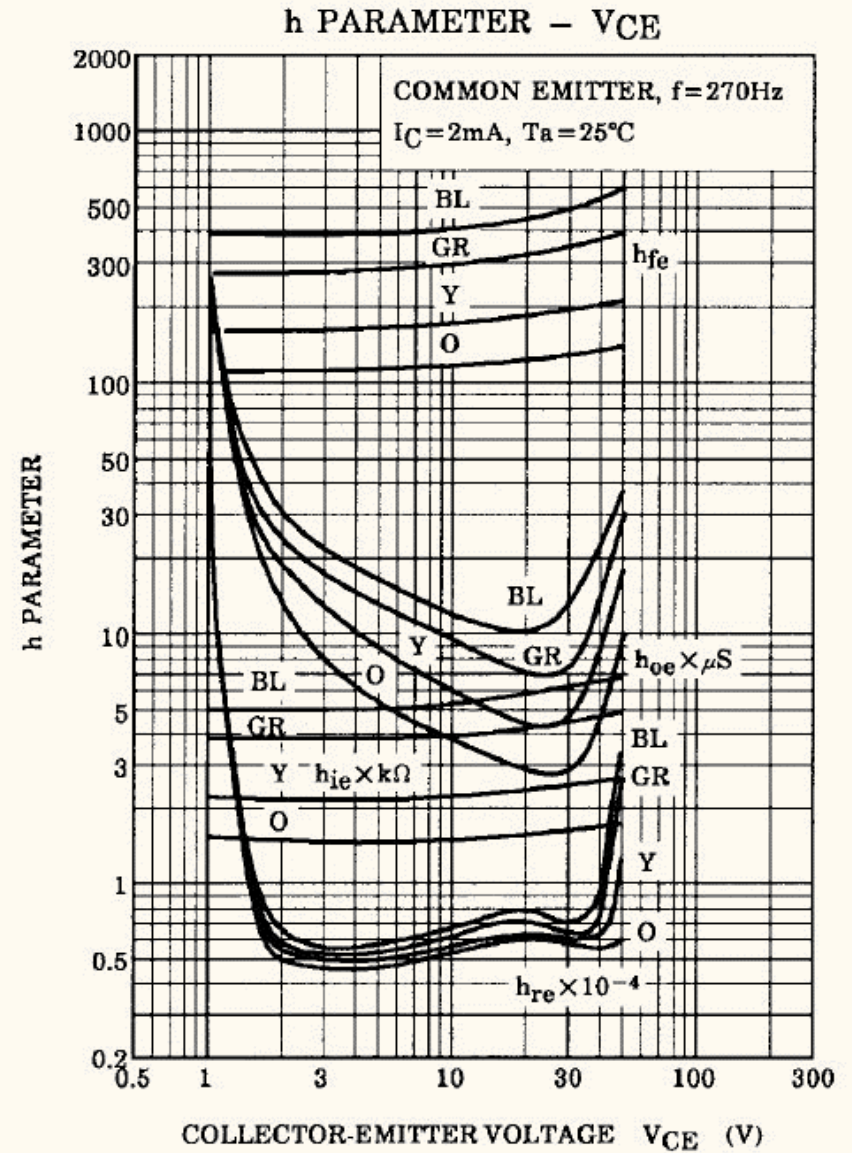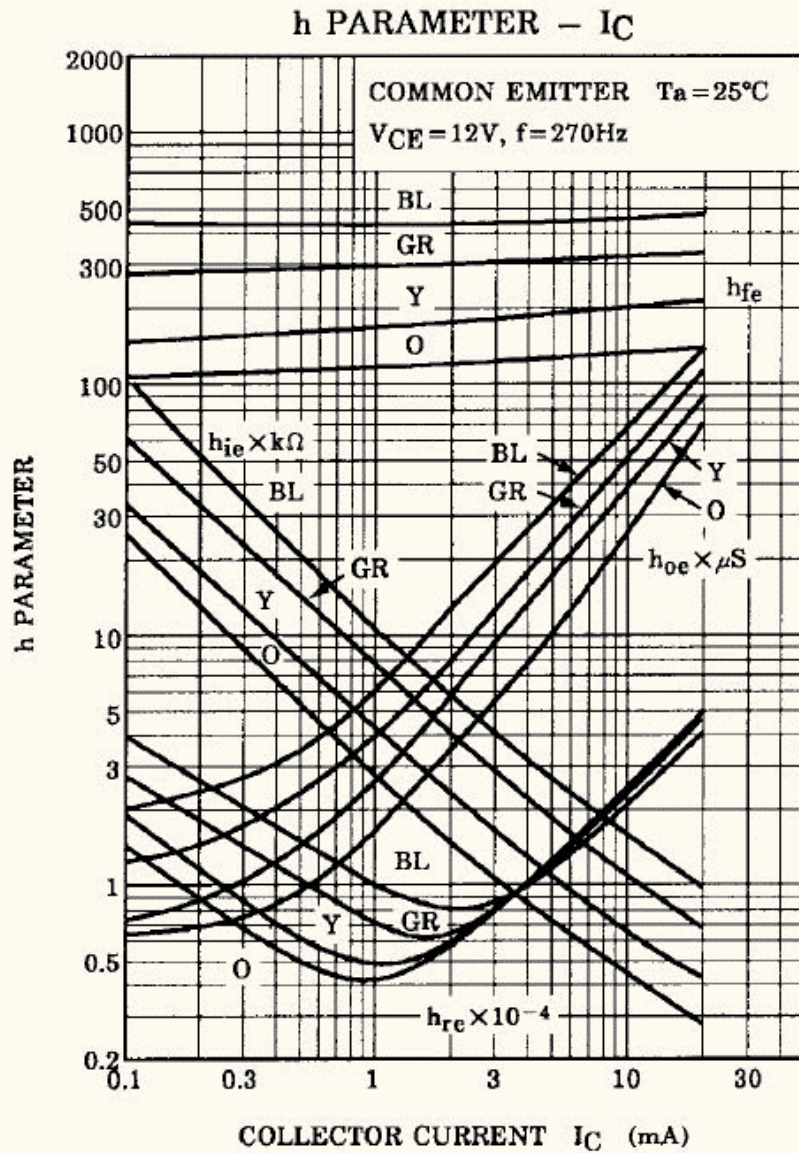

4.4 Field effect transistor (FET)

$$C = \frac{\epsilon \epsilon_0 S}{d} \equiv \frac{\epsilon_s}{d} S$$

pn junction in reverse bias condition

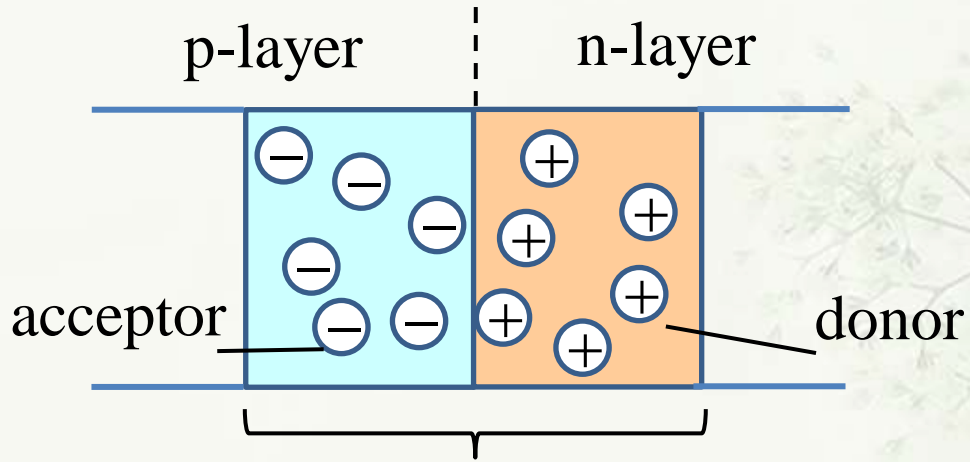



$$W_D = \sqrt{\frac{2\epsilon_s}{eN} \left(V_{bi} - V - \frac{2k_B T}{e} \right)}$$

$$C_D = \frac{\epsilon_s}{W_D} S$$

depletion layer (空乏層) forms built-in potential



Reverse bias voltage




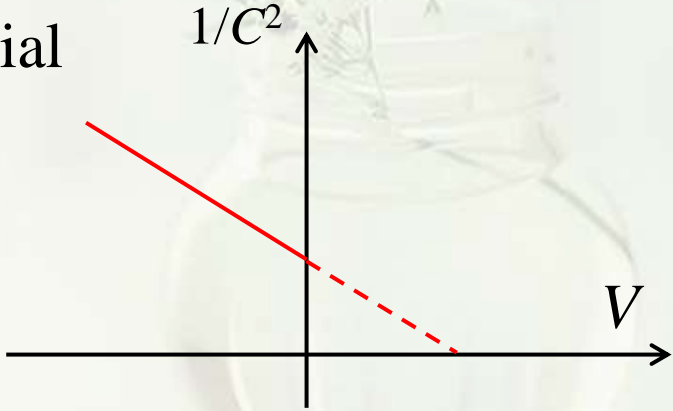
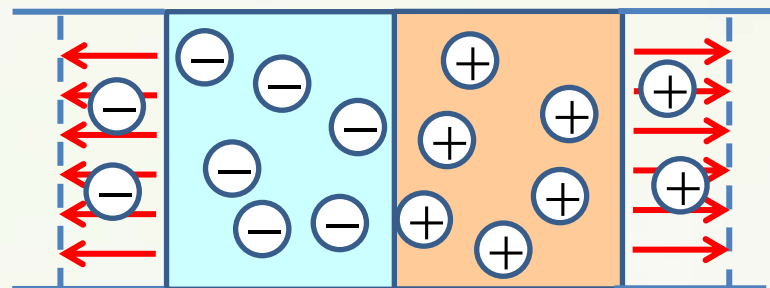


Varicap diode





4.4 Field effect transistor (FET)



Junction FET (JFET)

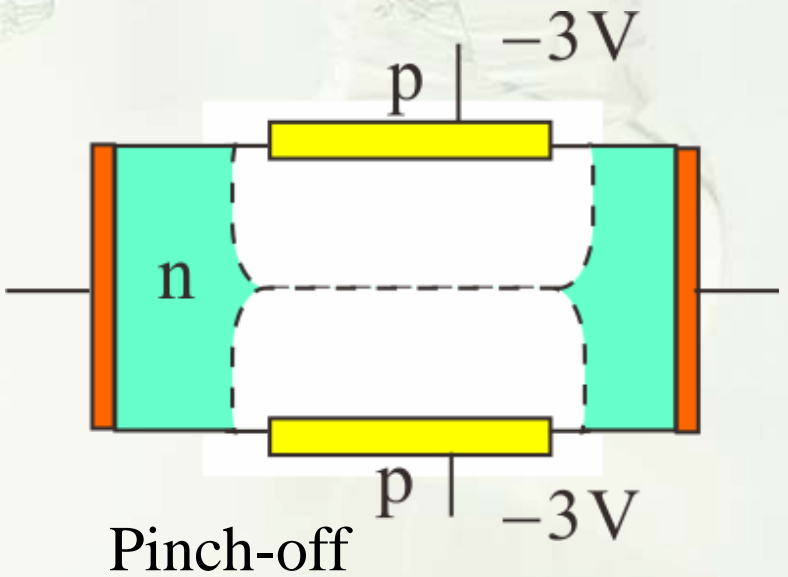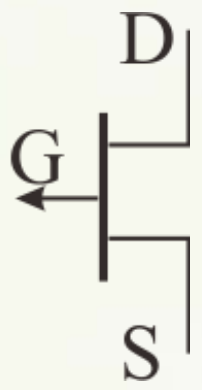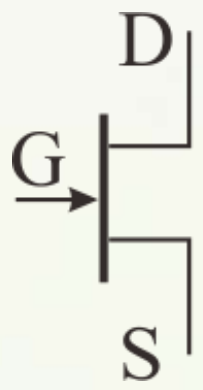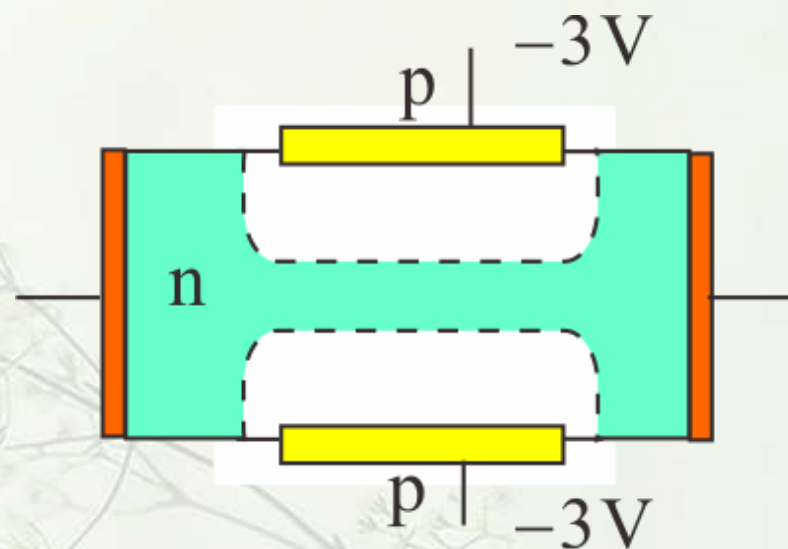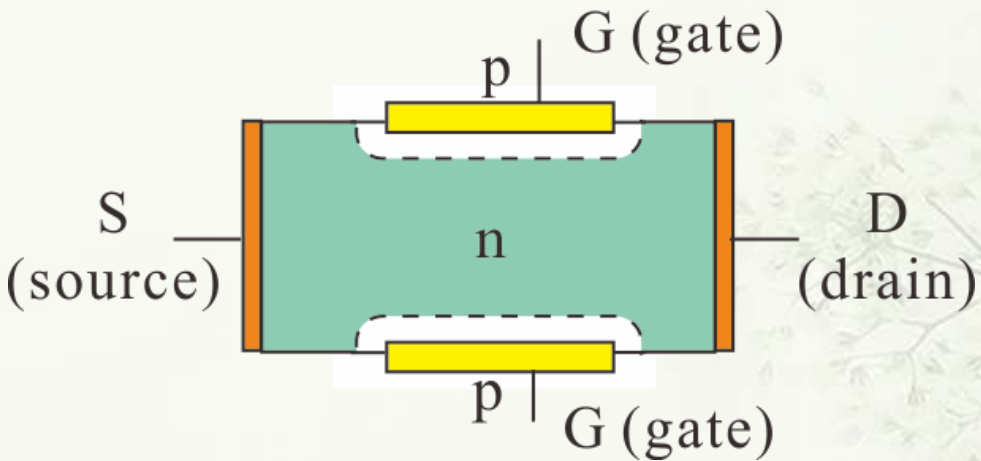

MESFET, MOSFET

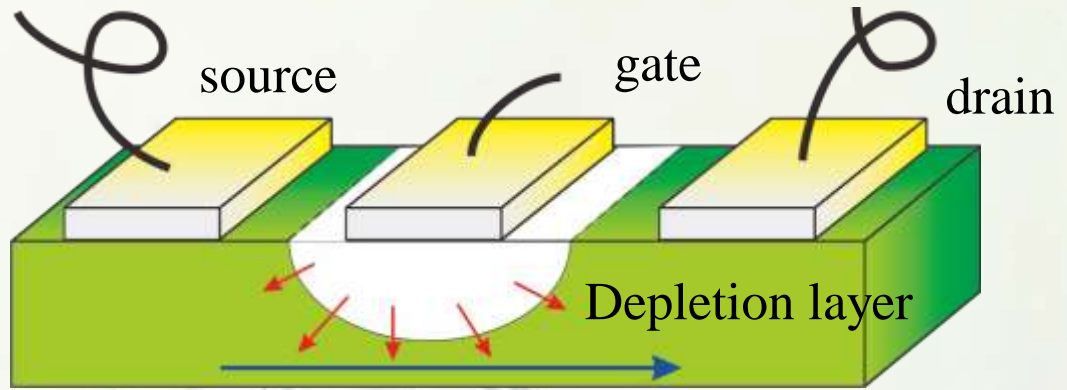
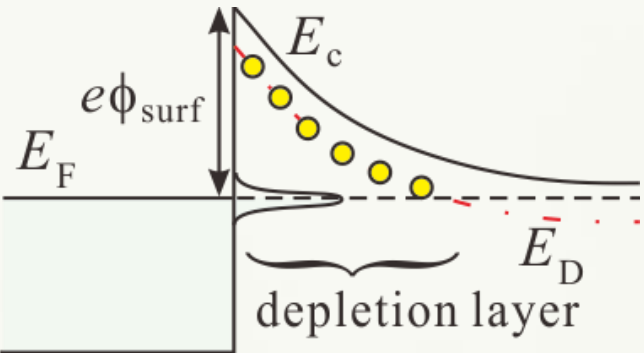


Conduction channel

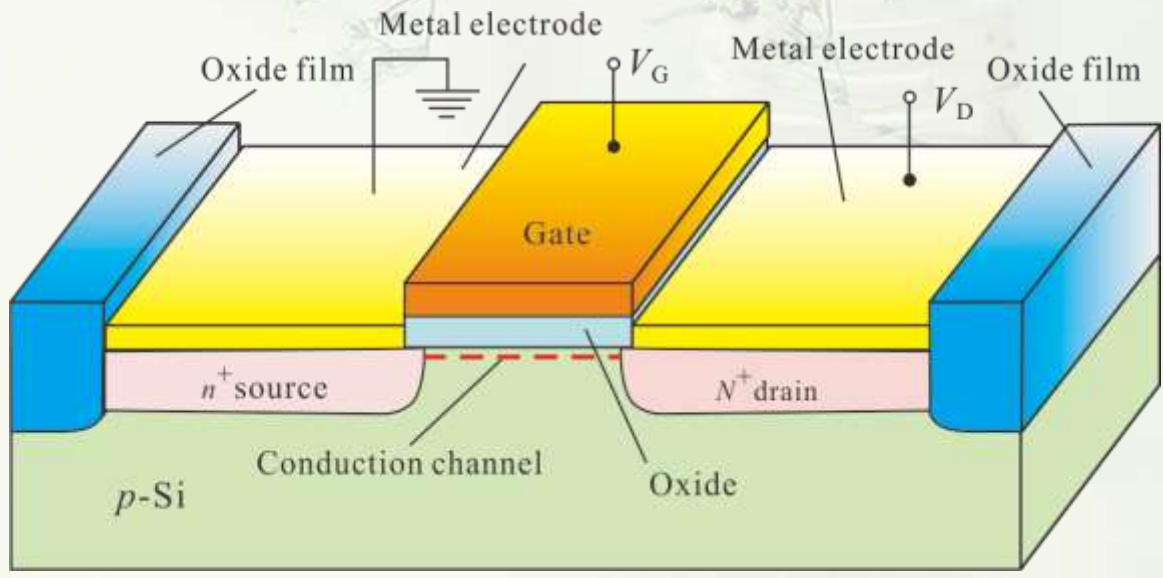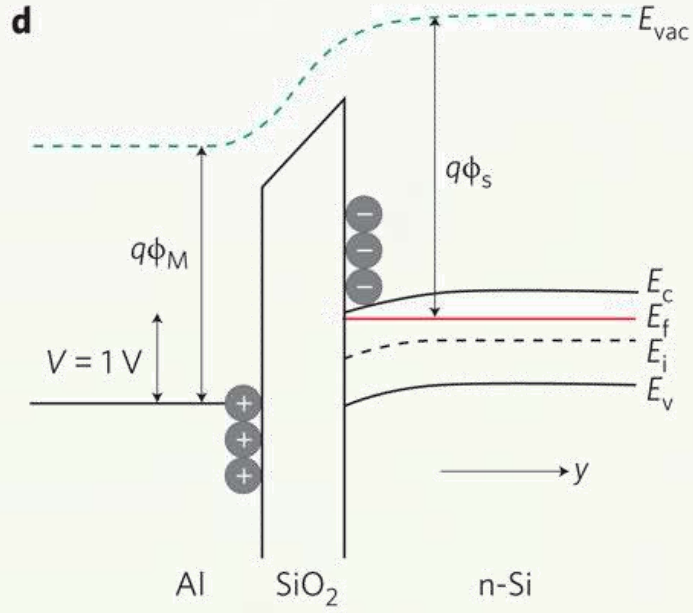

d

Static characteristics of FET

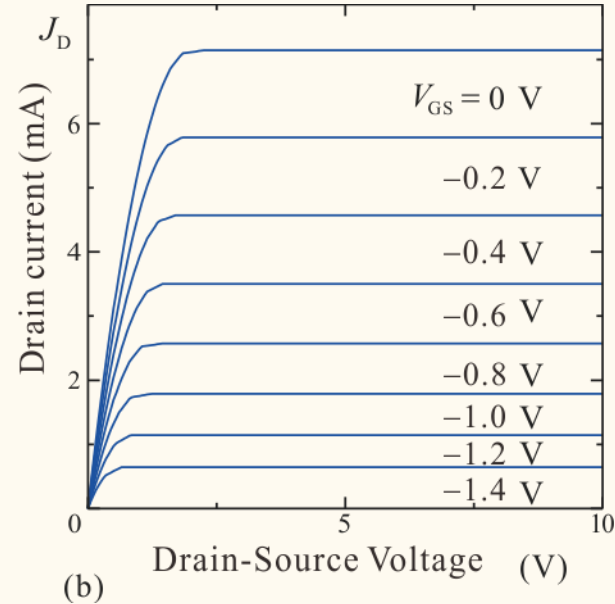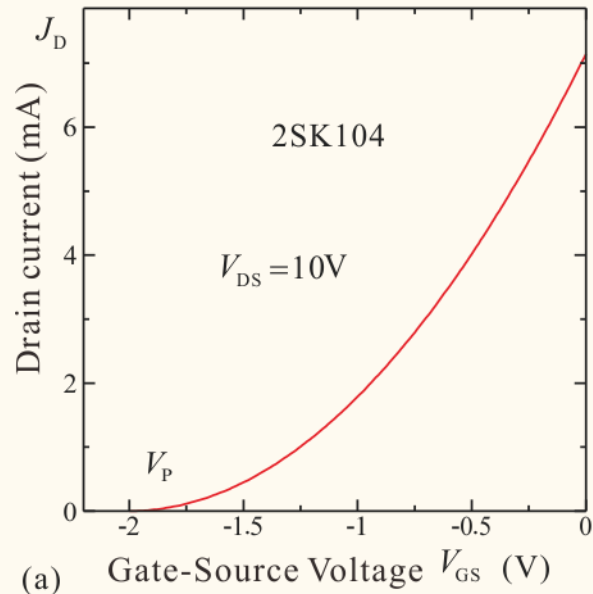

$$J_G \simeq 0, \quad g_m \equiv \left(\frac{\partial J_D}{\partial V_{GS}} \right)_{V_D = \text{const.}}, \quad \text{transconductance}$$

$$J_D = f(V_G, V_D) \quad r_d \equiv \left(\frac{\partial V_D}{\partial J_D} \right)_{V_{GS} = \text{const.}} \quad \text{drain resistance}$$



Locally linear approximation
$$\dot{j}_d = g_m v_{gs} + \frac{v_d}{r_d}$$

岡村迪夫「OPアンプ回路の設計」CQ出版社
松澤昭「基礎電子回路工学」電気学会


A. Agarwal, J. H. Lang “Foundations of Analog and Digital Electronic Circuits” (Elsevier, 2005).

S. M. Sze, K. K. Ng, “Physics of Semiconductor Devices” (Wiley, 2007).

Coaxial cable

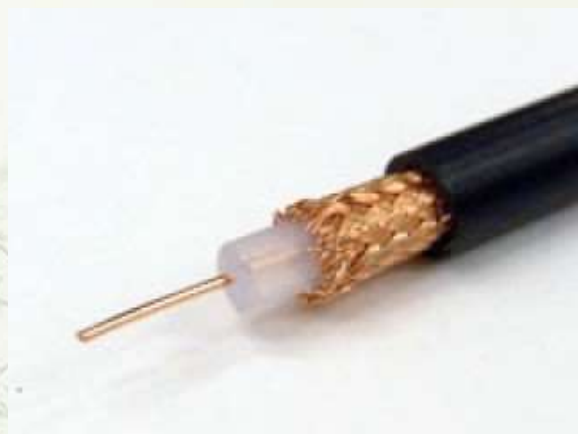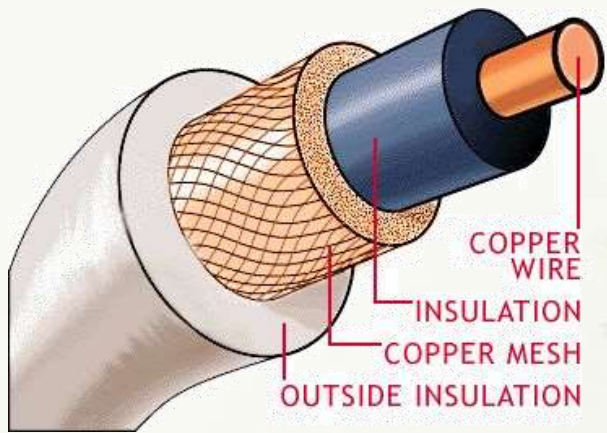

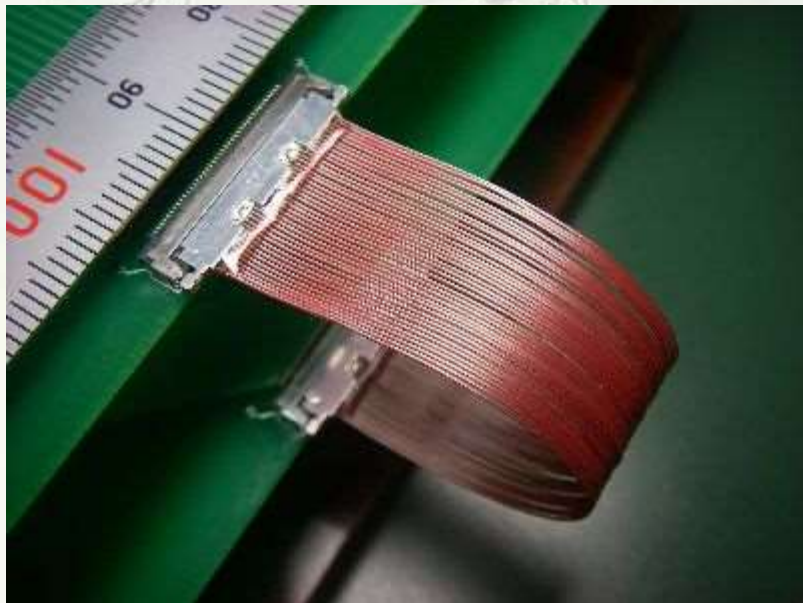Thin coaxial cable AWG50 ($\phi 25\mu\text{m}$)



Coaxial cable 2

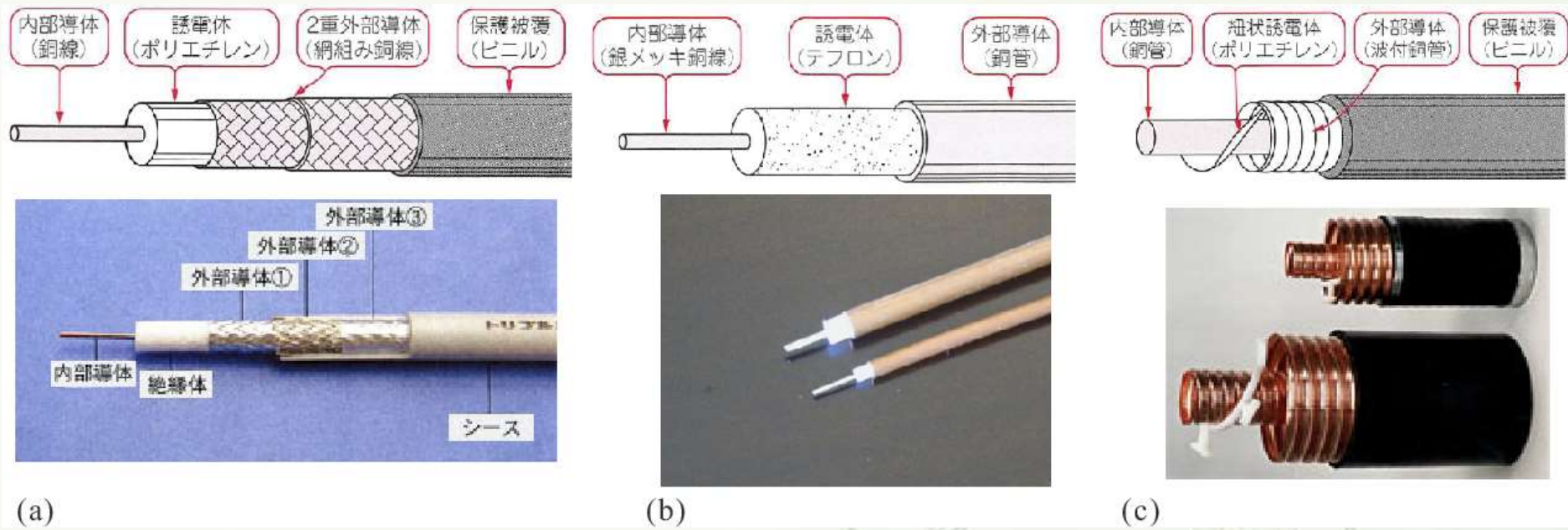


図12 同軸ケーブルの型名 (JIS C3501)



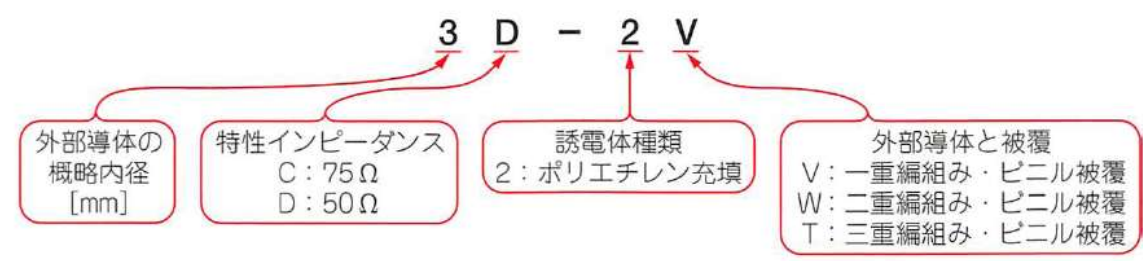


図13 MIL規格での同軸ケーブル型名の例

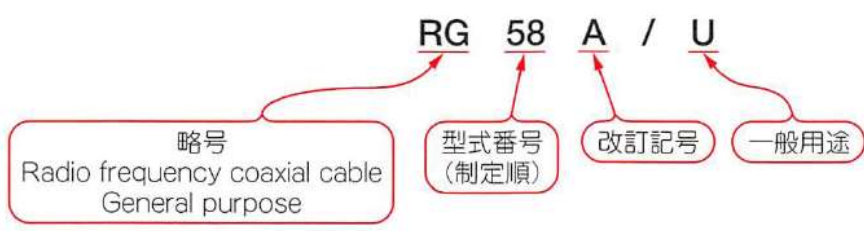

Coaxial connectors

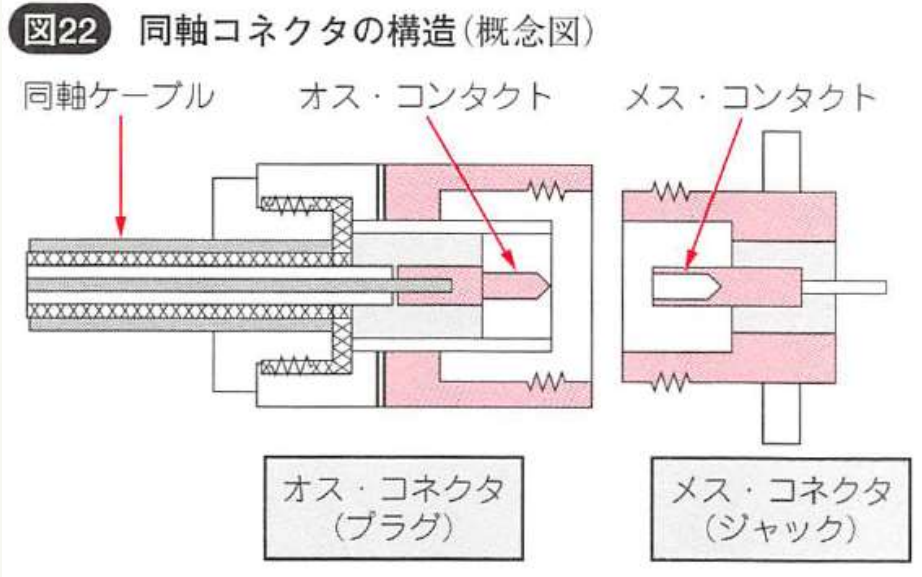

代表的な同軸コネクタの最高使用周波数例

形式	外部導体内径	最高使用周波数
BNC	約 7 mm	2 ~ 4 GHz
N	約 7 mm	10 ~ 18 GHz
7 mm	7 mm	~ 18 GHz
SMA	4.15 mm	18 GHz
3.5 mm	3.5 mm	26.5 GHz
K	2.92 mm	40 GHz
2.4 mm	2.4 mm	50 GHz
V	1.85 mm	65 GHz
W	1.1 mm	110 GHz
1.0 mm	1.0 mm	110 GHz

Coaxial connectors

写真2 N型コネクタ



(a) フランジ付きジャック




(b) プラグ




(c) プラグ [(b)を分解]


写真3 BNC型コネクタ

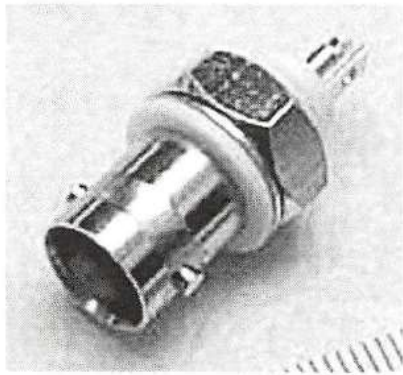

(a) 絶縁型ジャック
(高周波に向かない)

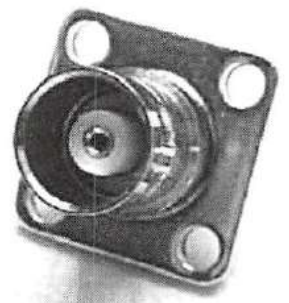


(b) フランジ付きジャック

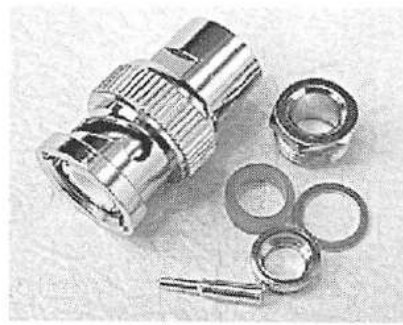

(c) プラグ

Coaxial connectors 2

SMA-type

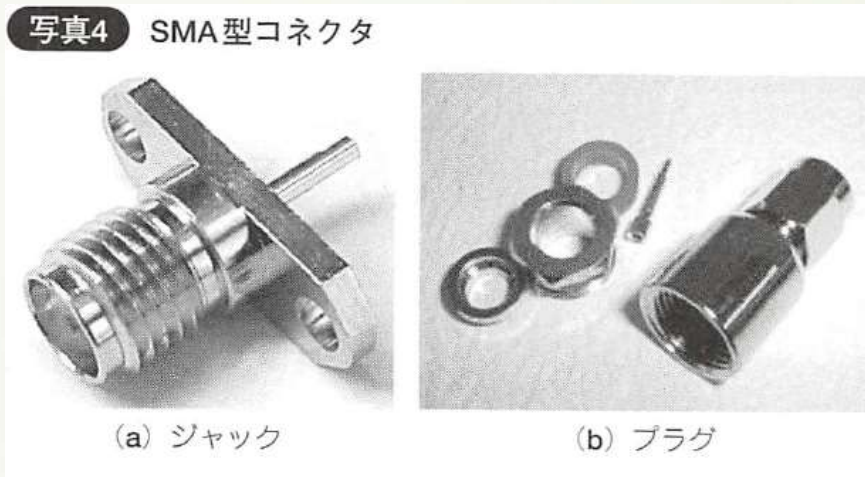


jack

plug


K-type

写真6 K型コネクタ

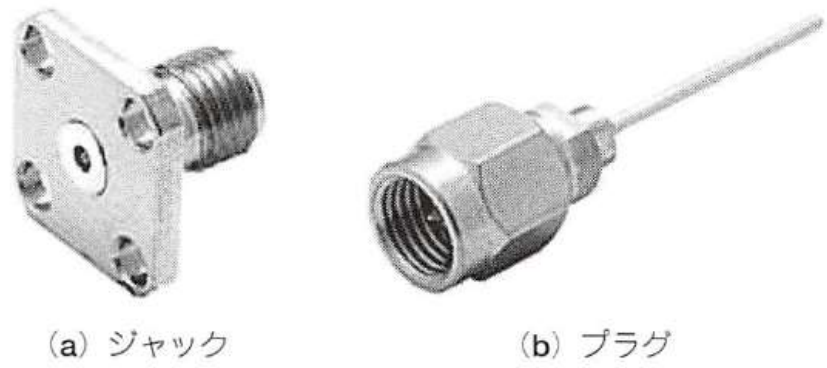

V-type

写真7 V型コネクタ

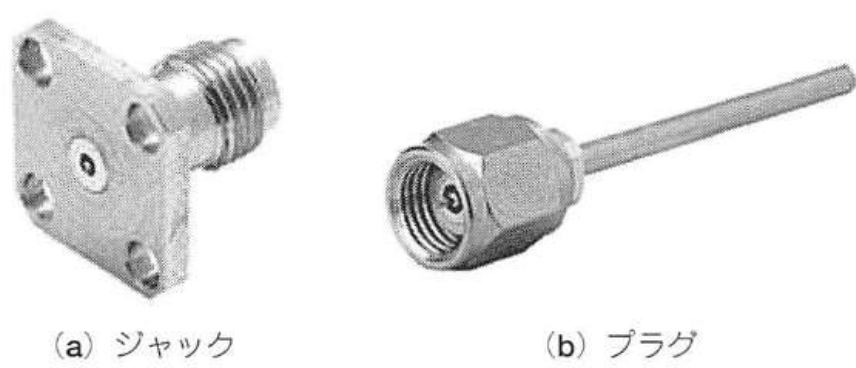

LEMO cables and connectors

MFBモデル



MSBモデル




<http://www.lemo.com/>


High-energy physics experiment,
etc.



Lecher line

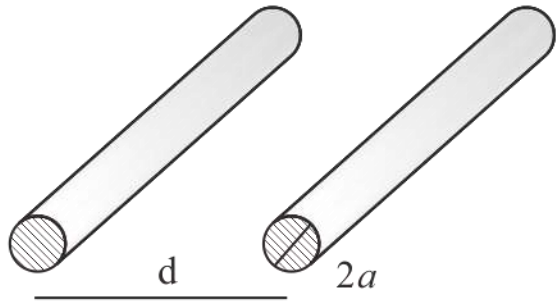

(a)

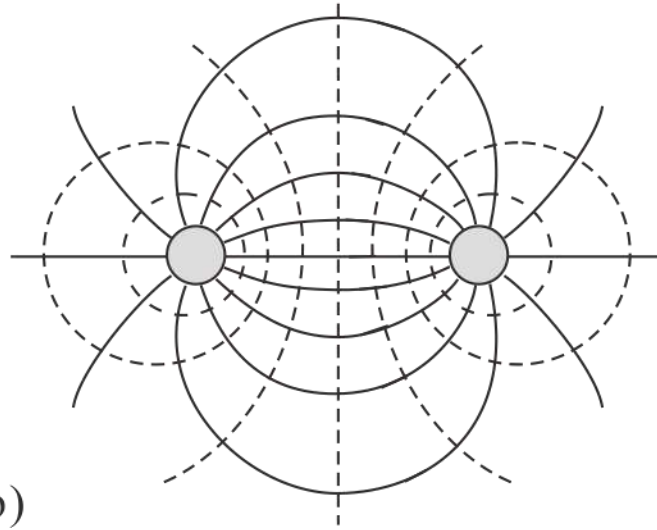


(b)



(c)

$$\phi_1 = -\phi_2 = \frac{J\sqrt{\mu}}{2\pi} \log \frac{d}{a} \quad Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{1}{\pi} \log \frac{d}{a}$$

Micro strip line

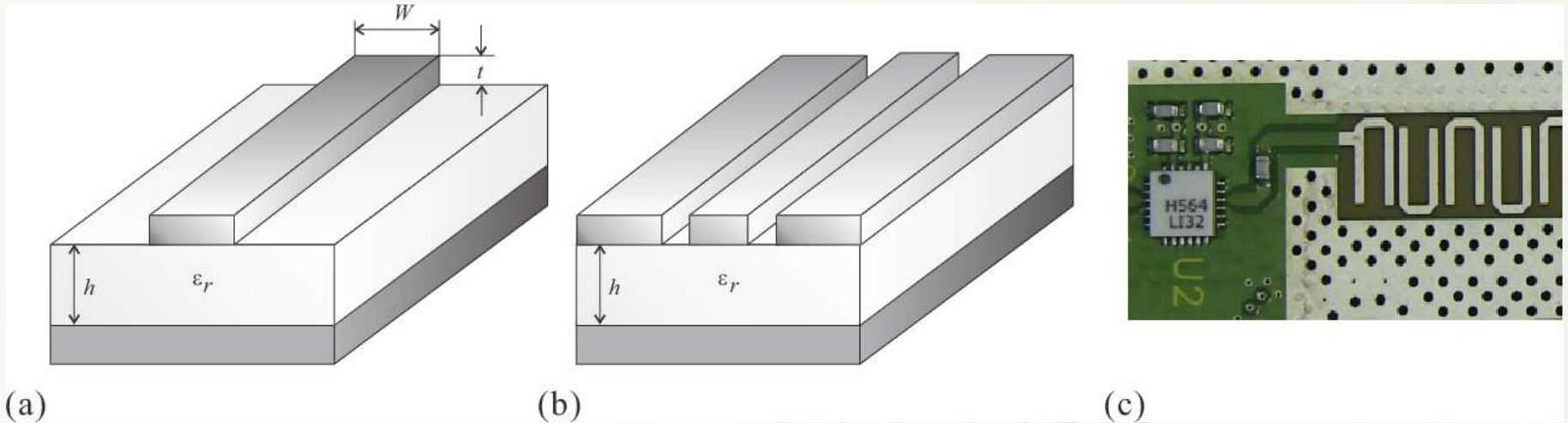


幅の広い ($W/h > 3.3$) ストリップ

$$Z(W, h, \epsilon_r) = \frac{Z_{F0}}{2\sqrt{\epsilon_r}} \left\{ \frac{W}{2h} + \frac{1}{\pi} \log 4 + \frac{\epsilon_r + 1}{2\pi\epsilon_r} \log \left[\frac{\pi e}{2} \left(\frac{W}{2h} + 0.94 \right) \right] \frac{\epsilon_r - 1}{2\pi\epsilon_r^2} \log \frac{e\pi^2}{16} \right\}^{-1}$$

幅の狭い ($W/h < 3.3$) ストリップ

$$Z(W, h, \epsilon_r) = \frac{Z_{F0}}{\pi\sqrt{2(\epsilon_r + 1)}} \left\{ \log \left[\frac{4h}{W} + \sqrt{\left(\frac{4h}{W} \right)^2 + 2} \right] - \frac{1}{2} \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(\log \frac{\pi}{2} + \frac{1}{\epsilon_r} \log \frac{4}{\pi} \right) \right\}$$

Exercise 4-1

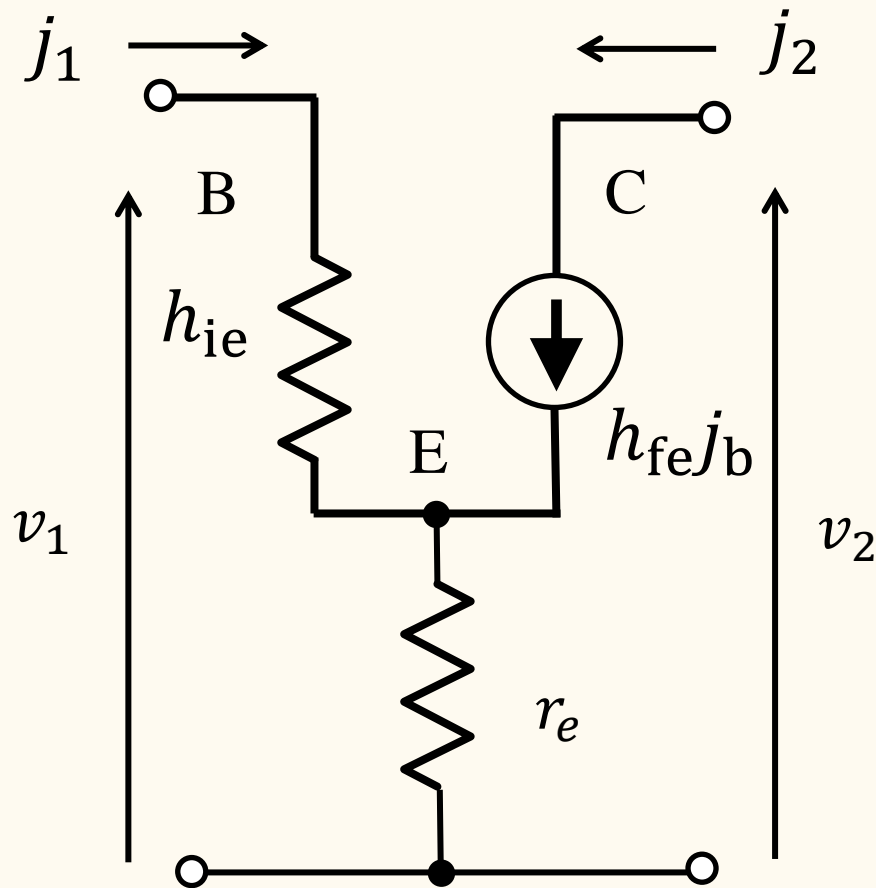


Let us view a bipolar transistor plus an emitter resistance as a four terminal circuit as shown in the left figure.

Obtain the Y (admittance) matrix defined below for this circuit.

Calculate each element in the Y matrix for
 $r_e = 25\Omega$, $h_{ie} = 500\Omega$, $h_{fe} = 200$

$$\begin{pmatrix} j_1 \\ j_2 \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix}$$

Exercise 4-2

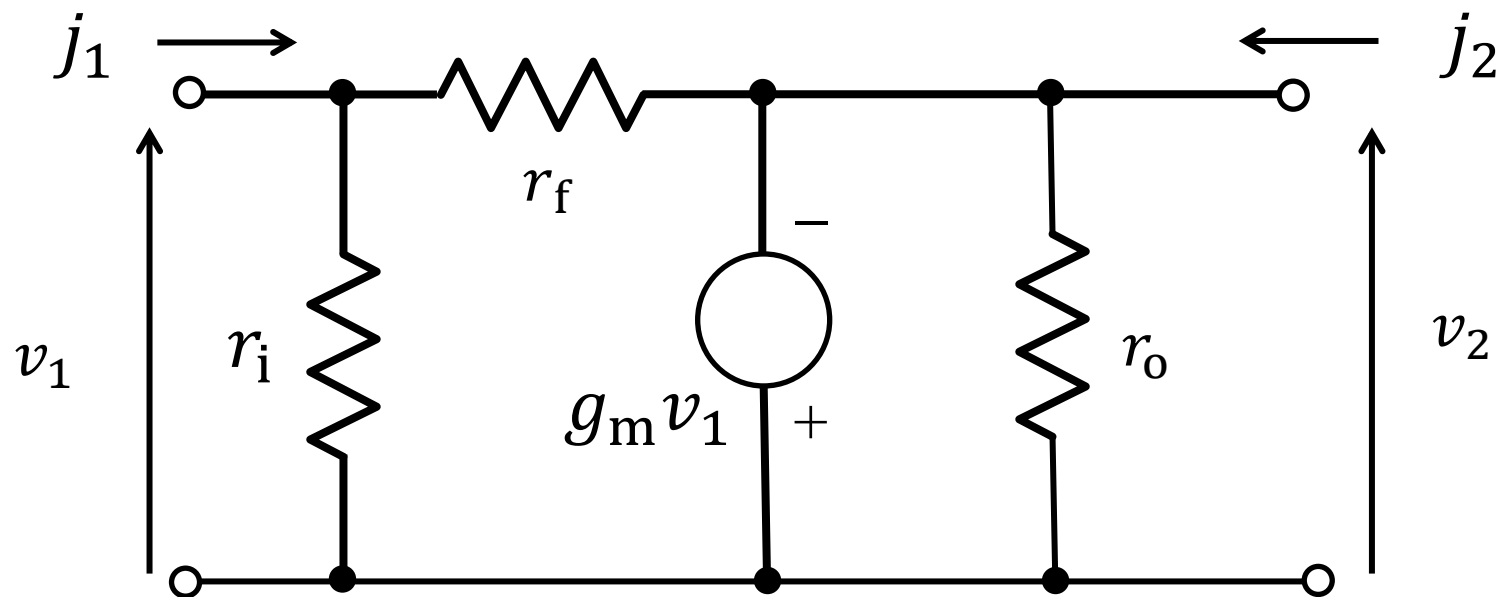

Obtain the Y matrix for the above equivalent circuit (π -shape circuit).

Exercise 4-3

$l=1\text{km}$ の伝送線路がある。終端側を短絡したところ、電源側から測定したインピダンスは $0.6i \Omega$ であった。一方、終端側を開放して電源側からアドミタンスを測定すると $4 \times 10^{-6}i \text{ S}$ であった。この伝送線路の特性インピダンスを求めよ。

Consider a transmission line with the length $l = 1\text{km}$. First we short-circuited the end and measured the impedance from the signal source and obtained $0.6i \Omega$. Next we opened the end and measured the admittance from the signal source and obtained $4 \times 10^{-6}i \text{ S}$.

What is the characteristic impedance of the transmission line?